

ENGR 101

Engineering Technology

Dr. [Kerese Manueli](#)

School of Engineering and Computer Science
Victoria University of Wellington

Victoria
UNIVERSITY OF WELLINGTON
*Te Whare Wānanga
o te Ūpoko o te Ika a Māui*



CAPITAL CITY UNIVERSITY

Week 4 Lecture 6b

- Main topics
 - Introduction to Engineering Technology
 - Number system
 - Logic Gates
 - Boolean Algebra
- Course web page:
https://ecs.wgtn.ac.nz/Courses/XMUT101_2021T1/
- kerese@ecs.vuw.ac.nz

Exercise 6.1

Use the Boolean rules to simplify the following expressions:

(Note: $\overline{A} = A'$ or $\overline{C} = C'$)



(a) $X = ABC + \overline{A}B + A\overline{B}\overline{C}$

(b) $X = \overline{A}B\overline{C} + A\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C$


(c) $AB + \overline{A}C + BC = AB + \overline{A}C$

(d) $(A + B)(\overline{A} + C)(B + C) = (A + B)(\overline{A} + C)$


Boolean Algebra Laws

	Name of Law	Properties
1.	Identity Law	$A+0=A$; $A+1=1$; $A.0=0$; $A.1=A$
2.	Commutative Law	$A.B = B.A$; $A+B = B+A$
3.	Associative Law	$A.(B.C) = A.B.C$; $A+(B+C) = A+B+C$
4.	Idempotent Law	$A.A = A$; $A+A = A$
5.	Double Negative Law	$A'' = A$
6.	Complement Law	$A.A' = 0$; $A+A' = 1$
7.	Law of Union	$A+1 = 1$; $A+0 = A$
8.	DeMorgan's Theorem	$(AB)' = A'+B'$; $(A+B)' = A'.B'$
9.	Distributive Law	$A.(B+C) = (A.B) + (A.C)$; $A+(BC) = (A+B).(A+C)$
10.	Absorption Law	$A.(A+B) = A$; $A+(A.B) = A$
11.	Common Identities Law	$A.(A'+B) = AB$; $A+(A'B) = A+B$

Exercise 6.1(a) $x = A B C + \bar{A} B + A B \bar{C} = ABC + A'B + ABC'$

	Boolean Law used
$x = ABC + A'B + ABC'$	
	
Common element	

Exercise 6.1(a) $x = A B C + \bar{A} B + A B \bar{C}$

	Boolean Law used
$x = ABC + A'B + ABC'$  Common term	3) Distributive Law $A.(B+C) = (A.B) + (A.C)$;

Exercise 6.1(a) $x = A B C + \bar{A} B + A B \bar{C}$

	Boolean Law used
$x = ABC + A'B + ABC'$	3) Distributive Law $A.(B+C) = (A.B) + (A.C)$
$= AB(C + C') + A'B$	

Parentheses (or normal brackets)



Exercise 6.1(a) $x = A B C + \bar{A} B + A B \bar{C}$

	Boolean Law used
$x = ABC + A'B + ABC'$	3) Distributive Law $A.(B+C) = (A.B) + (A.C)$
$= AB(C + C') + A'B$	
$= AB(1) + A'B$	6) Complement Law $A+A' = 1$

Exercise 6.1(a) $x = A B C + \bar{A} B + A B \bar{C}$

	Boolean Law used
$x = ABC + A'B + ABC'$	3) Distributive Law $A.(B+C) = (A.B) + (A.C)$
$= AB(C + C') + A'B$	
$= AB(1) + A'B$	6) Complement Law $A+A' = 1$
$= B(A + A')$	3) Distributive Law $A.(B+C) = (A.B) + (A.C)$
$= B$	

Exercise 6.1

(a) $X = ABC + \overline{A}B + AB\overline{C} = B$

(b) $X = \overline{A}B\overline{C} + A\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C$

(c) $AB + \overline{A}C + BC = AB + \overline{A}C$

(d) $(A + B)(\overline{A} + C)(B + C) = (A + B)(\overline{A} + C)$

Exercise 6.1(b) $x = \bar{A} B \bar{C} + A \bar{B} \bar{C} + \bar{A} \bar{B} \bar{C} + \bar{A} \bar{B} \bar{C}$

$$x = A'BC' + AB'C' + A'B'C' + A'B'C'$$

Boolean Law used

$x = A'BC' + AB'C' + A'B'C' + A'B'C'$	Boolean Law used

Exercise 6.1(b) $x = \bar{A} B \bar{C} + A \bar{B} \bar{C} + \bar{A} \bar{B} \bar{C} + \bar{A} \bar{B} \bar{C}$

$x = A'BC' + AB'C' + A'B'C' + A'B'C'$	Boolean Law used
$= A'BC' + AB'C' + A'B'C' + A'B'C'$	4. Idempotent Law $A + A = A$

Exercise 6.1(b) $x = \bar{A} B \bar{C} + A \bar{B} \bar{C} + \bar{A} \bar{B} \bar{C} + \bar{A} \bar{B} \bar{C}$

$x = A'BC' + AB'C' + A'B'C' + A'B'C'$	Boolean Law used
$= A'BC' + AB'C' + A'B'C' + A'B'C'$	4. Idempotent Law $A + A = A$
$= A'BC' + AB'C' + A'B'C'$	
$= A'BC' + B'C'(A + A')$	9. Distributive Law $A.(B+C) = (A.B) + (A.C)$

Exercise 6.1(b) $x = \bar{A} B \bar{C} + A \bar{B} \bar{C} + \bar{A} \bar{B} \bar{C} + \bar{A} \bar{B} \bar{C}$

$x = A'BC' + AB'C' + A'B'C' + A'B'C'$	Boolean Law used
$= A'BC' + AB'C' + A'B'C' + A'B'C'$	4. Idempotent Law $A + A = A$
$= A'BC' + AB'C' + A'B'C'$	
$= A'BC' + B'C'(A + A')$	9. Distributive Law $A.(B+C) = (A.B) + (A.C)$
$= A'BC' + B'C'(1)$	6. Complement Law $A+A' = 1$

Exercise 6.1(b) $x = \overline{A} B \overline{C} + A \overline{B} \overline{C} + \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} C$


$x = A'BC' + AB'C' + A'B'C' + A'B'C'$	Boolean Law used
$= A'BC' + AB'C' + A'B'C' + A'B'C'$	4. Idempotent Law $A + A = A$
$= A'BC' + AB'C' + A'B'C'$	
$= A'BC' + B'C'(A + A')$	9. Distributive Law $A.(B+C) = (A.B) + (A.C)$
$= A'BC' + B'C'(1)$	6. Complement Law $A+A' = 1$
$= A'BC' + B'C'$	
$= C' (A'B + B')$	9. Distributive Law $A.(B+C) = (A.B) + (A.C)$

Exercise 6.1(b) $x = \overline{A} B \overline{C} + A \overline{B} \overline{C} + \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} C$

$x = A'BC' + AB'C' + A'B'C' + A'B'C'$	Boolean Law used
$= A'BC' + AB'C' + A'B'C' + A'B'C'$	4. Idempotent Law $A + A = A$
$= A'BC' + AB'C' + A'B'C'$	
$= A'BC' + B'C'(A + A')$	9. Distributive Law $A.(B+C) = (A.B) + (A.C)$
$= A'BC' + B'C'(1)$	6. Complement Law $A+A' = 1$
$= A'BC' + B'C'$	
$= C' (A'B + B')$	9. Distributive Law $A.(B+C) = (A.B) + (A.C)$
$= A'C' + B'C'$	11. Common Identities Law $A.(A'+B) = AB$; $A+(A'B) = A+B$

Describing Logic Circuits Algebraically

Example 1

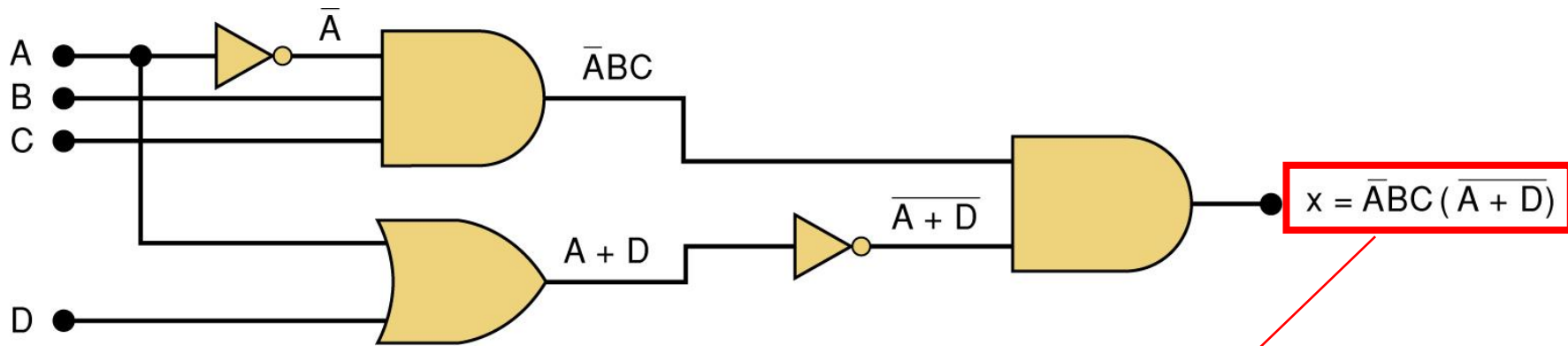

$$X = A'BC (A+D)'$$

Minimize $X = A'BC (A+D)'$ using Boolean Laws


	Name of Law	Properties
1.	Identity Law	$A+0=A$; $A+1=1$; $A.0=0$; $A.1=A$
2.	Commutative Law	$A.B = B.A$; $A+B = B+A$
3.	Associative Law	$A.(B.C) = A.B.C$; $A+(B+C) = A+B+C$
4.	Idempotent Law	$A.A = A$; $A+A = A$
5.	Double Negative Law	$A'' = A$
6.	Complement Law	$A.A' = 0$; $A+A' = 1$
7.	Law of Union	$A+1 = 1$; $A+0 = A$
8.	DeMorgan's Theorem	$(AB)' = A'+B'$; $(A+B)' = A'.B'$
9.	Distributive Law	$A.(B+C) = (A.B) + (A.C)$; $A+(BC) = (A+B).(A+C)$
10.	Absorption Law	$A.(A+B) = A$; $A+(A.B) = A$
11.	Common Identities Law	$A.(A'+B) = AB$; $A+(A'B) = A+B$

Minimize $X = A'BC (A+D)'$ using Boolean Laws

$X = A'BC (A+D)'$	Boolean Law used
$= A'BC (A'D)'$	DeMorgan's Theorems $(AB)' = A'+B'$; $(A+B)' = A'.B'$
$= A'(BCD)'$	Idempotent Law $A.A = A$
$= A'BCD$	Associative Law $A.(B.C) = A.B.C$


Describing Logic Circuits Algebraically

Example 1

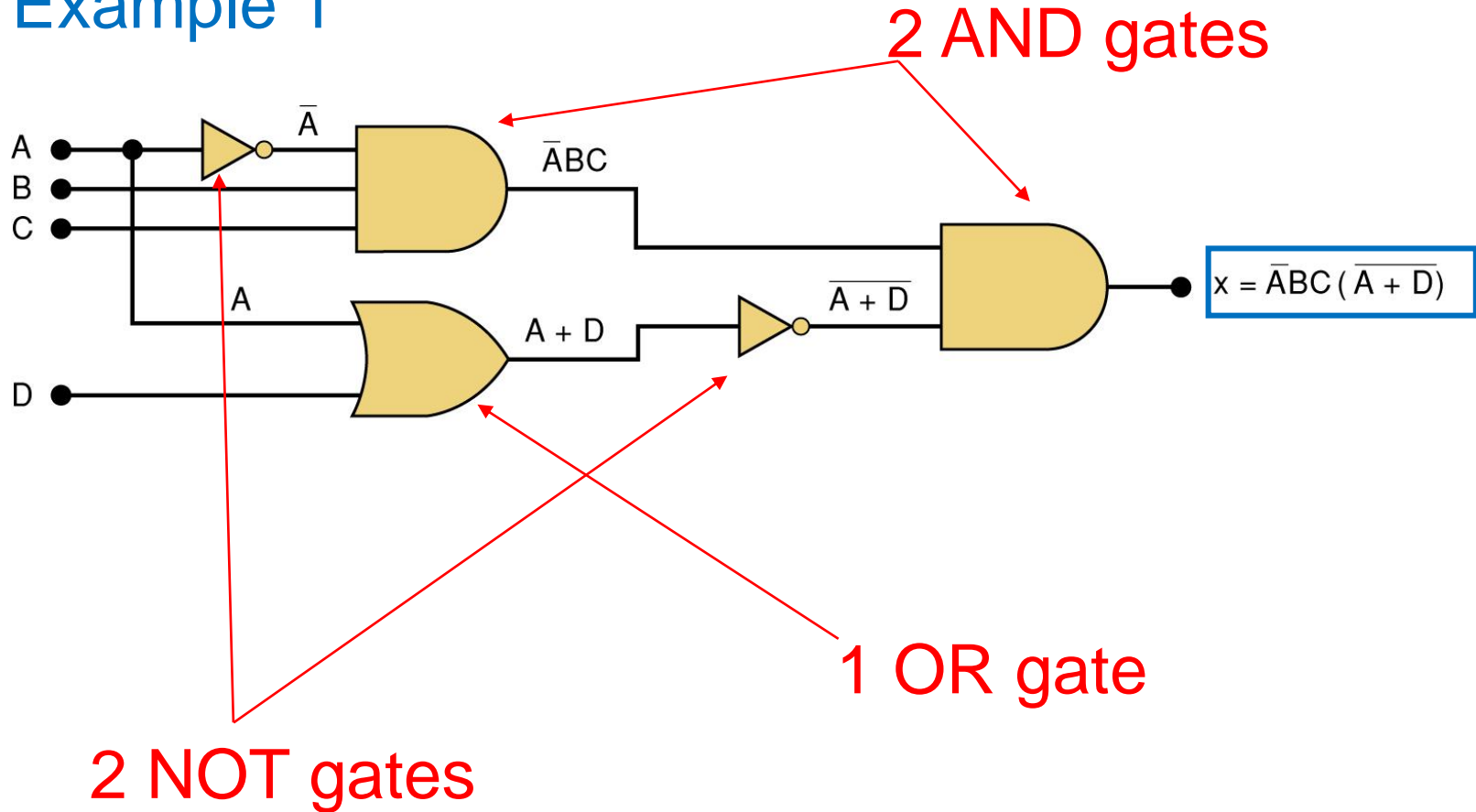


Describing Logic Circuits Algebraically

Example 1

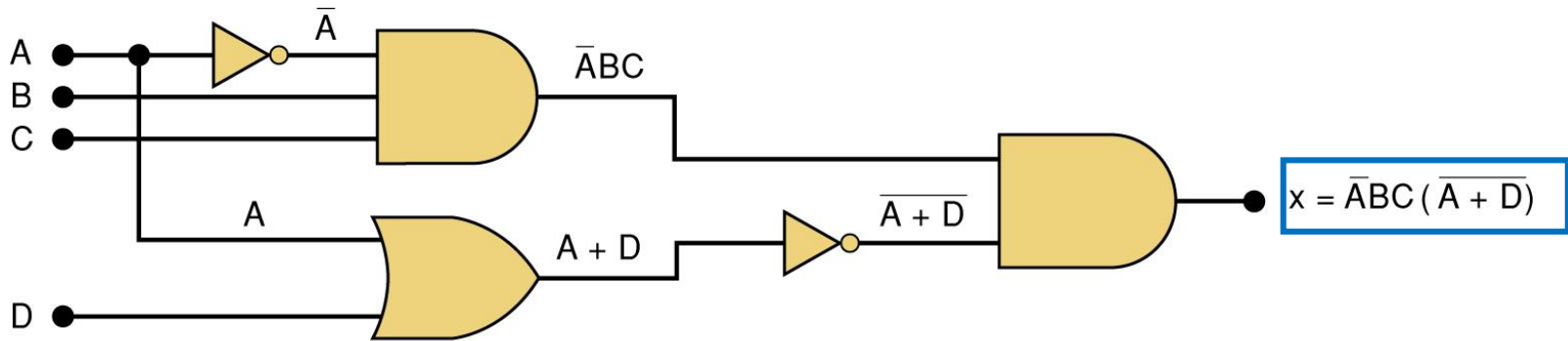

Simplified expression: $A'BCD$

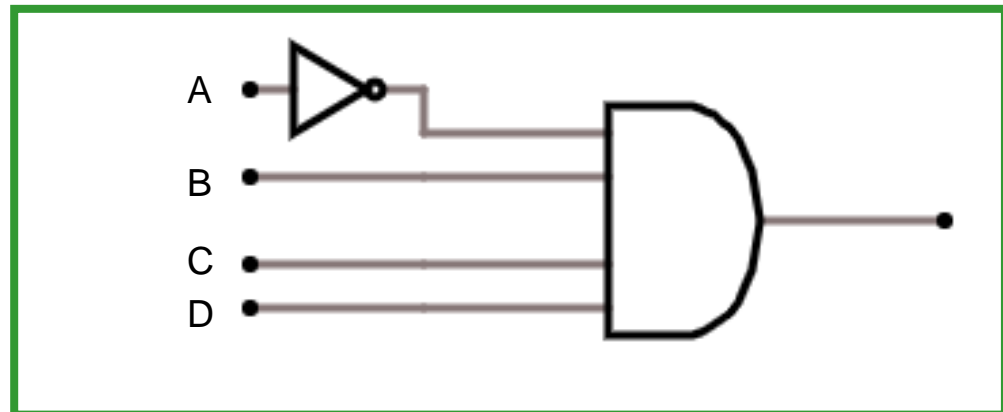

Exercise 6.1

Use the Boolean rules to simplify the following expressions:

(Note: $\overline{A} = A'$ or $\overline{C} = C'$)



(a) $X = ABC + \overline{A}B + AB\overline{C}$

(b) $X = \overline{A}B\overline{C} + A\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C$

(c) $AB + \overline{A}C + BC = AB + \overline{A}C$

(d) $(A + B)(\overline{A} + C)(B + C) = (A + B)(\overline{A} + C)$

Describing Logic Circuits Algebraically

Exercise 6.1 (a):

$$x = ABC + \bar{A}B + AB\bar{C}$$
$$= ABC + A'B + ABC'$$


Describing Logic Circuits Algebraically

Exercise 6.1 (a): $x = ABC + \bar{A}B + AB\bar{C}$
 $= \boxed{ABC} + A'B + ABC'$




Describing Logic Circuits Algebraically

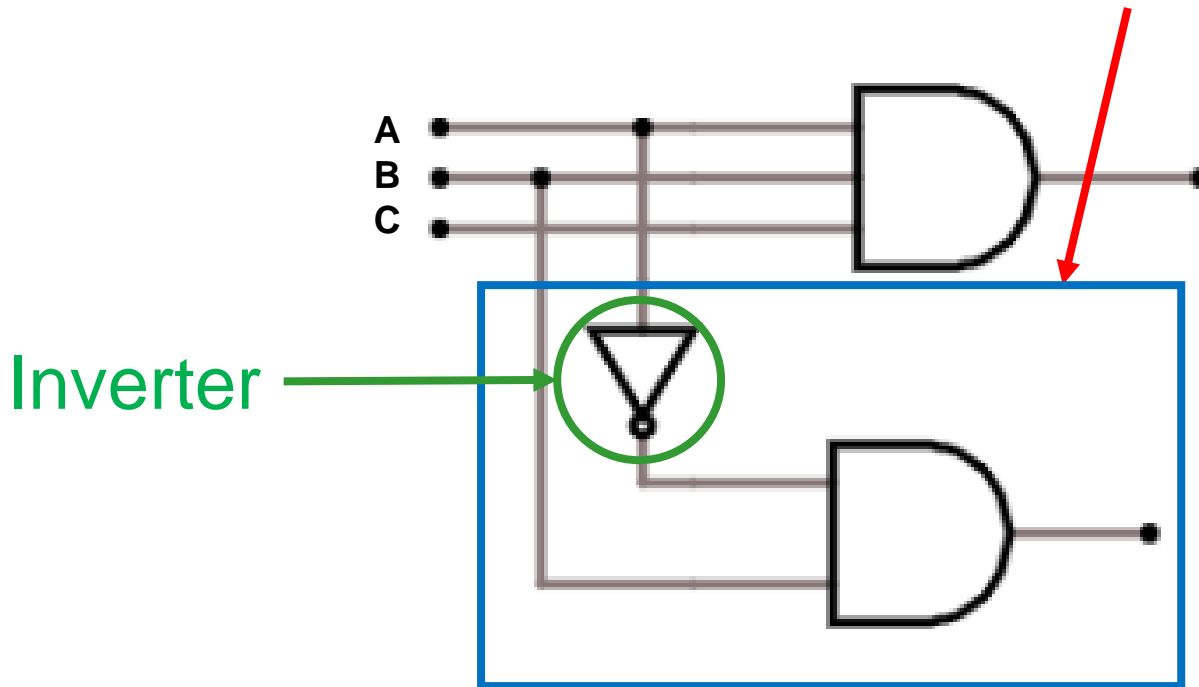Exercise 6.1 (a): $x = ABC + \bar{A}B + ABC\bar{C}$
 $= ABC + \boxed{A'B} + ABC\bar{C}$




Describing Logic Circuits Algebraically

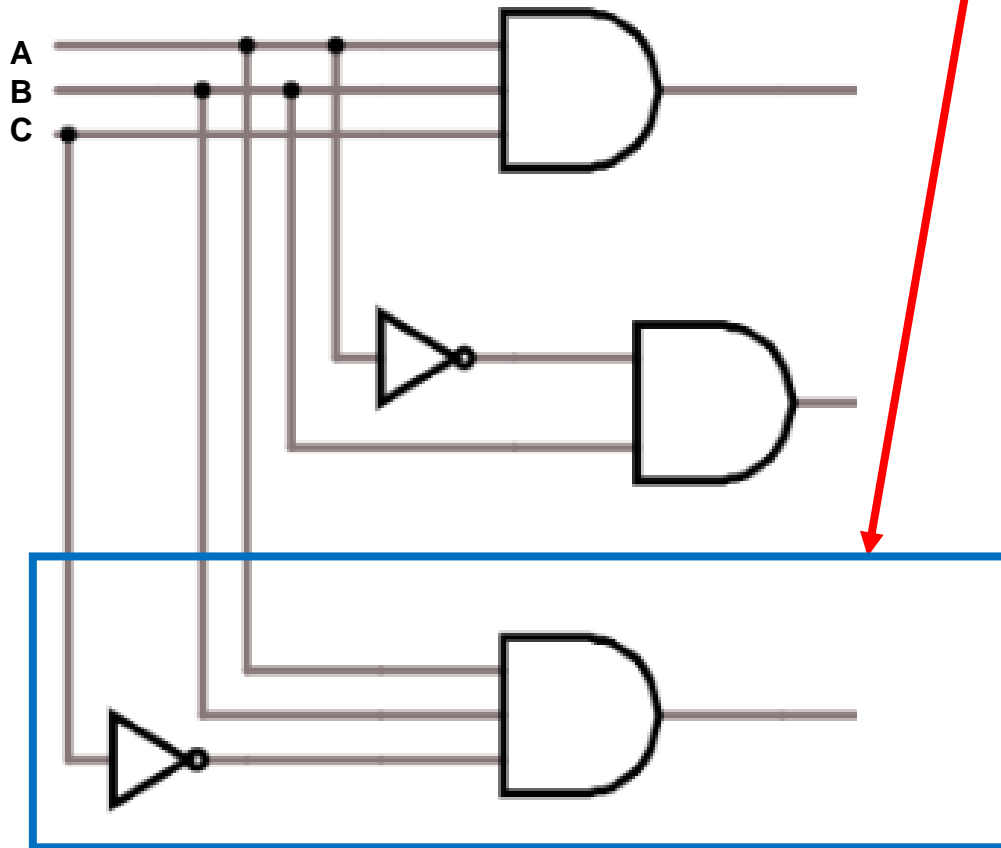Exercise 6.1 (a): $x = ABC + \bar{A}B + ABC\bar{C}$
 $= ABC + A'B + \boxed{ABC'}$ 3rd term



Describing Logic Circuits Algebraically

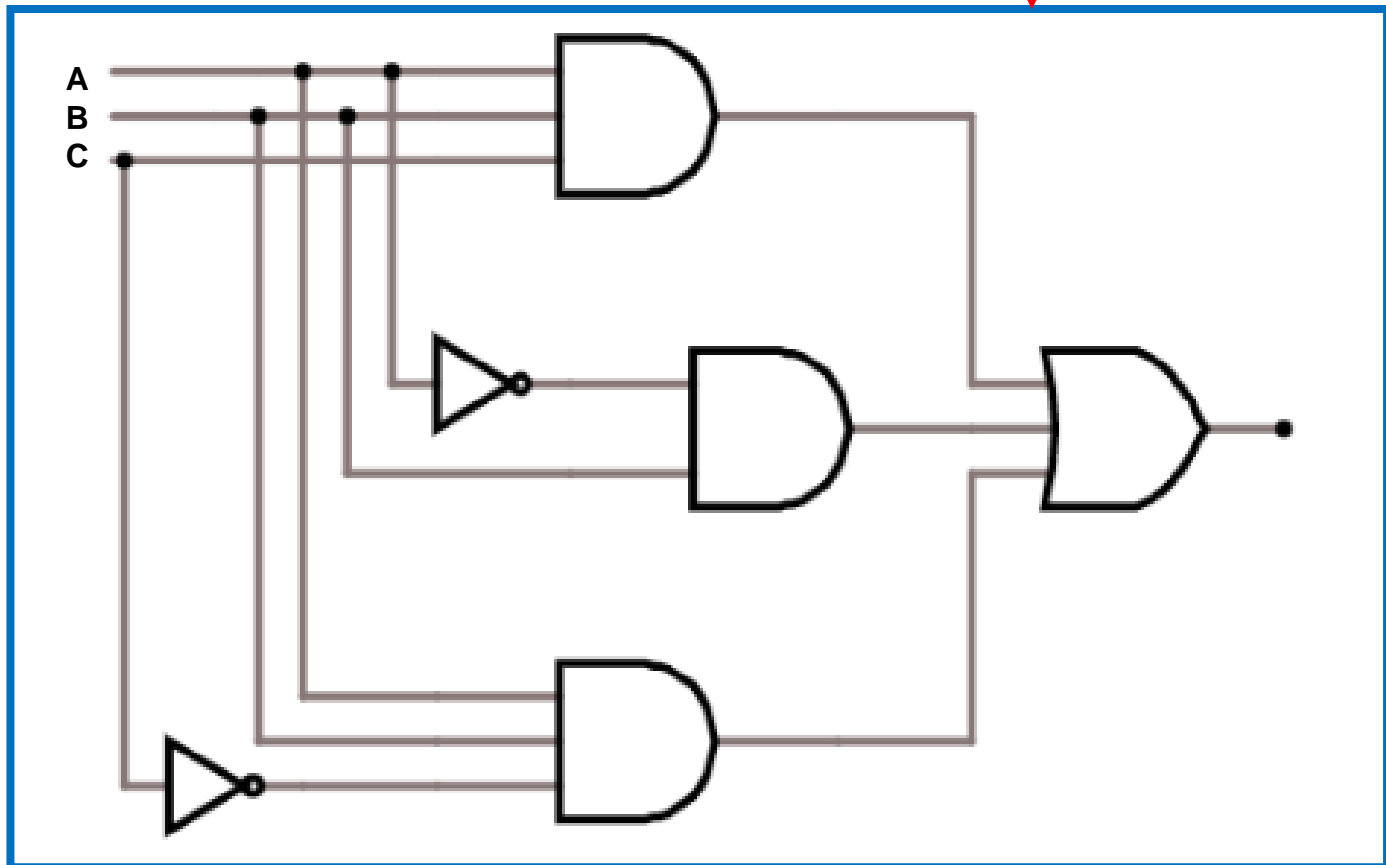Exercise 6.1 (a): $x = ABC + \bar{A}B + ABC\bar{C}$
 $= ABC + A'B + ABC'$



Describing Logic Circuits Algebraically

Example


$$\begin{aligned} & A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C \\ &= AB'C' + A'B'C' + A'BC' + A'B'C \end{aligned}$$

Describing Logic Circuits Algebraically

Example

$$\begin{aligned} & A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C \\ & = \boxed{AB'C'} + A'B'C' + A'BC' + A'B'C \end{aligned}$$

1st term

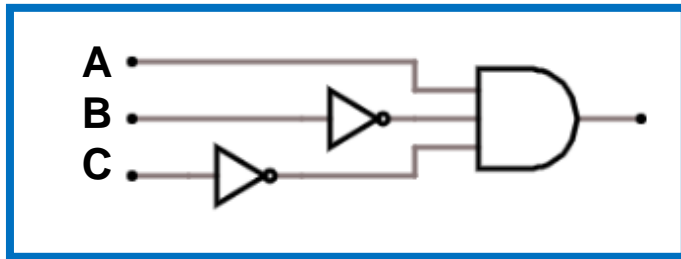


Logic circuit

Describing Logic Circuits Algebraically

Example

$$\begin{aligned} & A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C \\ &= AB'C' + \boxed{A'B'C'} + A'BC' + A'B'C \end{aligned}$$

2nd term

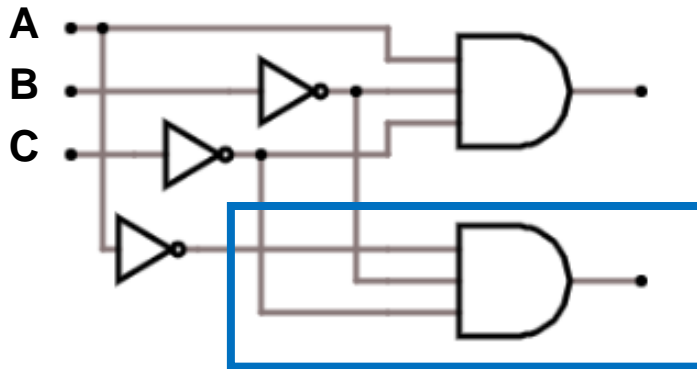


Logic circuit

Describing Logic Circuits Algebraically

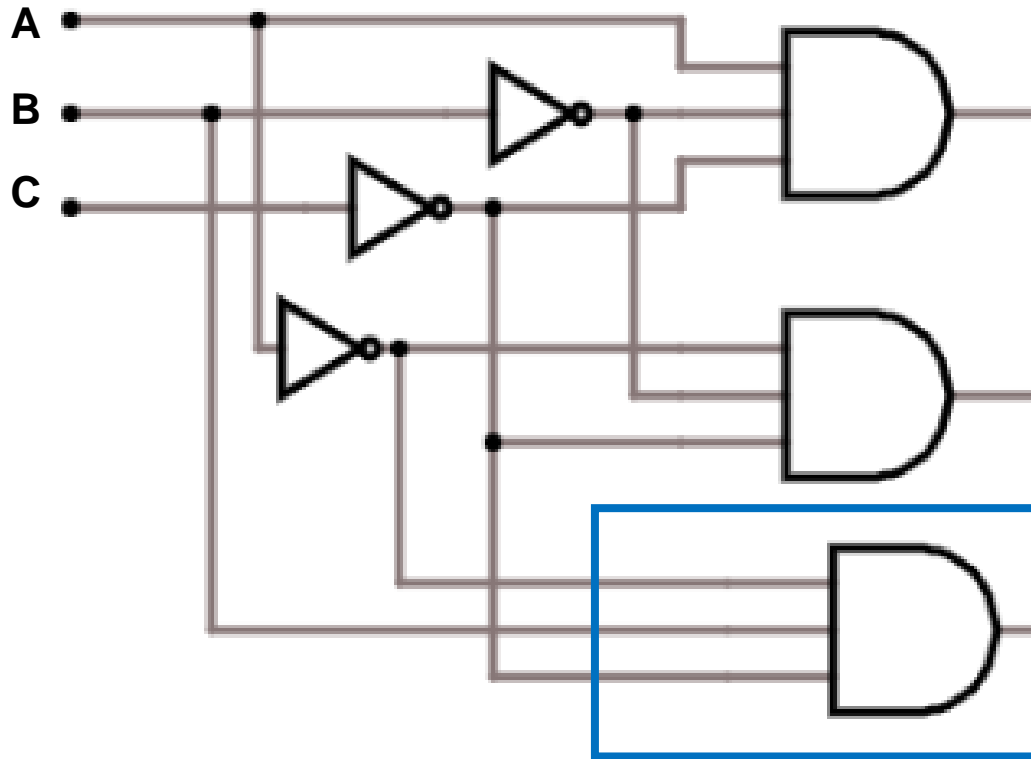Example

$$\begin{aligned} & \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}BC \\ & = AB'C' + A'B'C' + \boxed{A'BC'} + A'B'C \end{aligned}$$




3rd term

Logic circuit

Describing Logic Circuits Algebraically

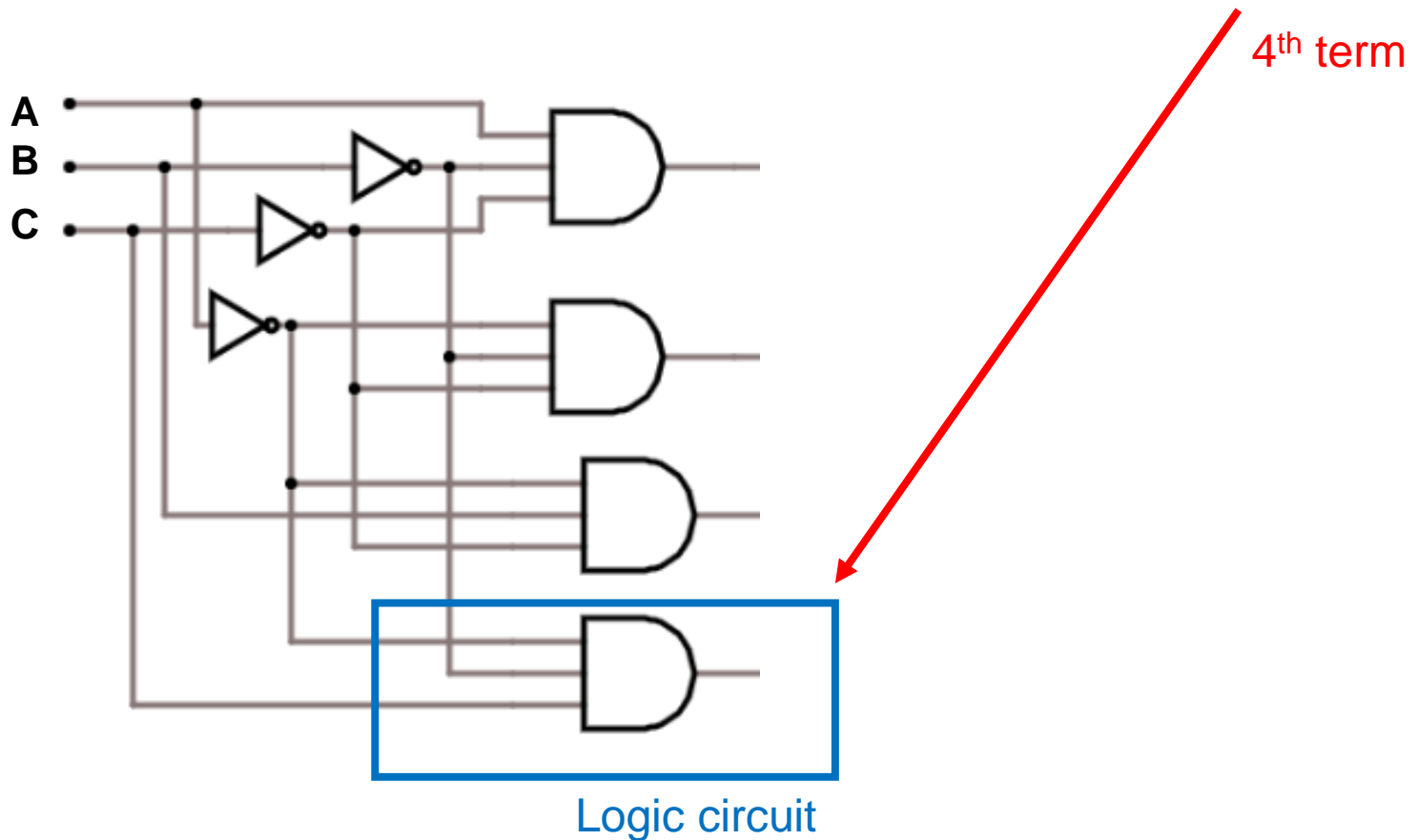Example


$$\begin{aligned} & \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}BC \\ & = AB'C' + A'B'C' + A'BC' + \boxed{A'B'C} \end{aligned}$$



Describing Logic Circuits Algebraically

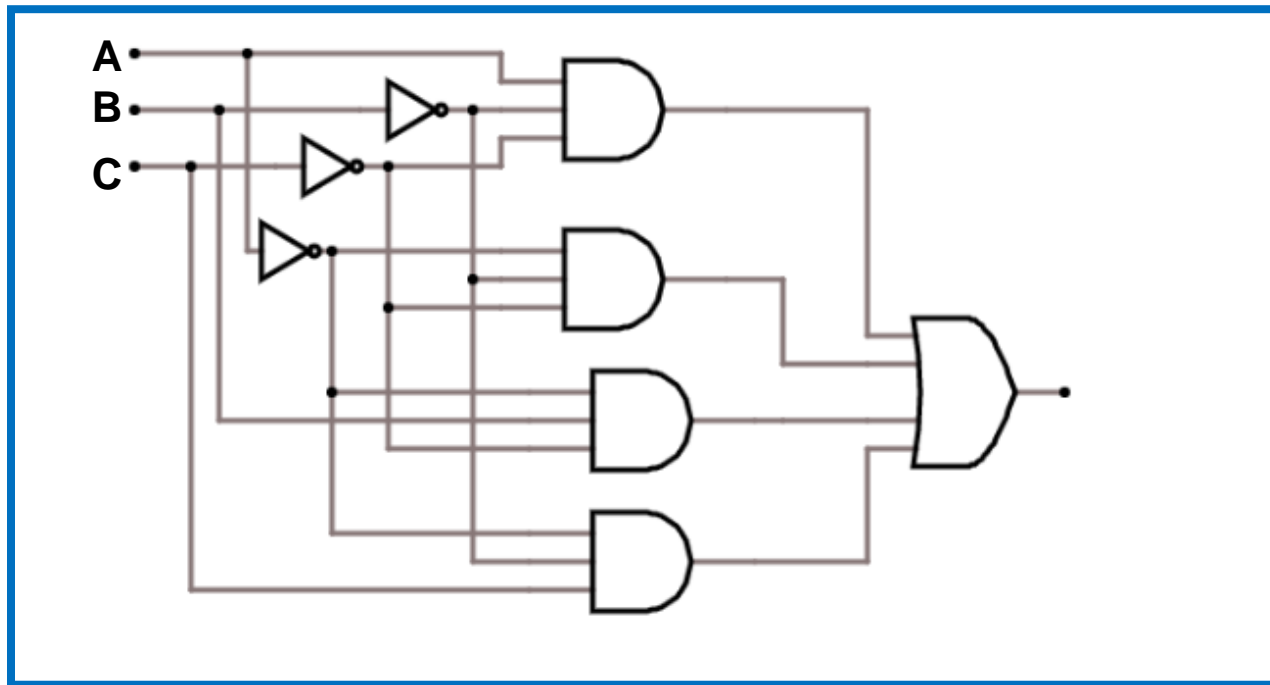Example


$$\begin{aligned} & A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C \\ & = AB'C' + A'B'C' + A'BC' + A'B'C \end{aligned}$$



Simplify the following Boolean expression

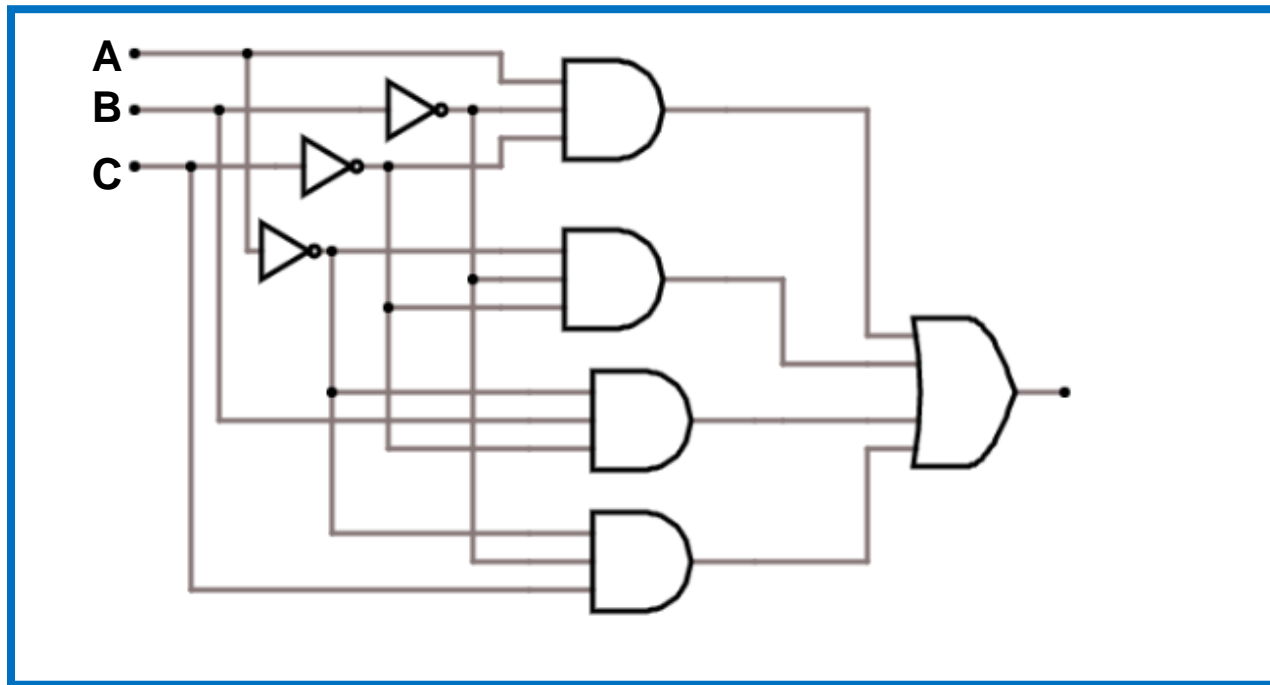Exercise

$$\begin{aligned} & A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C \\ &= AB'C' + A'B'C' + A'BC' + A'B'C \end{aligned}$$



Draw the logic circuit for the simplified expression.

Week 4 Lecture 6b

- Boolean Algebra
 - Minimizing Boolean expressions
 - Describing logic circuits algebraically

- Course web page:

https://ecs.wgtn.ac.nz/Courses/XMUT101_2021T1/

- `kerese@ecs.vuw.ac.nz`

Exercise 6.2

Use the Boolean rules to simplify the following expressions:

$$(i) \quad AB + AC + ABC \qquad (ii) \quad AB + A(\overline{B} + C) + AB\overline{C}$$

$$(iii) \quad \overline{A}BC + A\overline{B}C + ABC + AB\overline{C} + \overline{A}\overline{B}\overline{C}$$