

ENGR 101

Engineering Technology

Dr. [Kerese Manueli](#)

School of Engineering and Computer Science
Victoria University of Wellington

Victoria
UNIVERSITY OF WELLINGTON

*Te Whare Wānanga
o te Ūpoko o te Ika a Māui*



CAPITAL CITY UNIVERSITY

Week 6 Lecture 10b

- Karnaugh Map (K-Map)
- Assignment 1 – submit before midnight Friday
- Course web page:

https://ecs.wgtn.ac.nz/Courses/XMUT101_2021T1/

- kerese@ecs.vuw.ac.nz

Example 4 – 4 Variables

$$\text{Out} = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}BCD \\ + ABCD + ABC\overline{D} + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D}$$

$$= A'B'C'D' + A'B'C'D + A'BC'D + A'BCD + ABCD \\ + ABCD' + AB'C'D' + AB'CD'$$

Example 4 – 4 Variables

$$\text{Out} = A'B'C'D' + A'B'C'D + A'BC'D + A'BCD + ABCD \\ + ABCD' + AB'C'D' + AB'CD'$$

Step 1:
Draw the
K-Map

AB \ CD	C'D'	C'D	CD	CD'
A'B'				
A'B				
AB				
AB'				

Example 4 – 4 Variables

$$\text{Out} = A'B'C'D' + A'B'C'D + A'BC'D + A'BCD + ABCD \\ + ABCD' + AB'C'D' + AB'CD'$$

Step 2:
Insert 1
according
to each
term in the
Boolean
expression

AB \ CD	C'D'	C'D	CD	CD'
A'B'				
A'B				
AB				
AB'				

Example 4 – 4 Variables

$$\text{Out} = \mathbf{A'B'C'D'} + A'B'C'D + A'BC'D + A'BCD + ABCD + ABCD' + AB'C'D' + AB'CD'$$

First term

Step 2:
Insert 1
according
to each
term in the
Boolean
expression

AB \ CD	C'D'	C'D	CD	CD'
A'B'	1			
A'B				
AB				
AB'				

row

column

Example 4 – 4 Variables

$$\text{Out} = A'B'C'D' + A'B'C'D + A'BC'D + A'BCD + ABCD$$

Second term \rightarrow $+ ABCD' + AB'C'D' + AB'CD'$

Step 2:
Insert 1
according
to each
term in the
Boolean
expression

AB \ CD	C'D'	C'D	CD	CD'
A'B'	1	1		
A'B				
AB				
AB'				

row

column

Example 4 – 4 Variables

$$\text{Out} = A'B'C'D' + A'B'C'D + \mathbf{A'BC'D} + A'BCD + ABCD$$

Third term

$$+ ABCD' + AB'C'D' + AB'CD'$$

Step 2:
Insert 1
according
to each
term in the
Boolean
expression

AB \ CD	C'D'	C'D	CD	CD'
A'B'	1	1		
A'B		1		
AB				
AB'				

row

column

Example 4 – 4 Variables

$$\text{Out} = A'B'C'D' + A'B'C'D + A'BC'D + \mathbf{A'BCD} + ABCD \\ + ABCD' + AB'C'D' + AB'CD'$$

4th term

Step 2:
Insert 1
according
to each
term in the
Boolean
expression

AB \ CD	C'D'	C'D	CD	CD'
A'B'	1	1		
A'B		1	1	
AB				
AB'				

row

column

Example 4 – 4 Variables

$$\text{Out} = A'B'C'D' + A'B'C'D + A'BC'D + A'BCD + \text{ABCD} + ABCD' + AB'C'D' + AB'CD'$$

5th term

Step 2:
Insert 1
according
to each
term in the
Boolean
expression

AB \ CD	C'D'	C'D	CD	CD'
A'B'	1	1		
A'B		1	1	
AB			1	
AB'				

row

column

Example 4 – 4 Variables

$$\text{Out} = A'B'C'D' + A'B'C'D + A'BC'D + A'BCD + ABCD \\ + \text{ABCD}' + AB'C'D' + AB'CD'$$

6th term 

Step 2:
Insert 1
according
to each
term in the
Boolean
expression

AB \ CD	C'D'	C'D	CD	CD'
A'B'	1	1		
A'B		1	1	
AB			1	1
AB'				

row

column

Example 4 – 4 Variables

$$\text{Out} = A'B'C'D' + A'B'C'D + A'BC'D + A'BCD + ABCD + ABCD' + \mathbf{AB'C'D'} + AB'CD'$$

7th term

Step 2:
Insert 1
according
to each
term in the
Boolean
expression

AB \ CD	C'D'	C'D	CD	CD'
A'B'	1	1		
A'B		1	1	
AB			1	1
AB'	1			

column

row

Example 4 – 4 Variables

$$\text{Out} = A'B'C'D' + A'B'C'D + A'BC'D + A'BCD + ABCD + ABCD' + AB'C'D' + \text{AB'CD}'$$

← 8th term

Step 2:
Insert 1
according
to each
term in the
Boolean
expression

AB \ CD	C'D'	C'D	CD	CD'
A'B'	1	1		
A'B		1	1	
AB			1	1
AB'	1			1

row

column

Example 4 – 4 Variables

$$\text{Out} = A'B'C'D' + A'B'C'D + A'BC'D + A'BCD + ABCD + ABCD' + AB'C'D' + AB'CD'$$

Steps 3-6:
Loop 1s in
a pair,
or in a quad,
or in an octet

AB \ CD	C'D'	C'D	CD	CD'
A'B'	1	1		
A'B		1	1	
AB			1	1
AB'	1			1

Example 4 – 4 Variables

$$\text{Out} = A'B'C'D' + A'B'C'D + A'BC'D + A'BCD + ABCD + ABCD' + AB'C'D' + AB'CD'$$

Step 7:
Form the
OR sum of
terms

AB \ CD	C'D'	C'D	CD	CD'
A'B'	1	1		
A'B		1	1	
AB			1	1
AB'	1			1

$$\text{Out} = A'C'D + BCD + ACD' + B'C'D'$$

Example 4 – 4 Variables

$$\text{Out} = A'B'C'D' + A'B'C'D + A'BC'D + A'BCD + ABCD + ABCD' + AB'C'D' + AB'CD'$$

Step 7:
Form the
OR sum of
terms

AB \ CD	C'D'	C'D	CD	CD'
A'B'	1	1		
A'B		1	1	
AB			1	1
AB'	1			1

$$\text{Out} = A'B'C' + A'BD + ABC + AB'D'$$

Exercise 10.3: Use a K-map to simplify the following

$$X = A'B'C'D' + A'B'CD + A'BC'D' + A'BCD + ABC'D' \\ + ABC'D + ABCD + AB'C'D' + AB'CD$$

**10 minutes
to work this one!!**

Exercise 10.3: Use a K-map to simplify the following

$$X = A'B'C'D' + A'B'CD + A'BC'D' + A'BCD + ABC'D' + ABC'D + ABCD + AB'C'D' + AB'CD$$

Step 1:
Draw the
K-Map

AB \ CD	C'D'	C'D	CD	CD'
A'B'				
A'B				
AB				
AB'				

Exercise 10.3: Use a K-map to simplify the following

$$X = A'B'C'D' + A'B'CD + A'BC'D' + A'BCD + ABC'D' + ABCD + AB'C'D' + AB'CD$$

First term

Step 2:
 Insert 1
 according
 to each
 term in the
 Boolean
 expression

AB \ CD	C'D'	C'D	CD	CD'
A'B'	1			
A'B				
AB				
AB'				

row

column

7 minutes to insert 1 for all terms

Exercise 10.3: Use a K-map to simplify the following


$$X = A'B'C'D' + A'B'CD + A'BC'D' + A'BCD + ABC'D' \\ + ABC'D + ABCD + AB'C'D' + AB'CD$$

Steps 3-6:
Loop 1s in
a pair,
or in a quad,
or in an octet

AB \ CD	C'D'	C'D	CD	CD'
A'B'	1		1	
A'B	1		1	
AB	1	1	1	
AB'	1		1	

Exercise 10.3: Use a K-map to simplify the following

$$X = A'B'C'D' + A'B'CD + A'BC'D' + A'BCD + ABC'D' + ABCD + AB'C'D' + AB'CD$$

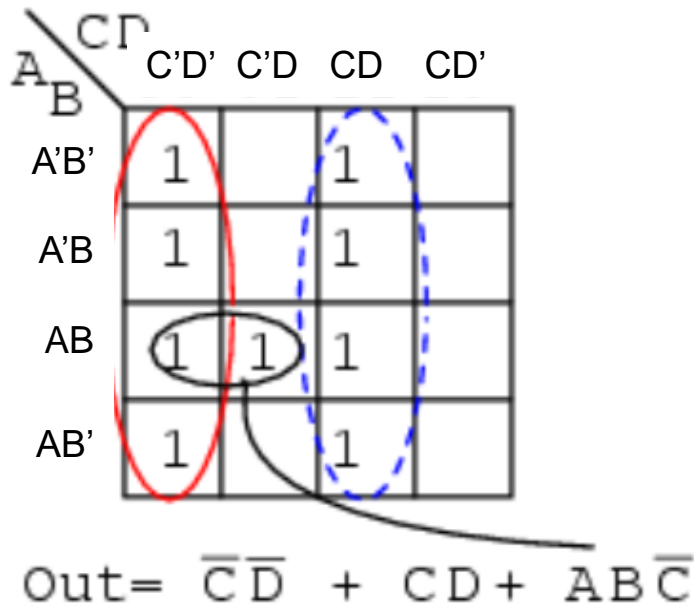

Exercise 10.3: Use a K-map to simplify the following

$$X = A'B'C'D' + A'B'CD + A'BC'D' + A'BCD + ABC'D' + ABCD + AB'C'D' + AB'CD$$

		$C \ D$			
		$C'D'$	$C'D$	CD	CD'
$A \ B$	$A'B'$	1		1	
	$A'B$	1		1	
	AB	1	1	1	
	AB'	1		1	

$$\text{out} = \bar{C}\bar{D} + CD + AB\bar{C}$$

		$C \ D$			
		$C'D'$	$C'D$	CD	CD'
$A \ B$	$A'B'$	1		1	
	$A'B$	1		1	
	AB	1	1	1	
	AB'	1		1	

$$\text{out} = \bar{C}\bar{D} + CD + ABD$$

Don't care Output Conditions

Can be changed 0/1 so that the simplest expression can be obtained from the K-Map. Typically occur when we know certain input conditions are impossible.

Truth Table

A	B	C	z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	x
1	0	0	x
1	0	1	1
1	1	0	1
1	1	1	1

} "don't care"

(a)

Don't care Output Conditions

Can be changed 0/1 so that the simplest expression can be obtained from the K-Map. Typically occur when we know certain input conditions are impossible.

Truth Table

A	B	C	z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	x
1	0	0	x
1	0	1	1
1	1	0	1
1	1	1	1

(a)

	\bar{C}	C
$\bar{A}\bar{B}$	0	0
$\bar{A}B$	0	x
AB	1	1
$A\bar{B}$	x	1

(b)

Don't care Output Conditions

Can be changed 0/1 so that the simplest expression can be obtained from the K-map. Typically occur when we know certain input conditions are impossible.


A	B	C	z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	x
1	0	0	x
1	0	1	1
1	1	0	1
1	1	1	1

"don't care"

(a)

	\bar{C}	C
$\bar{A}\bar{B}$	0	0
$\bar{A}B$	0	x
AB	1	1
$A\bar{B}$	x	1

(b)

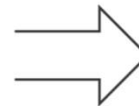

	\bar{C}	C
$\bar{A}\bar{B}$	0	0
$\bar{A}B$	0	0
AB	1	1
$A\bar{B}$	1	1

$z = A$

(c)

Problem:

Design a logic circuit for an elevator in a three storey building.



Problem: Design a logic circuit for a three storey elevator.

M = Logic signal indicating if the elevator is **moving** ($M = 1$) or **stationary** ($M = 0$)

Problem: Design a logic circuit for a three storey elevator.

M = Logic signal indicating if the elevator is moving (M = 1) or stationary (M = 0)

F1, F2 and F3 are the floor level signals, normally 0 but gets to 1 when a particular floor is reached.

Problem: Design a logic circuit for a three storey elevator.

M = Logic signal indicating if the elevator is moving (M = 1) or stationary (M = 0)

F1, F2 and F3 are the floor level signals, normally 0 but gets to 1 when a particular floor is reached.


The circuit output is the “Door Open” signal, should be normally 0 but changes to 1 when the door is to open

Problem: Design a logic circuit for a three storey elevator.

M = Logic signal indicating if the elevator is moving (M = 1) or stationary (M = 0)

F1, F2 and F3 are the floor level signals, normally 0 but gets to 1 when a particular floor is reached.

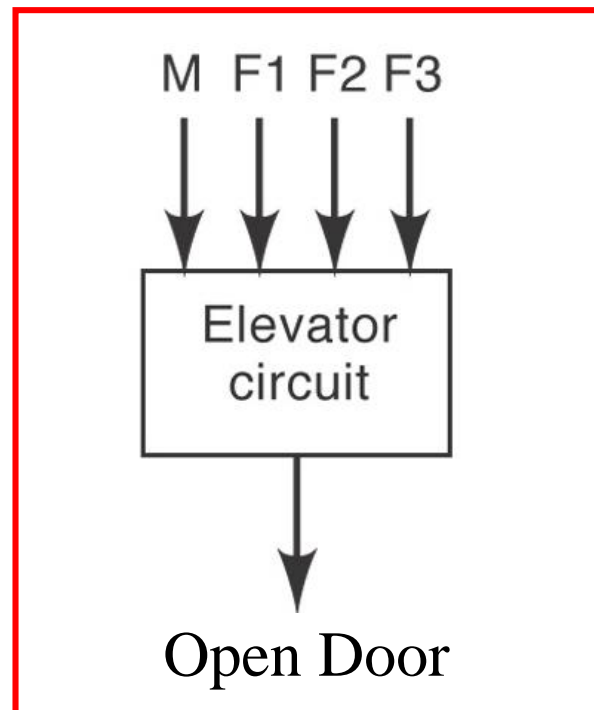The circuit output is the “Open Door” signal, should be normally 0 but changes to 1 when the door is to open.



Inputs

Output

M	F1	F2	F3	OPEN
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	X
0	1	0	0	1
0	1	0	1	X
0	1	1	0	X
0	1	1	1	X
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	X
1	1	0	0	0
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

Can only be on one floor at a time, only one floor input can be HI. The other floor inputs are then **don't care conditions**.

Use X to indicate the don't care conditions.

M	F1	F2	F3	OPEN
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	X
0	1	0	0	1
0	1	0	1	X
0	1	1	0	X
0	1	1	1	X
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	X
1	1	0	0	0
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

Can only be on one floor at a time, only one floor input can be HI. The other floor inputs are then don't care conditions.

Use X to indicate the don't care conditions.

$$\text{Open Door} = \overline{M}F1\overline{F2}\overline{F3} + \overline{M}F1F2\overline{F3} + \overline{M}F1\overline{F2}F3$$

$$\text{Open Door} = \overline{M}F_1\overline{F_2}F_3 + \overline{M}F_1\overline{F_2}\overline{F_3} + \overline{M}F_1F_2\overline{F_3}$$

		$\overline{F_2}\overline{F_3}$	$\overline{F_2}F_3$	F_2F_3	$F_2\overline{F_3}$
\overline{M}	$\overline{F_1}$	0	1	X	1
\overline{M}	F_1	1	X	X	X
M	F_1	0	X	X	X
M	$\overline{F_1}$	0	0	X	0

$$\text{Open Door} = \overline{M}\overline{F1}\overline{F2}\overline{F3} + \overline{M}\overline{F1}F2\overline{F3} + \overline{M}\overline{F1}F2F3$$

		$\overline{F2}\overline{F3}$	$\overline{F2}F3$	$F2F3$	$F2\overline{F3}$
$\overline{M}\overline{F1}$	0	1	1	1	
$\overline{M}F1$	1	1	1	1	
$M\overline{F1}$	0	0	0	0	
$MF1$	0	0	0	0	

M' F1 → (points to the red box)
 M' F2 → (points to the blue box)
 M' F3 → (points to the green box)

$$\text{Open Door} = \text{M' F1} + \text{M' F2} + \text{M' F3}$$

Week 6 Lecture 10b

- Karnaugh Map (K-Map)

- Course web page:

https://ecs.wgtn.ac.nz/Courses/XMUT101_2021T1/

- `kerese@ecs.vuw.ac.nz`