

ENGR 101

Engineering Technology

Dr. [Kerese Manueli](#)

School of Engineering and Computer Science
Victoria University of Wellington

Victoria
UNIVERSITY OF WELLINGTON
*Te Whare Wānanga
o te Ūpoko o te Ika a Māui*



CAPITAL CITY UNIVERSITY

Week 7 Lecture 12b

- Combinational circuit
- Assignment 2 – submit before midnight Monday
- Test 1 – Thursday 22 April (10:15 – 11:55am)

- Course web page:

https://ecs.wgtn.ac.nz/Courses/XMUT101_2021T1/

- `kerese@ecs.vuw.ac.nz`

Designing Combinational Logic Circuits

Design Procedure:

1. Set up truth table
2. Write AND term for each case where the output is HI
3. Write the SOP expression for the output
4. Simplify the expression
5. Implement the circuit

Designing Combinational Logic Circuits

Example 2:

Design a circuit which will perform addition for 2 binary digits (x and y).

1) Set up truth table

- Recall that for binary addition we have: $0 + 0 = 0$; $0 + 1 = 1$; $1 + 0 = 1$ and $1 + 1 = 0$ with a carry of 1

Inputs		Outputs	
x	y		
1st row →	0	0	
2nd row →	0	1	
3rd row →	1	0	
4th row →	1	1	

1) Set up truth table

- Recall that for binary addition we have: $0 + 0 = 0$; $0 + 1 = 1$; $1 + 0 = 1$ and $1 + 1 = 0$ with a carry of 1

Inputs		Outputs	
x	y	Sum	Carry
1st row →	0	0	0
2nd row →	0	1	0
3rd row →	1	1	0
4th row →	1	0	1

1) Set up truth table

2) Write AND term for each case where the output is HI

		Inputs		Outputs		
		x	y	Sum	Carry	
1st row	→	0	0	0	0	
2nd row	→	0	1	1	0	Sum = 1 → $x'y$
3rd row	→	1	0	1	0	Sum = 1 → xy'
4th row	→	1	1	0	1	Carry = 1 → xy

3) Write the SOP expression for the output

$$\text{Sum} = x'y + xy'$$

$$\text{Carry} = xy$$

4) Simplify the expression – using K-Map

$$\text{Sum} = x'y + xy'$$

	Y'	Y
X'		1
X	1	


$$\text{Carry} = xy$$

	Y'	Y
X'		
X		1

5) Implement circuit:

$$\text{Sum} = x'y + xy'$$



$$\text{Carry} = xy$$

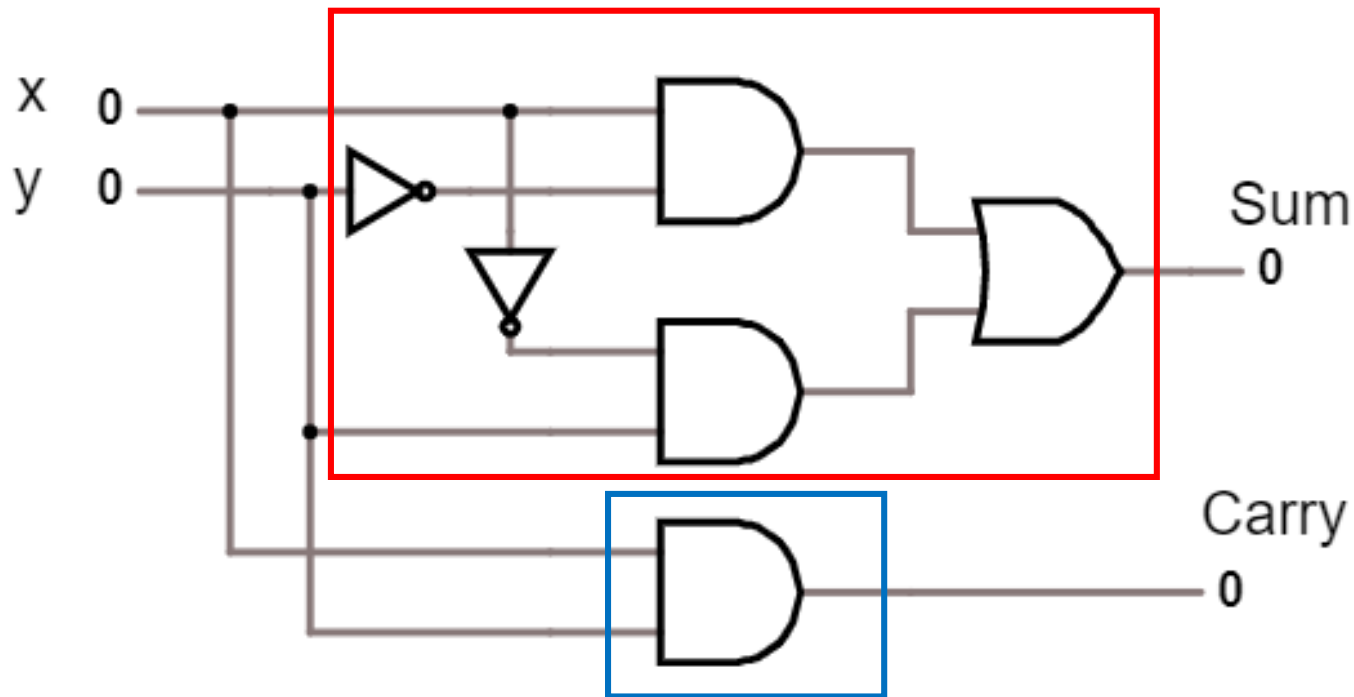

5) Implement circuit:

$$\text{Sum} = x'y + xy'$$

$$\text{Carry} = xy$$

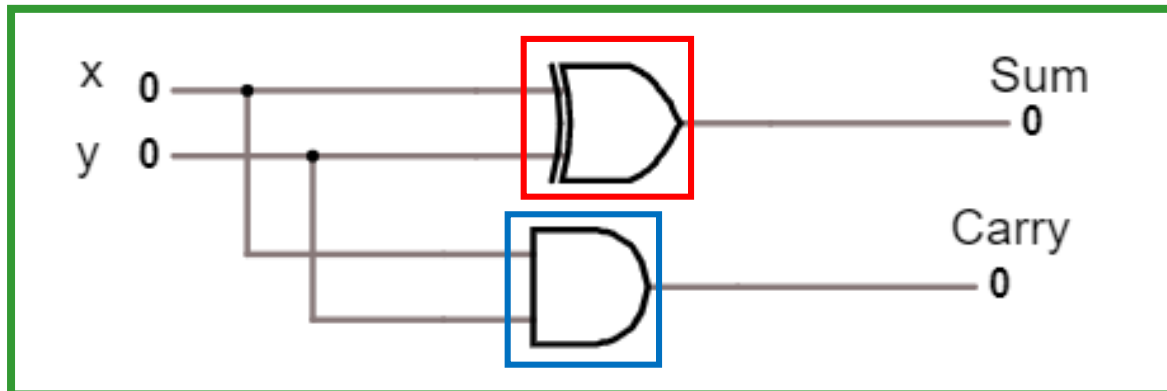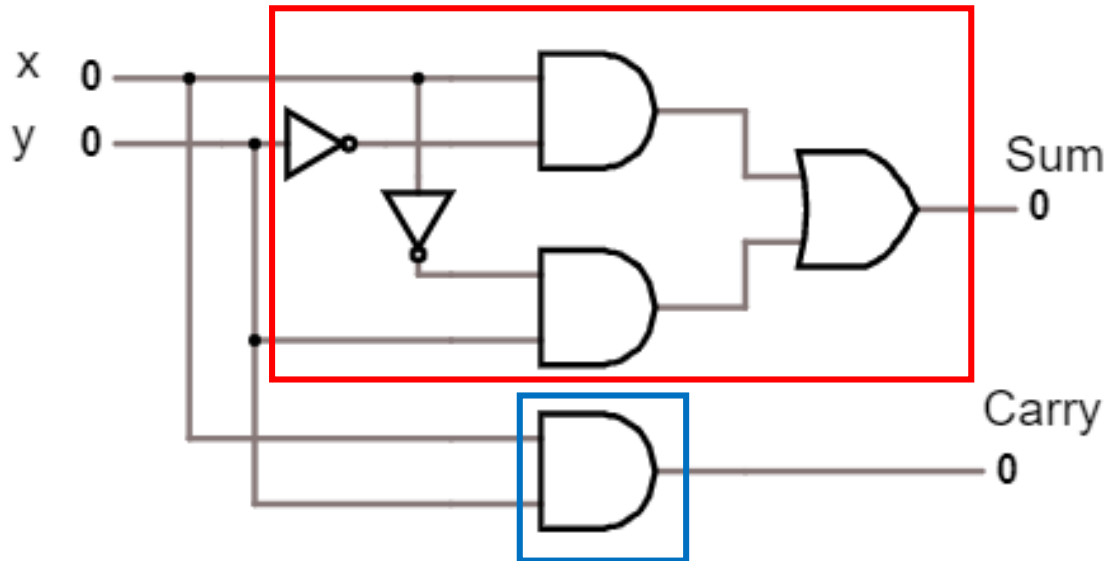

Designing Combinational Logic Circuits

Example 2:

Design a circuit which will perform addition for 3 binary digits (x, y and z).

1) Set up truth table

Example 3:

Design a circuit which will perform addition for 3 binary digits (x, y and z).

	Inputs			Outputs	
	x	y	z	Sum	Carry
1st row	0	0	0		
2nd row	0	0	1		
3rd row	0	1	0		
4th row	0	1	1		
	1	0	0		
	1	0	1		
	1	1	0		
	1	1	1		

1) Set up truth table

Example 3:

Design a circuit which will perform addition for 3 binary digits (x, y and z).

	Inputs			Outputs	
	x	y	z	Sum	Carry
1st row	0	0	0	0	0
2nd row	0	0	1	1	0
3rd row	0	1	0	1	0
4th row	0	1	1	0	1
5th row	1	0	0	1	0
6th row	1	0	1	0	1
7th row	1	1	0	0	1
8th row	1	1	1	1	1

1) Set up truth table

2) Write AND term for each case where the output is HI

Inputs			Outputs		
x	y	z	Sum	Carry	
0	0	0	0	0	
2nd row	0	0	1	0	$x'y'z$
3rd row	0	1	0	0	$x'yz'$
4th row	0	1	1	1	$x'yz$
5th row	1	0	0	1	$xy'z'$
6th row	1	0	1	0	$xy'z$
7th row	1	1	0	1	xyz'
8th row	1	1	1	1	xyz

3) Write the SOP expression for the output

$$\text{Sum} = x'y'z + x'yz' + xy'z' + xyz$$

$$\text{Carry} = x'yz + xy'z + xyz' + xyz$$

4) Simplify the expression – using K-Map

$$\text{Sum} = x'y'z + x'yz' + xy'z' + xyz$$

	z'	z
x'y'		1
x'y	1	
xy		1
xy'	1	

$$\text{Sum} = z'(xy' + x'y) + z(xy' + x'y)$$

$$\text{Carry} = x'yz + xy'z + xyz' + xyz$$


	z'	z
x'y'		
x'y		1
xy	1	1
xy'		1

$$\text{Carry} = xy + yz + xz$$

5) Implement circuit:

$$\text{Sum} = z'(xy' + x'y) + z(xy' + x'y)'$$

$$\text{Carry} = xy + yz + xz$$

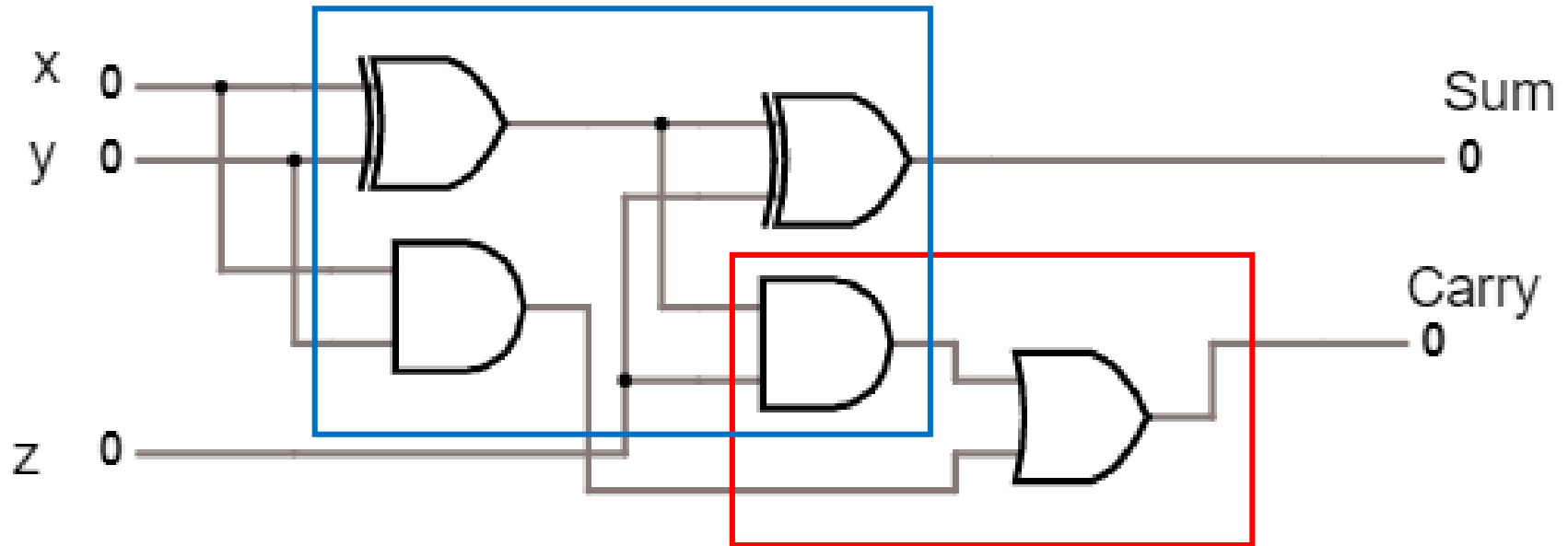

Week 7 Lecture 12b

- Combinational circuit
- Assignment 2 – submit before midnight Monday
- Course web page:

https://ecs.wgtn.ac.nz/Courses/XMUT101_2021T1/

- `kerese@ecs.vuw.ac.nz`