

# **ENGR 101**

# **Engineering Technology**

A/Prof. Paweł Dmochowski

School of Engineering and Computer Science  
Victoria University of Wellington



CAPITAL CITY UNIVERSITY

# Week 15


---

- Circuit simulator

<https://www.falstad.com/circuit/>

# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

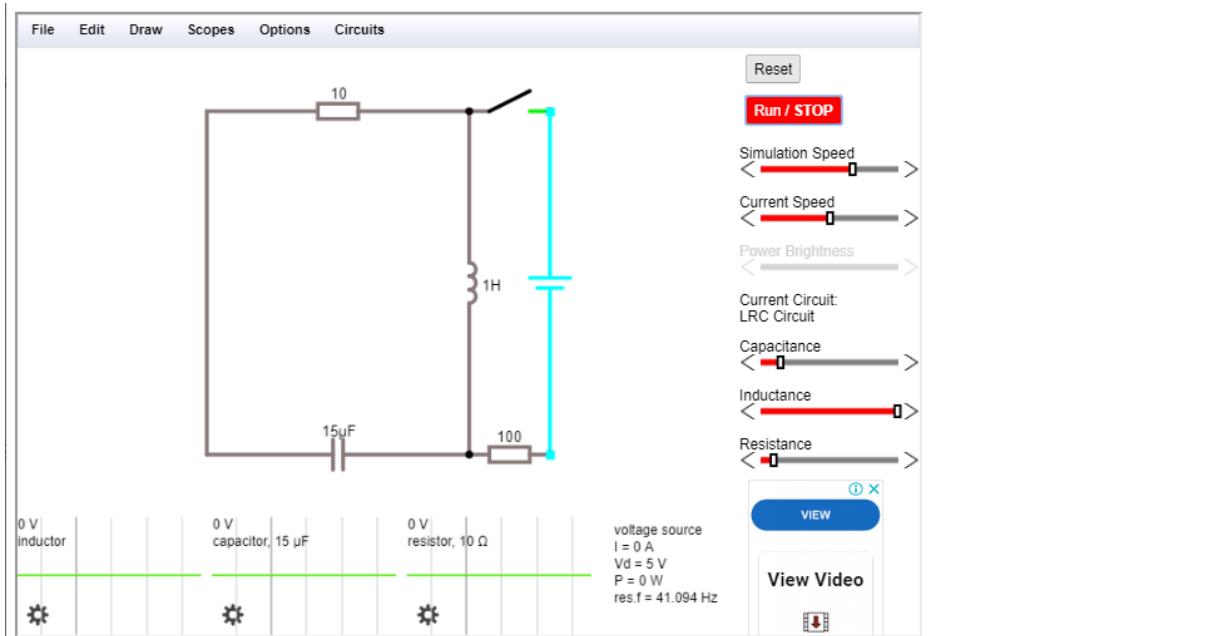

This is an electronic circuit simulator. When the applet starts up you will see an animated schematic of a simple LRC circuit. The green color indicates positive voltage. The gray color indicates ground. A red color indicates negative voltage. The moving yellow dots indicate current.

To turn a switch on or off, just click on it. If you move the mouse over any component of the circuit, you will see a short description of that component and its current state in the lower right corner of the window. To modify a component, move the mouse over it, click the right mouse button (or control-click if you have a Mac) and select "Edit".

The "Circuits" menu contains a lot of sample circuits for you to try.

[Full Screen version.](#)

[Directions.](#)

[Standalone \(offline\) version for Mac, and for Windows.](#)

[Index of Circuit Examples. \(Polish version\)](#)

[More applets.](#)

Javascript version. [Latest changes here](#), including [subcircuits](#).


[Report a problem/feature request](#)

Huge thanks to [Iain Sharp](#) for the Javascript port. You can still use the [original Java version](#). More acknowledgements in the about box.

Standalone  
version



<https://www.falstad.com/circuit/>

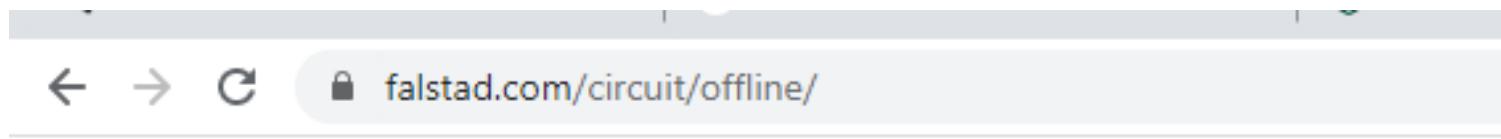

## Index of /circuit/offline

<u>Name</u>	<u>Last modified</u>	<u>Size</u>	<u>Description</u>
-------------	----------------------	-------------	--------------------

---


 <a href="#">Parent Directory</a>	-		
 <a href="#">CircuitJS1-mac.dmg</a>	2021-03-09 17:05	89M	
 <a href="#">circuitjs1-linux64.tgz</a>	2021-03-09 17:07	83M	
 <a href="#">circuitjs1-win.zip</a>	2021-03-09 17:08	76M	

---

Standalone versions

# Drawing Logic Circuits using on-line simulator


<https://www.falstad.com/circuit/>

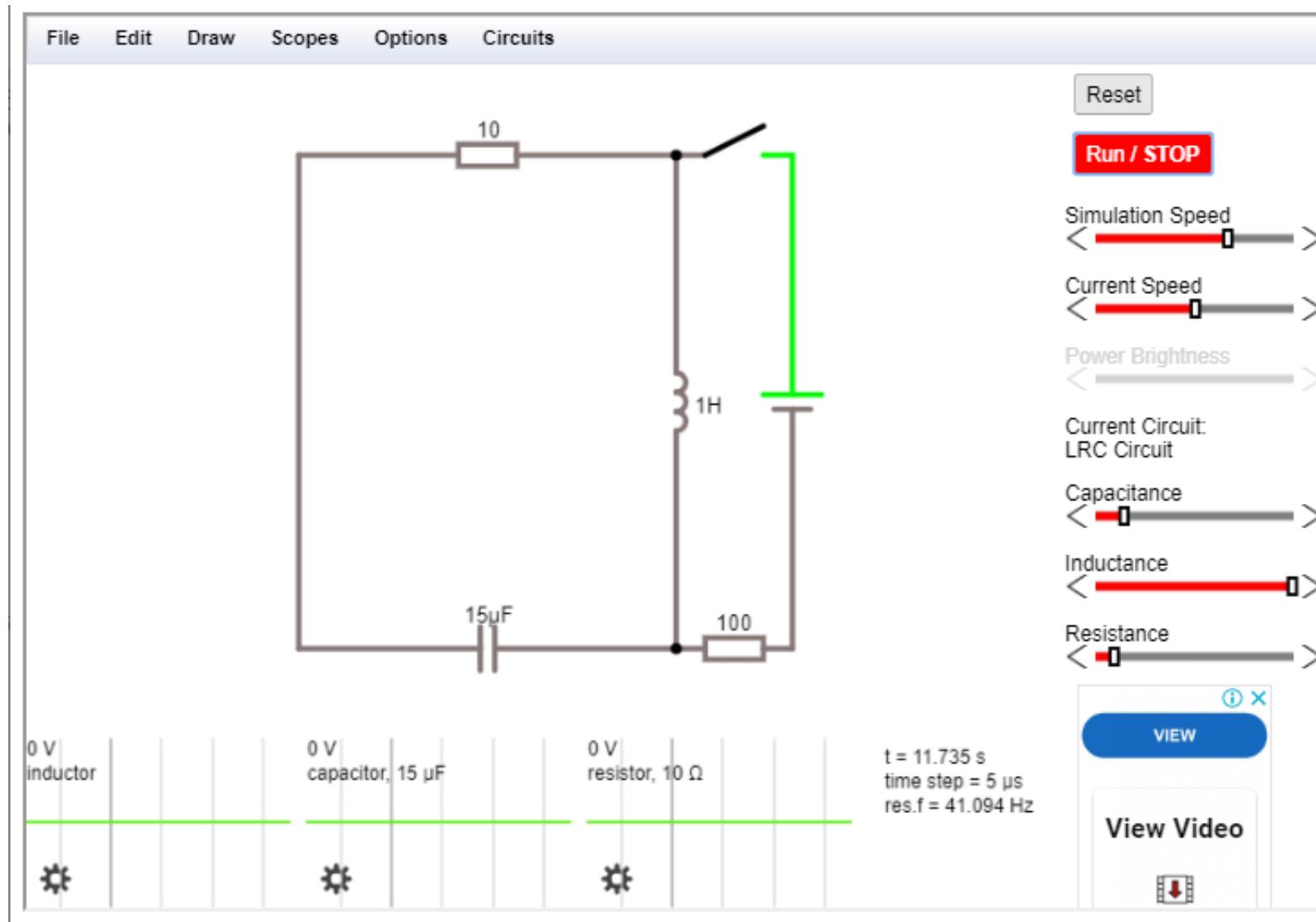

# Drawing Logic Circuits using on-line simulator


<https://www.falstad.com/circuit/>

1. Click on the Circuits drop-down menu

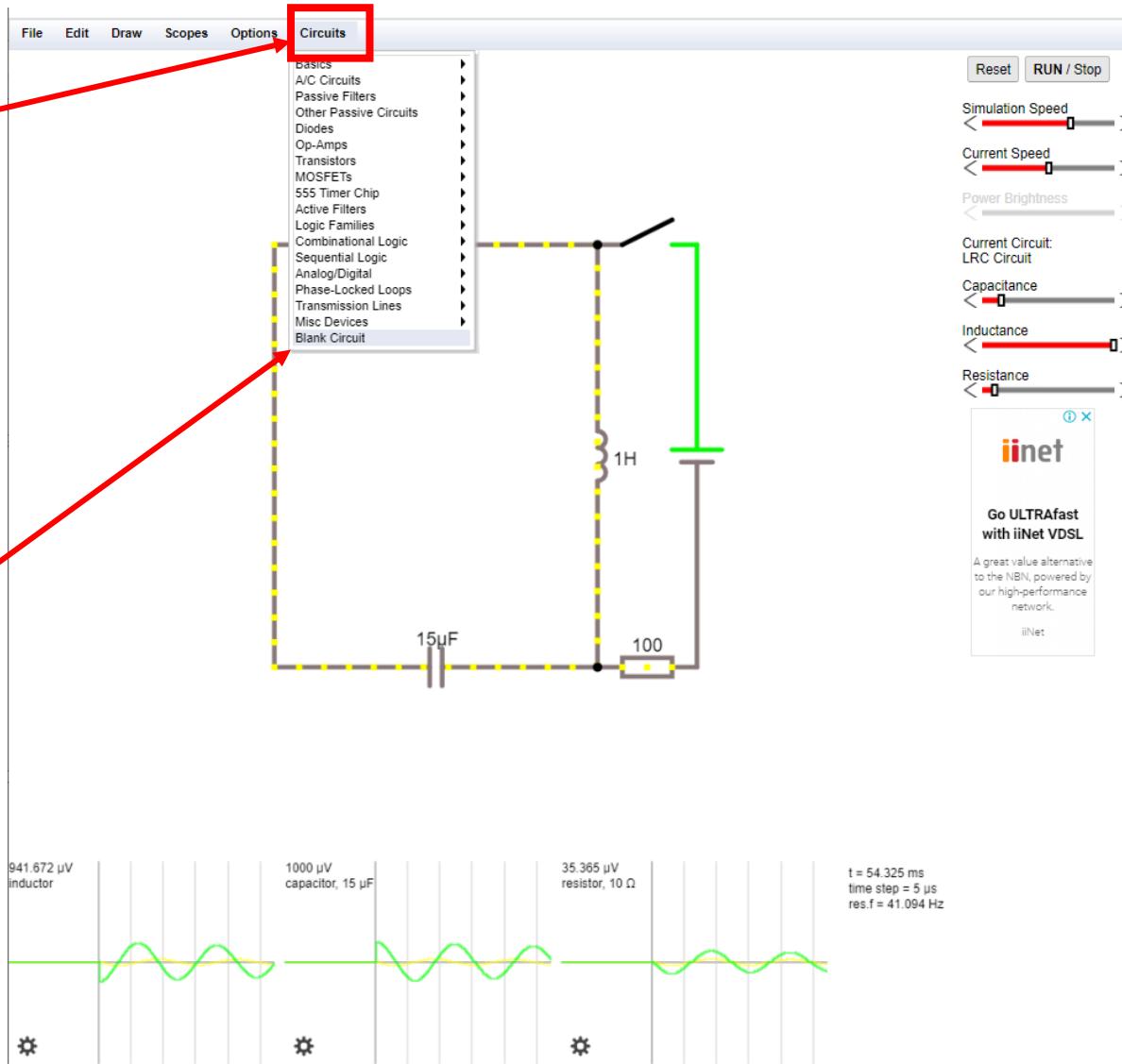

# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

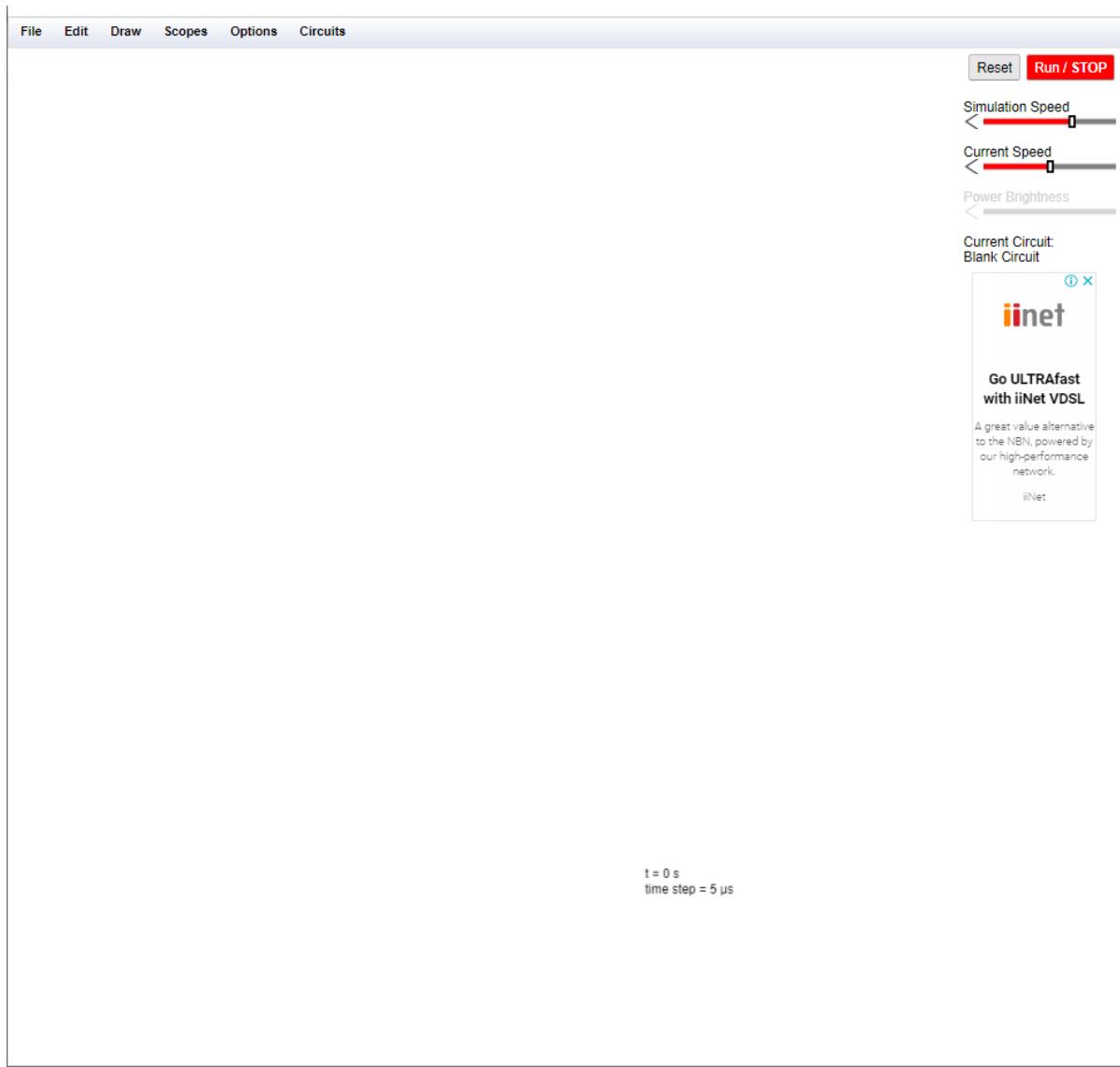

# Drawing Logic Circuits using on-line simulator

Esc (Escape)  
button




# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

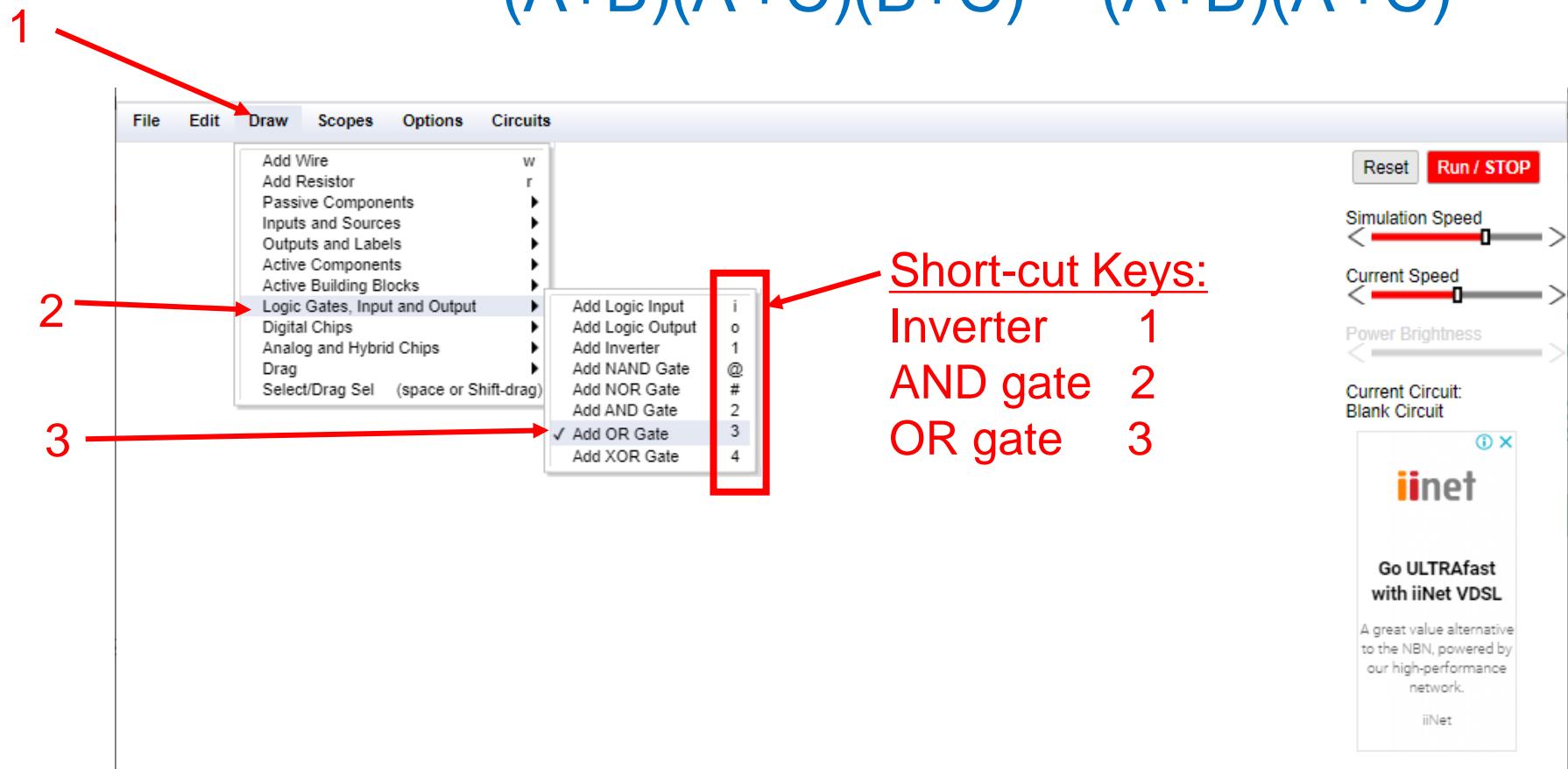


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

1

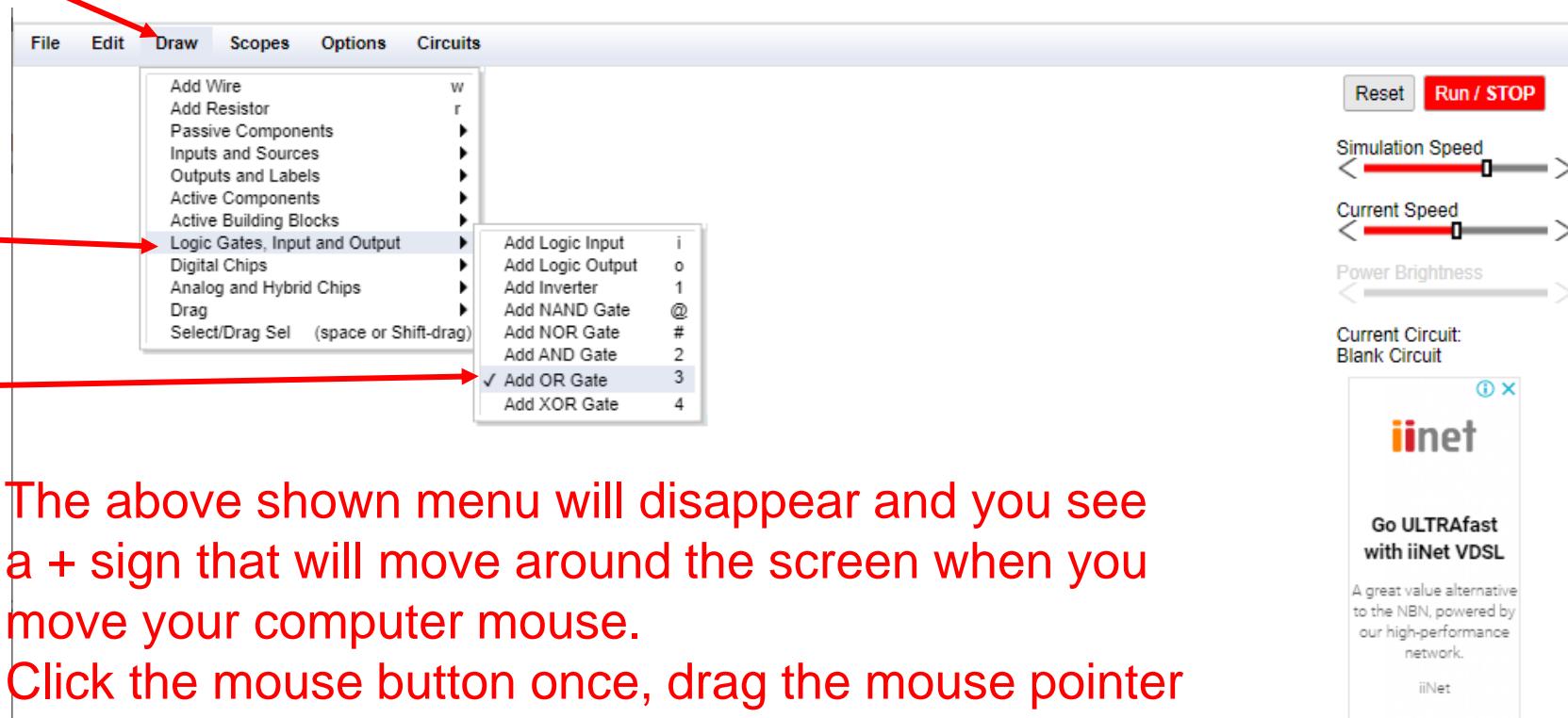


4. The above shown menu will disappear and you see a + sign that will move around the screen when you move your computer mouse.
5. Click the mouse button once, drag the mouse pointer and release the mouse button to draw the OR gate

# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

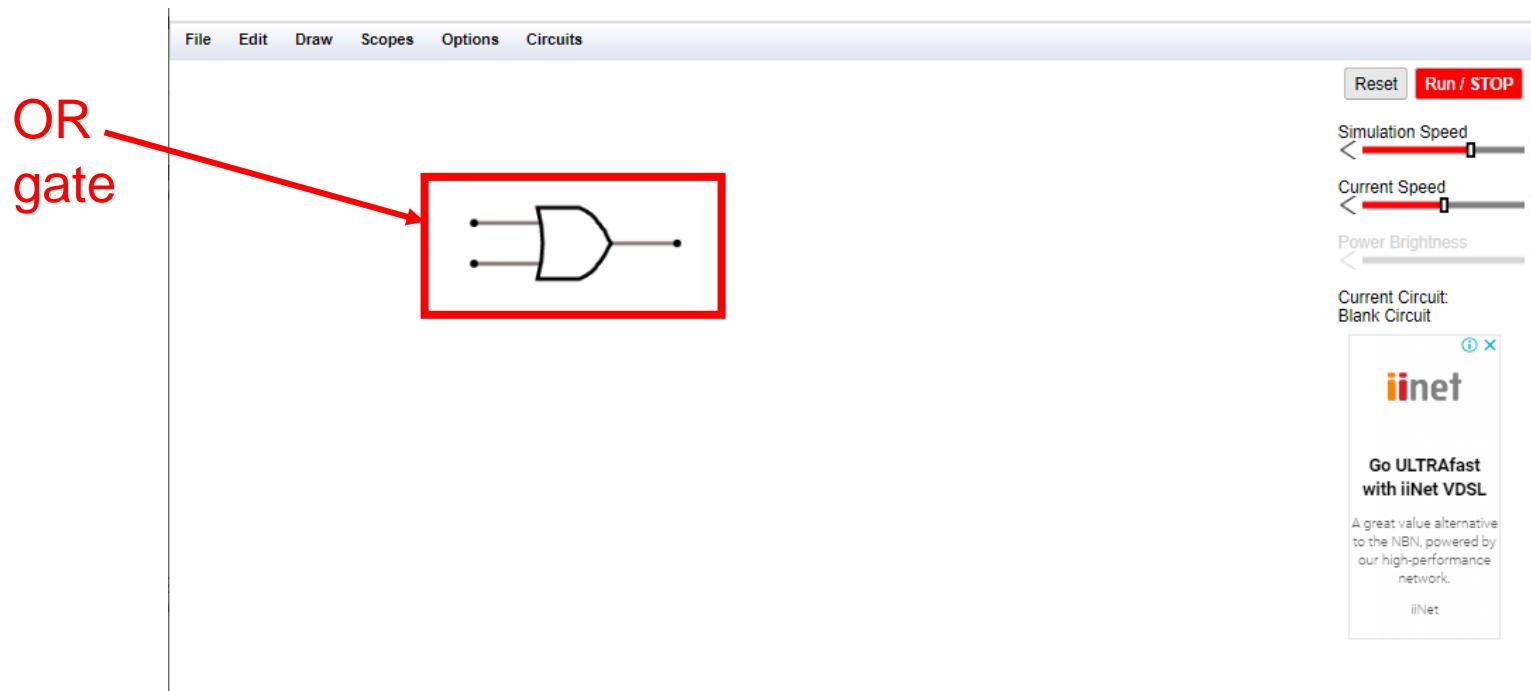


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$$

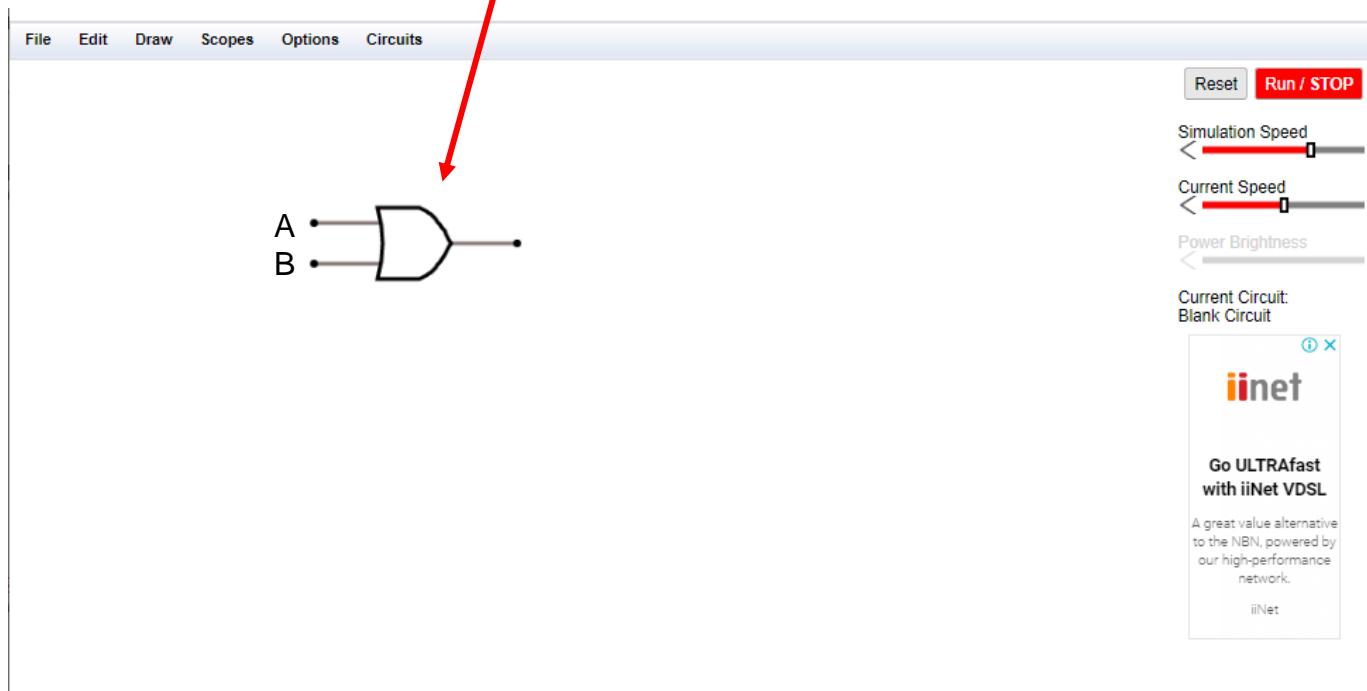


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

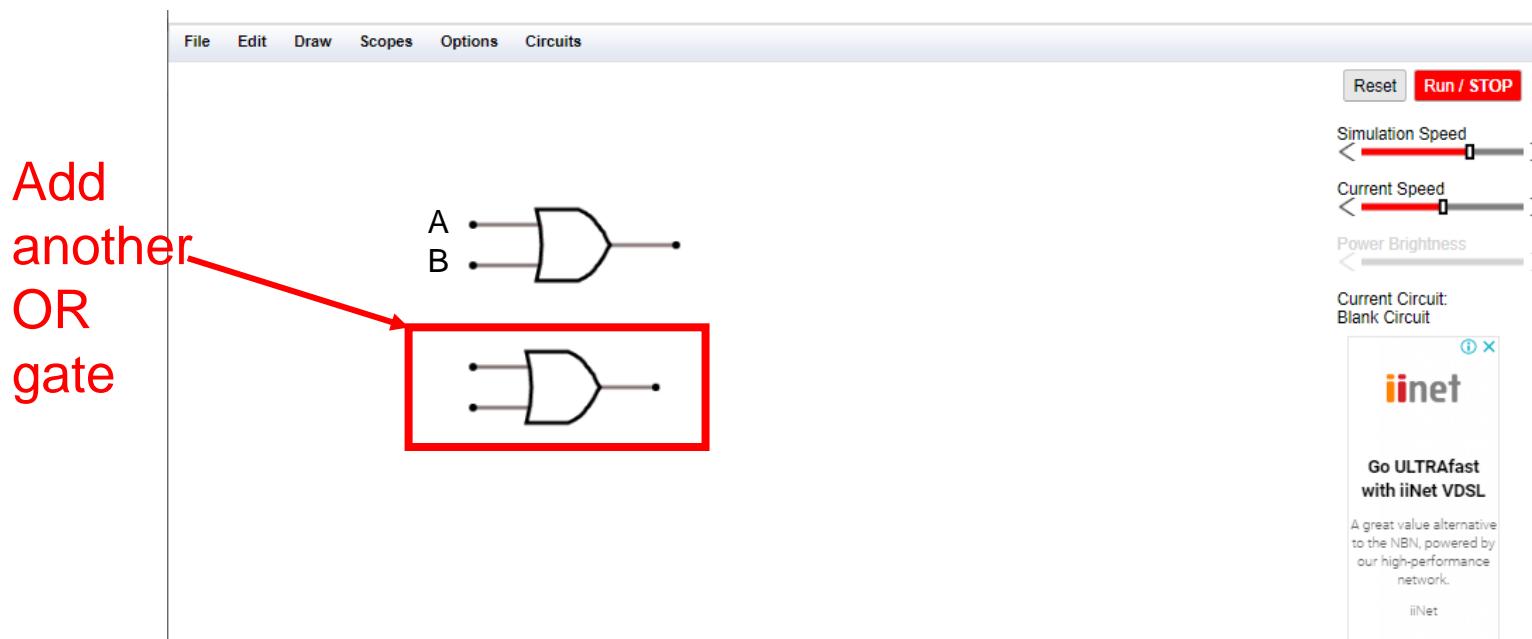

Add  
another  
OR  
gate


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

Add an  
INVERTER

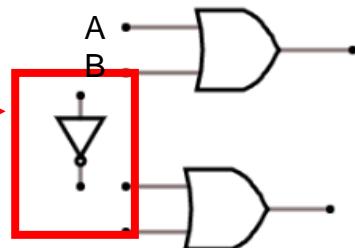

INVERTER  
to obtain A'

Reset Run / STOP

Simulation Speed < >

Current Speed < >

Power Brightness < >

Current Circuit: Blank Circuit

iinet

Go ULTRAfast with iiNet VDSL

A great value alternative to the NBN, powered by our high-performance network.


iiNet

# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$


1  
 $(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

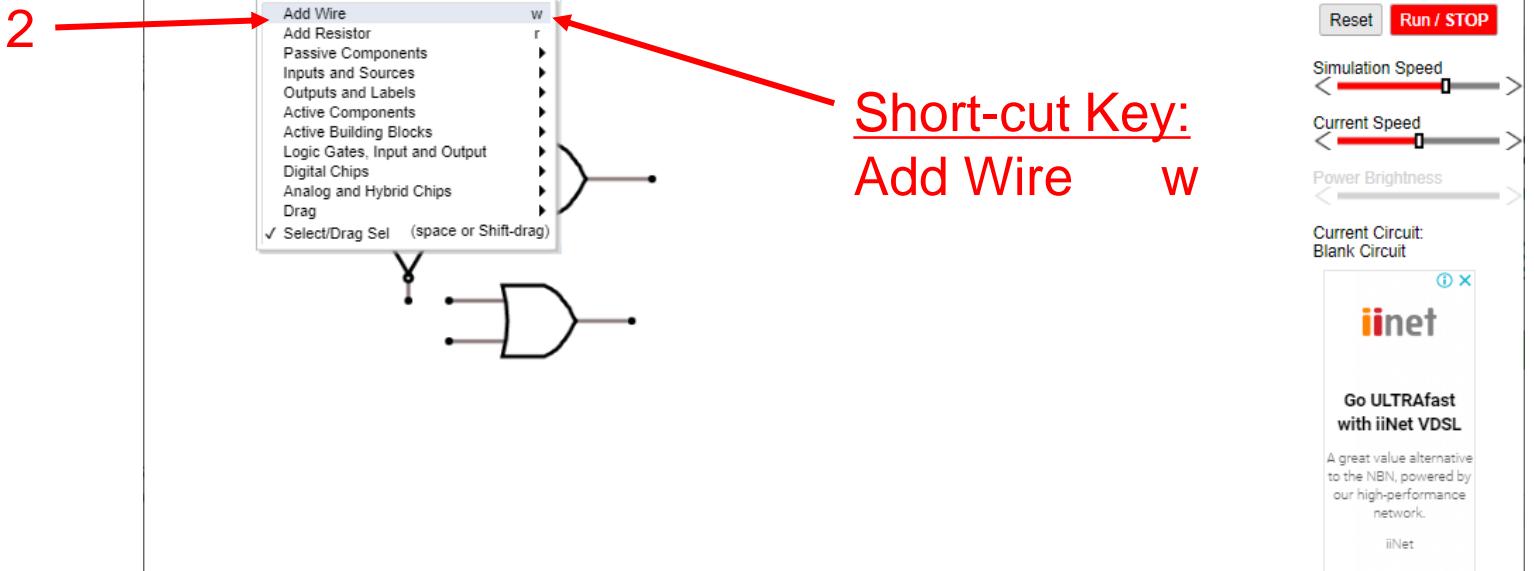

# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

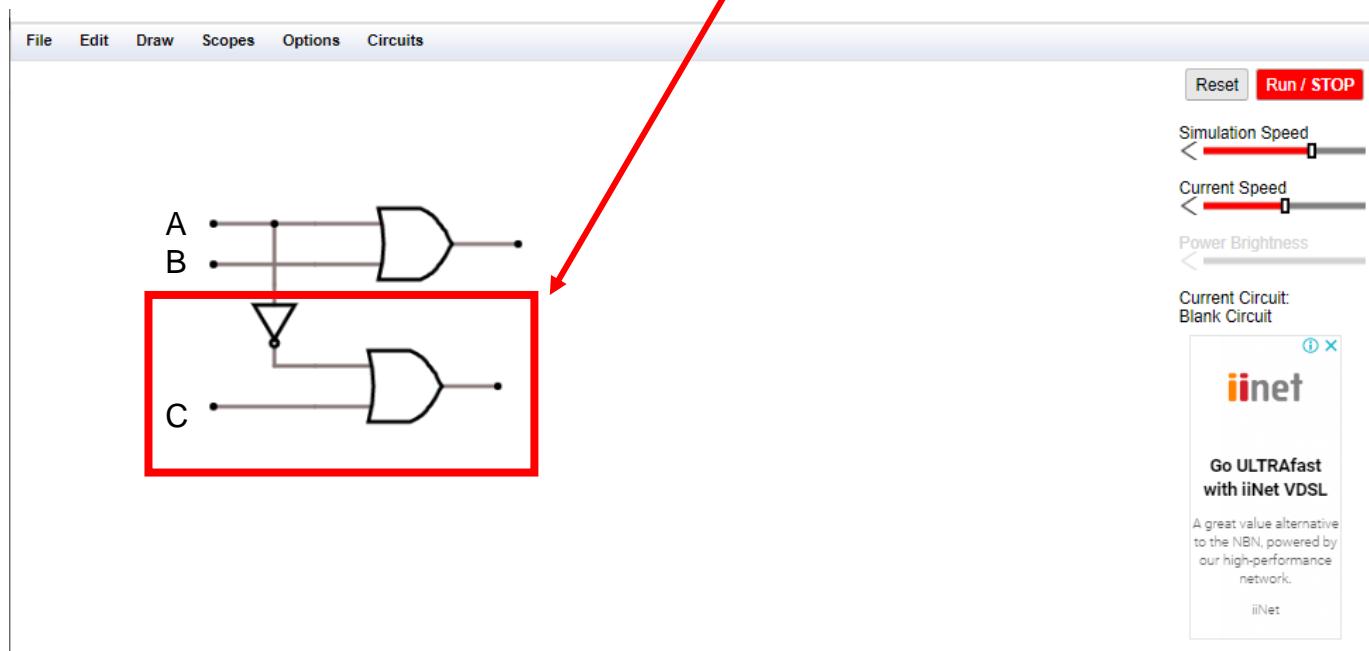Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$   
 $(A+B)(A'+C)(B+C) = (A+B)(A'+C)$




# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

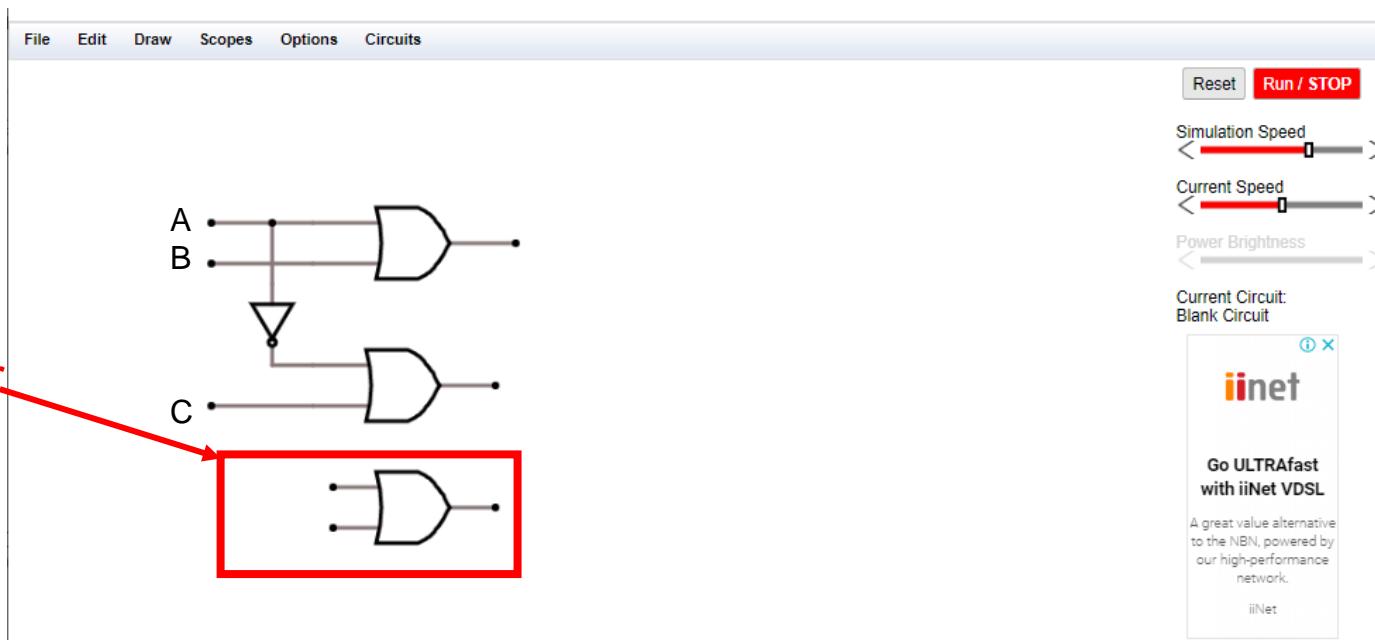


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

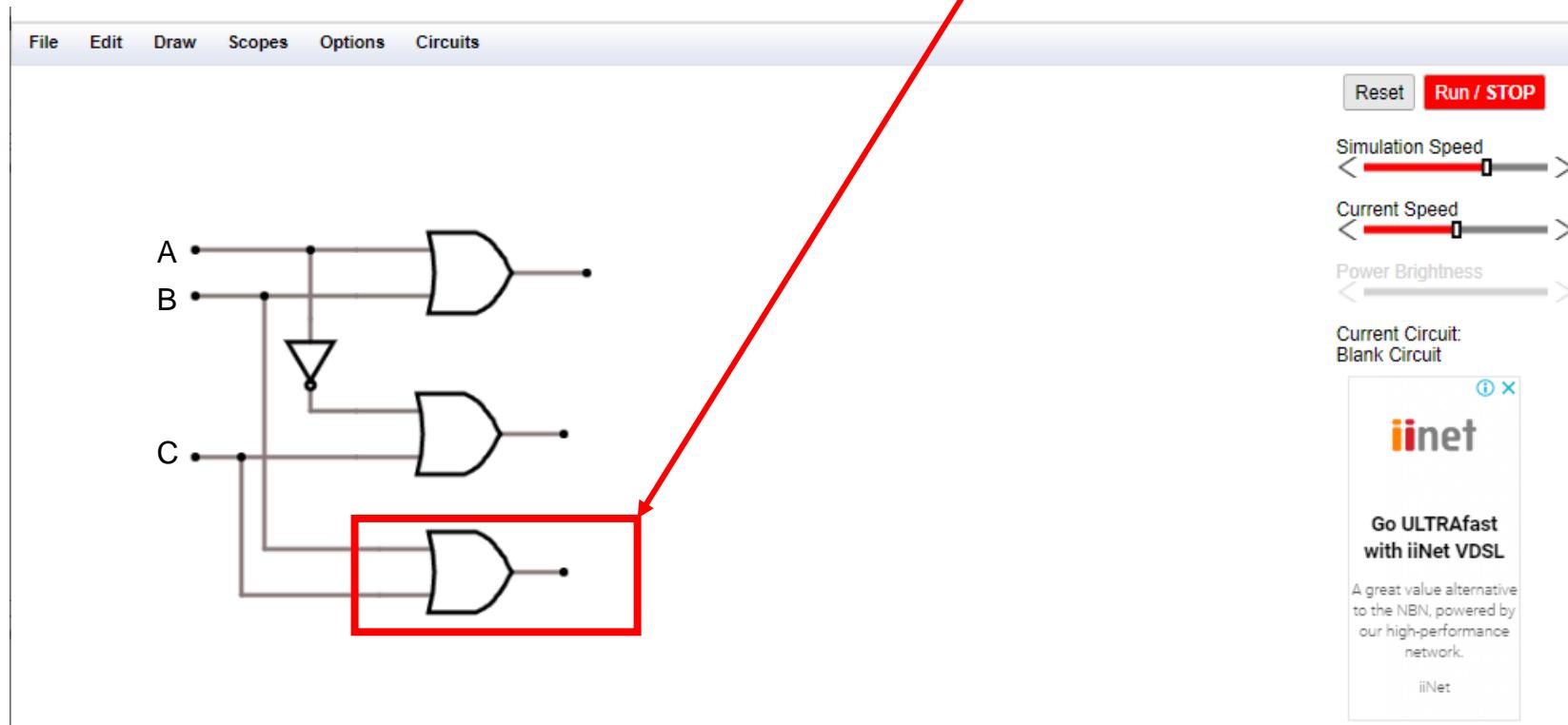


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

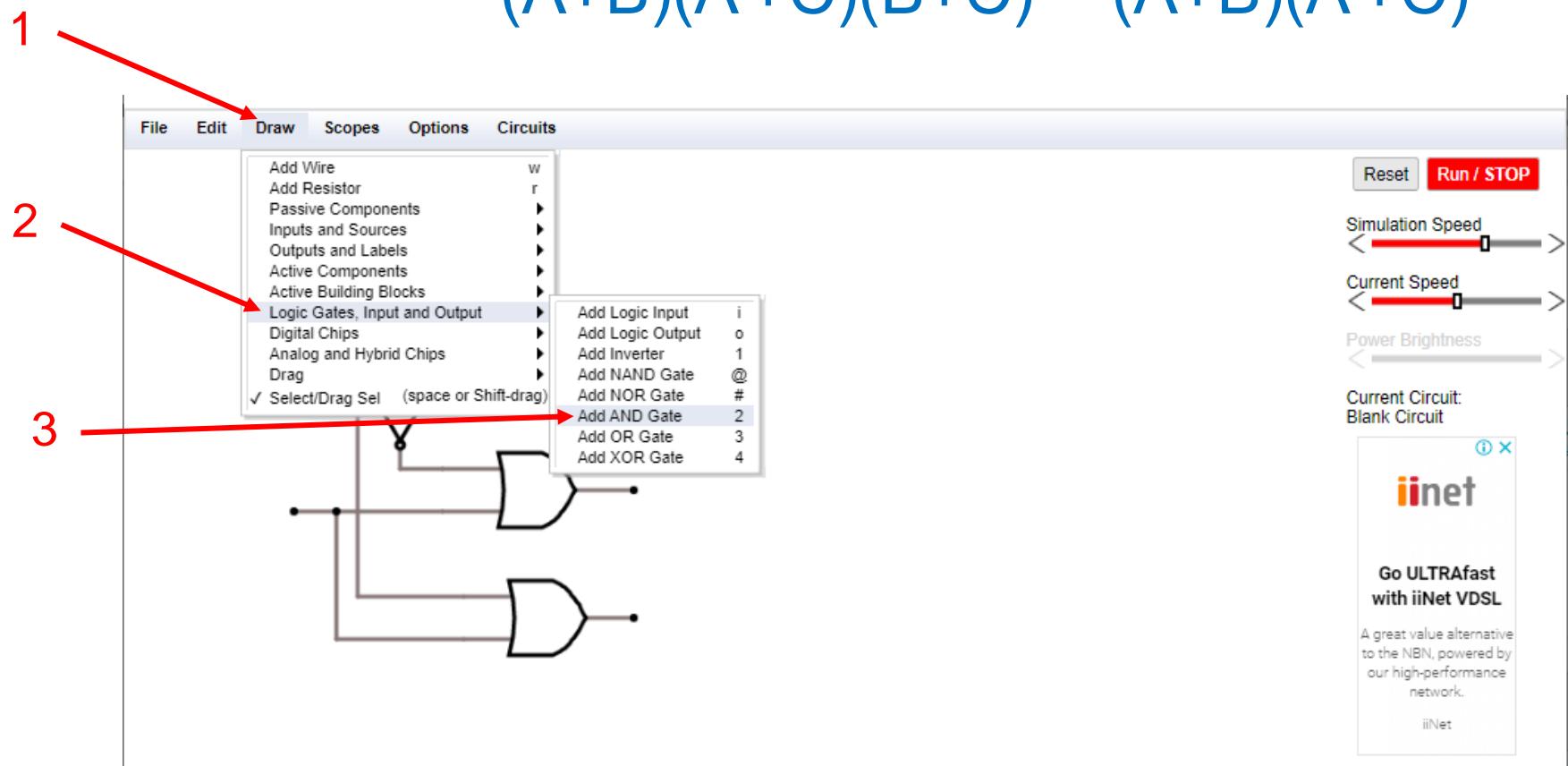


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$


$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

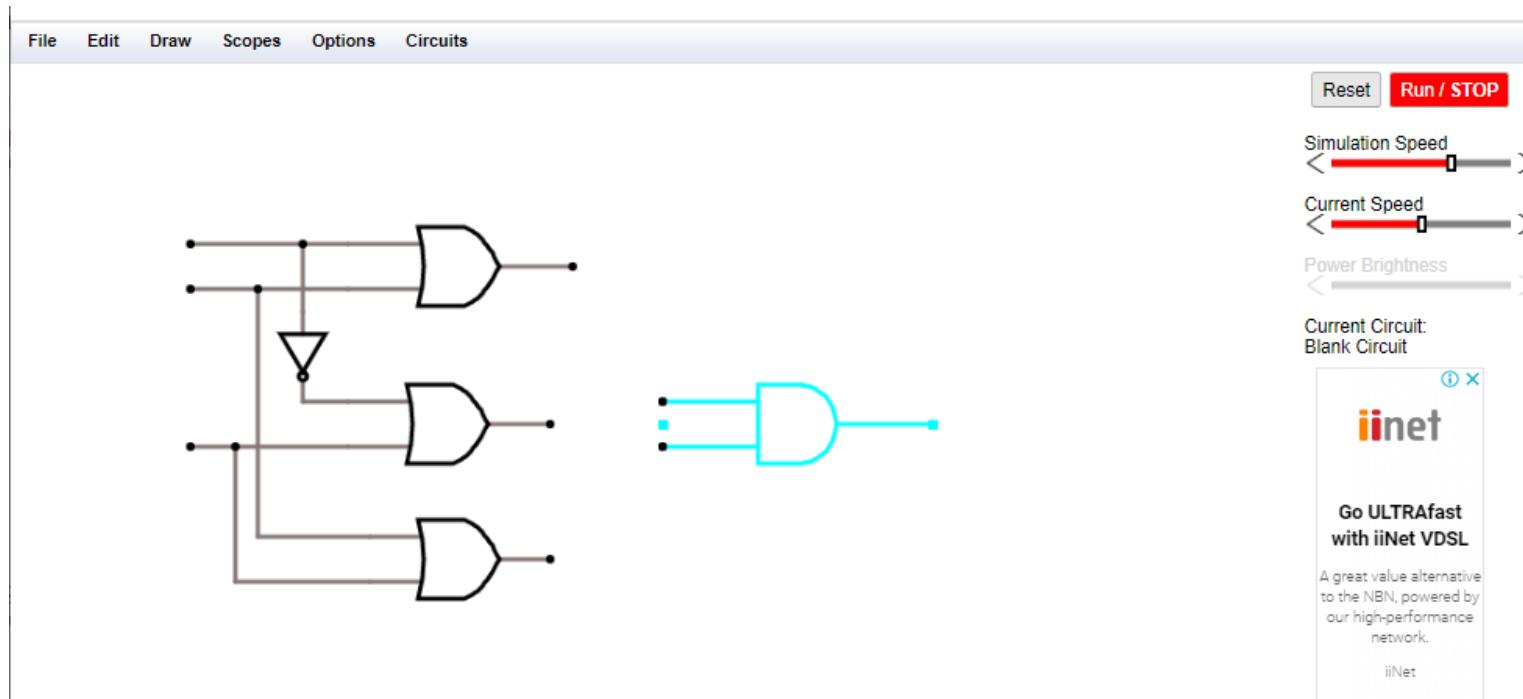

# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

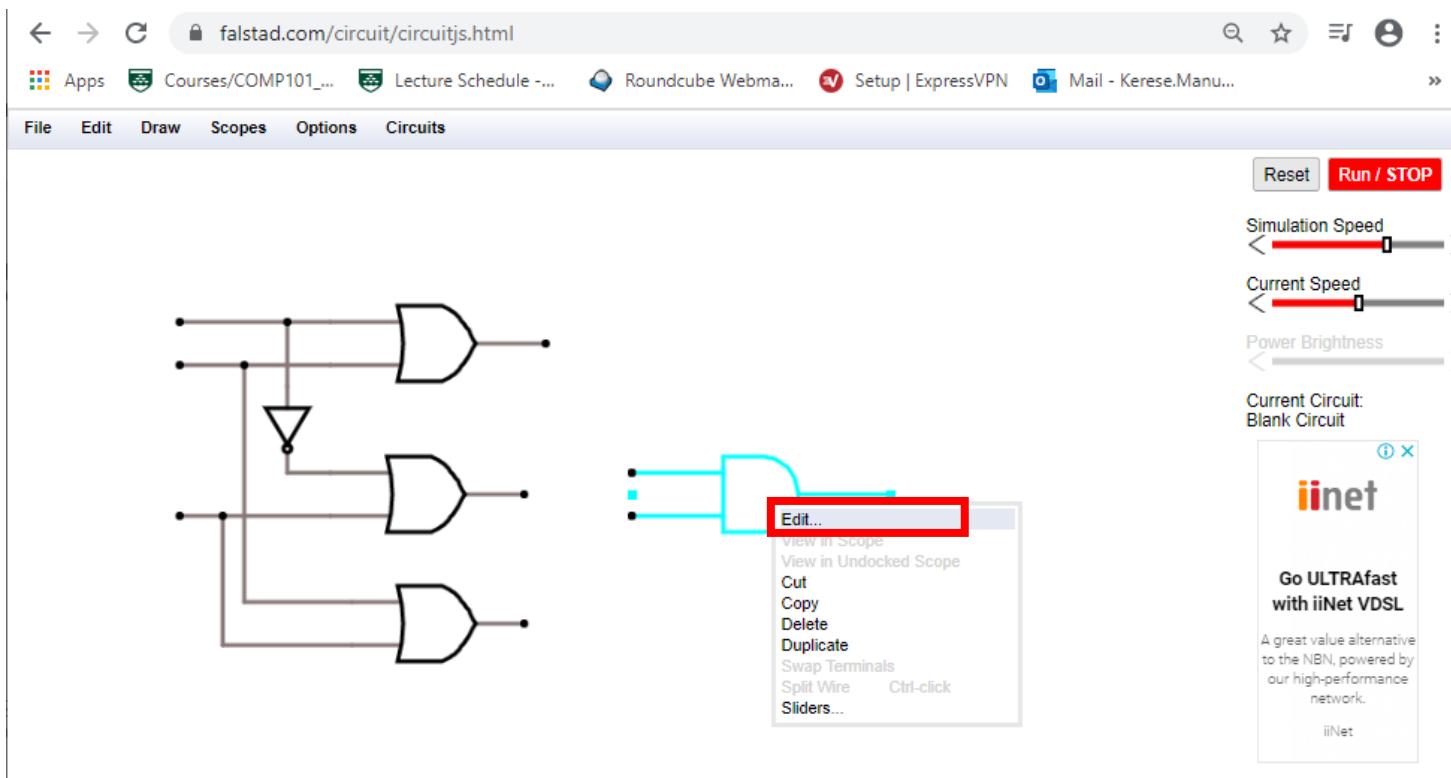Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$   
 $(A+B)(A'+C)(B+C) = (A+B)(A'+C)$




# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

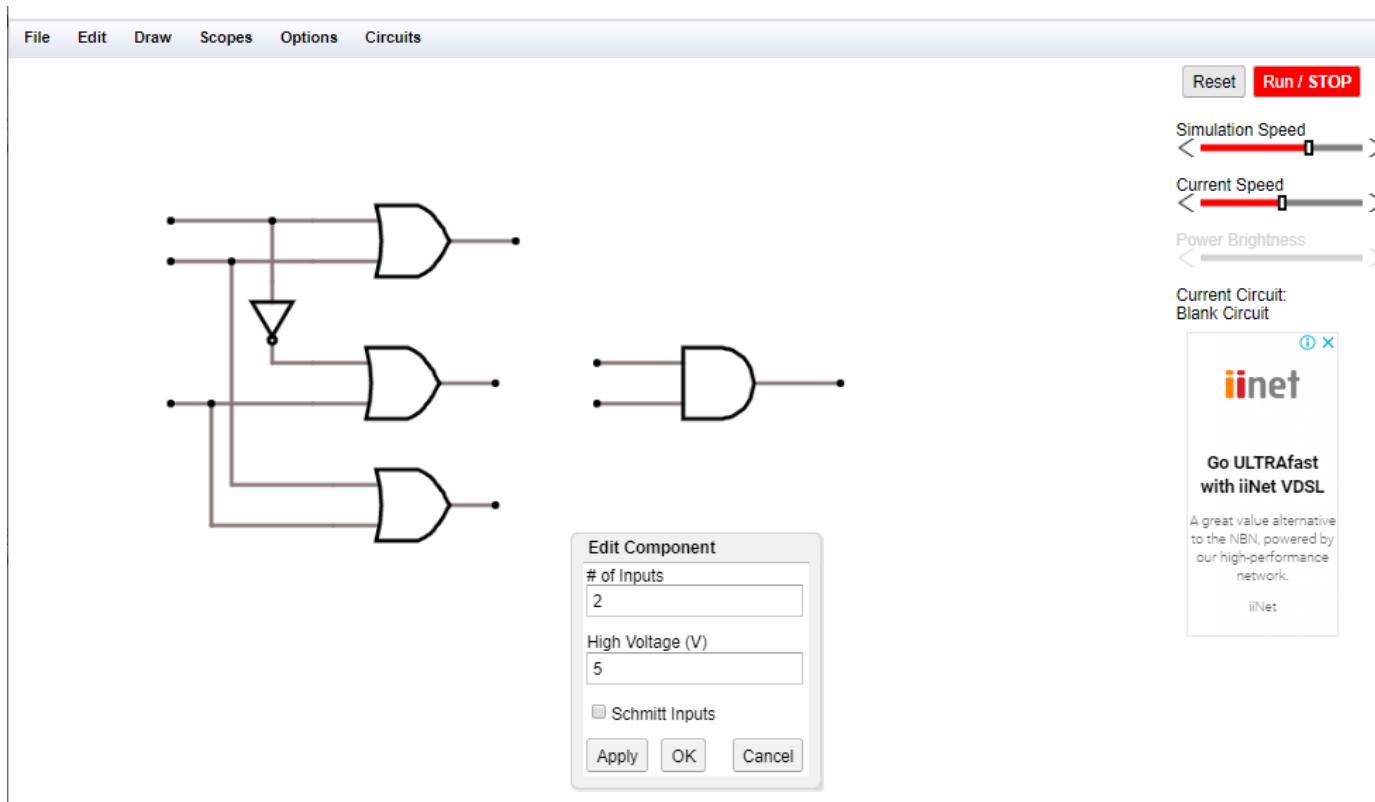


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

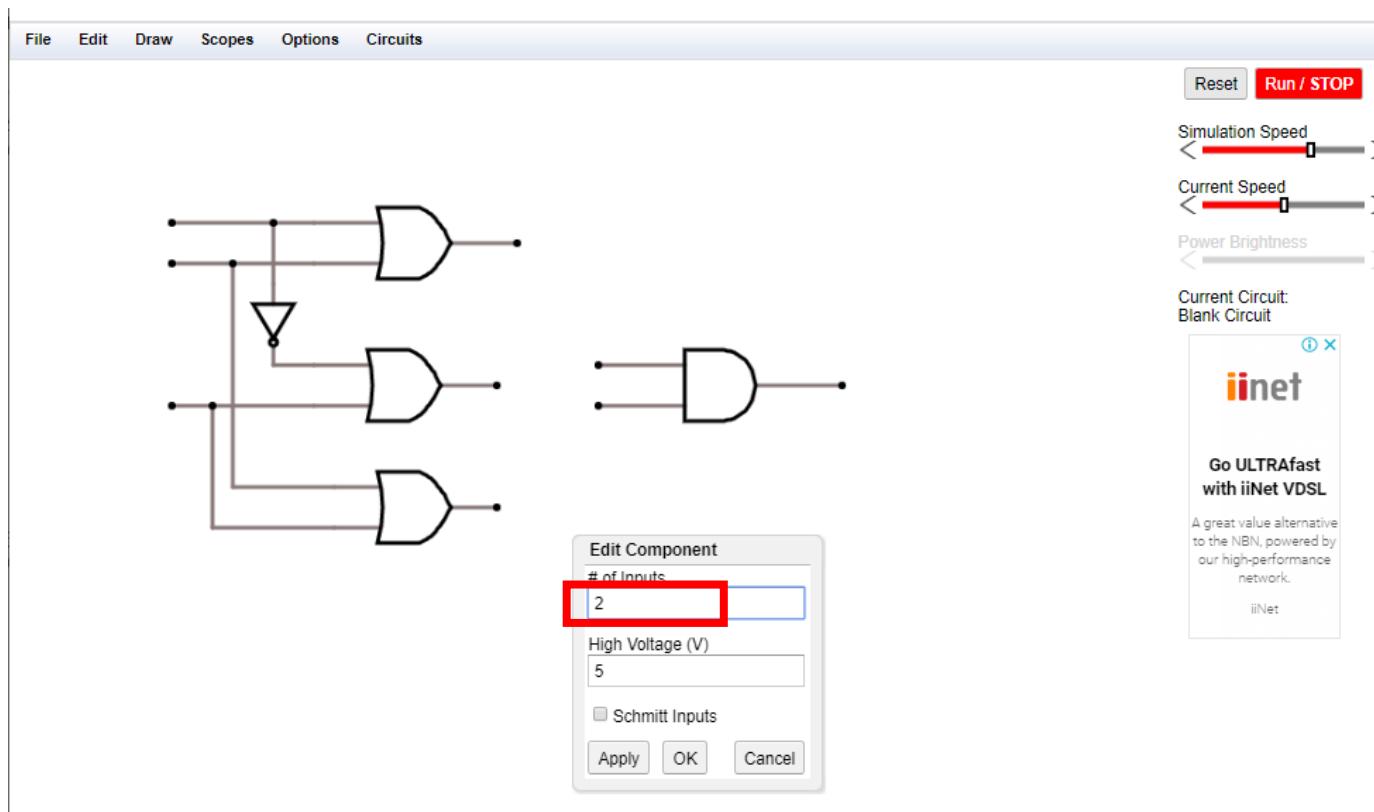


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

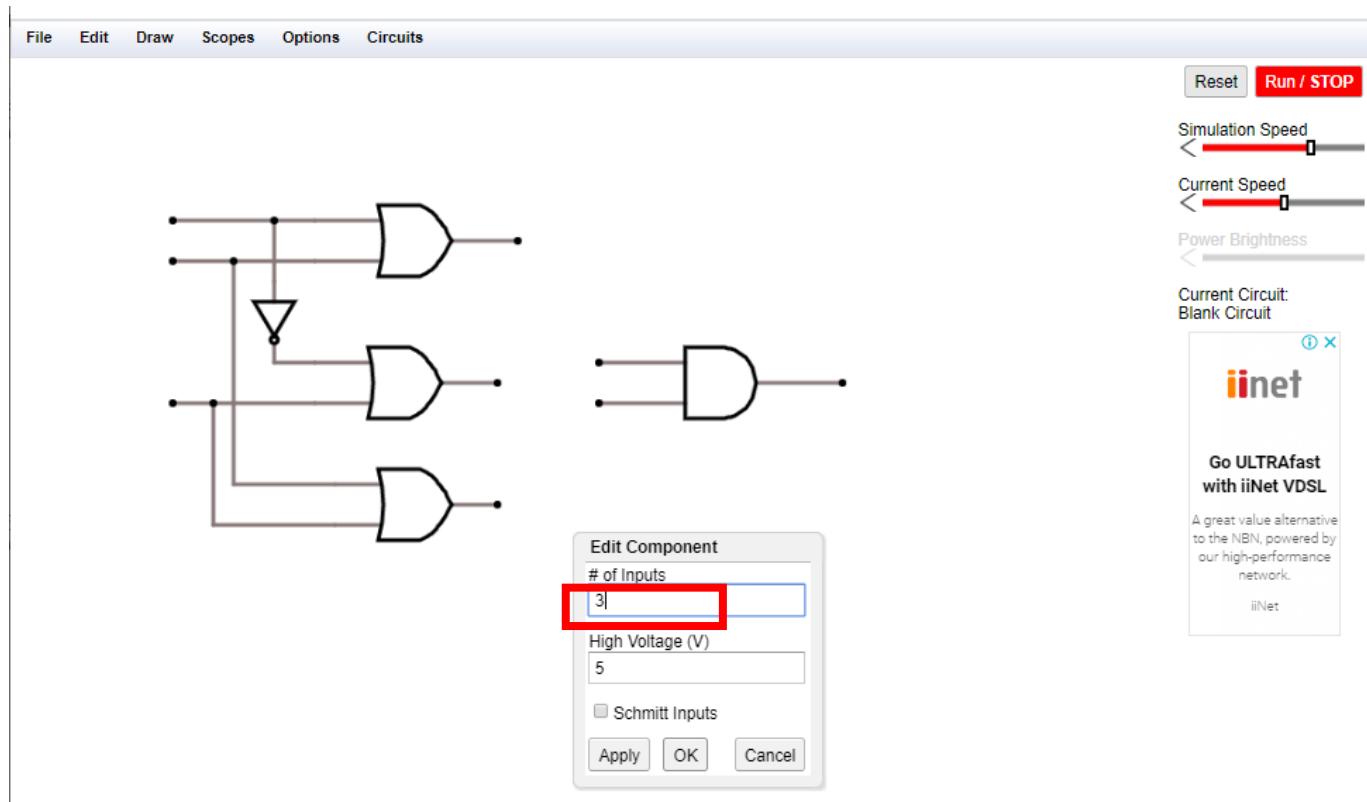


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

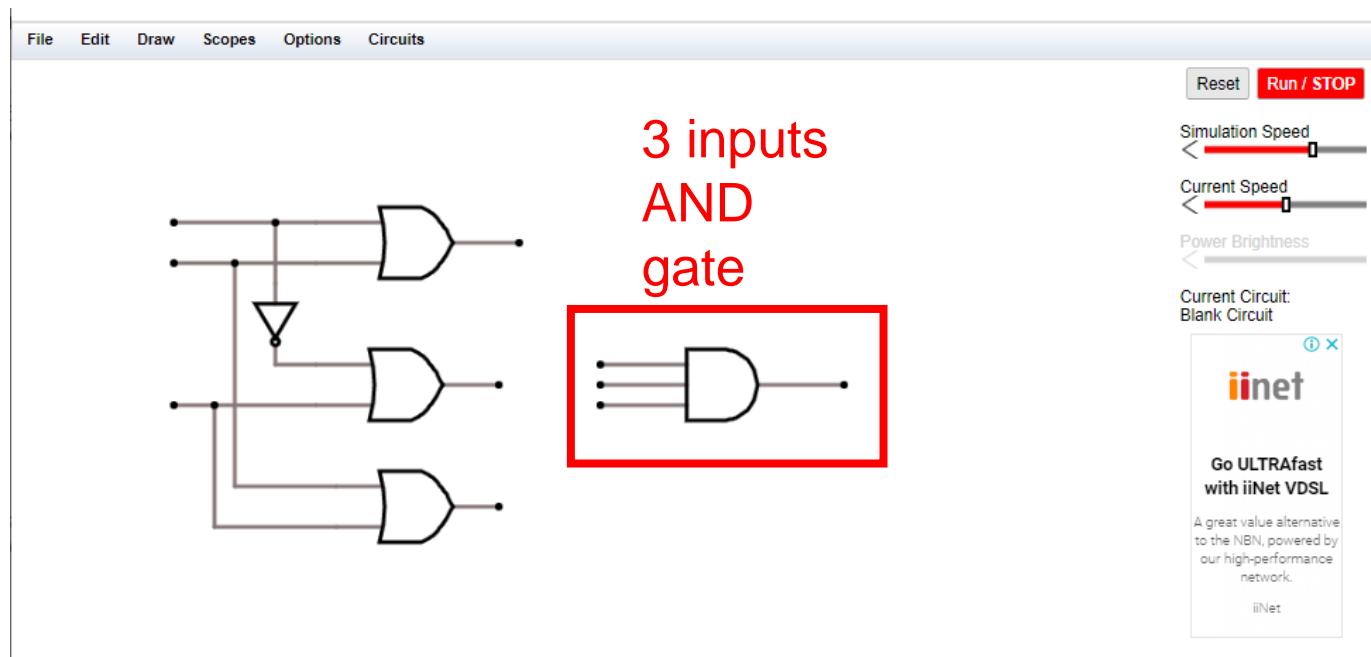


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

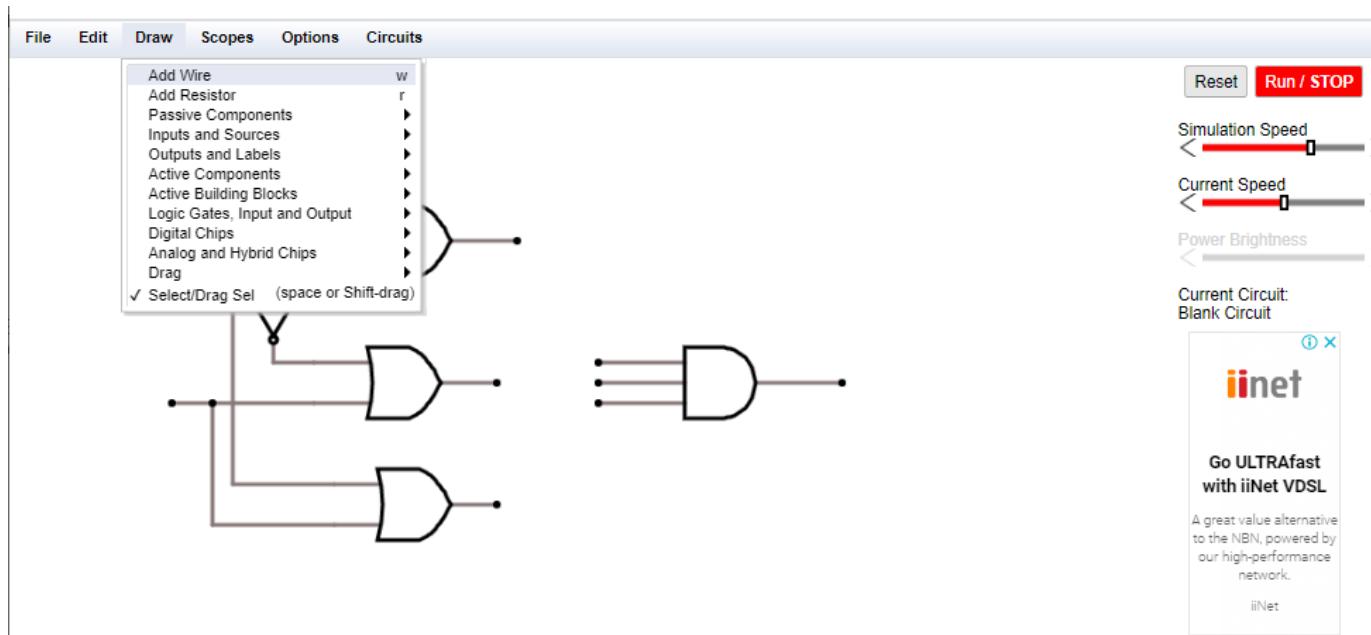


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$$

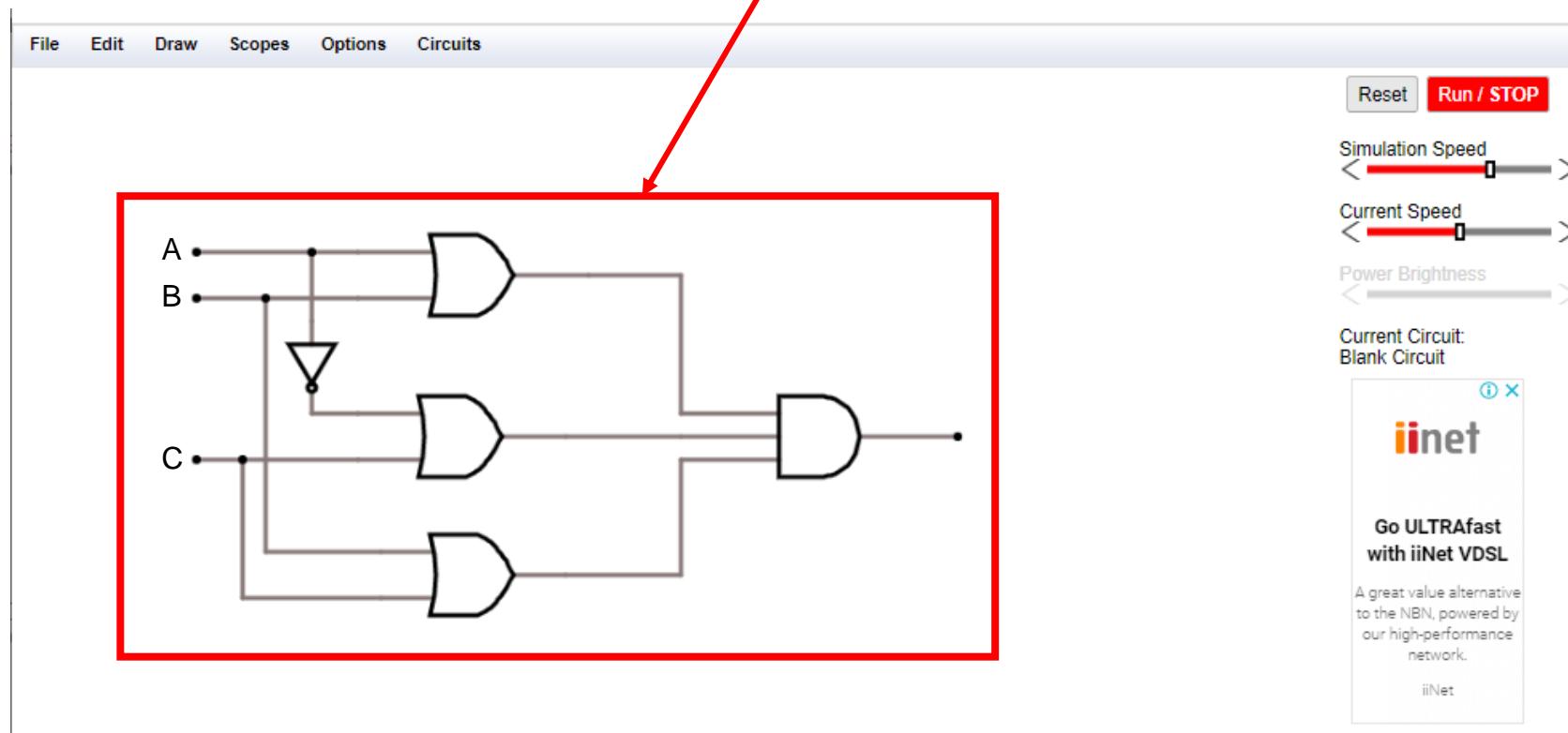


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$$

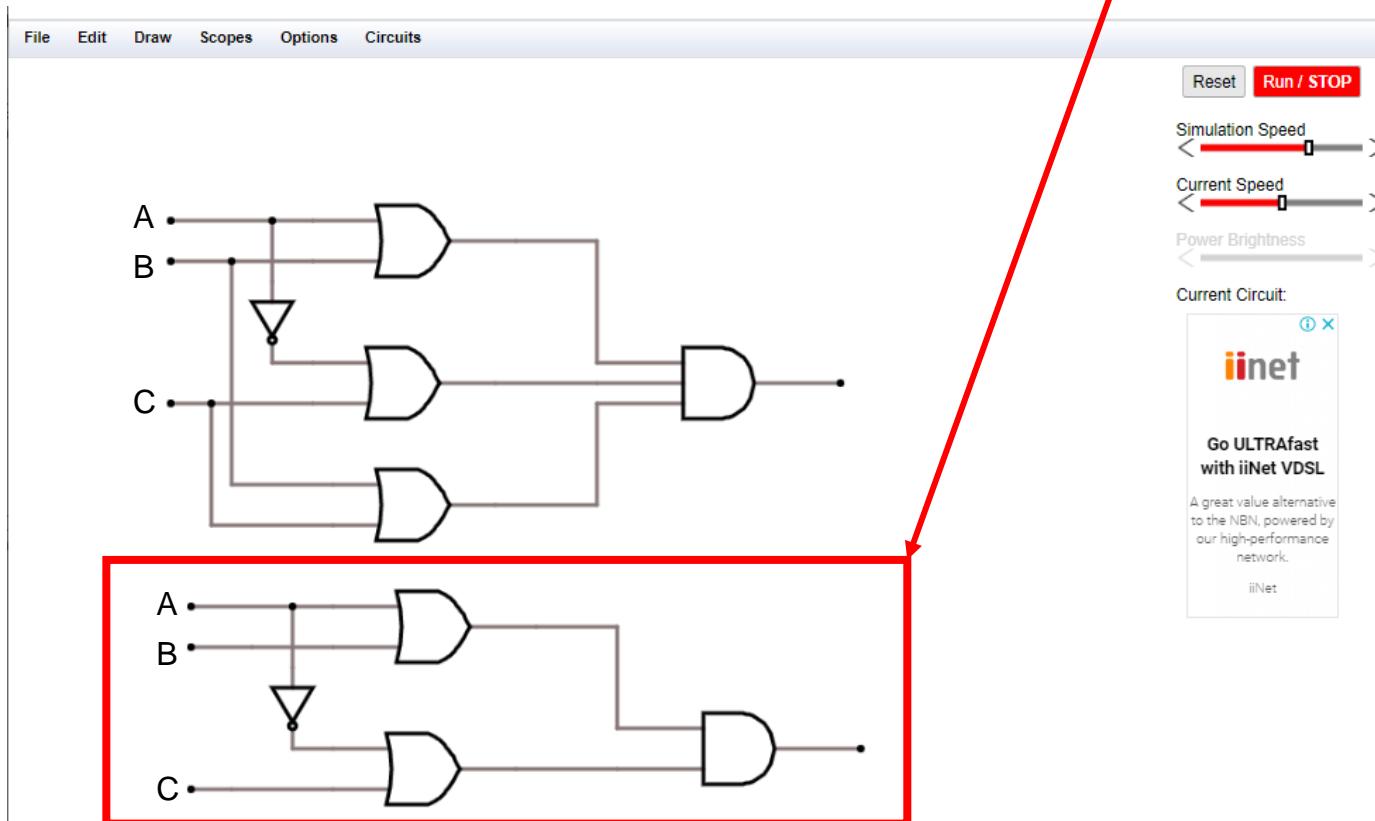

# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>


Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

1

2

3

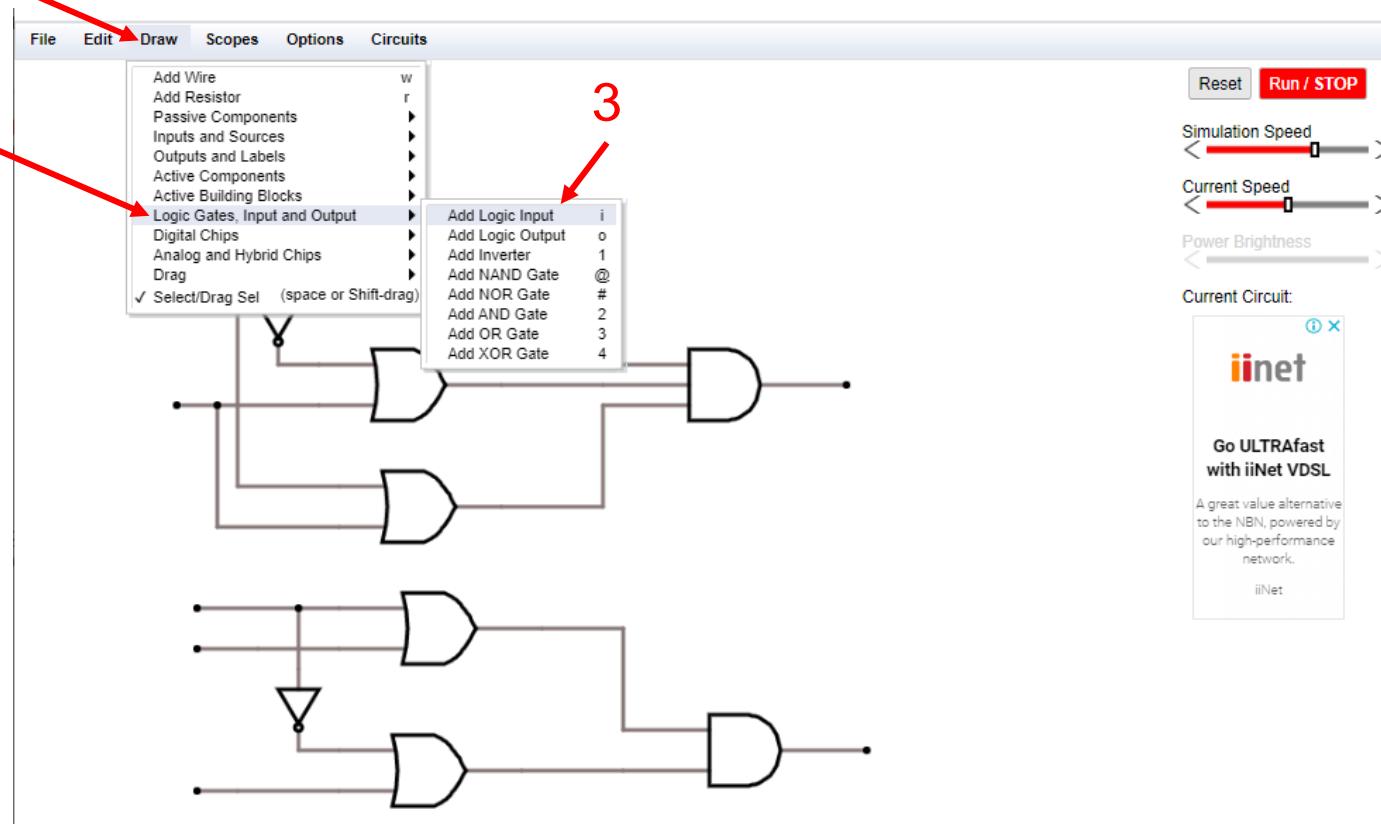


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

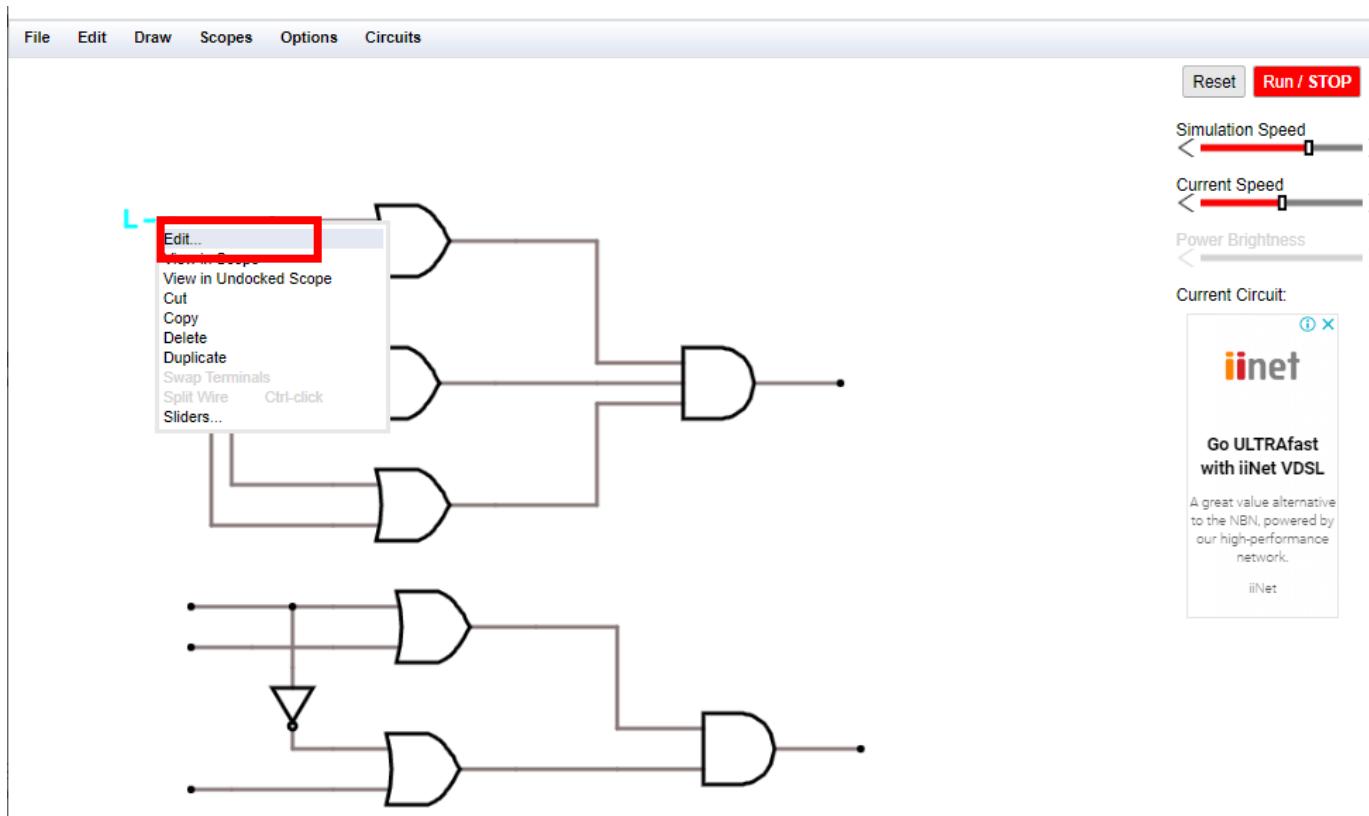


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

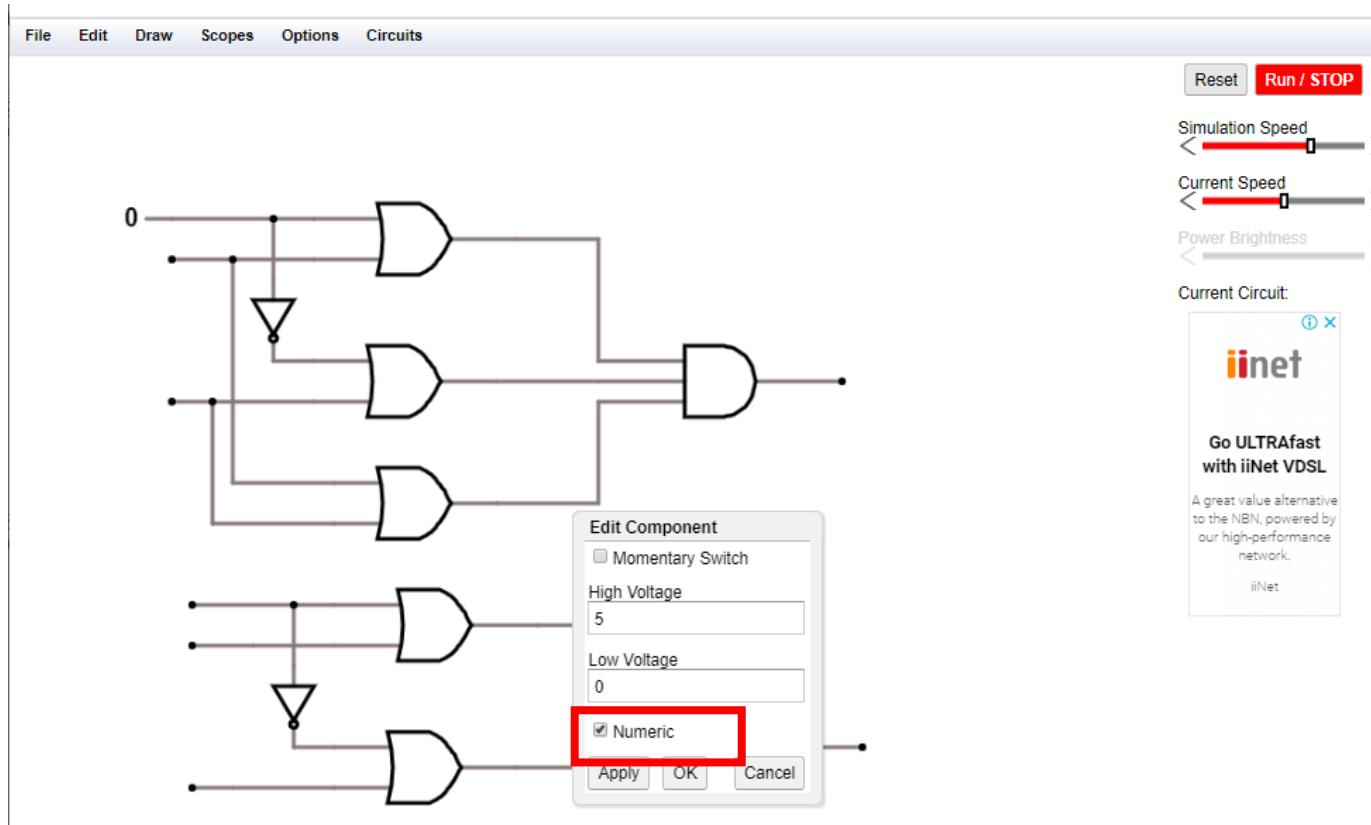


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$


$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

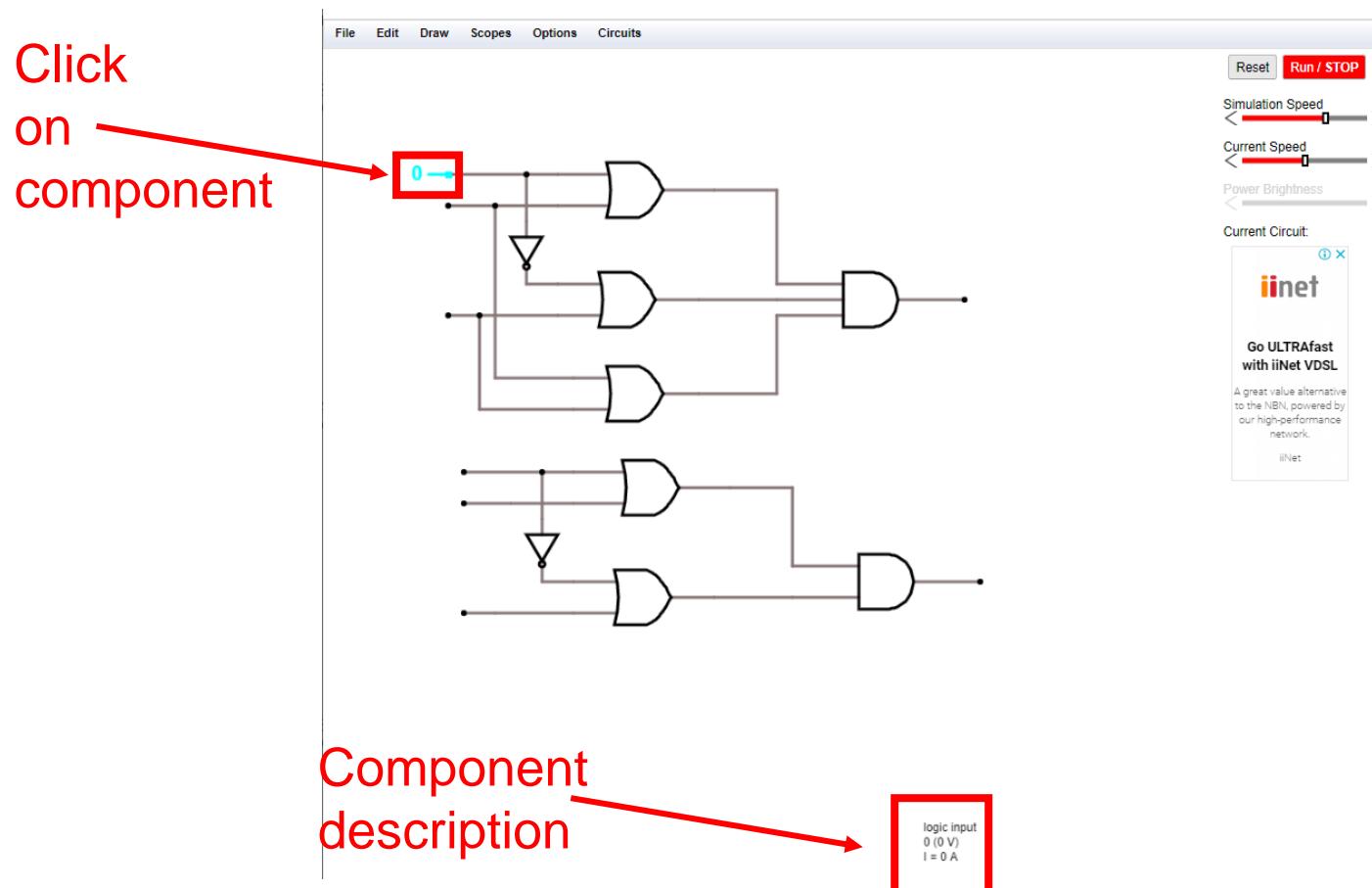

# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

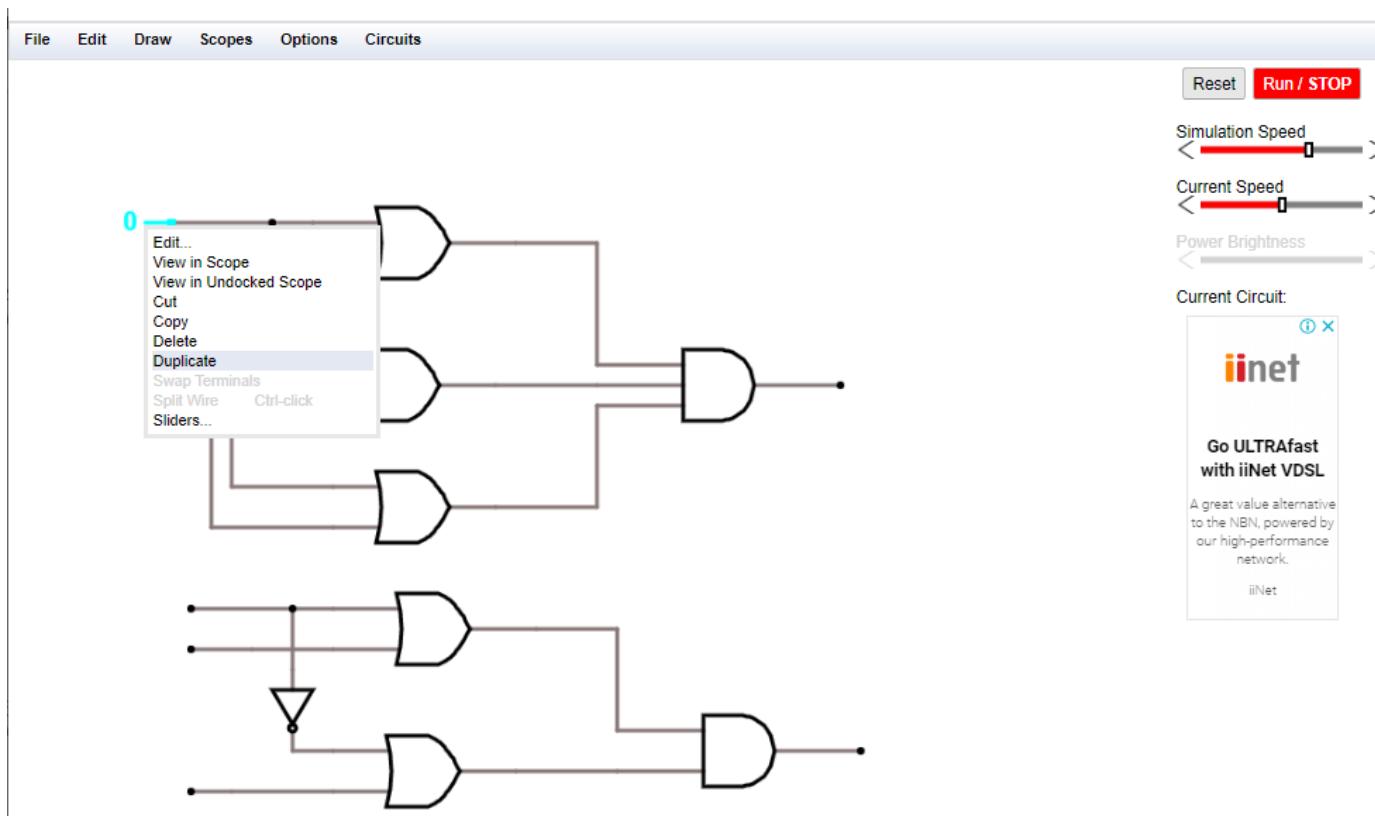Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$   
 $(A+B)(A'+C)(B+C) = (A+B)(A'+C)$




# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$$

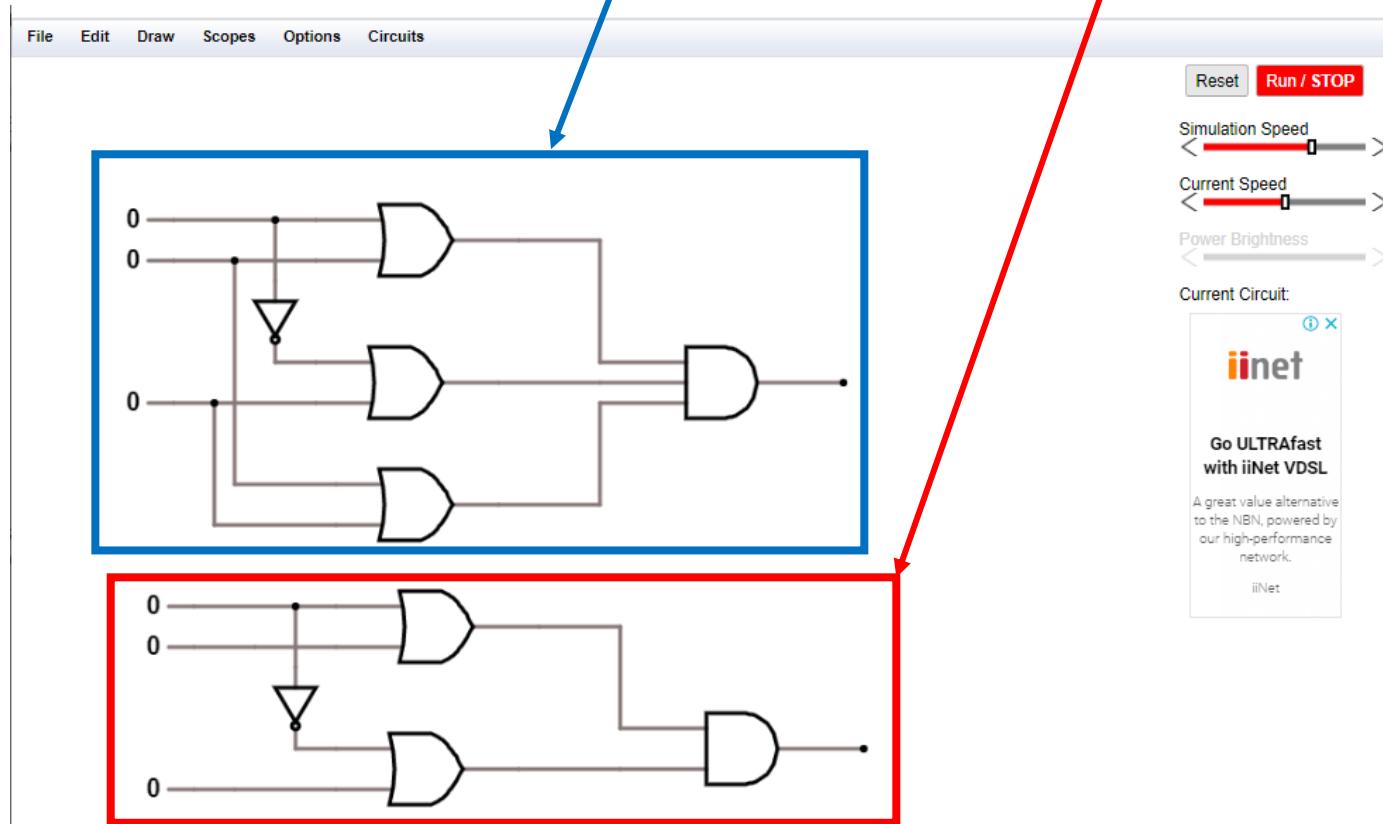


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

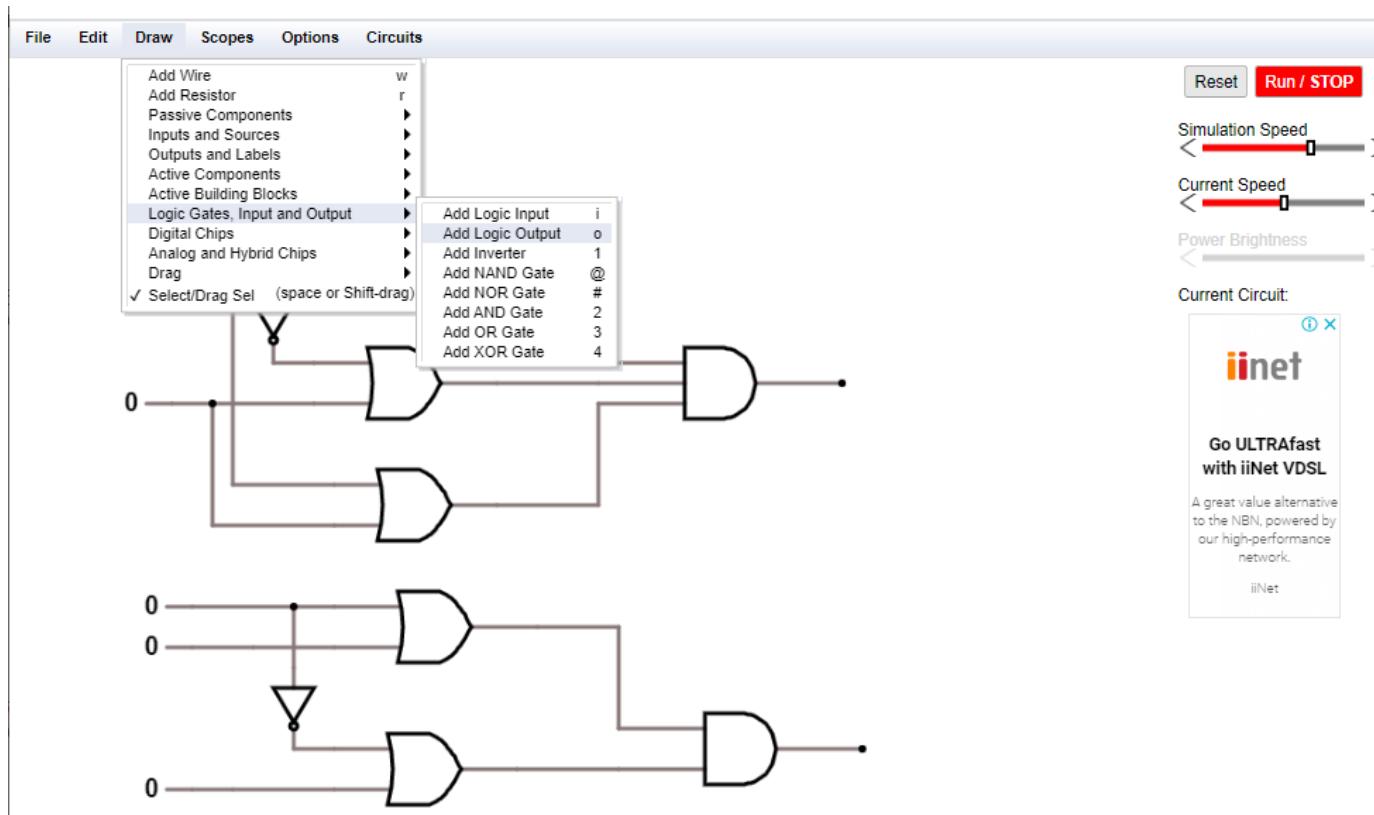


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$


$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

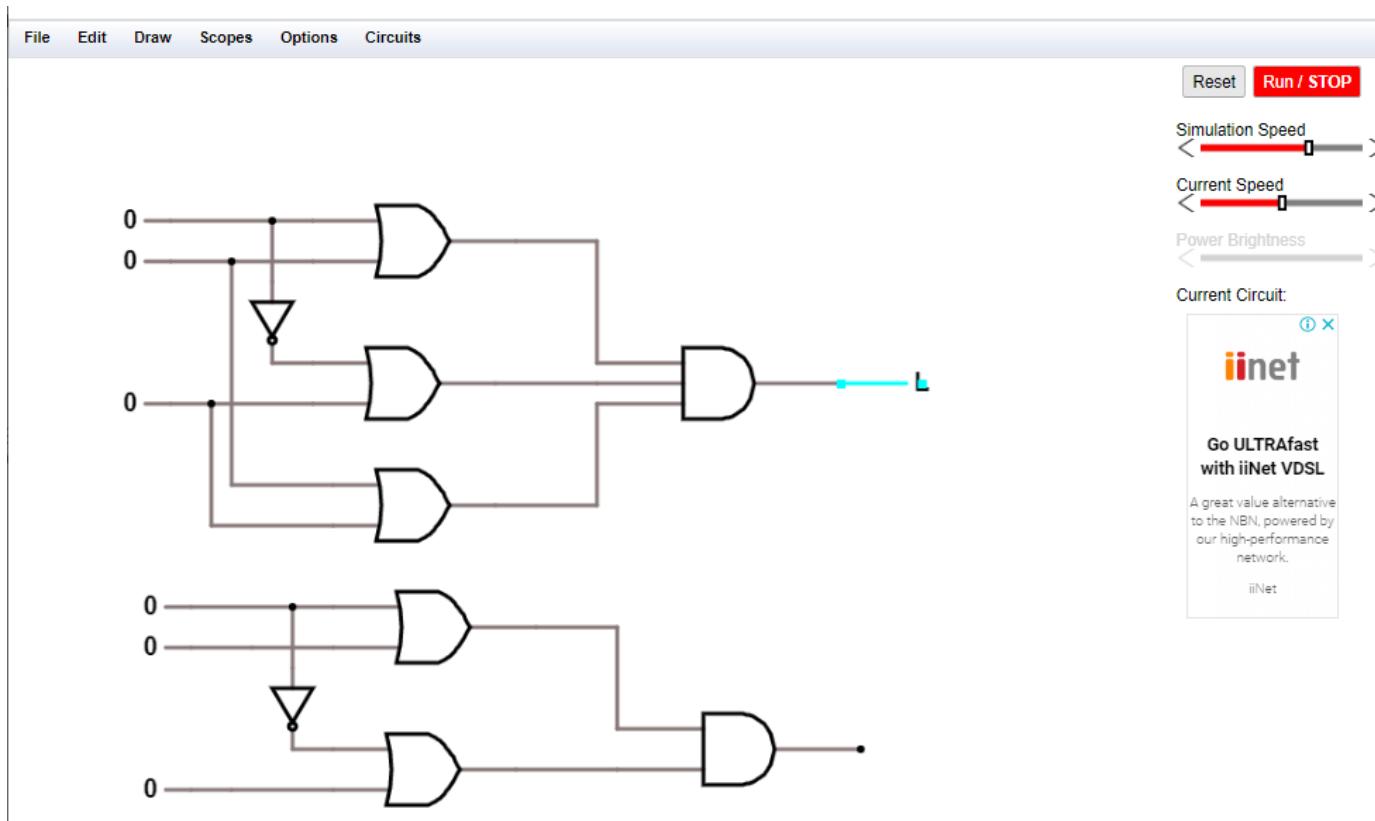

# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

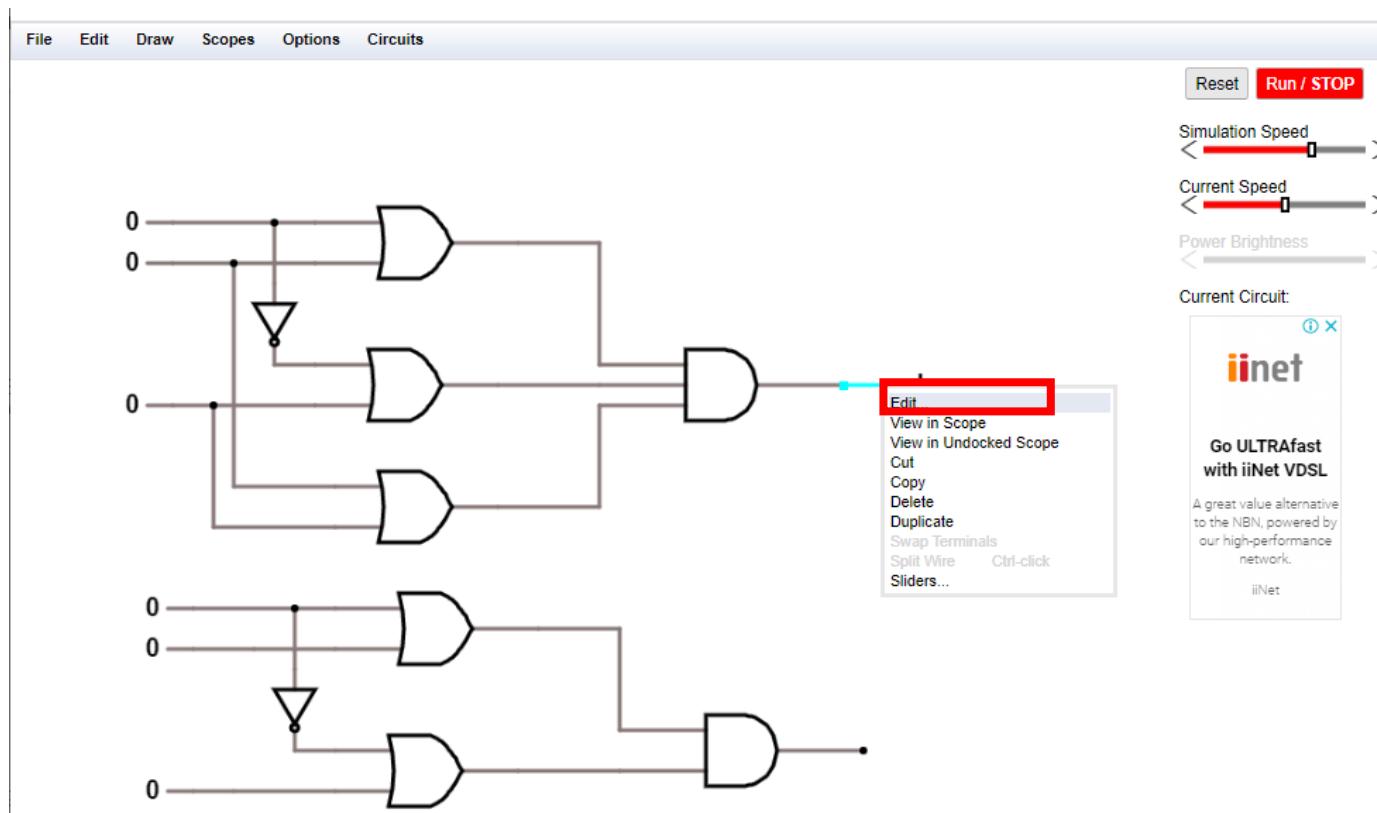
Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$   
 $(A+B)(A'+C)(B+C) = (A+B)(A'+C)$



# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

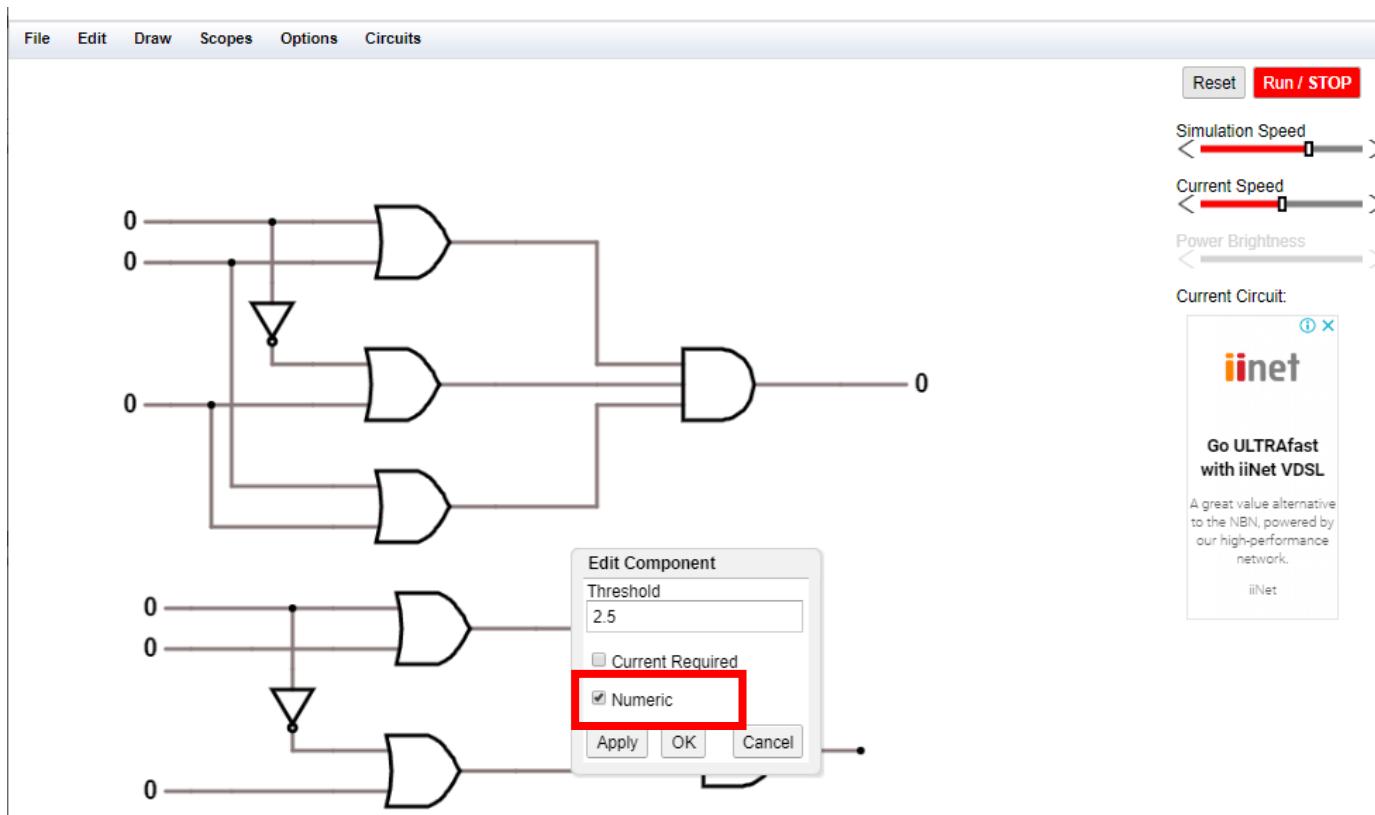
Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$   
 $(A+B)(A'+C)(B+C) = (A+B)(A'+C)$



# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

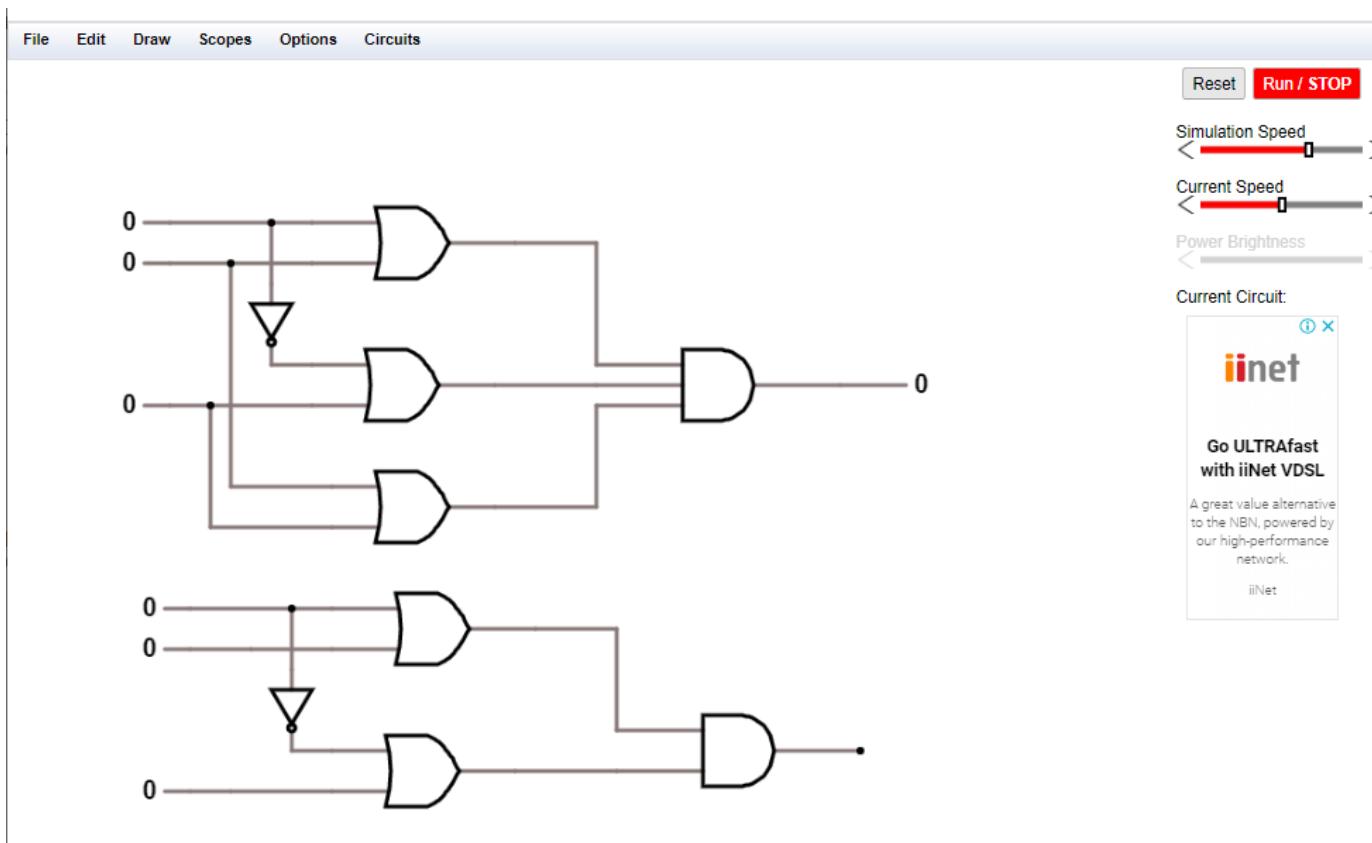
Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$   
 $(A+B)(A'+C)(B+C) = (A+B)(A'+C)$



# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

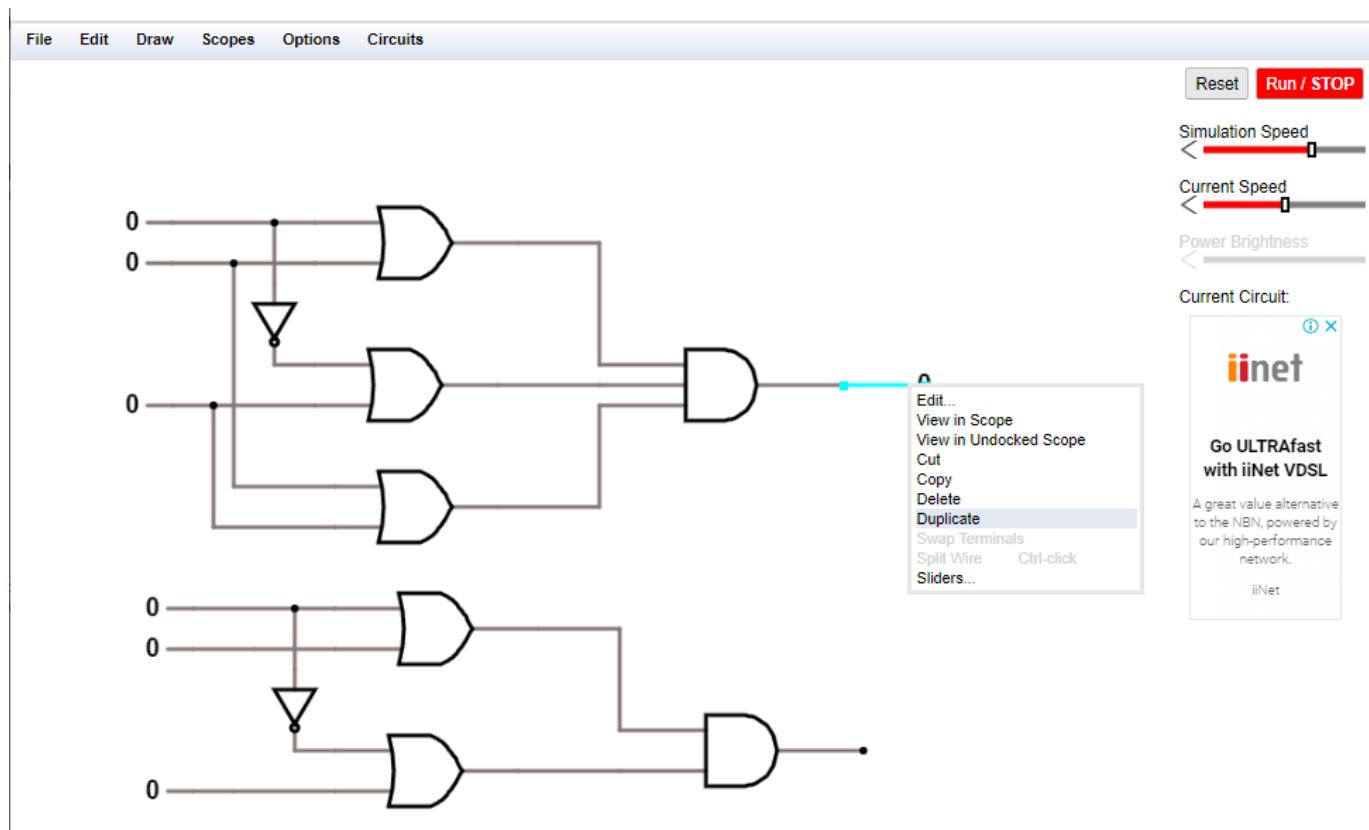
Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$   
 $(A+B)(A'+C)(B+C) = (A+B)(A'+C)$



# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

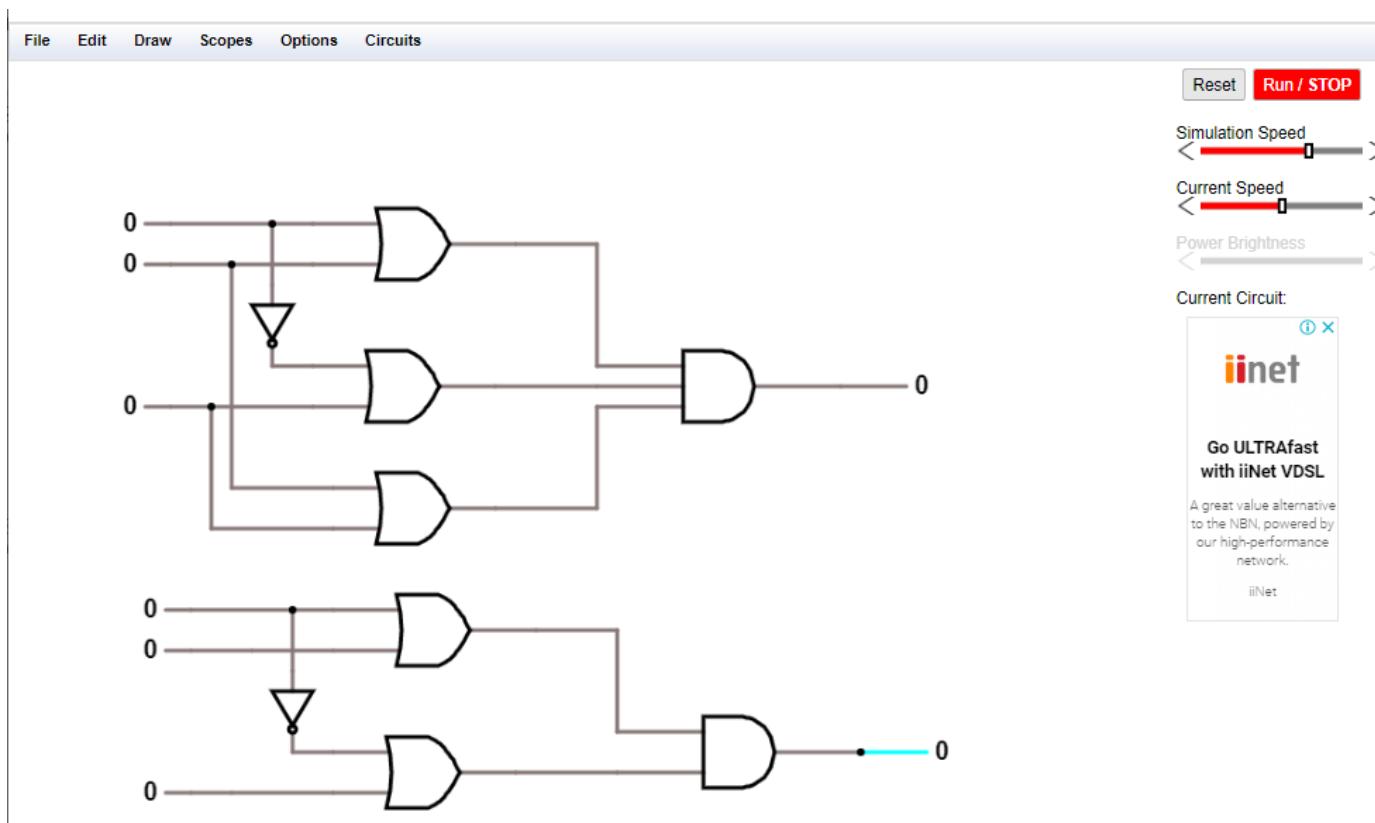Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$   
 $(A+B)(A'+C)(B+C) = (A+B)(A'+C)$




# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$$

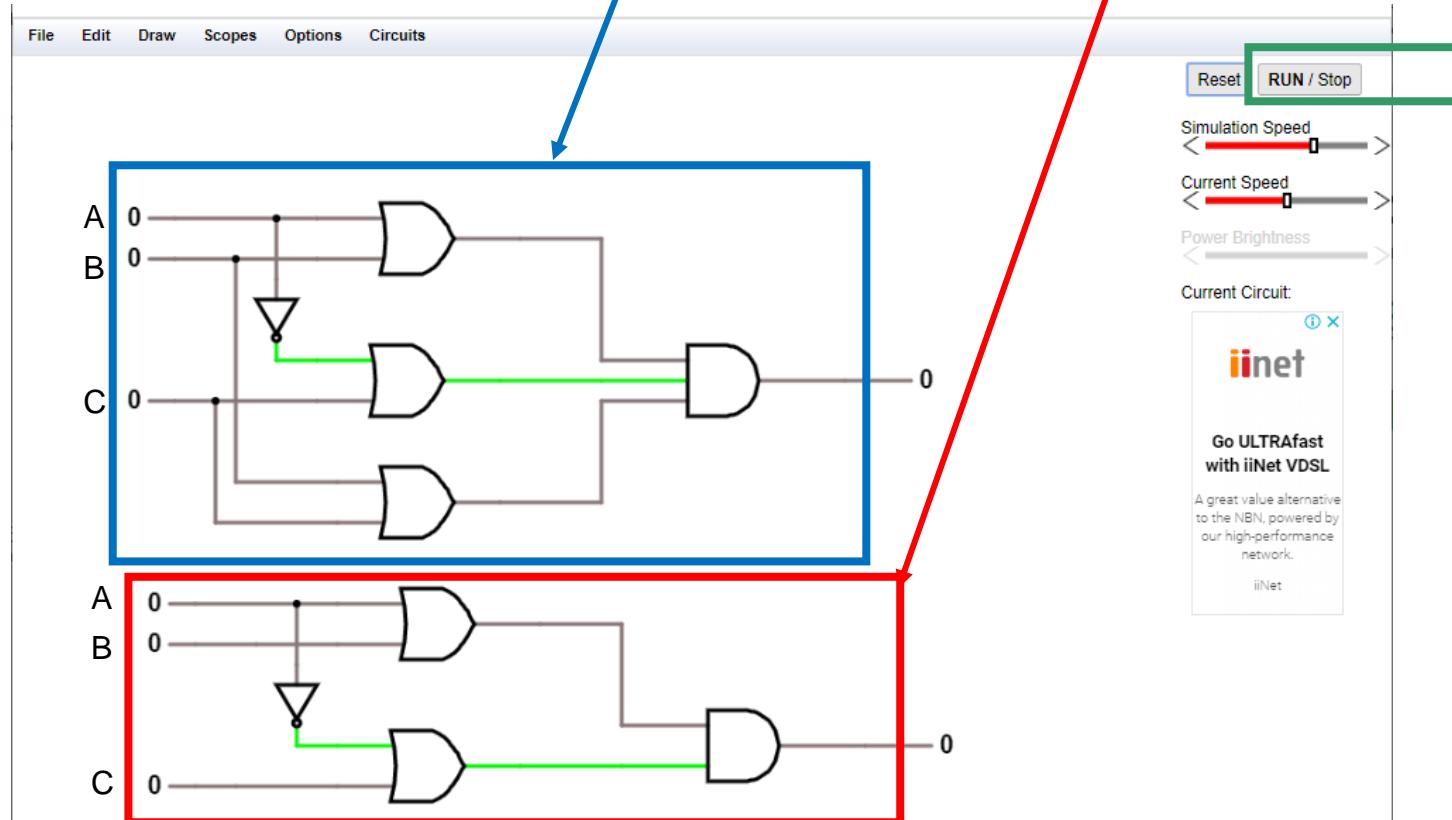


# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$


$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

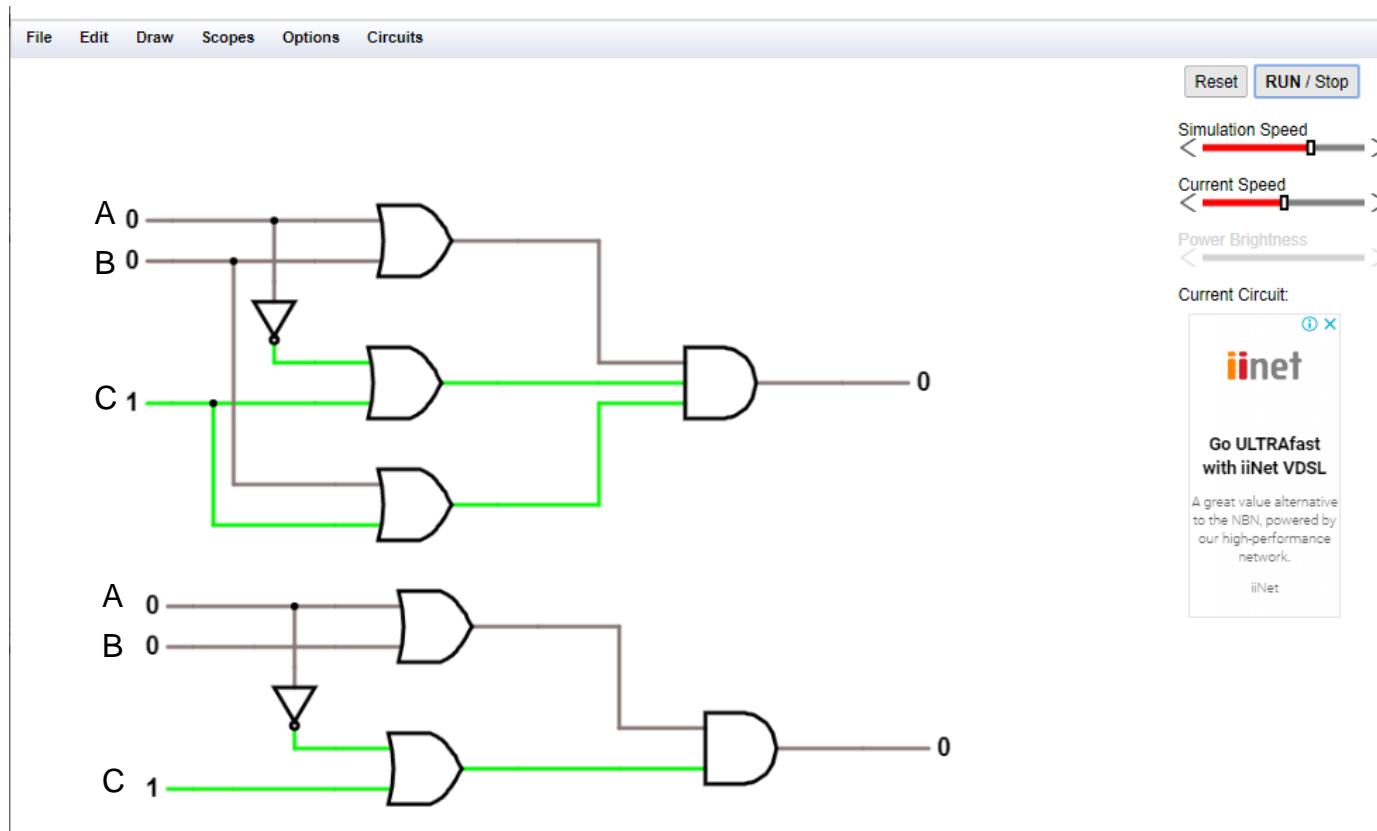

# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

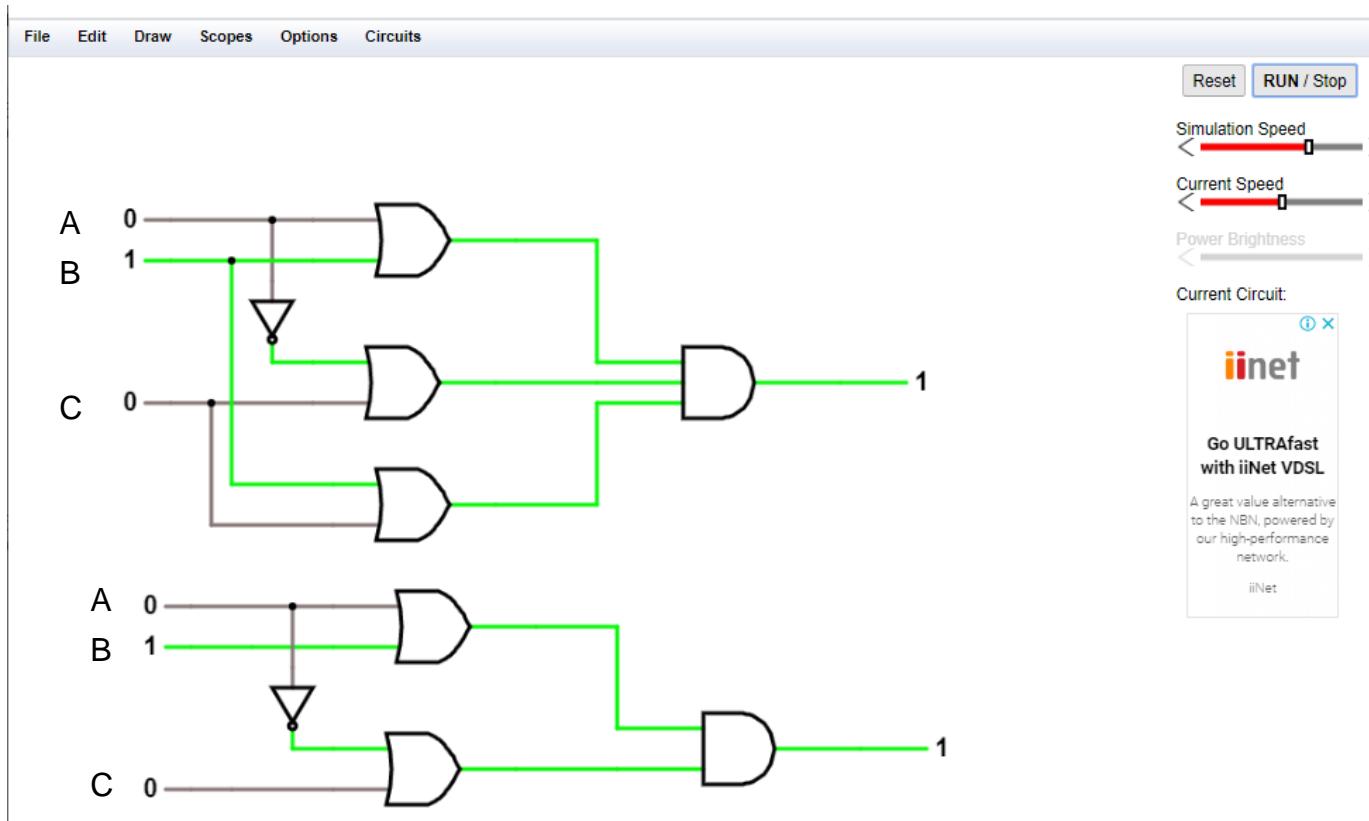
Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$   
 $(A+B)(A'+C)(B+C) = (A+B)(A'+C)$



# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

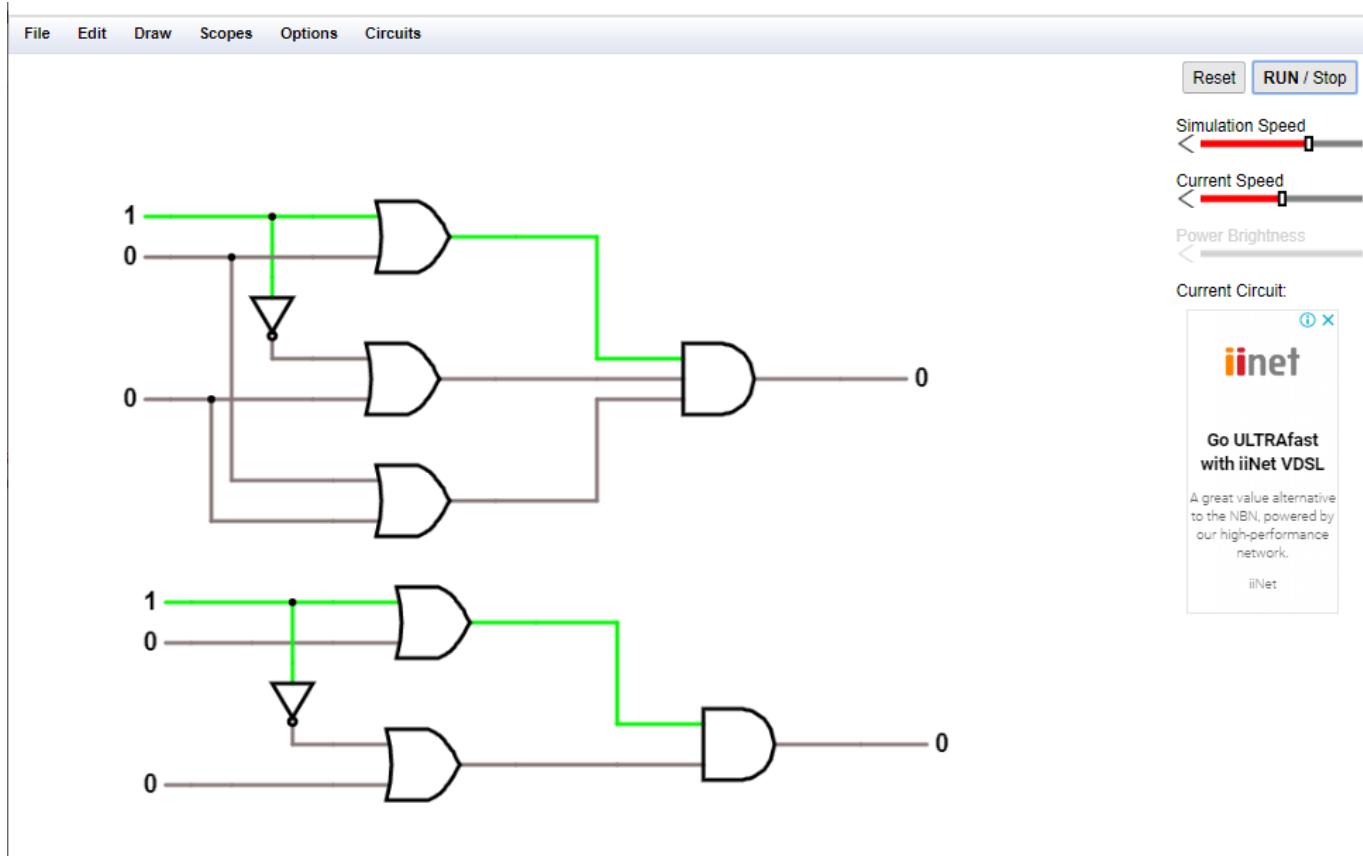Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$   
 $(A+B)(A'+C)(B+C) = (A+B)(A'+C)$




# Drawing Logic Circuits using on-line simulator

<https://www.falstad.com/circuit/>

Exercise 6.1 (d):  $(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$

$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$

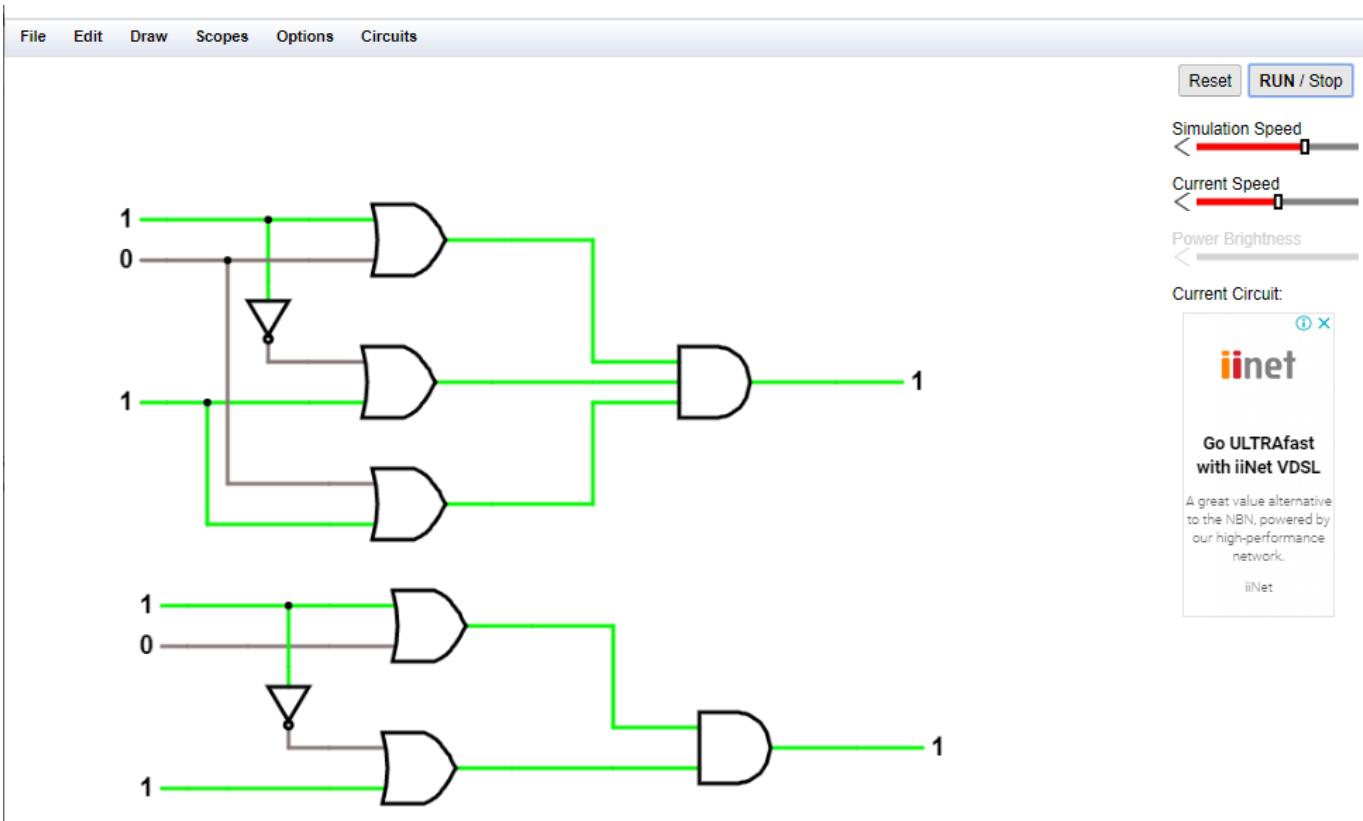

# Exercises: Simulator

---

- $C + (BC)'$
- $(AB)'(A' + B)(B' + B) = ? = A'$
- $AB + A'C + BC = ? = AB + A'$
- 3 bit Parity Generator Circuit

# Week 15

---

- Circuit simulator

<https://www.falstad.com/circuit/>