

ENGR101
ENGINEERING TECHNOLOGY
Practice Exam (June 12, 2024)

Time allowed: 120 MINUTES

CLOSED BOOK

You will be supplied with additional printed resources that you may use.
(Appendix section on pages 10-11)

Permitted materials:

Non-programmable calculators are allowed.

Only printed dictionaries are allowed.

Printed foreign to English language dictionaries are allowed.

Instructions:

There are 4 questions. Attempt ALL questions.

Space for working out your solutions is provided at the end of every question.

Question	Topic	Allocated Marks	Obtained Marks	Comments
1	Number Systems	25		
2	Boolean Algebra and K-Maps	25		
3	Logic Circuit Application	25		
4	Logic Circuit Application	25		
	TOTAL	100		

ID Number:

This blank space can be used to write your answers in case there is insufficient space in the allocated space after each question.

Question 1 – Number systems

25 marks

a) Convert the binary number 0 0 1 0 1 0 1 0 to its decimal number equivalent. (3 marks)

0	0	1	0	1	0	1	0
---	---	---	---	---	---	---	---

Answer : 42

Show your calculations in the space below. Write your answer in the space provided above.

$$2^5+2^3+2^1=42$$

b) Convert the decimal number 170 to its hexadecimal number equivalent. (2 marks)

(170)₁₀

		A	A
--	--	---	---

Show your calculations in the space below. Write your answer in the grid shown above starting from the right-hand side box.

$$\begin{array}{r} 170/16 = 10 \text{ R}10 \quad \text{A} \\ 10/16 = 0 \text{ R}10 \quad \text{A} \end{array}$$

c) Convert the following octal number to a decimal number. (2 marks)

$$123_8 = 83$$

Show your calculations in the space below. Write your answer in the space provided above.

$$1 \times 8^2 + 2 \times 8^1 + 3 = 83$$

d) Complete the following **binary** number **subtraction**: (4 marks)

$$1001011 - 110101$$

$$\begin{array}{r} 01 \\ 0101010 \\ 1001011 = 75 \\ \underline{110101} = 53 \\ 010110 = 22 \end{array}$$

e) Convert the decimal number $(-12)_{10}$ to 6-bit binary representation using (9 marks)

i. signed magnitude
 $+12 = 001010$
 $-12 = 101010$

ii. one's complement
 $-12 = 110101$

iii. two's complement
 $-12 = 110110$

f) Represent $(0.45)_{10}$ in binary. Stop after 4 decimal places and find the % rounding error. (5 marks)

$$0.011100110011001100$$

$$\begin{aligned} \text{Stopping after 4 decimal places is } 0.0111 &= 0.25 + 0.125 + 0.0625 = 0.4375 \\ \text{Error} &= (0.45 - 0.4375) / 0.45 = 0.0278 = 2.78\% \end{aligned}$$

ID Number:



Question 2 – Boolean Algebra and K-Maps
(Refer to Appendix for Boolean Laws summary)

25 marks

a) Use Boolean algebra to simplify


(5 marks)

$$X = AB + A(\bar{B} + C) + ABC\bar{C}$$

$$\begin{aligned} X &= AB + AB' + AC + ABC' \\ &= A(B + B') + AC + ABC' \\ &= A + AC + ABC' \\ &= A + ABC' = A \end{aligned}$$


b) Repeat a) but this time using a K-map.

(5 marks)

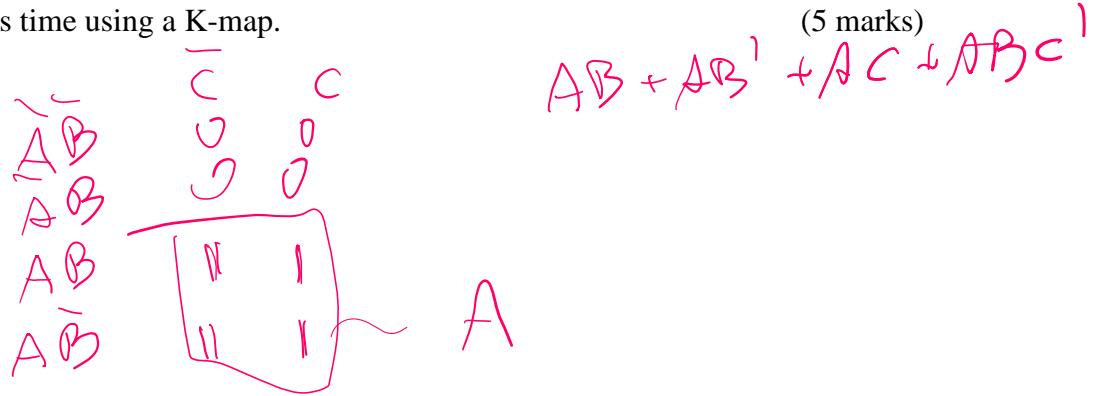

c) Write the expression for the output x and simplify it using Boolean Algebra

(5 marks)

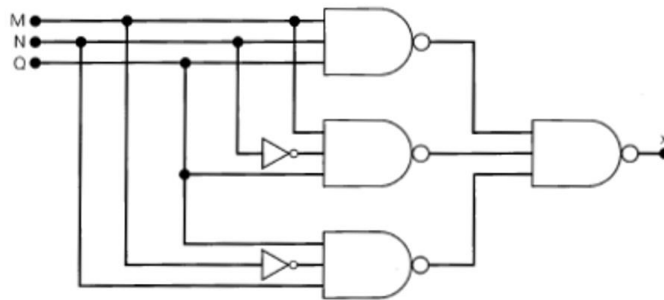


$$x = \overline{M N Q} \cdot \overline{M \bar{N} Q} \cdot \overline{\bar{M} N Q}$$

$$x = M N Q + M \bar{N} Q + \bar{M} N Q$$

$$x = M Q + N Q$$

$$x = Q(M + N)$$

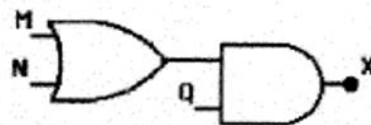

d) Simplify the following K-map and write the resulting Boolean expression. (5 marks)

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1	0	1	1
$\bar{A}B$	0	0	0	1
AB	1	0	1	1
$A\bar{B}$	1	0	0	1

$B'D' + CD' + AD' + ABC + A'B'C$

e) Simplify the following K-map and write the resulting Boolean expression. (5 marks)


	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1	0	1	1
$\bar{A}B$	1	0	x	0
AB	0	1	x	x
$A\bar{B}$	0	x	1	1

$B'C + AD + A'C'D'$

Question 3 – Logic Circuit Applications

(25 marks)

Figure below shows a multiplier circuit that takes *two 2-bit binary numbers* x_1x_0 and y_1y_0 , and produces an output binary number $z_3z_2z_1z_0$ that is equal to the **product of the input numbers**..

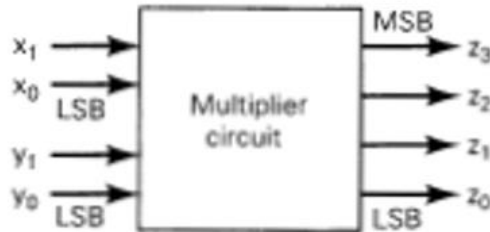

a) Produce a truth table for outputs z_3, z_2, z_1 and z_0 .

(10 marks)

x_1	x_0	y_1	y_0	z_3	z_2	z_1	z_0	
0	0	0	0	0	0	0	0	
0	0	0	1	0	0	0	0	
0	0	1	0	0	0	0	0	
0	0	1	1	0	0	0	0	
0	1	0	0	0	0	0	0	
0	1	0	1	0	0	0	1	
0	1	1	0	0	0	1	0	
0	1	1	1	0	0	1	1	
1	0	0	0	0	0	0	0	
1	0	0	1	0	0	1	0	2
1	0	1	0	0	1	0	0	4
1	0	1	1	0	1	1	0	6
1	1	0	0	0	0	0	0	
1	1	0	1	0	0	1	1	3
1	1	1	0	0	1	1	0	6
1	1	1	1	1	0	0	1	9

b) Write the SOP expressions for the outputs z_3, z_2, z_1 and z_0 .

(5 marks)

$Z_3 = x_1x_0y_1y_0$

$Z_2 = x_1x_0'y_1y_0' + x_1x_0'y_1y_0 + x_1x_0y_1y_0'$


$Z_1 = x_1'x_0y_1y_0' + x_1'x_0y_1y_0 + x_1x_0'y_1'y_0 + x_1x_0'y_1y_0 + x_1x_0y_1'y_0 + x_1x_0y_1y_0'$

$Z_0 = x_1'x_0y_1'y_0 + x_1'x_0y_1y_0 + x_1x_0y_1'y_0 + x_1x_0y_1y_0$

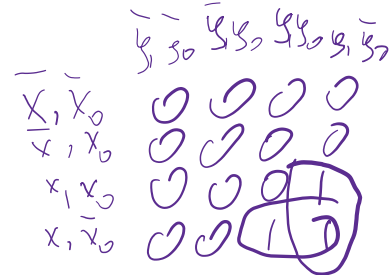
c) If needed, simplify the expressions for z_3, z_2, z_1, z_0 . You don't have to use K-maps. (10 marks)

$Z_3 = x_1 x_0 y_1 y_0$ nothing to simplify

$$\begin{aligned} Z_2 &= x_1 x_0' y_1 y_0' + x_1 x_0' y_1 y_0 + x_1 x_0 y_1 y_0' \\ &= x_1 x_0' y_1 y_0' + x_1 x_0' y_1 y_0 + x_1 x_0' y_1 y_0' + x_1 x_0 y_1 y_0' \\ &= x_1 x_0' y_1 (y_0' + y_0) + x_1 y_1 y_0' (x_0 + x_0') \\ &= x_1 x_0' y_1 + x_1 y_1 y_0' \end{aligned}$$



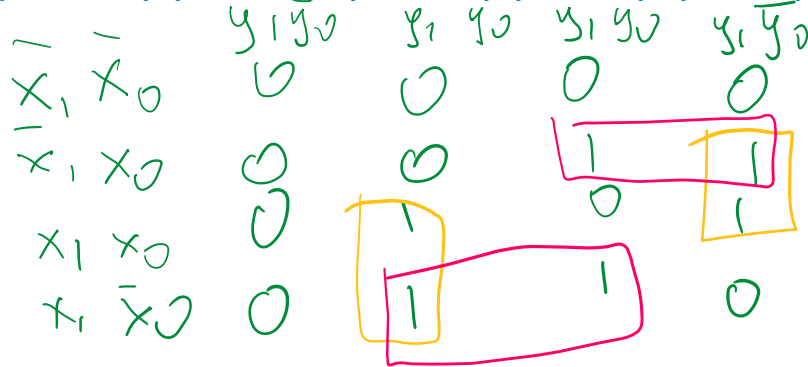
$$Z_1 = x_1' x_0 y_1 y_0' + x_1' x_0 y_1 y_0 + x_1 x_0' y_1' y_0 + x_1 x_0' y_1 y_0 + x_1 x_0 y_1' y_0 + x_1 x_0 y_1 y_0'$$



$$\begin{aligned} Z_1 &= x_1 x_0' y_0 + x_1 y_1' y_0 + x_1' x_0 y_1 + x_0 y_1 y_0' \\ &= x_1 y_0 (x_0' + y_1') + x_0 y_1 (x_1' + y_0') \end{aligned}$$
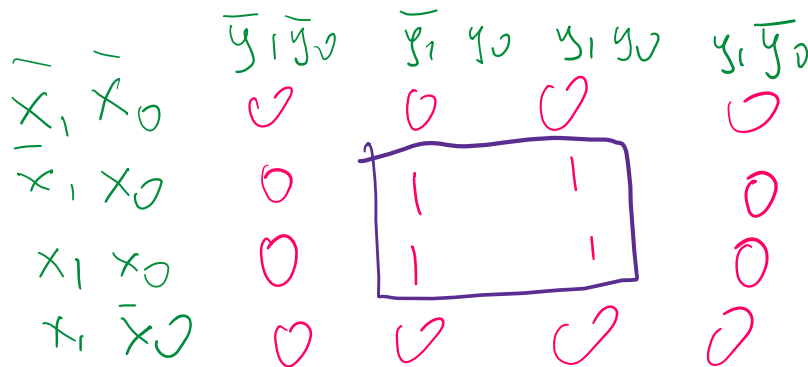
$$Z_0 = x_1' x_0 y_1' y_0 + x_1' x_0 y_1 y_0 + x_1 x_0 y_1' y_0 + x_1 x_0 y_1 y_0$$




$$Z_0 = x_0 y_0$$

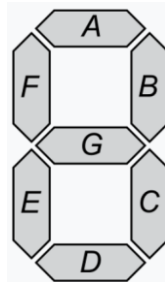Question 4 – Logic Circuit Applications

25 marks

We want to design a logic circuit for a 7-segment LED display shown below.



The inputs are 4 binary digits **d**, **c**, **b**, **a**, which represent the number to be displayed on the LED. Bit **d** is the most significant bit (MSB), and **a** is the least significant bit (LSB). Each LED segment (labelled A, B, C, ... G on the diagram) has its own logic. For example, LED E is ON when **dcba** represent decimal numbers 0, 2, 6 or 8.

d) Produce a truth table to drive LED labelled C. **0 1 3 4 5 6 7 8 9** (6 marks)

d	c	b	a	C	
0	0	0	0	1	$d'c'b'a'$
0	0	0	1	1	$d'c'b'a$
0	0	1	0	0	
0	0	1	1	1	$d'c'ba$
0	1	0	0	1	$d'cb'a'$
0	1	0	1	1	$d'cb'a$
0	1	1	0	1	$d'cba'$
0	1	1	1	1	$d'cba$
1	0	0	0	1	$dc'b'a'$
1	0	0	1	1	$da'b'a'$
1	0	1	0	X	
1	0	1	1	X	
1	1	0	0	X	
1	1	0	1	X	
1	1	1	0	X	
1	1	1	1	X	

e) Write the sum-of-products (SOP) expression for C (4 marks)

$$C = d'c'b'a' + d'c'b'a + d'c'ba + d'cb'a' + d'cb'a + d'cba' + d'cba + dc'b'a' + da'b'a'$$

f) Use a K-map to simplify the logic expression for C. (8 marks)

(Write your answer in the table provided below. Clearly mark the loop(s) of adjacent 1s.

	$\bar{b}\bar{a}$	$\bar{b}a$	ba	$b\bar{a}$
$\bar{d}\bar{c}$	1	1	1	0
$\bar{d}c$	1	1	1	1
dc	x	x	x	x
$d\bar{c}$	1	1	x	x

$C = c + b' + a$

It is tempting to solve for $C' = d'c'ba'$ and invert using DeMorgan. This leads to $C'' = C = d + c + b' + a$.


This is correct, but not as simple as possible.

Instead, we can include the first don't care condition:

$C' = d'c'ba' + dc'ba'$ which gives $C' = c'ba'$, which after inverting gives

$C'' = C = c + b' + a$ which is what we obtained using the K-Map

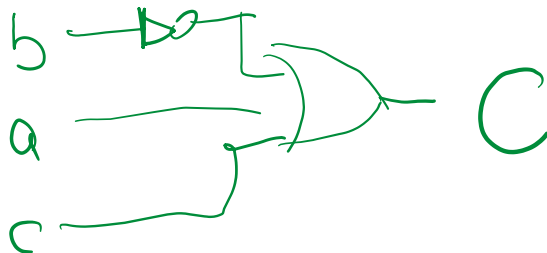g) Draw a logic diagram for G using as few gates as possible. (7 marks)



Fundamental Laws and Theorems of Boolean Algebra

- | | | | |
|-----|--|--------------------------|----------------------|
| 1. | $X + 0 = X$ | } | OR operations |
| 2. | $X + 1 = 1$ | | |
| 3. | $X + X = X$ | | |
| 4. | $X + \overline{X} = 1$ | | |
| 5. | $X \cdot 0 = 0$ | } | AND operations |
| 6. | $X \cdot 1 = X$ | | |
| 7. | $X \cdot X = X$ | | |
| 8. | $X \cdot \overline{X} = 0$ | | |
| 9. | $\overline{\overline{X}} = X$ | Double complement | |
| 10. | $X + Y = Y + X$ | } | Commutative laws |
| 11. | $XY = YX$ | | |
| 12. | $(X + Y) + Z = X + (Y + Z)$ | } | Associative laws |
| 13. | $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$ | | |
| 14. | $X(Y + Z) = XY + XZ$ | Distribution Law | |
| 15. | $X + Y \cdot Z = (X + Y) \cdot (X + Z)$ | Dual of Distributive Law | |
| 16. | $X + XZ = X$ | } | Laws of absorption |
| 17. | $X(X + Z) = X$ | | |
| 18. | $X + \overline{X}Y = X + Y$ | } | Identity Theorems |
| 19. | $X(\overline{X} + Y) = XY$ | | |
| 20. | $\overline{X + Y} = \overline{X} \cdot \overline{Y}$ | } | De Morgan's Theorems |
| 21. | $\overline{\overline{X} \cdot \overline{Y}} = \overline{X} + \overline{Y}$ | | |

Standard Logic Symbols

Used in lectures

Used in text

book

