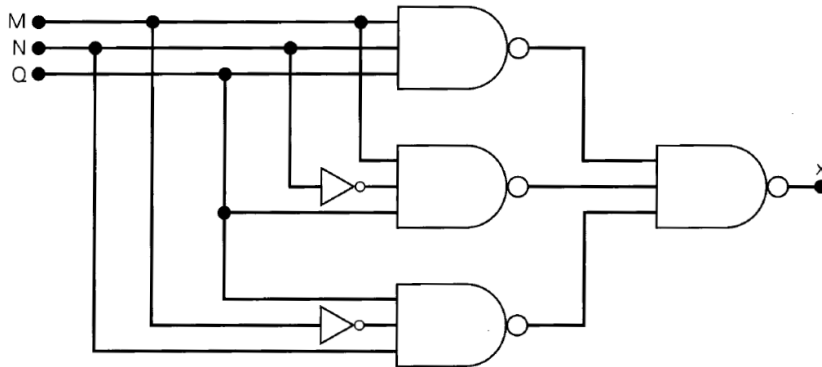


Due Monday 10 June 2024 before midnight.

1. Simplify the circuit below using Boolean algebra



2. Determine the minimum expression for each K map below.

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1	1	1	1
$\bar{A}B$	1	1	0	0
AB	0	0	0	1
$A\bar{B}$	0	0	1	1

(a)

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1	0	1	1
$\bar{A}B$	1	0	0	1
AB	0	0	0	0
$A\bar{B}$	1	0	1	1

(b)

	\bar{C}	C
$\bar{A}\bar{B}$	1	1
$\bar{A}B$	0	0
AB	1	0
$A\bar{B}$	1	X


(c)

3. Simplify the following expressions using Boolean algebra

(a) $x = \bar{A}\bar{B}\bar{C} + \bar{A}BC + ABC + A\bar{B}\bar{C} + A\bar{B}C$

(b) $x = \overline{C + D} + \bar{A}C\bar{D} + A\bar{B}\bar{C} + \bar{A}\bar{B}CD + AC\bar{D}$

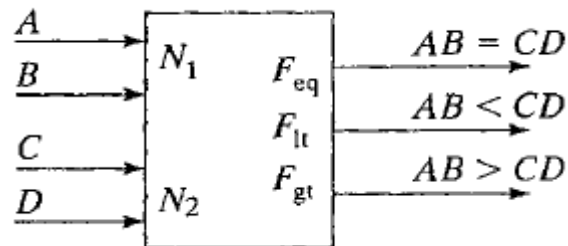4. You are to design a circuit that compares two 2-bit numbers, N_1 and N_2 . Specifically, as shown, the circuit generates three outputs F_{eq} , F_{lt} and F_{gt} whose values are TRUE if $N_1 = N_2$, $N_1 < N_2$ and $N_1 > N_2$, respectively. The numbers N_1 and N_2 are denoted by single bit inputs A , B and C , D , respectively, where A and C are the most significant bits.




- (a) Find the Boolean expressions for each of the outputs F_{eq} , F_{lt} and F_{gt} . Use K-maps to simplify them (if possible).
- (b) Simplify F_{eq} using Boolean algebra and express the final answer using XNOR operators.
5. Use J-K flip flops to design a **synchronous** counter that will go through the following sequence: **000**, **010**, **101**, **110** and repeat. The undesired (unused) states must always go to 000 on the next clock pulse.

Build the counter using the circuit simulator. Save your answer using the filename format: StudentIDNumberA2Q5 (Eg. 2012409101A2Q5.txt)

6. Redesign the counter of (Q5) without any requirement on the unused states, so that their next state can be a don't care state. Compare to the previous counter design.

Build the counter using the circuit simulator. Save your answer using the filename format: StudentIDNumberA2Q6 (Eg. 2012409101A2Q6.txt)

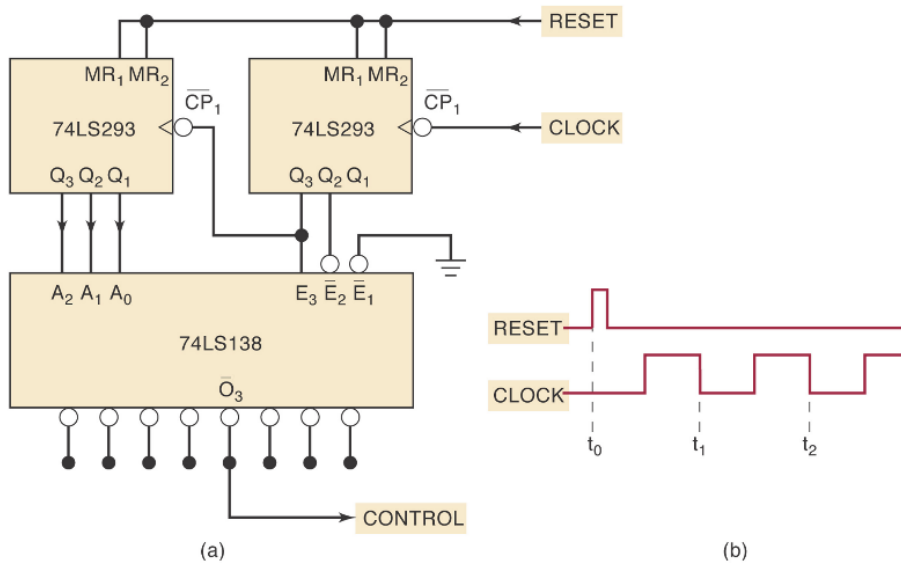7. Examine the circuit below, identify each of the ICs used and explain the operation of the circuit. Now modify the circuit so that it will produce a control signal that will remain LO from CLK t_{20} to t_{24} .



You need to submit a compressed file which contains 2 circuit diagrams (for Questions 5 and 6) and pdf file which contains your answers for all other Questions. The compressed file to be submitted must be named using your student ID number.