

XMUT 202

Digital Electronics

A/Prof. Pawel Dmochowski

School of Engineering and Computer Science
Victoria University of Wellington


Victoria
UNIVERSITY OF WELLINGTON

*Te Whare Wānanga
o te Ūpoko o te Ika a Māui*



CAPITAL CITY UNIVERSITY

Asynchronous Down Counter

 

A: Toggles as normal


B: Toggles when A goes LO to HI

C: Toggles when B goes LO to HI

Solution: Drive each clock input from the inverted input of the preceding FF



Asynchronous Down Counter

MOD 8 down counter

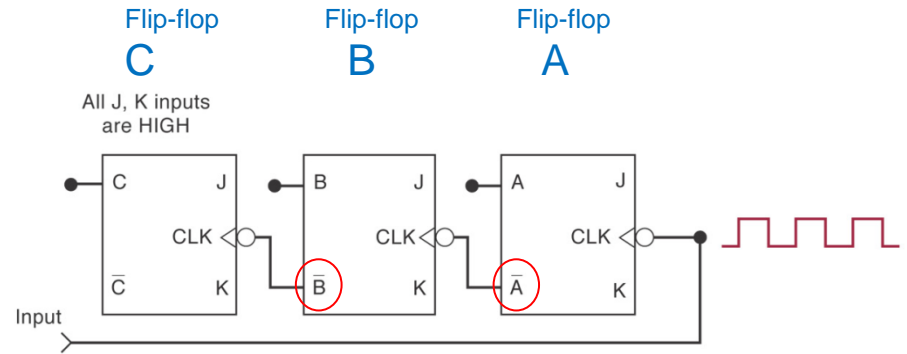

Asynchronous Down Counter

MOD 8 down counter

 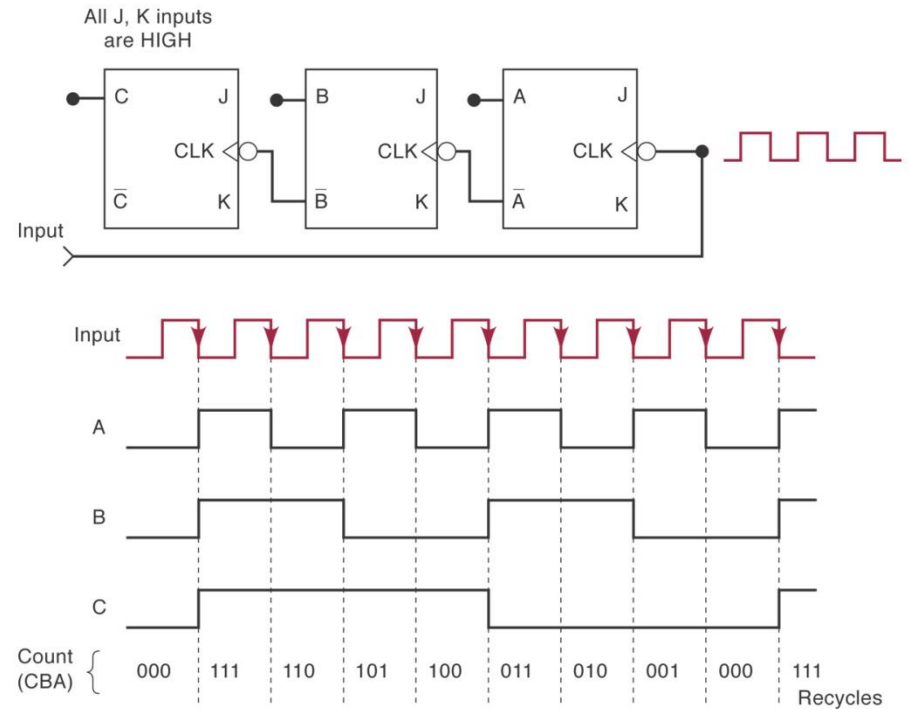



The Problem with Ripple Counters: Propagation Delay

For proper operation:

$$T_{\text{clock}} \geq N \times t_{pd}$$

$$F_{\text{max}} = 1 / (N \times t_{pd})$$

where N = number of FFs.

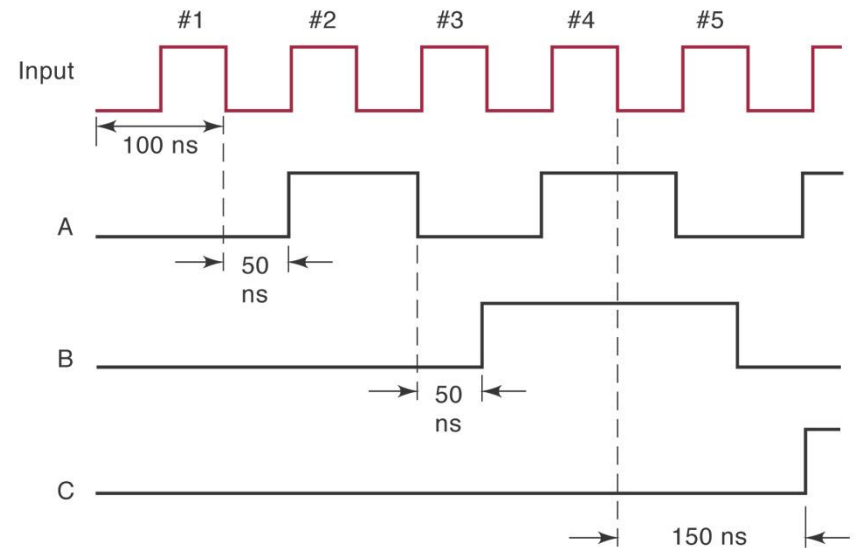 

The 100 ns condition does not occur.

(b)

Example: Four bit ripple counter constructed from a 74LS112 J-K flip flop.

$$t_{\text{PLH}} = 16 \text{ ns and } t_{\text{PHL}} = 24 \text{ ns}$$

What is highest frequency that can be used ?

Example: Four bit ripple counter constructed from a 74LS112 J-K FF.

$$t_{\text{PLH}} = 16 \text{ ns and } t_{\text{PHL}} = 24 \text{ ns}$$

What is highest frequency that can be used ?

$$f_{\text{max}} = 1/(4 \times 24 \text{ ns}) = 10.4 \text{ MHz}$$

This frequency limitation inhibits the use of asynchronous counters at moderately high frequencies

Example: What is the highest frequency that a ripple counter with a MOD number 60 constructed from a 74LS112 J-K flip flop can operate at?

$$t_{\text{PLH}} = 16 \text{ ns and } t_{\text{PHL}} = 24 \text{ ns}$$

Example: What is the highest frequency that a ripple counter with a MOD number 60 constructed from a 74LS112 J-K flip flop can operate at?

$$t_{\text{PLH}} = 16 \text{ ns and } t_{\text{PHL}} = 24 \text{ ns}$$

$$f_{\text{max}} = 1/(6 \times 24 \text{ ns}) = 6.9 \text{ MHz}$$

Synchronous (Parallel) Counters

- Solution to the previous problem - All FFs are triggered by CPs simultaneously

Synchronous (Parallel) Counters

- Solution to the previous problem - All FFs are triggered by CPs simultaneously
- Each FF has J and K inputs connected so they are HIGH only when the outputs of all lower-order FFs are HIGH.


Synchronous (Parallel) Counters

- Solution to the previous problem - All FFs are triggered by CPs simultaneously
- Each FF has J and K inputs connected so they are HIGH only when the outputs of all lower-order FFs are HIGH.
- The total propagation delay will be the same for any number of FFs.

Synchronous (Parallel) Counters


- Solution to the previous problem - All FFs are triggered by CPs simultaneously
- Each FF has J and K inputs connected so they are HIGH only when the outputs of all lower-order FFs are HIGH.
- The total propagation delay will be the same for any number of FFs.
- Synchronous counters can operate at much higher frequencies than asynchronous counters.

Synchronous MOD 16 counter

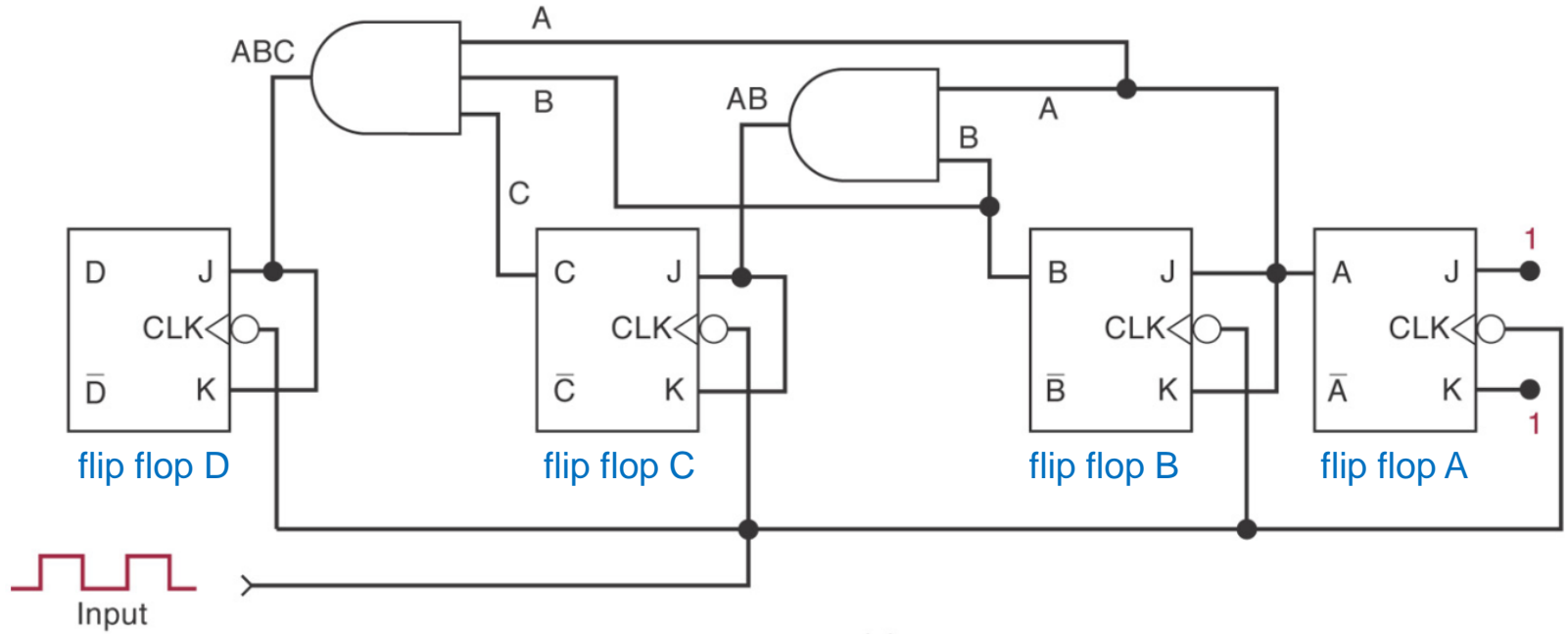

(a)

Synchronous MOD 16 counter

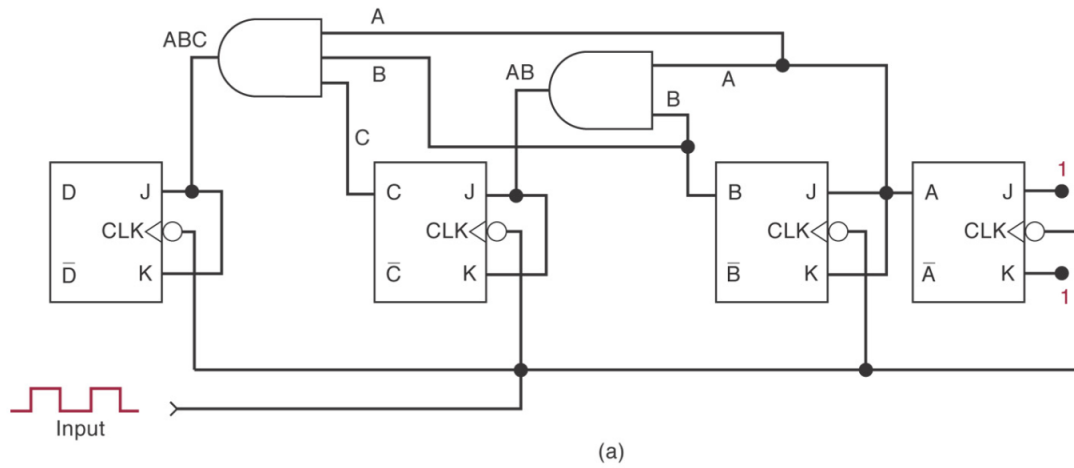

Truth table

Count	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1
0	0	0	0	0
.
.
.	.	etc.	.	.

(b)

Synchronous Down and Up Counters

- The synchronous counter can be converted to a down counter by using the inverted FF outputs to drive the JK inputs.


Synchronous Down and Up Counters

- The synchronous counter can be converted to a down counter by using the inverted FF outputs to drive the JK inputs.
- A synchronous counter can be made an up/down counter by suitable connections.


Synchronous Down and Up Counters

- The synchronous counter can be converted to a down counter by using the inverted FF outputs to drive the JK inputs.
- A synchronous counter can be made an up/down counter by suitable connections.
- Available in IC form with Up/Down control input.


Synchronous Down and Up Counters

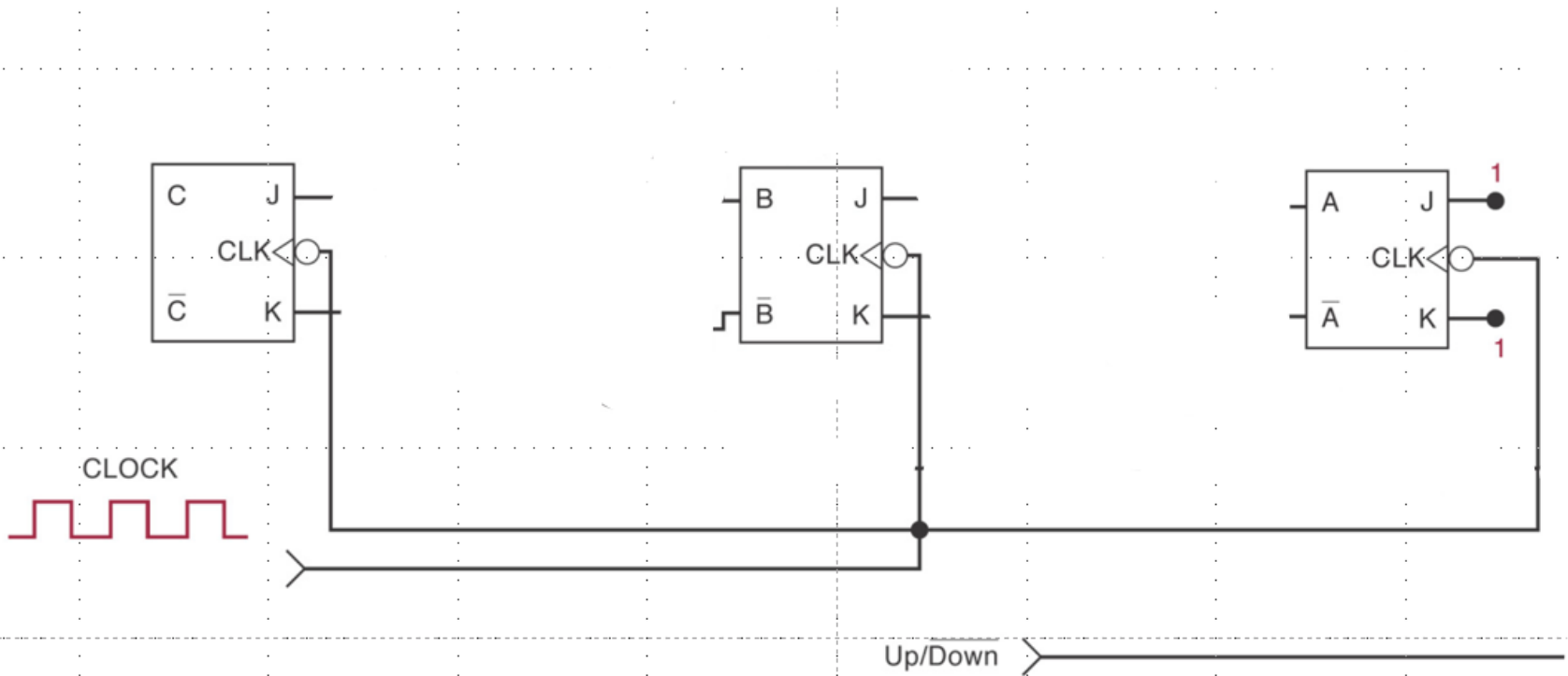

MOD 8 Up/Down Counter

 

(a)

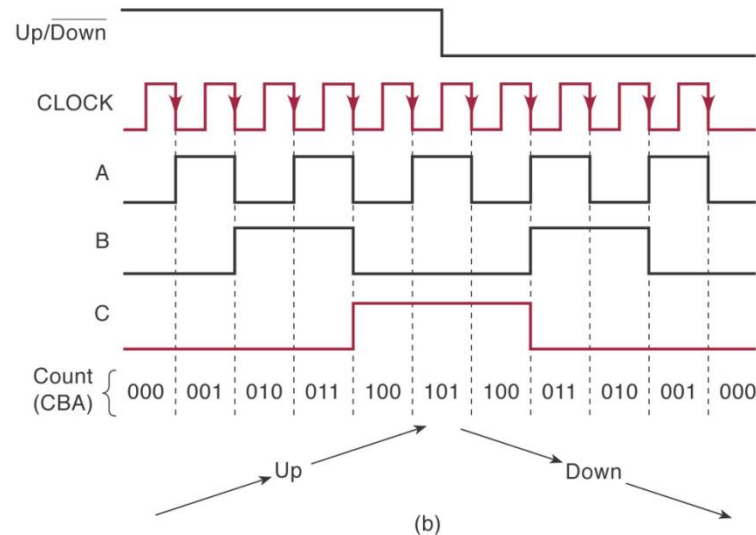


(b)

Presetable Counters



- A presetable counter can be set to any desired starting point either asynchronously or synchronously.
- The preset operation is also called parallel loading the counter.
- The next figure illustrates an asynchronous preset.
- There are several TTL and CMOS devices that provide both synchronous and asynchronous presetting.

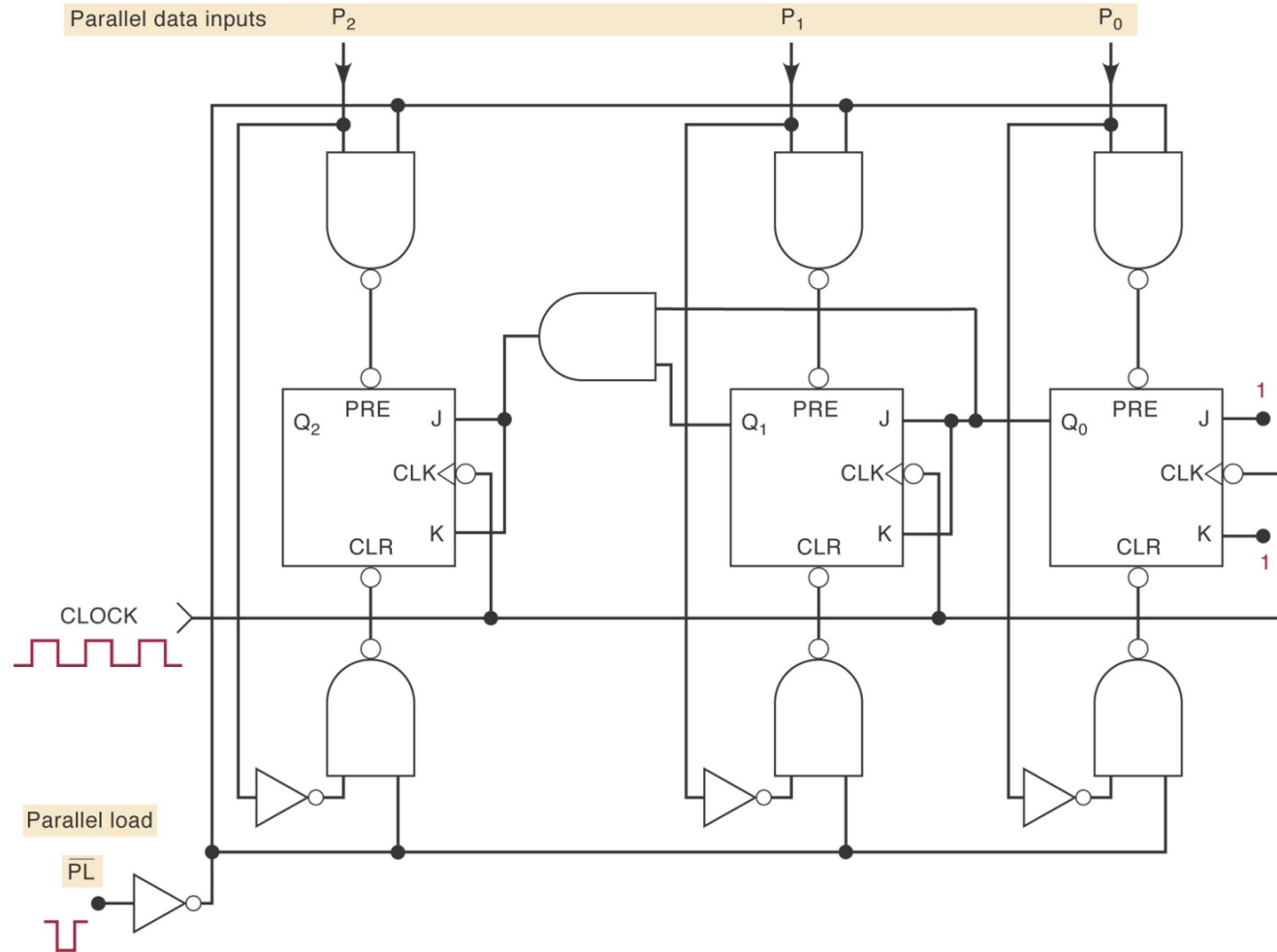Presettable counter with asynchronous reset.



Decoding a Counter

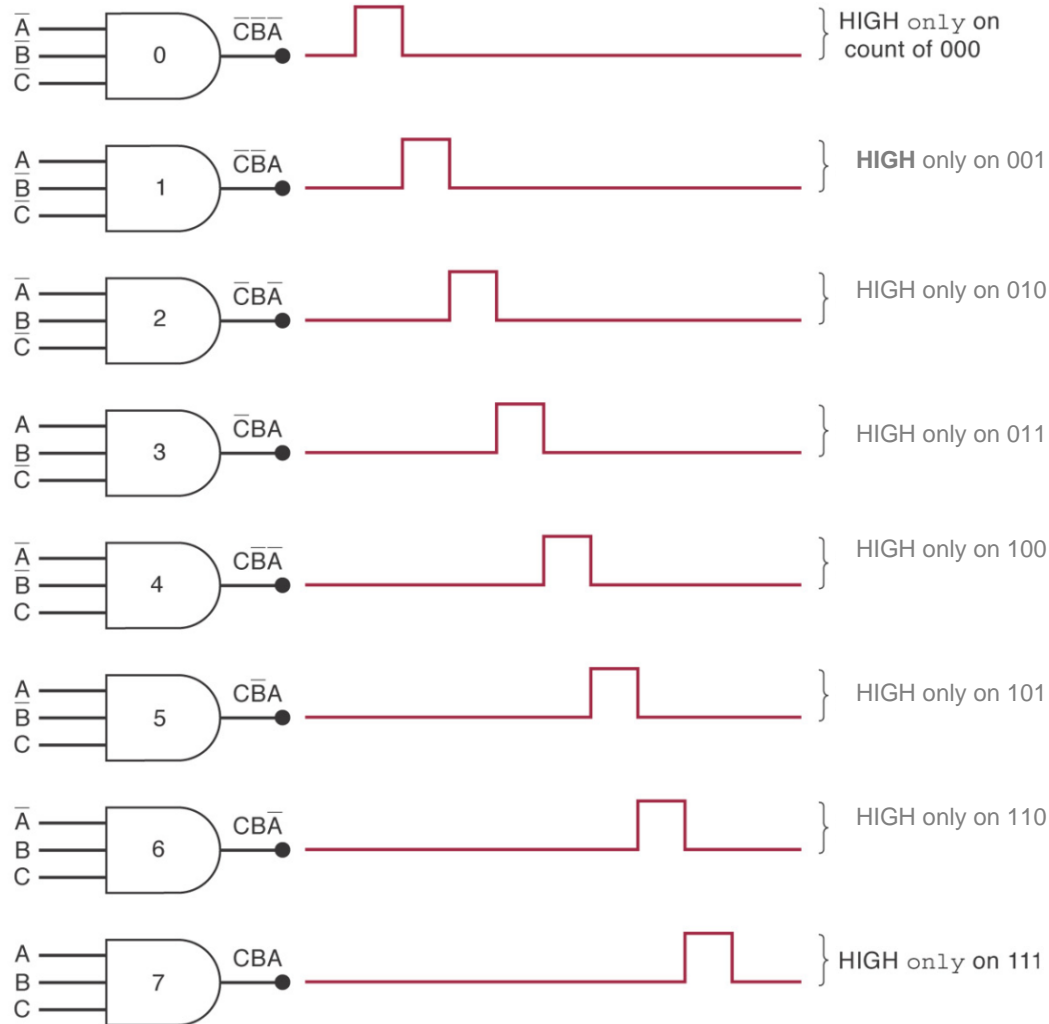 - Decoding is the conversion of a binary output to a decimal value.
- The active high decoder shown in the next figure could be used to light an LED representing each decimal number 0 to 7
- Active low decoding is obtained by replacing the AND gates with NAND gates.




Problem:


Design a 3 – bit synchronous counter that will decode binary state 2 and binary state 7.

Decode

$$2 = 010_2$$

$$7 = 111_2$$

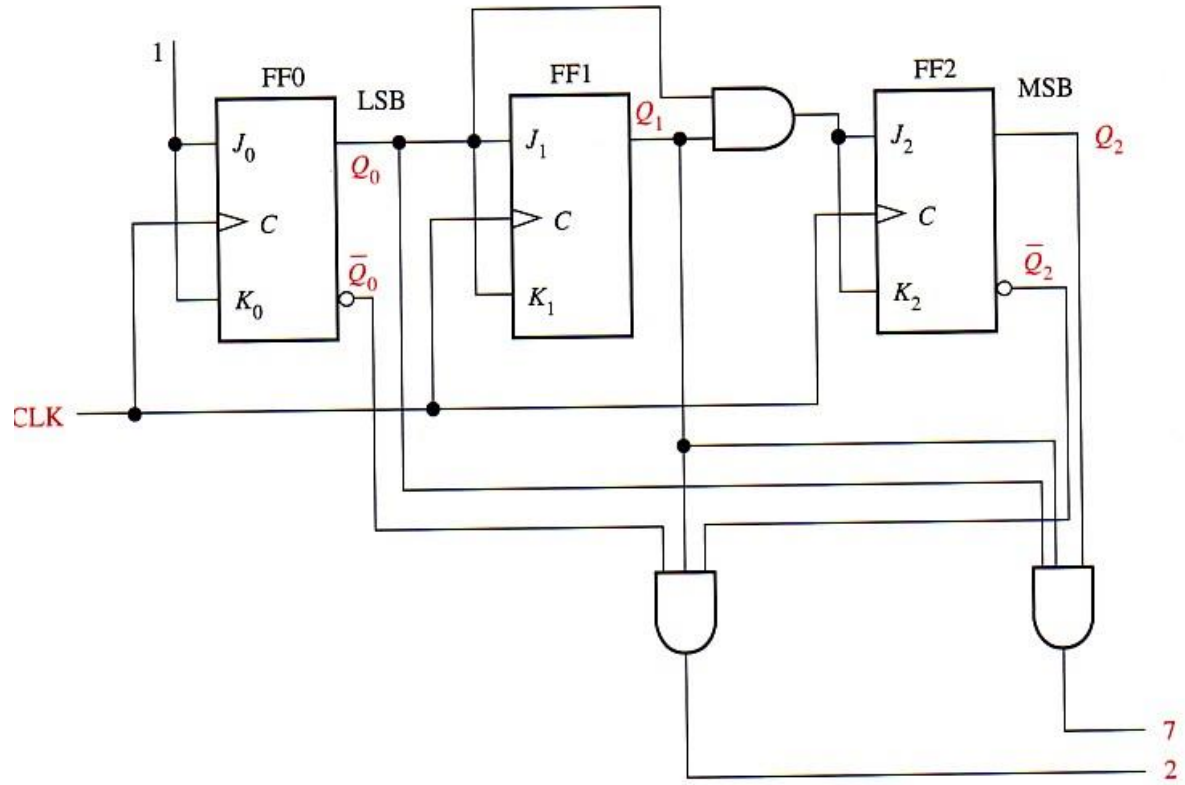


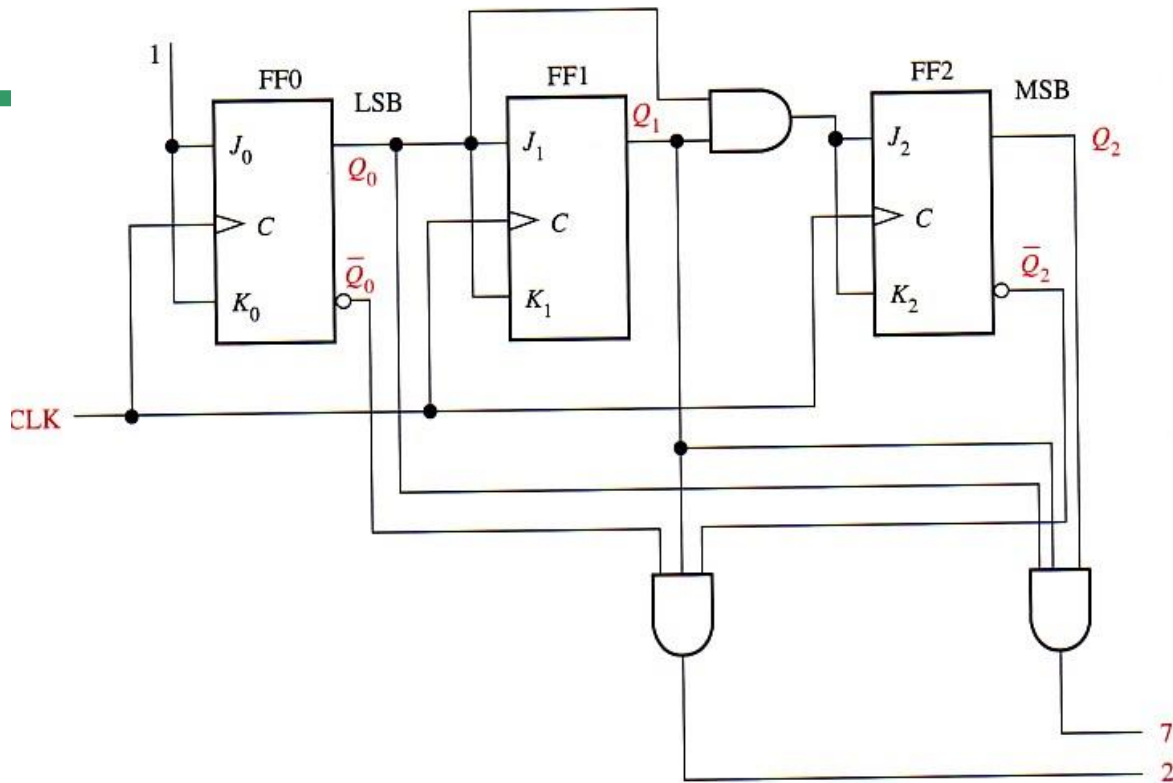

Decode


$$2 = 010_2$$

$$7 = 111_2$$

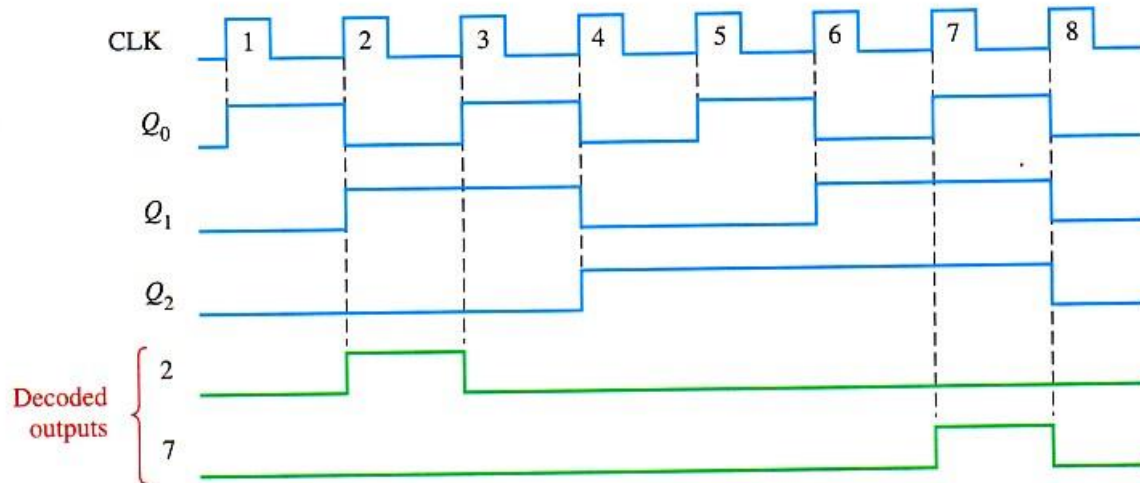

Cascading BCD Counters

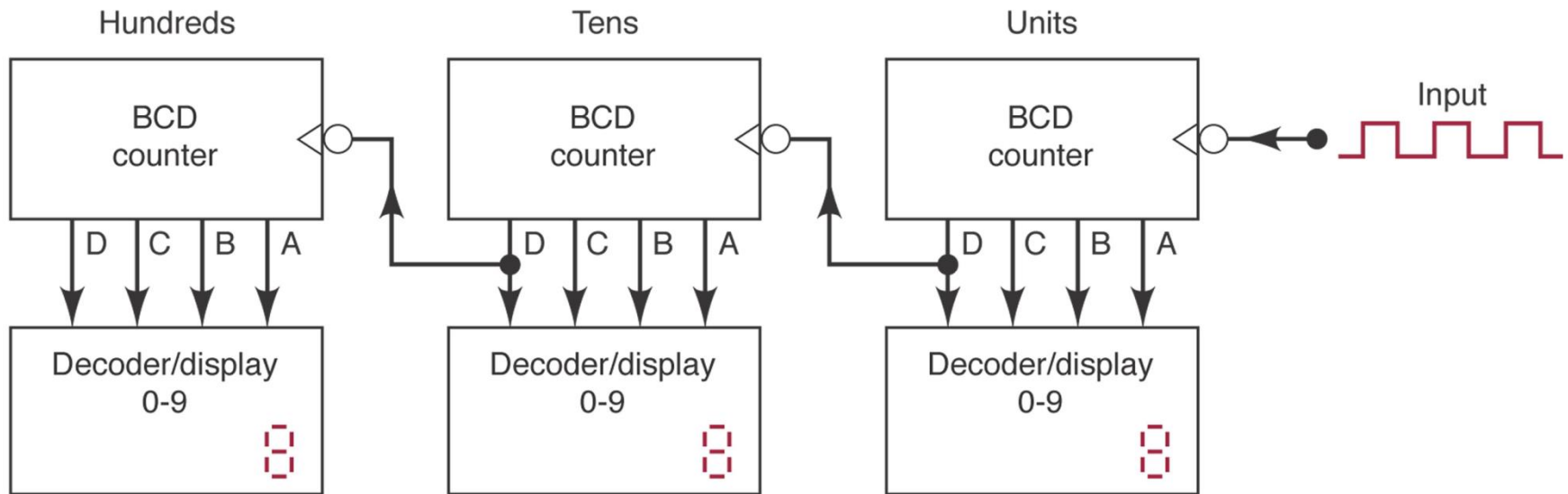- Operation of a decimal 000 to 999 BCD counter



Cascading BCD Counters

- Initially all counters are reset to 0
- Each input pulse advances the first counter once.
- The 10th input pulse causes the counter to recycle, which advances the second counter 1.
- This continues until the second counter (10's digit) recycles, which advances the third counter 1.
- The cycle repeat until 999 is reached and all three counters start again at zero.