

ID Number: .....

Full Name: .....

|  |
|--|
| <p style="text-align: center;"><b>ECEN202</b><br/><b>DIGITAL ELECTRONICS</b><br/><b>Practice TEST</b><br/>2024</p> |
|--|

**Time allowed:** 60 MINUTES

**CLOSED BOOK**

**Permitted materials:** No programmable calculators are allowed.

No electronic dictionaries are allowed.

Paper foreign to English language dictionaries are allowed.

**Instructions:** Attempt ALL questions.

There are 4 questions in this test paper:

**Space for working out your solutions is provided at the end of every section.**


| <b>Question</b> | <b>Topic</b>                    | <b>Allocated Marks</b> | <b>Obtained Marks</b> |  |
|-----------------|---------------------------------|------------------------|-----------------------|--|
| 1               | Logic and Boolean Algebra       | 25                     |                       |  |
| 2               | Combinational Logic             | 35                     |                       |  |
| 3               | Latches and Flip Flops          | 15                     |                       |  |
| 4               | Counters and Frequency Dividers | 25                     |                       |  |
|                 | <b>TOTAL</b>                    | <b>100</b>             |                       |  |

[CLEARLY write your ID number in the space shown above]

**Question 1 – Logic and Boolean Algebra**

**25 marks**

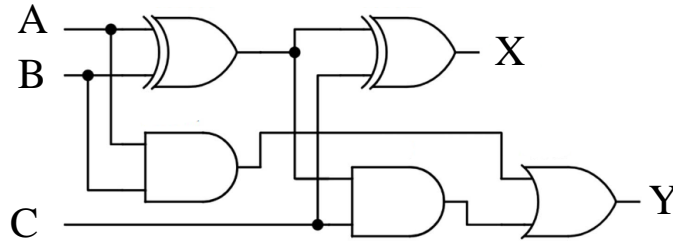a) Write the Boolean expression for the outputs X and Y of the following circuit. (10 marks)




$X = A \text{ xor } B \text{ xor } C = (A'B + AB')C' + (A'B + AB')'C$

—

$Y = AB + C(A \text{ xor } B)$

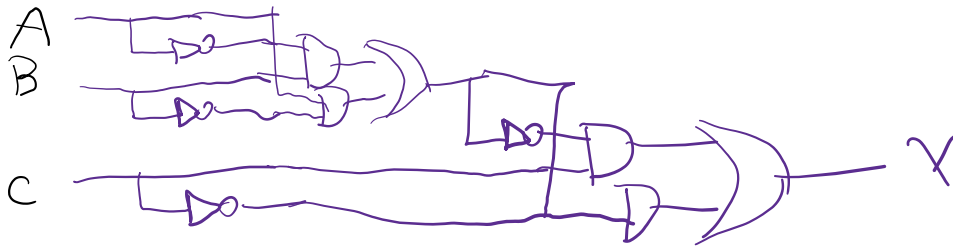b) Draw a circuit diagram for X in part a) using only AND, OR and NOT gates. (8 marks)



c) Simplify using Boolean Algebra (3 marks)

$$\begin{aligned}
 X &= (\overline{AB})(\overline{A} + B)(\overline{B} + B) \\
 &= (\overline{A} + \overline{B})(\overline{A} + B) \\
 &= \overline{A} + \overline{A}B + \overline{A}\overline{B} + B\overline{B} \\
 &= \overline{A} + \overline{A}\overline{B} = \overline{A}
 \end{aligned}$$

a) Simplify using Boolean Algebra (4 marks)


$$\begin{aligned}
 X &= ABC + A\overline{B}(\overline{A}\overline{C}) \\
 &= ABC + A\overline{B}(A + C) \\
 &= ABC + A\overline{B} + A\overline{B}C \\
 &= AC + A\overline{B} \\
 &= A(C + \overline{B})
 \end{aligned}$$

[CLEARLY write your ID number in the space shown above]

**Question 2 – Combinational Logic**

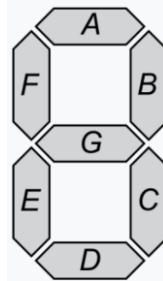**35 marks**

We want to design a logic circuit for a 7-segment LED display shown below.



The inputs are 4 binary digits **d**, **c**, **b**, **a**, which represent the number to be displayed on the LED. Bit **d** is the most significant bit (MSB), and **a** is the least significant bit (LSB). Each LED segment (labelled A, B, C, ... G on the diagram) has its own logic. For example, LED D is ON when **dcb**a represent decimal numbers 0, 2, 3, 5, 6, 8 or 9.

a) Produce a truth table to drive LED labelled **E** **0 2 6 8** (10 marks)

| <b>d</b> | <b>c</b> | <b>b</b> | <b>a</b> | <b>E</b> |
|----------|----------|----------|----------|----------|
| 0        | 0        | 0        | 0        | 1        |
| 0        | 0        | 0        | 1        | 0        |
| 0        | 0        | 1        | 0        | 1        |
| 0        | 0        | 1        | 1        | 0        |
| 0        | 1        | 0        | 0        | 0        |
| 0        | 1        | 0        | 1        | 0        |
| 0        | 1        | 1        | 0        | 1        |
| 0        | 1        | 1        | 1        | 0        |
| 1        | 0        | 0        | 0        | 1        |
| 1        | 0        | 0        | 1        | 0        |
| 1        | 0        | 1        | 0        | X        |
| 1        | 0        | 1        | 1        | X        |
| 1        | 1        | 0        | 0        | X        |
| 1        | 1        | 0        | 1        | X        |
| 1        | 1        | 1        | 0        | X        |
| 1        | 1        | 1        | 1        | X        |

b) Write the sum-of-products (SOP) expression for E (5 marks)

**$E = d'c'b'a' + d'c'ba' + d'cba' + dcb'a'$**

[CLEARLY write your ID number in the space shown above]


c) Use a K-map to simplify the logic expression for E. (10 marks)

(Write your answer in the table provided below. Clearly mark the loop(s) of adjacent 1s.)

|      | b'a' | b'a | ba | ba' |
|------|------|-----|----|-----|
| d'c' | 1    | 0   | 0  | 1   |
| d'c  | 0    | 0   | 0  | 1   |
| dc   | x    | x   | x  | x   |
| dc'  | 1    | 0   | x  | x   |

$$E = c'a' + ba' = a'(b+c')$$

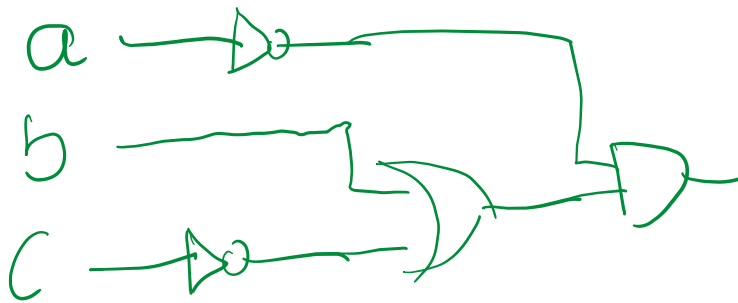d) Draw a logic diagram for G using as few gates as possible. (10 marks)





[CLEARLY write your ID number in the space shown above]

**Question 3 – Latches and Flip Flops**

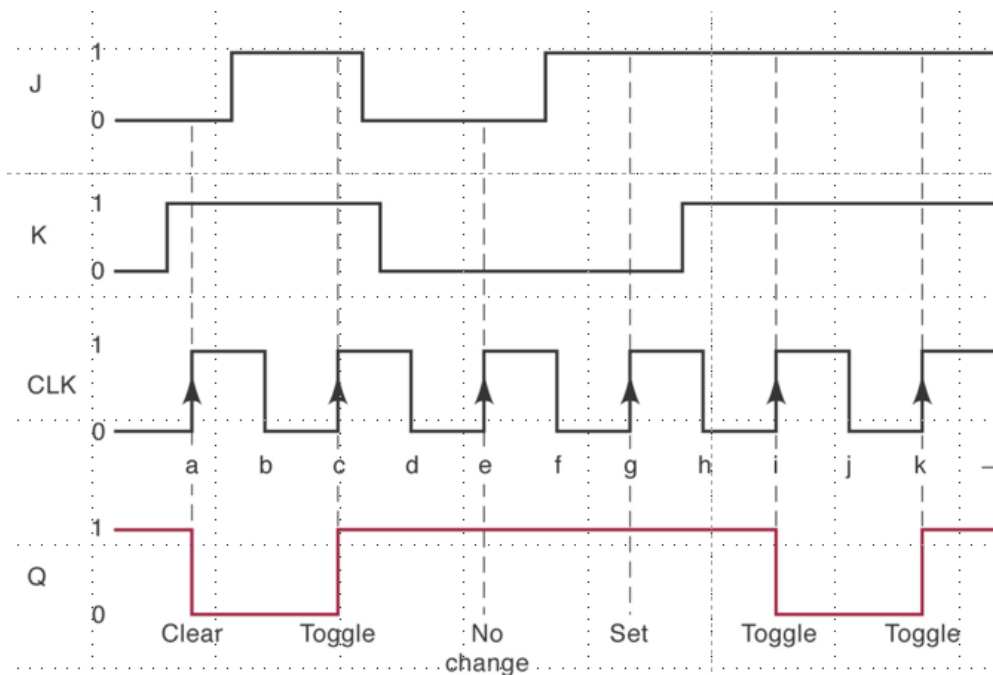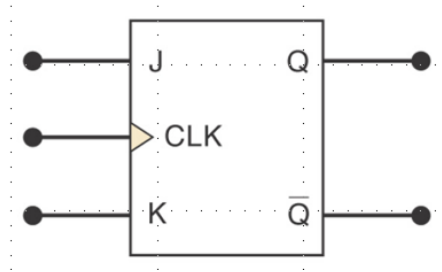**15 marks**

For the Flip Flop and the timing diagram below, draw the resulting output waveform Q. Explain the reason for each change in the value of Q. Assume Q starts **high**.




[CLEARLY write your ID number in the space shown above]

**Question 4 – Counters and Frequency Dividers**

**25 marks**

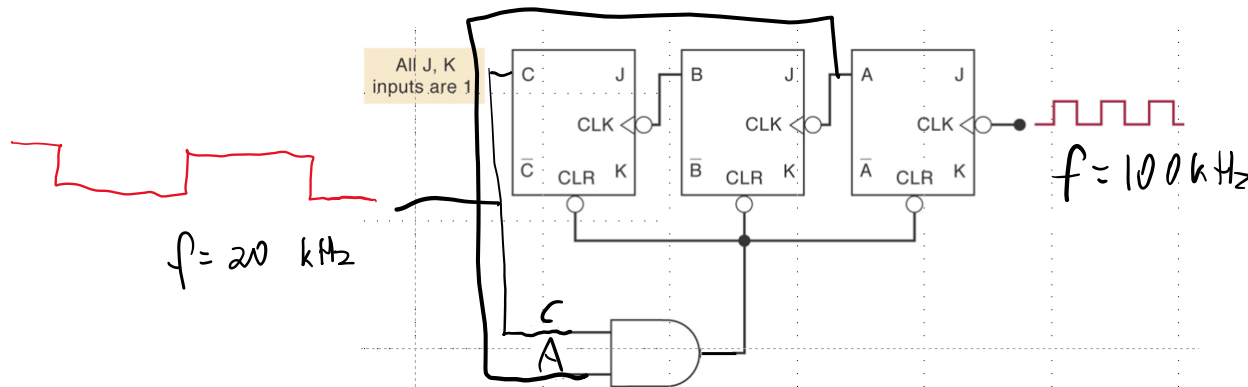- a) Using J-K Flip Flops, design a circuit that produces a 20 kHz clock from a 100kHz clock. You must use an **asynchronous** design. (7 marks)

To divide the clock by 5, we need a MOD 5 counter. Thus, we use 3 JK FFs and use C=A=1 to reset it at 5. All J,K inputs = 1.



- b) Using J-K Flip Flops, design a logic circuit that produces a 30 kHz clock from a 90 kHz clock. This time use a **synchronous** design. (18 marks)

Hint: What is the Mod Number? How many FFs do you need? You can use the JK excitation table at the back of the test.

We require a MOD 3 counter, so 2 FFs are needed. The states of the counter are: 00 – 01 – 10 – 00 ... Use excitation table for JK:

| Q(n) |   | Q(n+1) |   | J1 | K1 | J0 | K0 |
|------|---|--------|---|----|----|----|----|
| B    | A | B      | A |    |    |    |    |
| 0    | 0 | 0      | 1 | 0  | x  | 1  | x  |
| 0    | 1 | 1      | 0 | 1  | x  | x  | 1  |
| 1    | 0 | 0      | 0 | x  | 1  | 0  | x  |
| 1    | 1 | x      | x | x  | x  | x  | x  |


|           |    |   |
|-----------|----|---|
| <b>J1</b> | A' | A |
| B'        | 0  | 1 |
| B         | x  | x |

|           |    |   |
|-----------|----|---|
| <b>K1</b> | A' | A |
| B'        | x  | x |
| B         | 1  | x |

|           |    |   |
|-----------|----|---|
| <b>J0</b> | A' | A |
| B'        | 1  | x |
| B         | 0  | x |

|           |    |   |
|-----------|----|---|
| <b>K0</b> | A' | A |
| B'        | x  | 1 |
| B         | x  | x |

J1=A, J0=B', K1=1, K0=1;

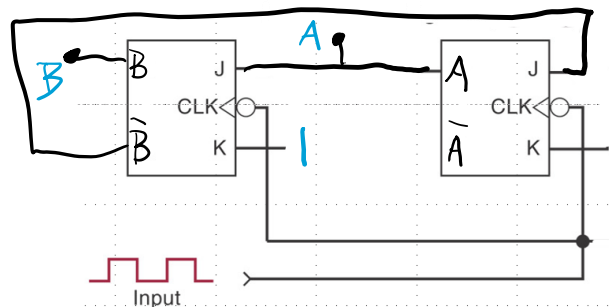

**ID Number:** .....

[CLEARLY write your ID number in the space shown above]

---

[CLEARLY write your ID number in the space shown above]

---


**Fundamental Laws and Theorems of Boolean Algebra**

- |     |  |   |                          |
|-----|--|---|--------------------------|
| 1.  | $X + 0 = X$  | } | OR operations            |
| 2.  | $X + 1 = 1$  |   |                          |
| 3.  | $X + X = X$  |   |                          |
| 4.  | $X + \overline{X} = 1$                               |   |                          |
| 5.  | $X \cdot 0 = 0$                                      | } | AND operations           |
| 6.  | $X \cdot 1 = X$                                      |   |                          |
| 7.  | $X \cdot X = X$                                      |   |                          |
| 8.  | $X \cdot \overline{X} = 0$                           |   |                          |
| 9.  | $\overline{\overline{X}} = X$                        |   | Double complement        |
| 10. | $X + Y = Y + X$                                      | } | Commutative laws         |
| 11. | $XY = YX$  |   |                          |
| 12. | $(X + Y) + Z = X + (Y + Z)$                          | } | Associative laws         |
| 13. | $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$          |   |                          |
| 14. | $X(Y + Z) = XY + XZ$                                 |   | Distribution Law         |
| 15. | $X + Y \cdot Z = (X + Y) \cdot (X + Z)$              |   | Dual of Distributive Law |
| 16. | $X + XZ = X$   | } | Laws of absorption       |
| 17. | $X(X + Z) = X$                                       |   |                          |
| 18. | $X + \overline{X}Y = X + Y$                          | } | Identity Theorems        |
| 19. | $X(\overline{X} + Y) = X \cdot Y$                    |   |                          |
| 20. | $\overline{X+Y} = \overline{X} \cdot \overline{Y}$   | } | De Morgan's Theorems     |
| 21. | $\overline{X \cdot Y} = \overline{X} + \overline{Y}$ |   |                          |



[CLEARLY write your ID number in the space shown above]

**Logic Gate Symbols:**

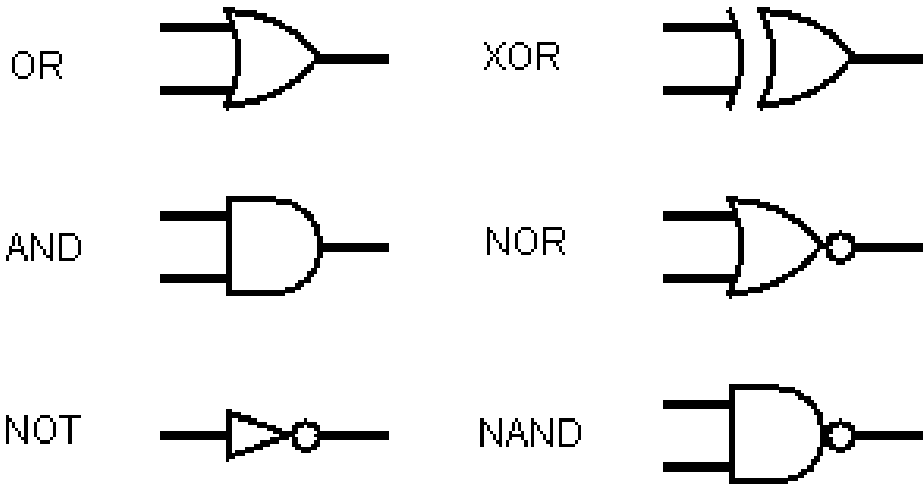

**Excitation tables:**

**JK FF:**

| Present Q | Next Q | J | K |
|-----------|--------|---|---|
| 0         | 0      | 0 | x |
| 0         | 1      | 1 | x |
| 1         | 0      | x | 1 |
| 1         | 1      | x | 0 |

**D FF:**

| Present State Q(n) | Next State Q(n+1) | Input D |
|--------------------|-------------------|---------|
| 0                  | 0                 | 0       |
| 0                  | 1                 | 1       |
| 1                  | 0                 | 0       |
| 1                  | 1                 | 1       |