

ID Number: .....

Full Name: .....

<p style="text-align: center;"><b>ECEN202</b> <b>DIGITAL ELECTRONICS</b> <b>Practice TEST</b> 2024</p>
--

**Time allowed:** 60 MINUTES

**CLOSED BOOK**

**Permitted materials:** No programmable calculators are allowed.

No electronic dictionaries are allowed.

Paper foreign to English language dictionaries are allowed.

**Instructions:** Attempt ALL questions.

There are 4 questions in this test paper:

**Space for working out your solutions is provided at the end of every section.**


<b>Question</b>	<b>Topic</b>	<b>Allocated Marks</b>	<b>Obtained Marks</b>	
1	Logic and Boolean Algebra	25		
2	Combinational Logic	35		
3	Latches and Flip Flops	15		
4	Counters and Frequency Dividers	25		
	<b>TOTAL</b>	<b>100</b>		

[CLEARLY write your ID number in the space shown above]

**Question 1 – Logic and Boolean Algebra**

**25 marks**

 a) Write the Boolean expression for the outputs X and Y of the following circuit. (10 marks)



X = \_\_\_\_\_

Y = \_\_\_\_\_

b) Draw a circuit diagram for X in part a) using only AND, OR and NOT gates. (8 marks)

c) Simplify using Boolean Algebra (3 marks)

$$X = (\overline{AB})(\overline{A} + B)(\overline{B} + B)$$

a) Simplify using Boolean Algebra (4 marks)

$$X = ABC + A\overline{B}(\overline{A}\overline{C})$$



[CLEARLY write your ID number in the space shown above]

c) Use a K-map to simplify the logic expression for E. (10 marks)

(Write your answer in the table provided below. Clearly mark the loop(s) of adjacent 1s.


E =



d) Draw a logic diagram for G using as **few gates as possible**. (10 marks)

[CLEARLY write your ID number in the space shown above]

**Question 3 – Latches and Flip Flops**

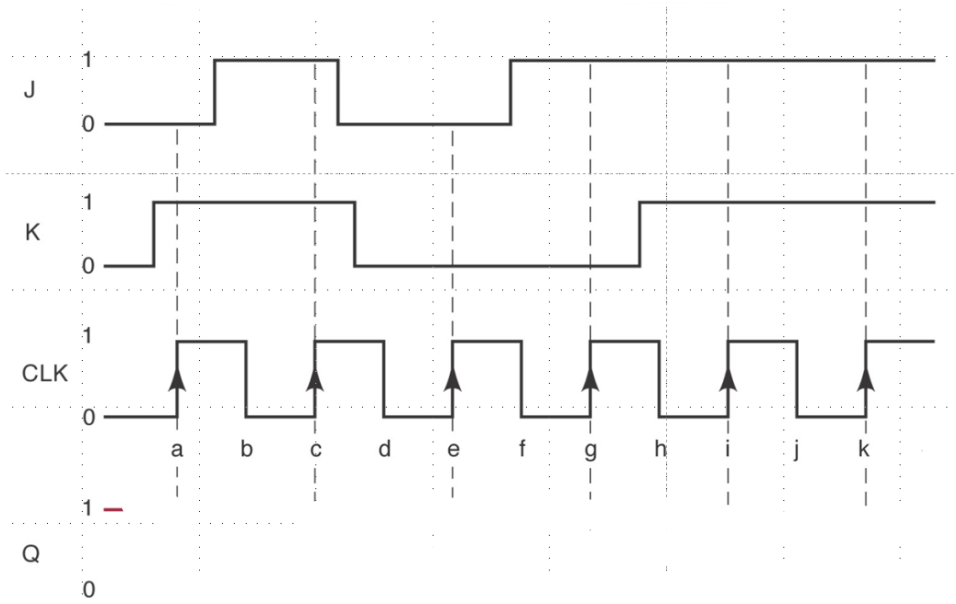 **15 marks**

For the Flip Flop and the timing diagram below, draw the resulting output waveform Q. Explain the reason for each change in the value of Q. Assume Q starts **high**.



[CLEARLY write your ID number in the space shown above]

---

**Question 4 – Counters and Frequency Dividers**

**25 marks**

- a) Using J-K Flip Flops, design a circuit that produces a 20 kHz clock from a 100kHz clock. You must use an **asynchronous** design. (7 marks)

- b) Using J-K Flip Flops, design a logic circuit that produces a 30 kHz clock from a 90 kHz clock. This time use a **synchronous** design. (18 marks)  
Hint: What is the Mod Number? How many FFs do you need? You can use the JK excitation table at the back of the test.

**ID Number:** .....

[**CLEARLY** write your ID number in the space shown above]

---

[CLEARLY write your ID number in the space shown above]

---


**Fundamental Laws and Theorems of Boolean Algebra**

- |     |  |                          |                      |
|-----|--|--------------------------|----------------------|
| 1.  | $X + 0 = X$  | }                        | OR operations        |
| 2.  | $X + 1 = 1$  |                          |                      |
| 3.  | $X + X = X$  |                          |                      |
| 4.  | $X + \overline{X} = 1$                               |                          |                      |
| 5.  | $X \cdot 0 = 0$                                      | }                        | AND operations       |
| 6.  | $X \cdot 1 = X$                                      |                          |                      |
| 7.  | $X \cdot X = X$                                      |                          |                      |
| 8.  | $X \cdot \overline{X} = 0$                           |                          |                      |
| 9.  | $\overline{\overline{X}} = X$                        | Double complement        |                      |
| 10. | $X + Y = Y + X$                                      | }                        | Commutative laws     |
| 11. | $XY = YX$  |                          |                      |
| 12. | $(X + Y) + Z = X + (Y + Z)$                          | }                        | Associative laws     |
| 13. | $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$          |                          |                      |
| 14. | $X(Y + Z) = XY + XZ$                                 | Distribution Law         |                      |
| 15. | $X + Y \cdot Z = (X + Y) \cdot (X + Z)$              | Dual of Distributive Law |                      |
| 16. | $X + XZ = X$   | }                        | Laws of absorption   |
| 17. | $X(X + Z) = X$                                       |                          |                      |
| 18. | $X + \overline{X}Y = X + Y$                          | }                        | Identity Theorems    |
| 19. | $X(\overline{X} + Y) = X \cdot Y$                    |                          |                      |
| 20. | $\overline{X + Y} = \overline{X} \cdot \overline{Y}$ | }                        | De Morgan's Theorems |
| 21. | $\overline{X \cdot Y} = \overline{X} + \overline{Y}$ |                          |                      |



[CLEARLY write your ID number in the space shown above]

**Logic Gate Symbols:**

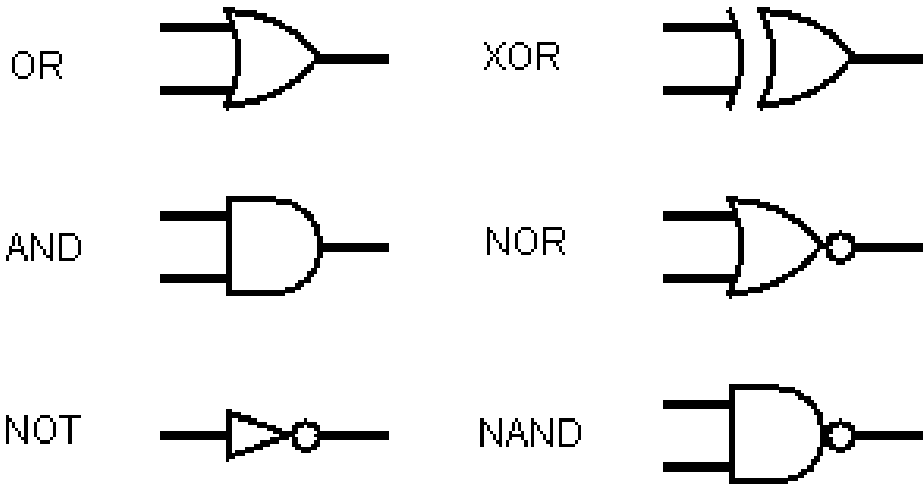

**Excitation tables:**

**JK FF:**

Present Q	Next Q	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

**D FF:**

Present State Q(n)	Next State Q(n+1)	Input D
0	0	0
0	1	1
1	0	0
1	1	1