

# XMUT 202

## Digital Electronics

Felix Yan

School of Engineering and Computer Science  
Victoria University of Wellington

# Logic Gates

---

- We have learned about:
  - AND, OR, NOT Boolean operations
  - Logic circuit diagrams
  - Truth tables
  
- Today
  - NOR and NAND gates
  - Boolean Theorems (for simplifying Boolean expressions)
  - De Morgan's Theorems (for simplifying Boolean expressions)

# Implementing Circuits From Boolean Expressions

---

- It is important to be able to draw a logic circuit from a Boolean expression.

# Implementing Circuits from Boolean Expressions

- It is important to be able to draw a logic circuit from a Boolean expression.

- Simple expression:  $X = A.B.C$

# Implementing Circuits from Boolean Expressions

- It is important to be able to draw a logic circuit from a Boolean expression.

- Simple expression:  $X = A.B.C$

- A more complex example expression:

$$y = AC + \overline{B}\overline{C} + \overline{A}BC$$

Logic circuit for the Boolean expression:


---

$$y = AC + B\bar{C} + \bar{A}BC$$

# Logic circuit for the Boolean expression:

$$y = AC + B\bar{C} + \bar{A}BC$$


OR operations

 

3 inputs

OR gate
 
# Logic circuit for the Boolean expression:



$$y = \bar{A}\bar{C} + \bar{B}C + ABC$$



# NOR Gate

---

- Combine basic AND, OR, and NOT operations.

# NOR Gate

---


- Combine basic AND, OR, and NOT operations.
- The NOR gate is an inverted OR gate. An inversion “bubble” is placed at the output of the OR gate.

# NOR Gate

- Combine basic AND, OR, and NOT operations.
- The NOR gate is an inverted OR gate. An inversion “bubble” is placed at the output of the OR gate.


- The Boolean expression is  $X = \overline{A + B}$

# (a) NOR symbol

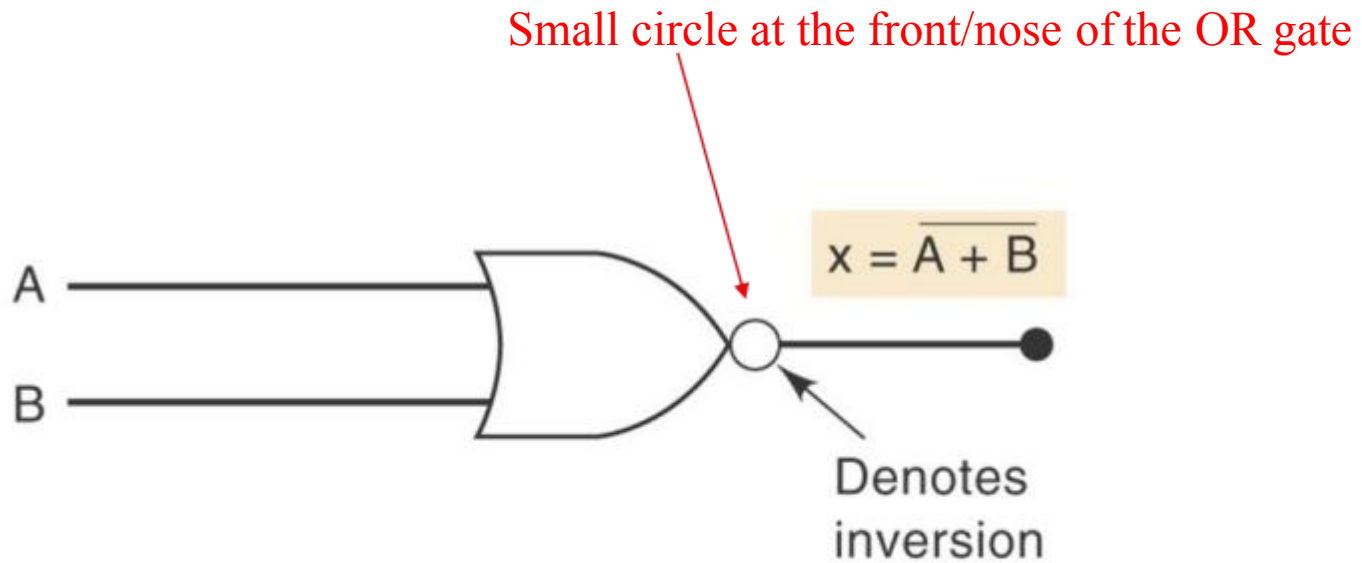


# (a) NOR symbol; (b) equivalent circuit

bubble at the front/nose of the OR gate

 



(a) ↓

 

(b)

# (a) NOR symbol; (b) equivalent circuit; (c) truth table.

bubble at the front/nose of the OR gate

  

A	B	OR		NOR	
		A + B	$\overline{A + B}$		
0	0	0	1		
0	1	1	0		
1	0	1	0		
1	1	1	0		

(c)

Truth table

# NAND Gate

---

- The NAND gate is an inverted AND gate.

# NAND Gate

---

- The NAND gate is an inverted AND gate.

- An inversion “bubble” is placed at the output of an AND gate.



# NAND Gate

---

- The NAND gate is an inverted AND gate.
- An inversion “bubble” is placed at the output of an AND gate.

- The Boolean expression is  $X = \overline{AB}$

# NOR Gates and NAND Gates

---

- The output of NAND and NOR gates may be found by simply determining the output of an AND or OR gate and inverting it.

# NOR Gates and NAND Gates

---


- The output of NAND and NOR gates may be found by simply determining the output of an AND or OR gate and inverting it.
- The truth tables for NOR and NAND gates show the complement of truth tables for OR and AND gates.

# Boolean Theorems

## Single variable theorems

1)


$$x \cdot 0 = 0$$

 


# Boolean Theorems

## Single variable theorems

1)  $x \cdot 0 = 0$

 


2)  $x \cdot 1 = x$

 


# Boolean Theorems

## Single variable theorems


1)  $x \cdot 0 = 0$

 


2)  $x \cdot 1 = x$

 

3)  $x \cdot x = x$

 


4)  $x \cdot \bar{x} = 0$

 


# Boolean Theorems

## Single variable theorems


1)  $x \cdot 0 = 0$

 


2)  $x \cdot 1 = x$

 


3)  $x \cdot x = x$

 


4)  $x \cdot \bar{x} = 0$

 


5)  $x + 0 = x$

 


6)  $x + 1 = 1$

 

7)  $x + x = x$

 

8)  $x + \bar{x} = 1$

 

# Boolean Theorems

Multivariable  
theorems:

$$1) x + y = y + x$$

$$2) x \cdot y = y \cdot x$$

$$3) x + (y + z) = (x + y) + z = x + y + z$$

$$4) x(yz) = (xy)z = xyz$$

$$5) x(y + z) = xy + xz$$

$$6) (w + x)(y + z) = wy + xy + wz + xz$$

$$7) x + xy = x$$

$$8) \underline{x} + xy = \underline{x} + y$$

$$9) x + xy = x + y$$



# De Morgan's Theorems

---

- When the OR sum of two variables is inverted, it is equivalent to inverting each variable individually and ANDing them.

# De Morgan's Theorems

---

- When the OR sum of two variables is inverted, it is equivalent to inverting each variable individually and ANDing them.
- When the AND product of two variables is inverted, it is equivalent to inverting each variable individually and ORing them.

# De Morgan's Theorems

---

- A NOR gate is equivalent to an AND gate with inverted inputs.

$$\overline{(x + y)} = \bar{x} \cdot \bar{y}$$

# De Morgan's Theorems

- A NOR gate is equivalent to an AND gate with inverted inputs.

$$\overline{(x + y)} = \bar{x} \cdot \bar{y}$$

- A NAND gate is equivalent to an OR gate with inverted inputs.

$$\overline{(x \cdot y)} = \bar{x} + \bar{y}$$

# Universality of NAND and NOR gates

---



- NAND or NOR gates can be used to create the three basic logic operations (OR, AND, and NOT also known as the INVERTER)

# Universality of NAND and NOR gates


---

- NAND or NOR gates can be used to create the three basic logic operations (OR, AND, and INVERTER)
- How combinations of NANDs or NORs are used to create the three basic logic operations.

  
# NAND gates can be used to implement any Boolean function.



 
# NAND gates can be used to implement any Boolean function.




(a)

 

INVERTER

 

(b)

 


AND




# NAND gates can be used to implement any Boolean function.




(a)

 


INVERTER

 

(b)

 

AND

 


(c)




OR

 
# NOR gates can be used to implement any Boolean function.





(a)

 

 
# NOR gates can be used to implement any Boolean function.




(a)

  



(b)

 


 
NOR gates can be used to implement any Boolean function.



(a)

  

(b)

  

(c)

