

XMUT 202

Digital Electronics

Felix Yan

School of Engineering and Computer Science
Victoria University of Wellington



Test yourself:

Use a K-map to simplify:

$$y = \overline{C}(\overline{A}\overline{B}\overline{D} + D) + A\overline{B}C + \overline{D}$$

$$y = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{C}\overline{D} + A\overline{B}C + \overline{D}$$


	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$	1	1	0	1
$\overline{A}B$	1	1	0	1
AB	1	1	0	1
$A\overline{B}$	1	1	1	1

$$y = A\overline{B} + \overline{C} + \overline{D}$$

Exclusive OR and Exclusive NOR Circuits

- The exclusive OR, abbreviated XOR produces a HIGH output whenever the two inputs are at opposite levels.
- The exclusive NOR, abbreviated XNOR produces a HIGH output whenever the two inputs are at the same level.
- XOR and XNOR outputs are opposite.

FIGURE 4-20 (a) Exclusive-OR circuit and truth table; (b) traditional XOR gate symbol; (c) IEEE/ANSI symbol for XOR gate.

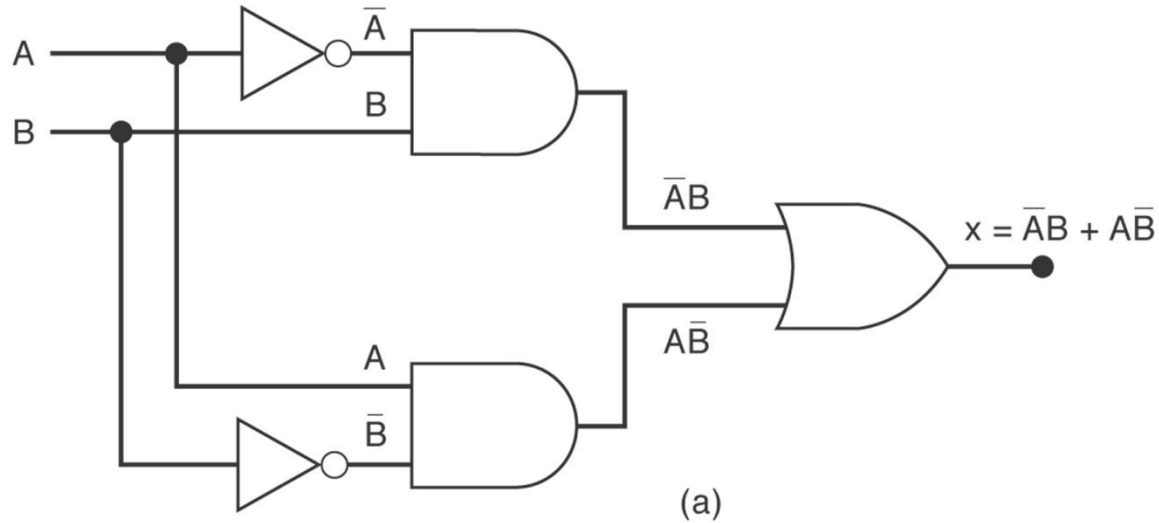

A	B	x
0	0	0
0	1	1
1	0	1
1	1	0

XOR gate symbols



 
 
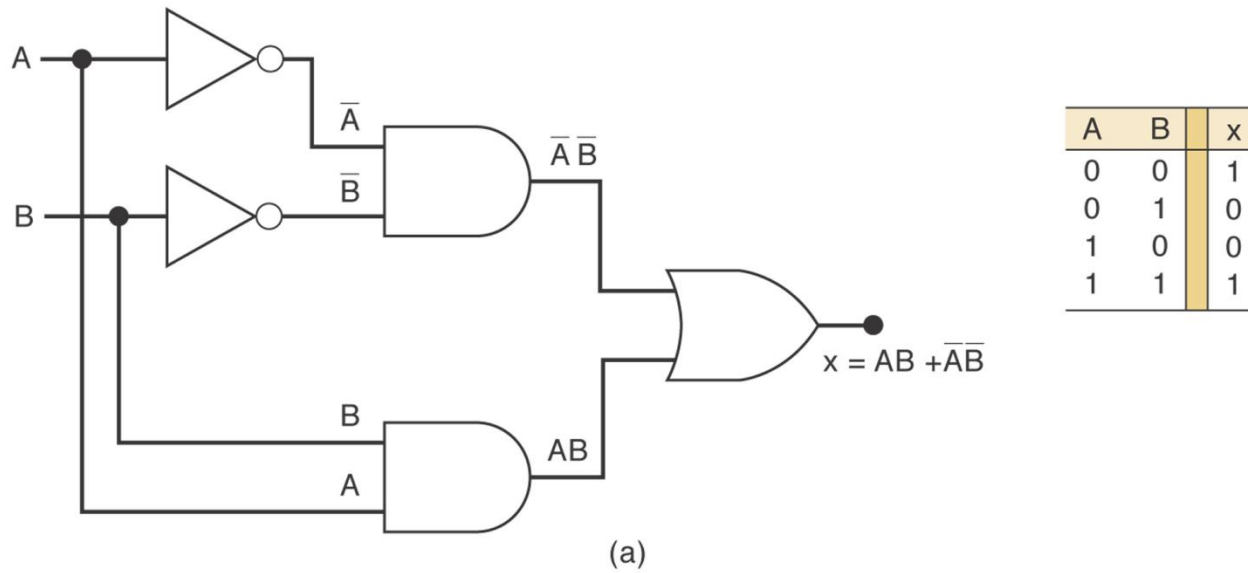




FIGURE 4-21 (a) Exclusive-NOR circuit; (b) traditional symbol for XNOR gate; (c) IEEE/ANSI symbol.

 

XNOR gate symbols

 

  
Determine the O/P waveform of the circuit below:



O/P Hi when I/P at different levels

Design a circuit so that the O/P will only be HI when the combination of two sets of two bit binary numbers are equal.

x_1	x_0	y_1	y_0	z (Output)
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

 

Parity Generator and Checker

- Parity bit: extra bit included with data to make the number of 1's even (for even parity) or odd (for odd parity)
- It is used to detect error in transmission
- Example: if we use an even parity system:
 - Data: 1 1 1 0 – we add a parity bit 1
 - Data: 1 1 0 0 – we add parity bit 0
 - Data: 0 0 0 0 – we add a parity bit 0
- A Parity Checker will return a TRUE error bit if the number of 1's is odd (for even parity) and if the number of 1's is even (for odd parity)

Parity Generator

$$A \oplus B = \bar{A}B + A\bar{B}$$

$$\overline{A \oplus B} = \bar{A}\bar{B} + AB$$

- How to construct an even parity generator (3 bits input)?
- Truth table:

A	B	C	P
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Parity Generator

$$A \oplus B = \bar{A}B + A\bar{B}$$

$$\overline{A \oplus B} = \overline{A\bar{B}} + \overline{\bar{A}B}$$

- How to construct an even parity generator (3 bits input)?
- Truth table:

A	B	C	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$P = \overline{A}BC + \overline{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

Parity Generator

$$A \oplus B = \bar{A}B + A\bar{B}$$

$$\overline{A \oplus B} = \bar{A}\bar{B} + AB$$

- How to construct an even parity generator (3 bits input)?
- Truth table:

A	B	C	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$\begin{aligned} P &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC \\ &= \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + BC) \\ &= \bar{A}(B \oplus C) + A(\overline{B \oplus C}) \\ &= \bar{A}X + A\bar{X} \\ &= A \oplus B \oplus C \end{aligned}$$


Parity Checker

- Homework exercise:
 - Design an even parity checker (3 data bits) using a truth table
 - Express it using XOR or XNOR gates


A	B	C	P	E

Parity Generator and Checker

Similarly for 4 bits:

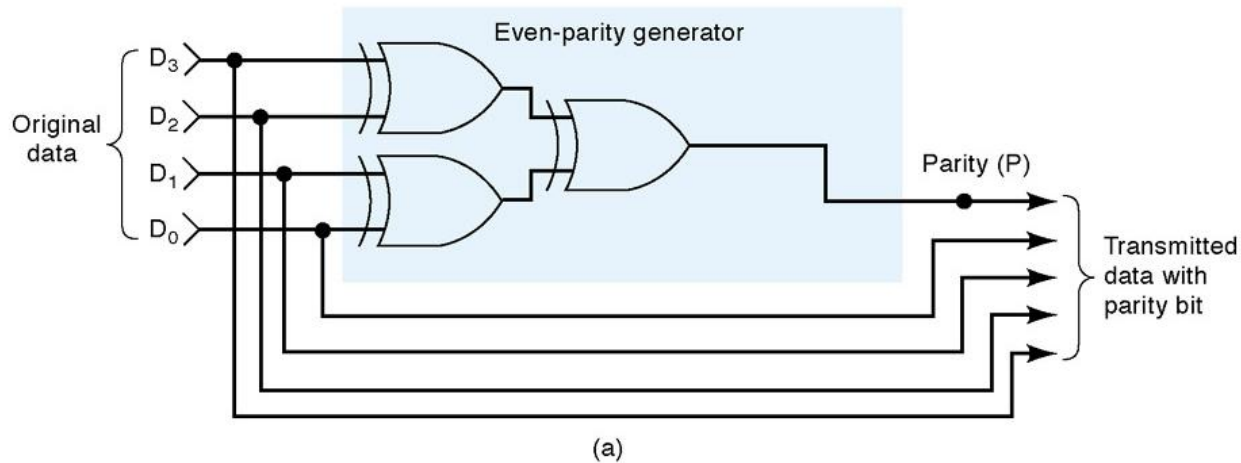

Even Parity:

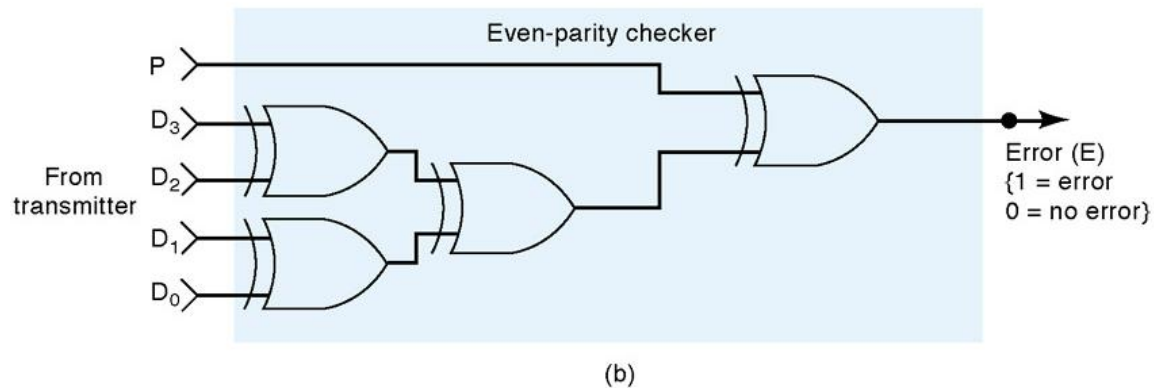

Enable/Disable Circuits

- A circuit is enabled when it allows the passage of an input signal to the output.
- A circuit is disabled when it prevents the passage of an input signal to the output.
- Situations requiring enable/disable circuits occur frequently in digital circuit design.

FIGURE 4-26 Four basic gates can either enable or disable the passage of an input signal, *A*, under control of the logic level at control input *B*.

