



LEC 1. INTRODUCTION

ECEN203

Analogue Circuits and Systems

Introduction


- Learn about circuit terminology;
- Differentiate between active and passive devices;
- Differentiate between a system, circuit and device;
- What is AC and DC?
- Relate electric charge to current, voltage to energy, power to current and voltage, and apply the passive sign convention.
- Describe the properties of dependent and independent sources.

Circuit Terminology

- Electronics
 - ▣ Devices – active vs. passive
 - ▣ Circuits
 - ▣ Systems

Active devices (such as transistors and ICs) require an external power source to operate; in contrast, passive devices (resistors, capacitors, and inductors) do not.

Analysis vs. Synthesis

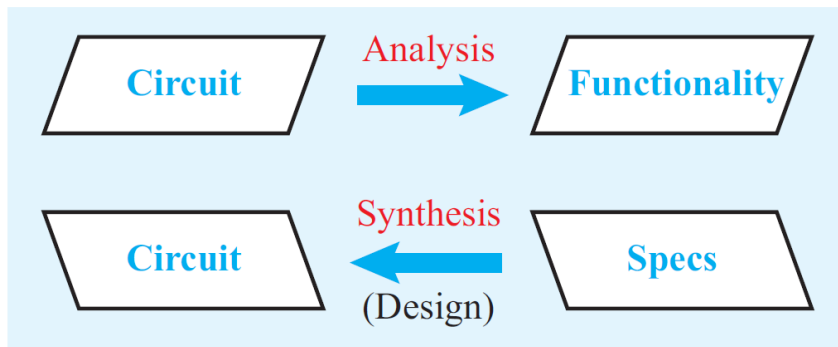

Cell-Phone Architecture

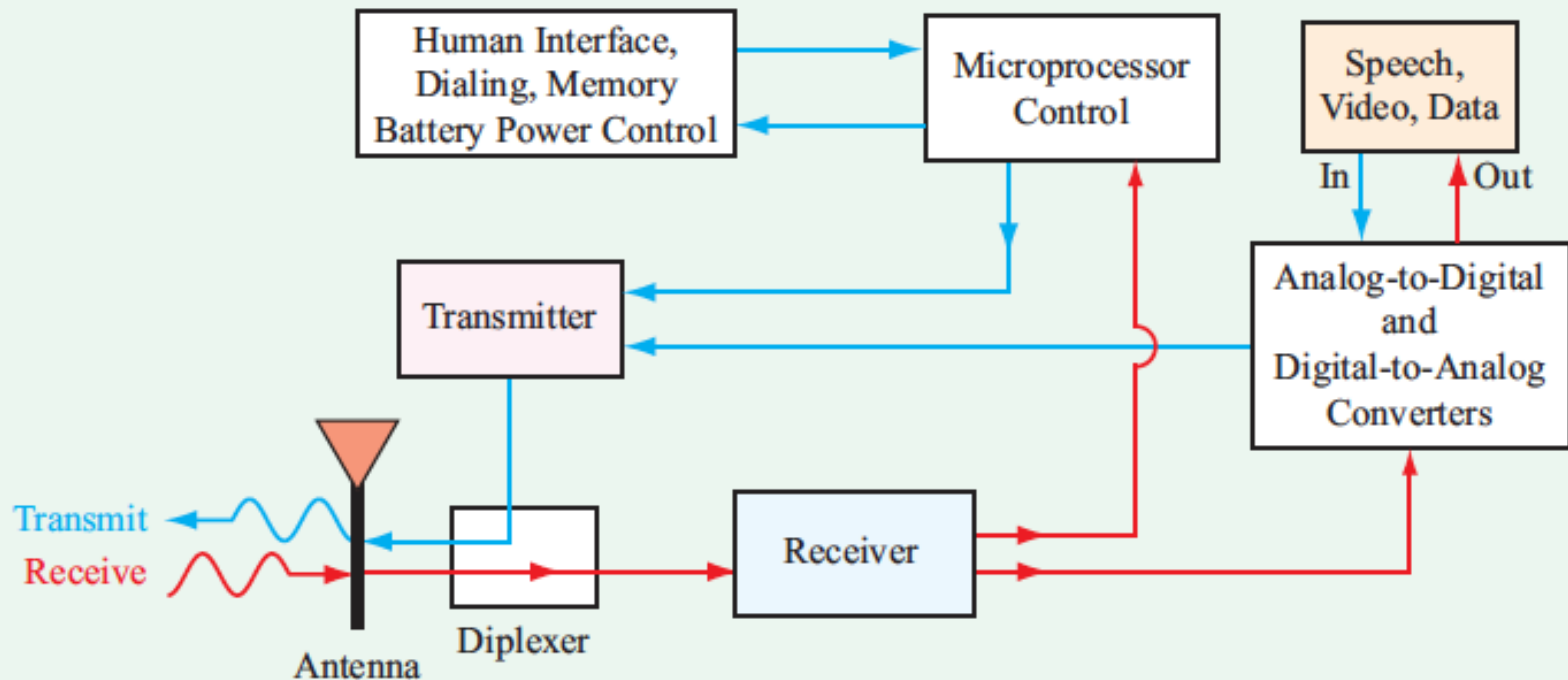


Figure 1-2: Basic cell-phone block diagram. Each block consists of multiple circuits that together provide the required functionality.

Units, Multiples, Notation

Table 1-1: Fundamental SI units.

Dimension	Unit	Symbol
Length	meter	m
Mass	kilogram	kg
Time	second	s
Electric Current	ampere	A
Temperature	kelvin	K
Amount of substance	mole	mol

Table 1-2: Multiple and submultiple prefixes.

Prefix	Symbol	Magnitude
exa	E	10^{18}
peta	P	10^{15}
tera	T	10^{12}
giga	G	10^9
mega	M	10^6
kilo	k	10^3
milli	m	10^{-3}
micro	μ	10^{-6}
nano	n	10^{-9}
pico	p	10^{-12}
femto	f	10^{-15}
atto	a	10^{-18}

As a general rule, we shall use:

- A lowercase letter, such as i for current, to represent the general case:

i *may or may not be time varying*

- A lowercase letter followed with (t) to emphasize time:

$i(t)$ *is a time-varying quantity*



- An uppercase letter if the quantity is not time varying; thus:

I *is of constant value (dc quantity)*


- A letter printed in boldface to denote that:

I *has a specific meaning, such as a vector, a matrix, the phasor counterpart of $i(t)$, or the Laplace or Fourier transform of $i(t)$*


Circuit Representation

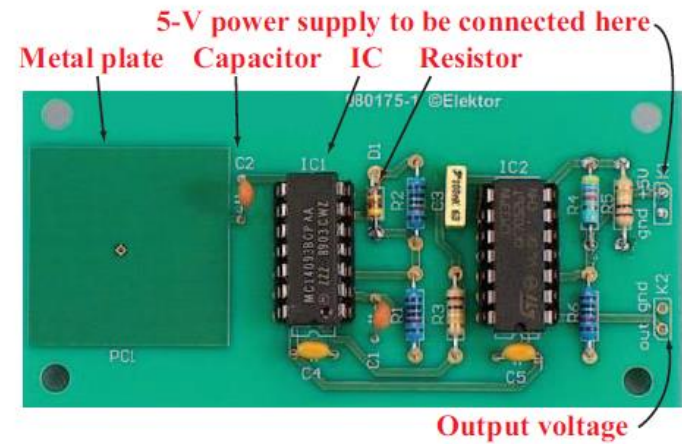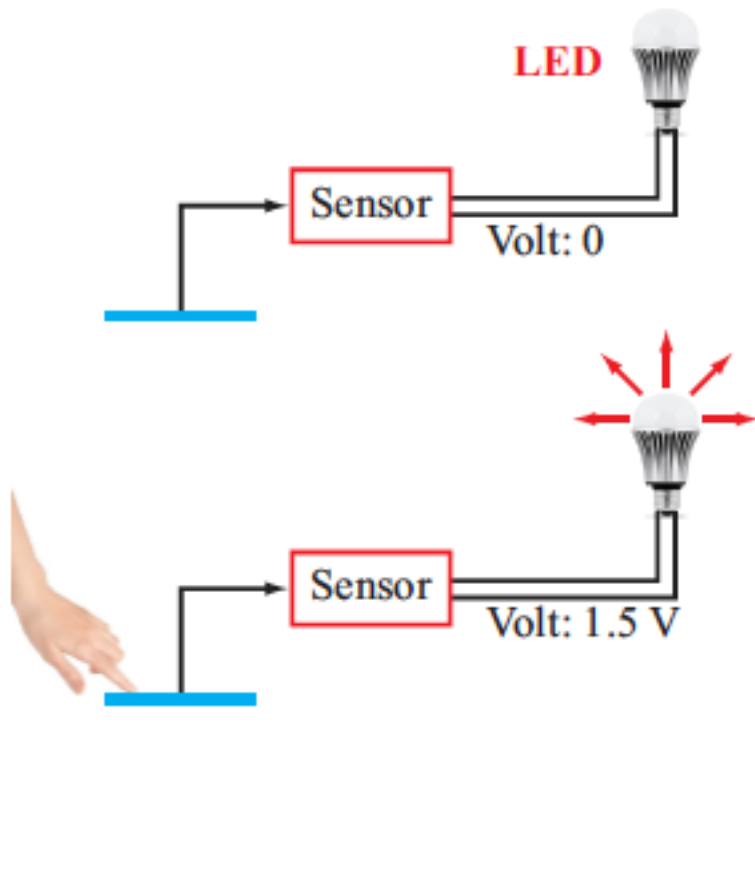

(a) Actual circuit

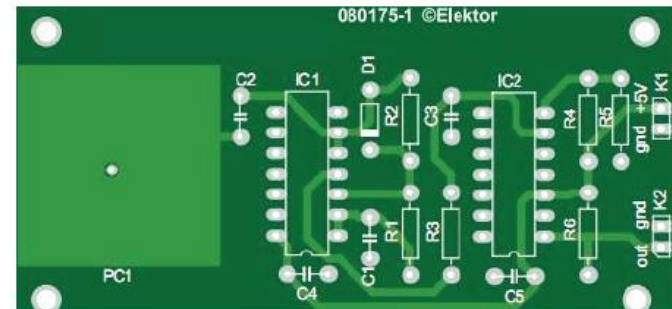






(b) PC board

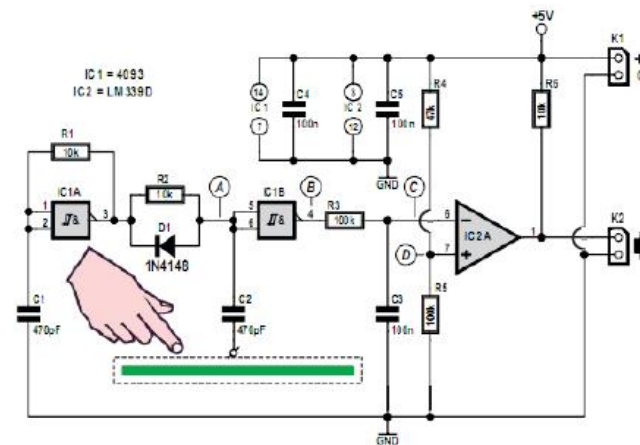

(c) Circuit diagram

Common Circuit Elements

Table 1-3: Symbols for common circuit elements.

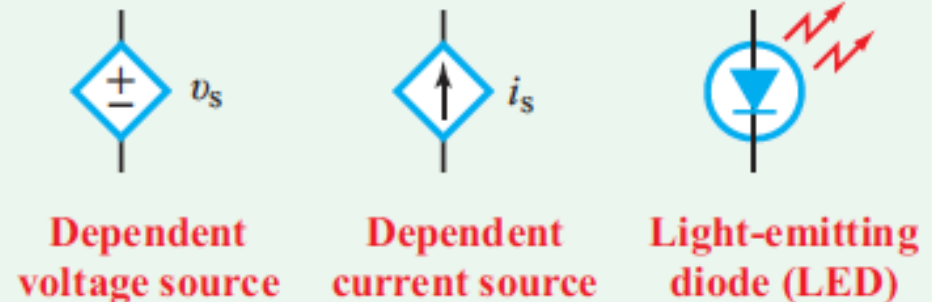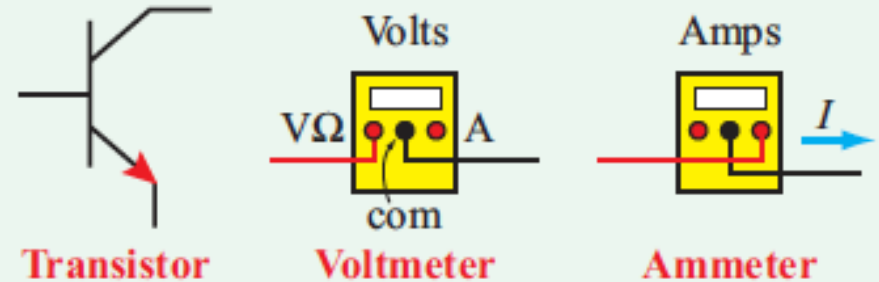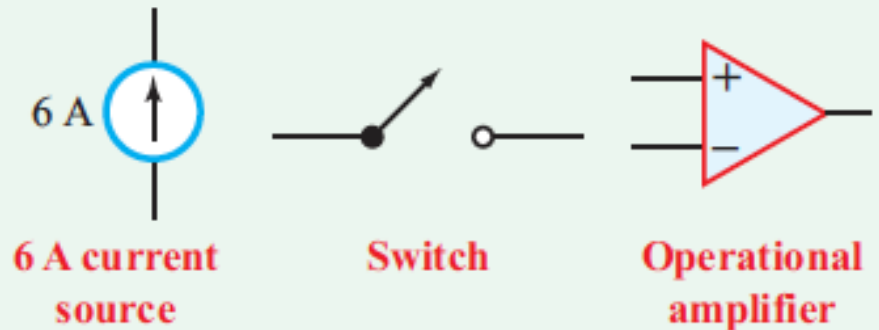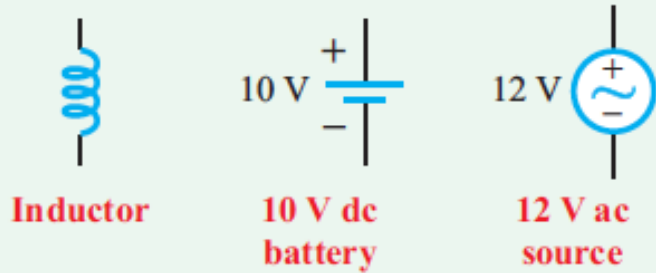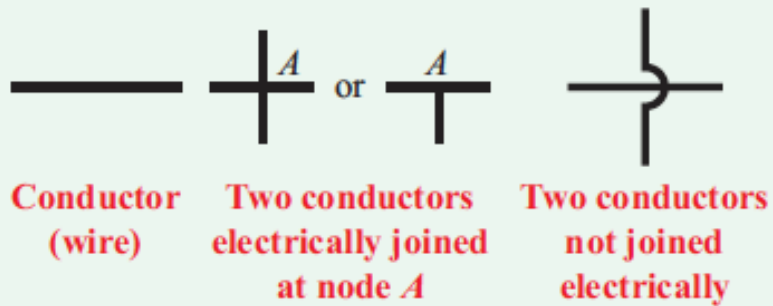


Circuit Topology

Branch: single element, such as a resistor or source

Node: connection point between two or more branches


Extraordinary Node: connection point between at least 3 branches

Loop: closed path in a circuit

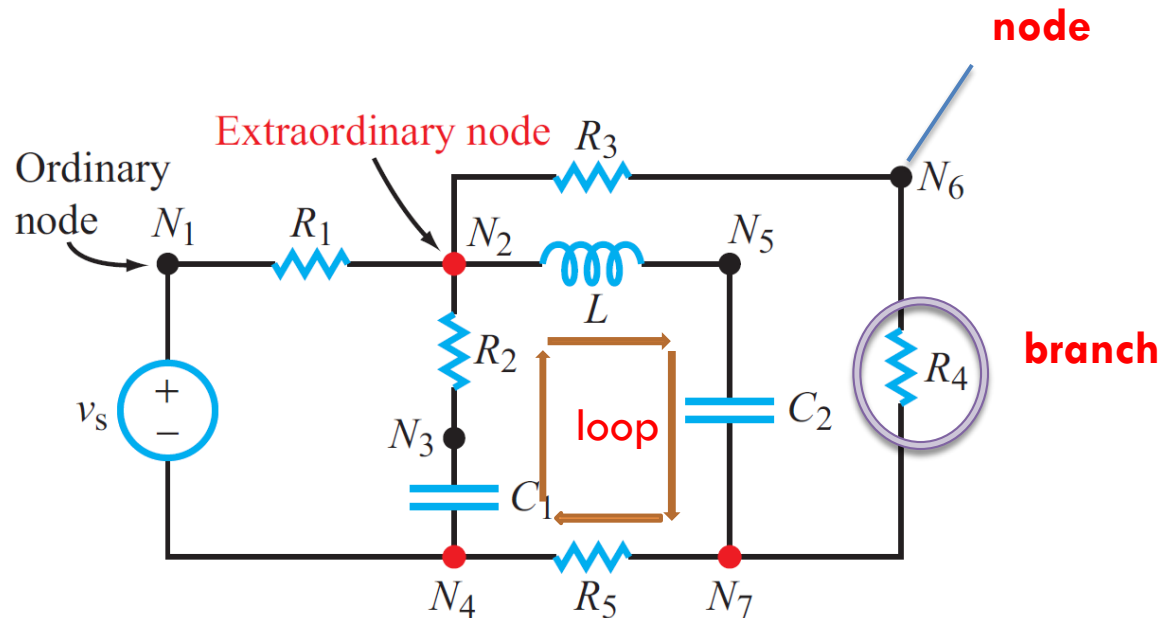


Series and Parallel Connections

In-Series: Same current

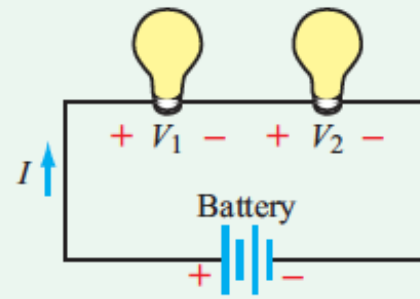


(a) Series circuit

In-Parallel: Same voltage

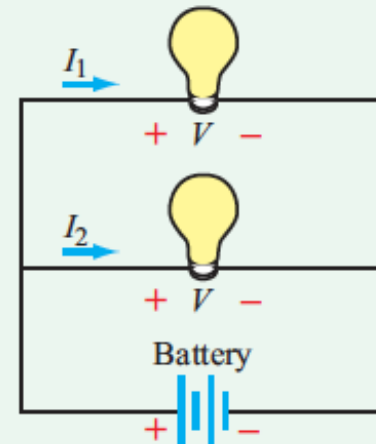

(b) Parallel circuit

Terminology

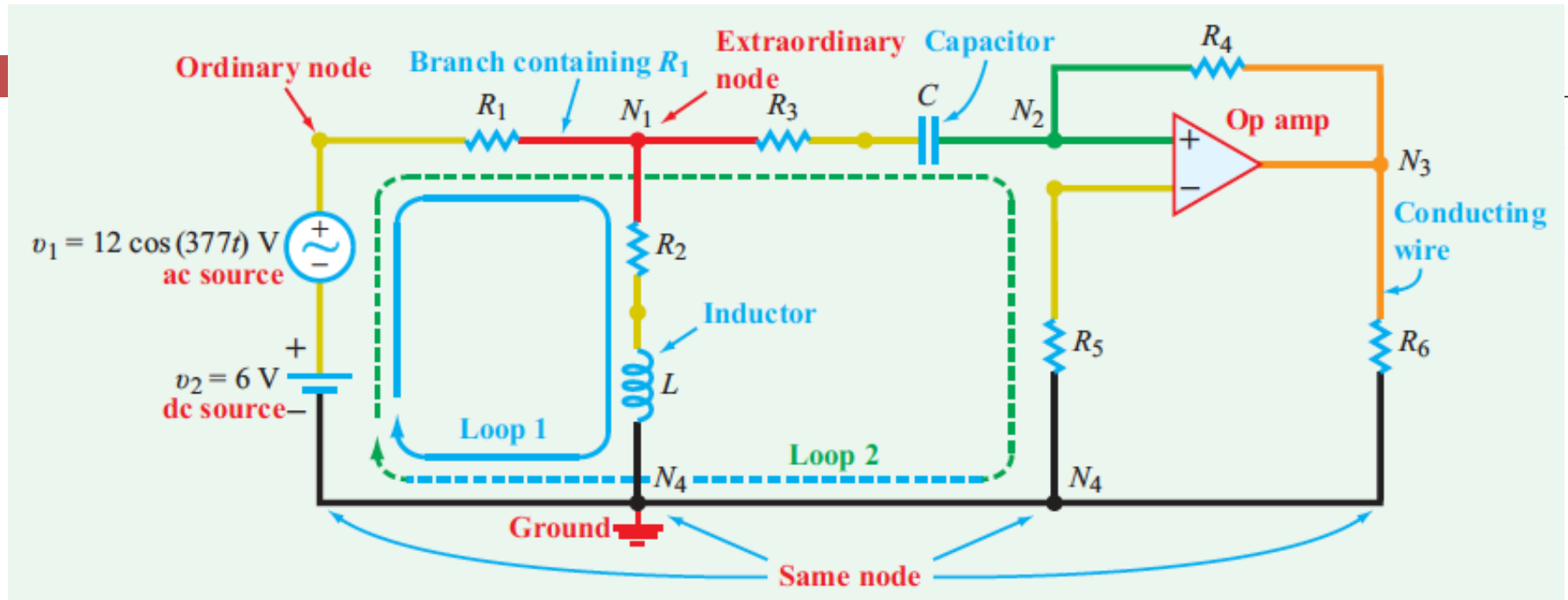

Ordinary node: An electrical connection point that connects to only two elements.

Extraordinary node: An electrical connection point that connects to three or more elements.

Branch: Trace between two consecutive nodes with only one element between them.

Path: Continuous sequence of branches with no node encountered more than once.

Extraordinary path: Path between two adjacent extraordinary nodes.

Loop: Closed path with the same start and end node.

Independent loop: Loop containing one or more branches not contained in any other independent loop.

Mesh: Loop that encloses no other loops.


In-series: Elements that share the same current.

In-parallel: Elements that share the same voltage.

Example 1-1

□ For this circuit,

- (1) Which current is the same as I_2 ?
- (2) Under what circumstance would $I_1 = I_2$?

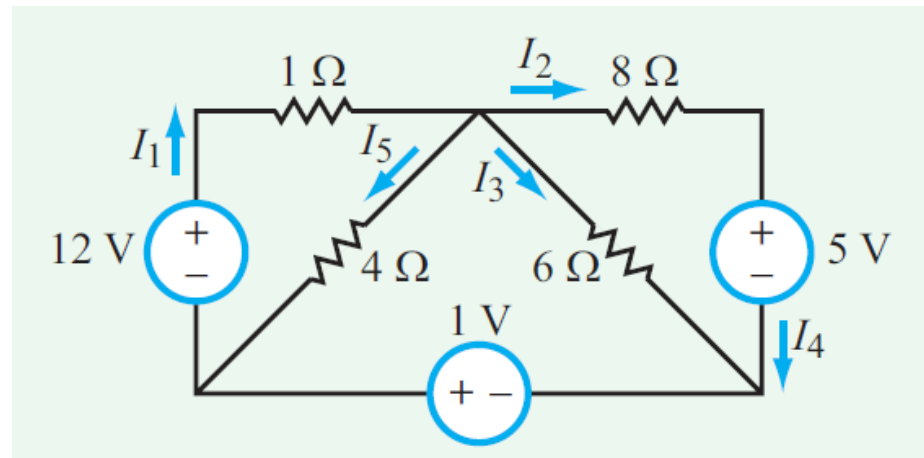

Example 1-1 (solution)

- Two currents are the same if they flow in the same branch and in the same direction. So,


$$(1) \ I_2 = I_4.$$

$$(2) \ I_1 = I_2 \text{ only if } I_3 = I_5 = 0.$$

Example 1-2

□ For this circuit,

- (1) Which node voltages are at the same voltage as node 4?
- (2) Which node voltages are the same as the ground voltage?


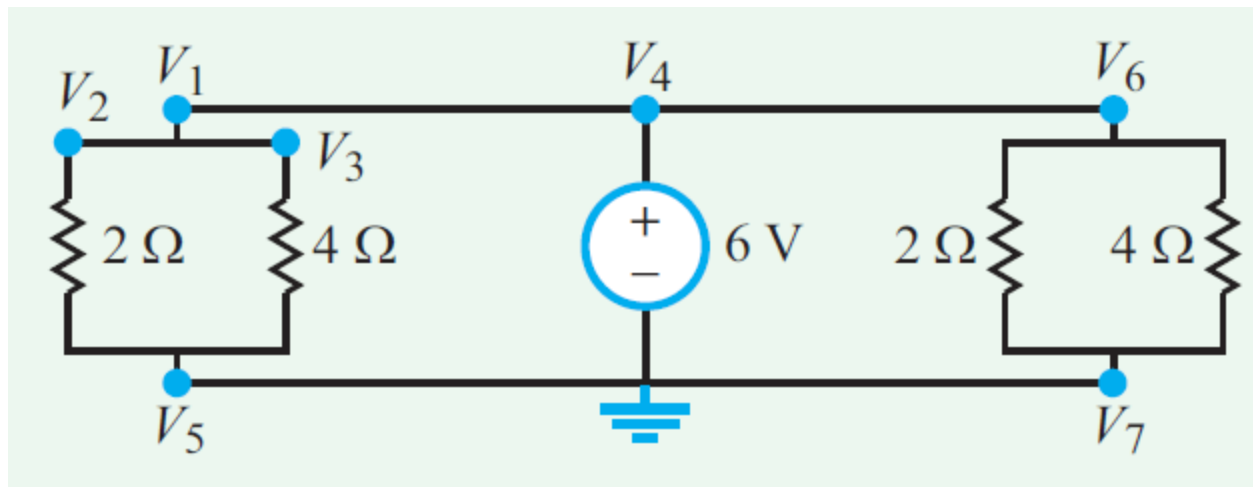


Example 1-2 (solution)

- Two nodes are electrically the same if the only connection between them is a short circuit. So,
 - (1) $V_1 = V_2 = V_3 = V_4 = V_6$, relative to the ground node.
Hence, all five nodes are electrically the same.
 - (2) Nodes V_5 and V_7 are the same as the ground node.

Example 1-3

- Which elements, or combinations of elements, in the circuits are connected in series and which are connected in parallel?

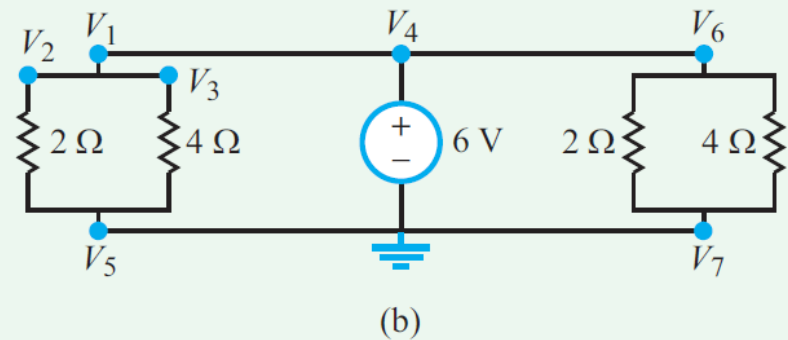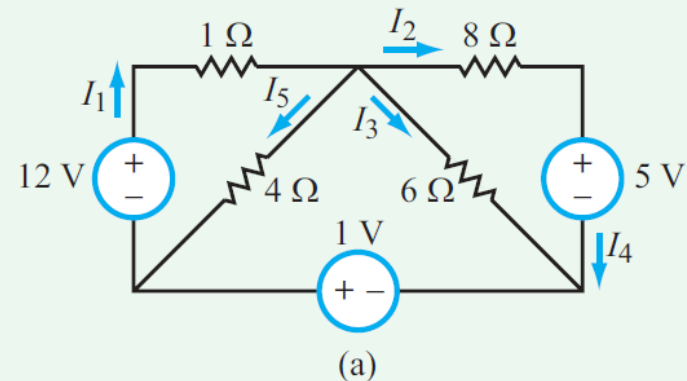

Example 1-3 (solution)

□ For circuit (a),

In series: $8\ \Omega$ resistor and 5 V voltage source (call it combination 1).

In series: $1\ \Omega$ resistor and 12 V voltage source (call it combination 2).

In parallel: $6\ \Omega$ resistor and combination 1. (Call this combination 3.)

In parallel: $4\ \Omega$ resistor and combination 2. (Call this combination 4.)

Also, combination 3, combination 4, and the 1 V source are all in series.


□ For circuit (b),

In series: none.

In parallel: all five elements.


Planar Circuits

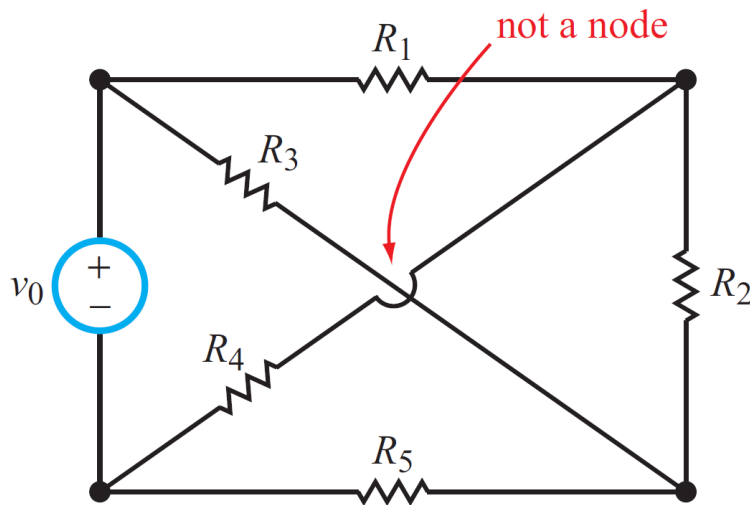- **Planar circuits:** can be drawn in 2-D without branches crossing each other
- Whenever possible, re-draw circuit to simplify!



(a)

Original circuit

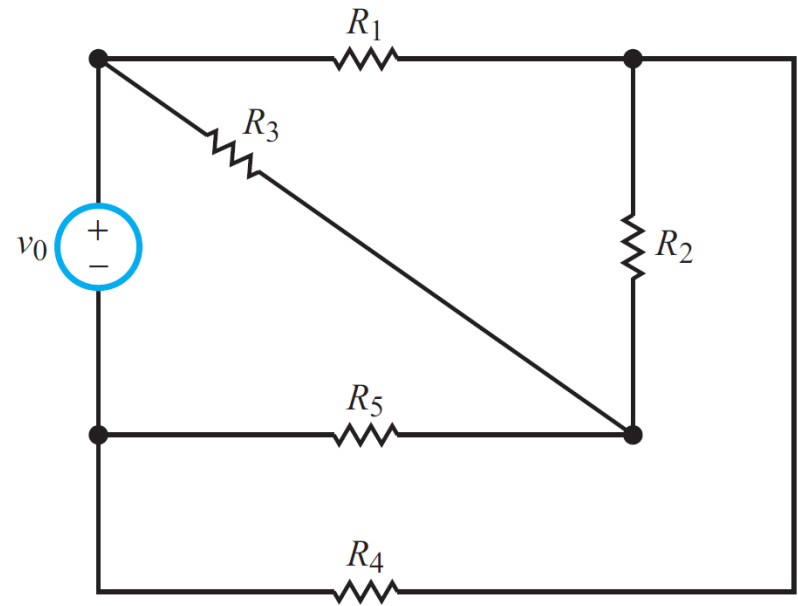


(b)

Redrawn

Non-planar circuits

- This circuit is non-planar because no matter how to redraw, it will always include at least one crossover of branches of branches.

(try it yourself!)

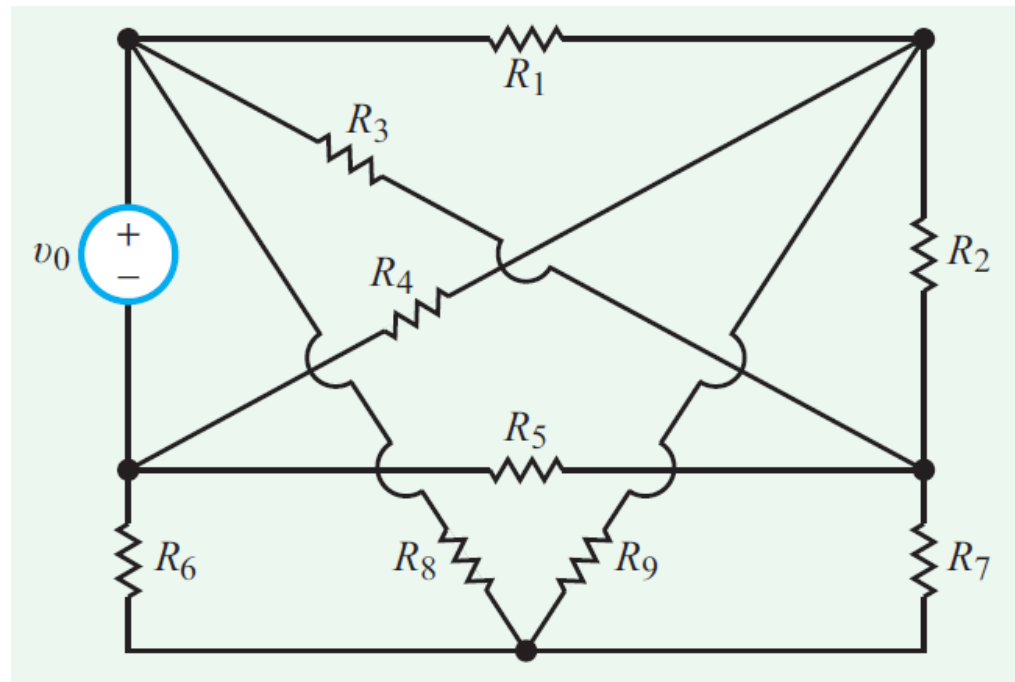

Charge

- **Unit of charge** = coulomb (C)
- Symbol used to represent charge is q $e = 1.6 \times 10^{-19}$ (C)
- Proton is e , electron is $-e$.
- Charge implies “net charge” = sum of all protons – sum of all electrons
- Charge is always an integral multiple of e .

1. Charge can be either positive or negative.
2. The fundamental (smallest) quantity of charge is that of a single electron or proton. Its magnitude usually is denoted by the letter e .
3. According to the law of conservation of charge, the (net) charge in a closed region can neither be created nor destroyed.
4. Two like charges repel one another, whereas two charges of opposite polarity attract.

Current


- Movement of charge, creates electric current.
- Governed by Ohm's law.

► **Electric current** is defined as the time rate of transfer of electric charge across a specified cross section. ◀


$$i = \frac{dq}{dt} \quad (\text{A}),$$

► The direction of electric current I is defined to be the same as the direction of flow that positive charges would follow, which is opposite to the direction of flow of electrons e^- . ◀

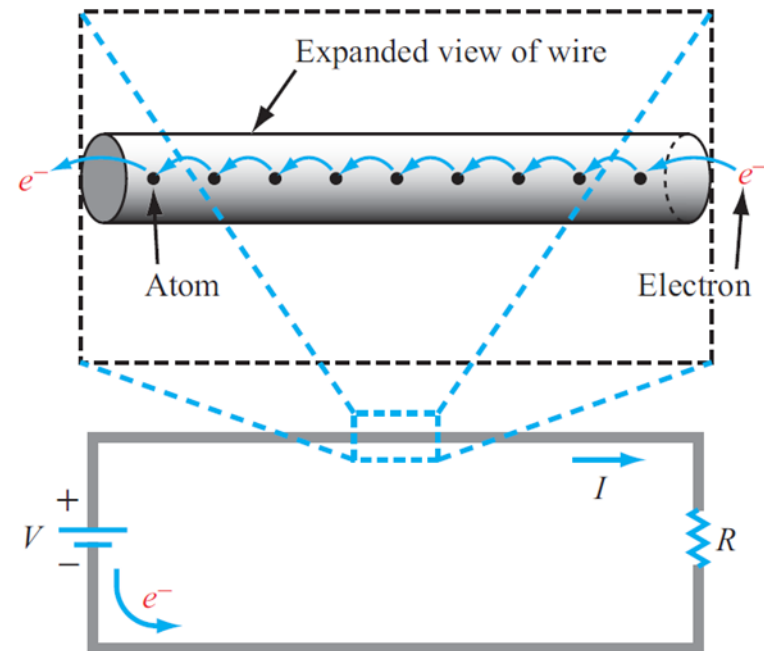
► The current flows from the positive (+) terminal of the battery to its negative (−) terminal, along the path **external** to the battery. ◀




Current

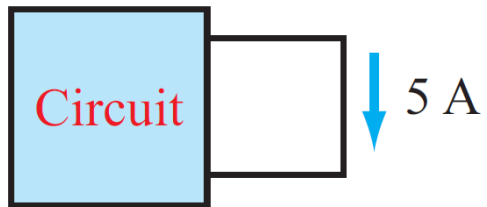


(a)

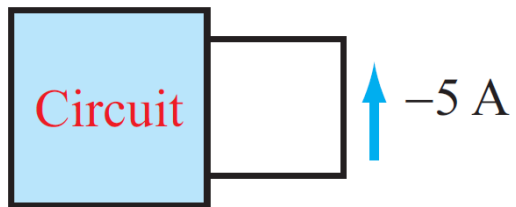


(b)

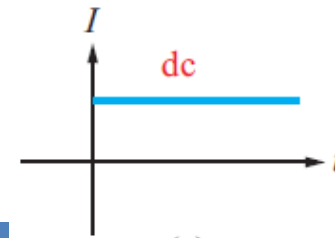


(a)

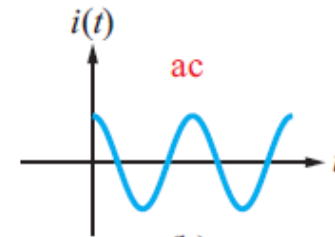


(b)

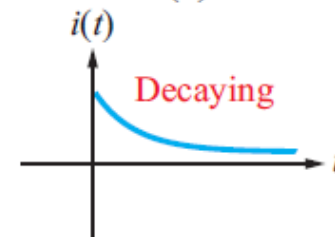

(c)

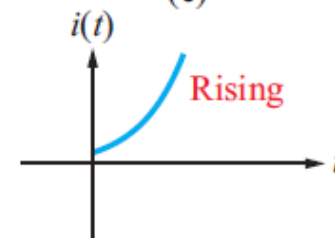

(d)

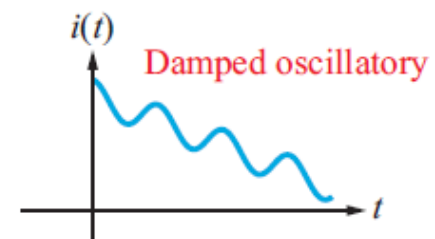


(e)

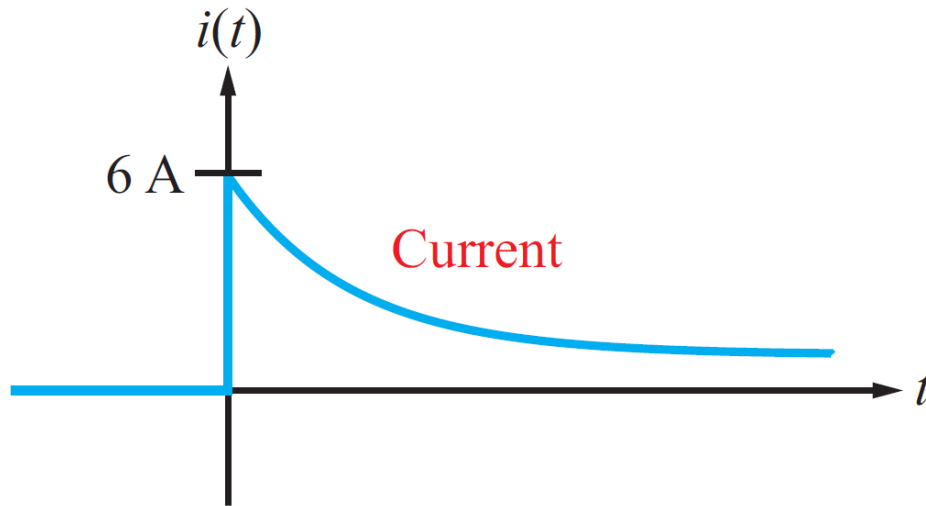Example 1-4: Charge Transfer

□ **Given:**

$$i(t) = \begin{cases} 0 & \text{for } t < 0, \\ 6e^{-0.2t} \text{ A} & \text{for } t \geq 0. \end{cases}$$



Determine: (a) $q(t)$
(b) $\Delta Q(1, 2)$

Solution:

$$dq = i dt$$

$$\int_{-\infty}^t dq = \int_{-\infty}^t i dt$$

$$q(t) - q(-\infty) = \int_{-\infty}^t i dt$$

$$q(t) = \int_{-\infty}^t i dt \quad (\text{C}).$$

Example 1-4: Charge Transfer (cont.)


$$q(t) = \int_0^t 6e^{-0.2t} dt = \frac{-6}{0.2} e^{-0.2t} \Big|_0^t = 30[1 - e^{-0.2t}] \text{ C.}$$

(b)

$$\begin{aligned} \Delta Q(t_1, t_2) &= q(t_2) - q(t_1) \\ &= \int_{-\infty}^{t_2} i dt - \int_{-\infty}^{t_1} i dt = \int_{t_1}^{t_2} i dt. \end{aligned}$$

For $t_1 = 1$ s, $t_2 = 2$ s, and $i(t)$ as given by Eq. (1.4),

$$\begin{aligned} \Delta Q(1, 2) &= \int_1^2 6e^{-0.2t} dt = \frac{6e^{-0.2t}}{-0.2} \Big|_1^2 \\ &= -30(e^{-0.4} - e^{-0.2}) = 4.45 \text{ C.} \end{aligned}$$

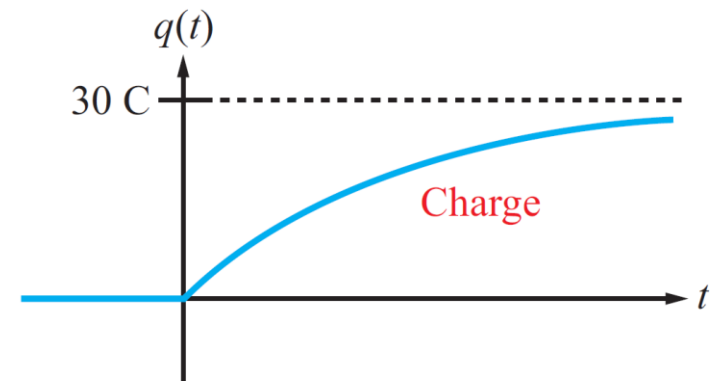

Example 1-5

The charge flowing past a certain location in a wire is given by

$$q(t) = \begin{cases} 0 & \text{for } t < 0, \\ 5te^{-0.1t} \text{ C} & \text{for } t \geq 0. \end{cases}$$

Determine (a) the current at $t = 0$ and (b) the instant at which $q(t)$ is a maximum and the corresponding value of q .

Example 1-5 (solution)

(a)
$$i = \frac{dq}{dt} = \frac{d}{dt}(5te^{-0.1t}) = 5e^{-0.1t} - 0.5te^{-0.1t}$$
$$= (5 - 0.5t)e^{-0.1t} \text{ A.}$$

Setting $t = 0$ in the expression gives $i(0) = 5 \text{ A}$.

Note that $i \neq 0$, even though $q(t) = 0$ at $t = 0$.

(b)

$$\frac{dq}{dt} = (5 - 0.5t)e^{-0.1t} = 0,$$

which is satisfied when

$$5 - 0.5t = 0 \quad \text{or} \quad t = 10 \text{ s,}$$

as well as when

$$e^{-0.1t} = 0 \quad \text{or} \quad t = \infty.$$


be verified either by graphing $q(t)$ or by taking the second derivative of $q(t)$ and evaluating it at $t = 10 \text{ s}$ and at $t = \infty$.

At $t = 10 \text{ s}$,


$$q(10) = 5 \times 10e^{-0.1 \times 10} = 50e^{-1} = 18.4 \text{ C.}$$

The first value ($t = 10 \text{ s}$) corresponds to a maximum and the second value ($t = \infty$) corresponds to a minimum (which can

Voltage & Power

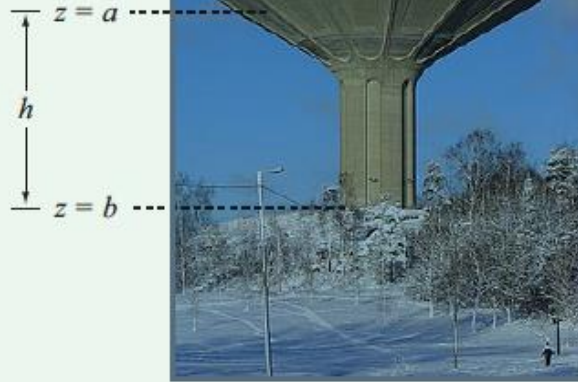


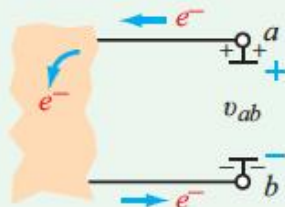
(a) Raising water from ground level at b to height a



(b) Moving charge from a to b

Figure 1-15: Moving charge dq through the material in (b) is analogous to raising mass dm in (a).

$$v_{ab} = \frac{dw}{dq}$$

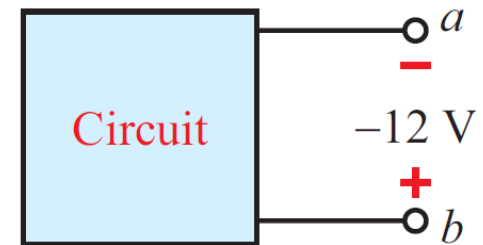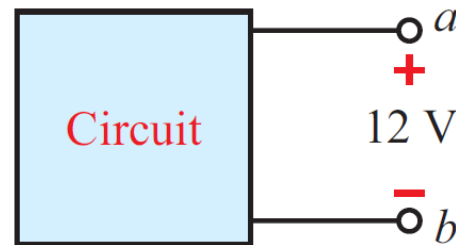

$$V_{ab} = -V_{ba}$$

The voltage between location a and location b is the ratio of dw to dq , where dw is the energy in joules (J) required to move (positive) charge dq from b to a (or negative charge from a to b).

Reference/Ground



- Choose reference point for potential
- Assign potential at reference = 0, called **ground**
- Now all potentials are relative to ground terminal

Example 1-6

- In (a), node 4 was selected as the ground node.
- Supposed node 1 is now selected as the ground node, as shown in (b), use information in (a) to determine node voltages V_2 to V_4 when defined relative to V_1 at node 1.

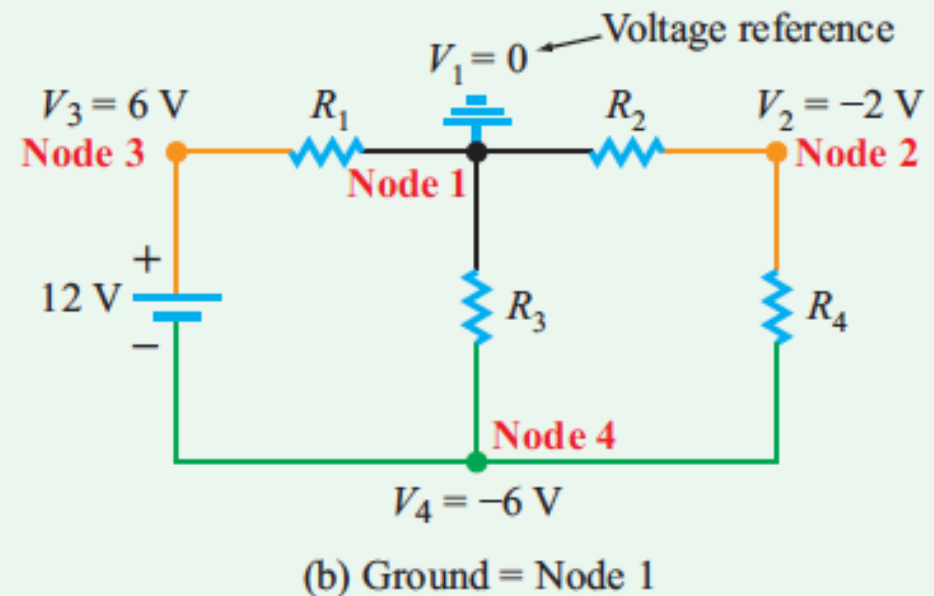
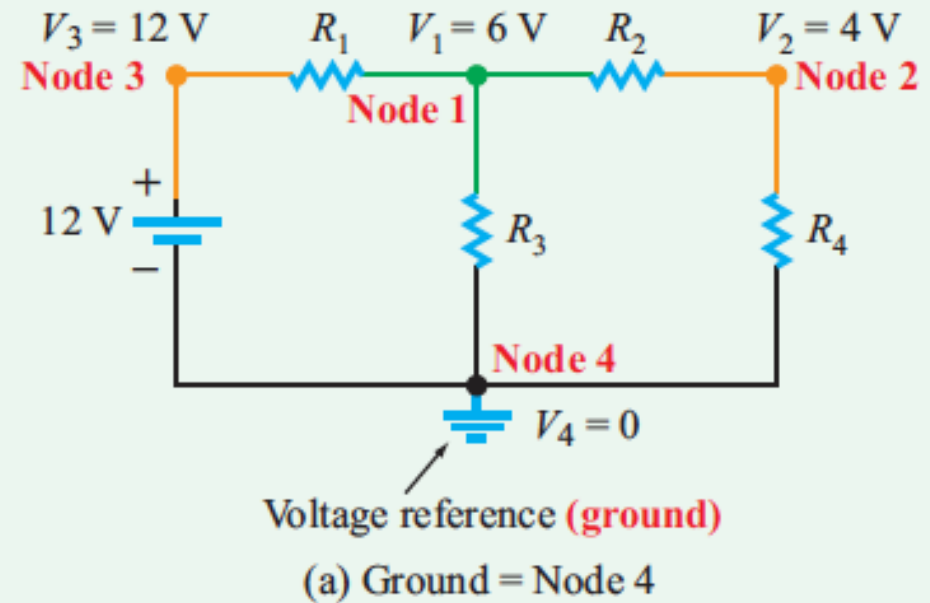


Figure 1-17: Ground is any point in the circuit selected to serve as a reference point for all points in the circuit.

Example 1-6 (solution)


Solution: In the circuit of **Fig. 1-17(a)**, V_2 is 2 V lower in level than V_1 (4 V compared to 6 V). Hence, in the new configuration in **Fig. 1-17(b)**, V_2 will still be 2 V lower than V_1 , and since $V_1 = 0$, it follows that $V_2 = -2$ V. Similarly, $V_3 = 6$ V and $V_4 = -6$ V.

To summarize:


	node 4 = ground	node 1 = ground
$V_1 =$	6 V	0
$V_2 =$	4 V	-2 V
$V_3 =$	12 V	6 V
$V_4 =$	0 V	-6 V

Measuring Voltage & Current

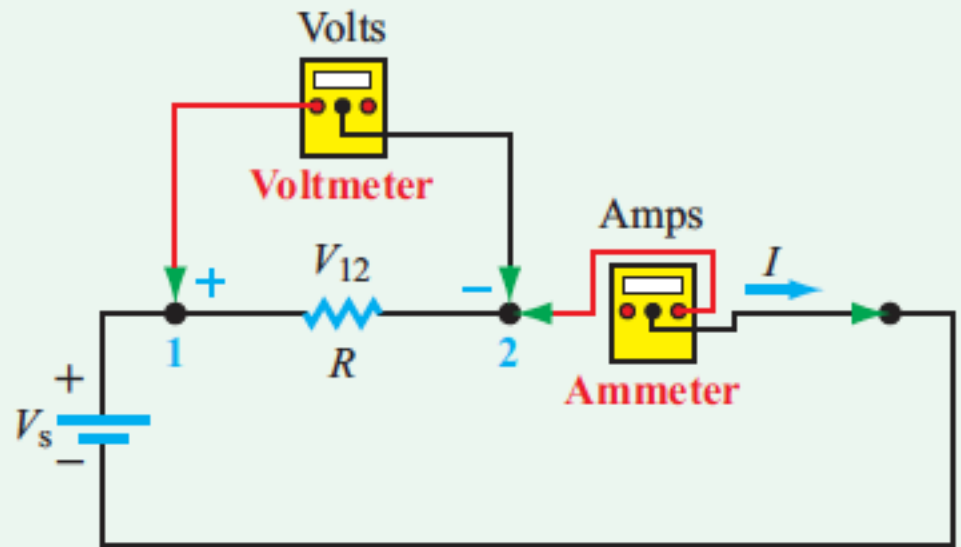- **Voltmeter**: measures voltage
- without drawing current
- **Ammeter**: measures current
- without dropping voltage




(a) Voltmeter and ammeter connections

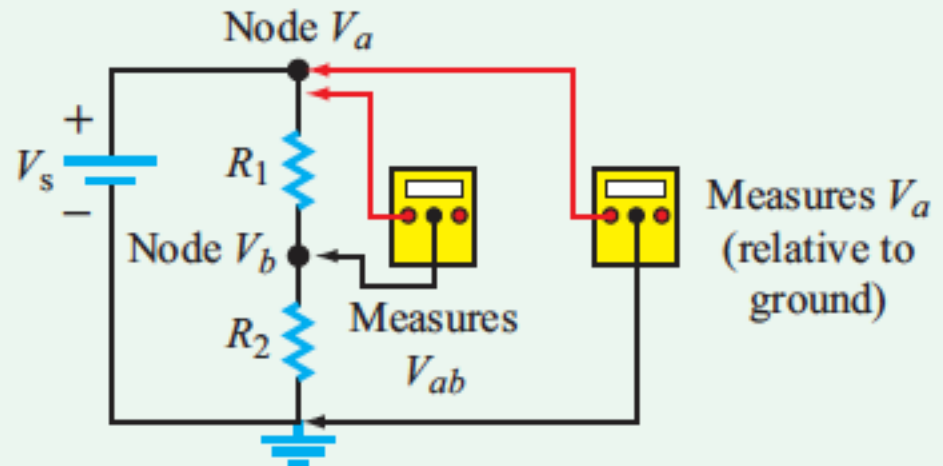

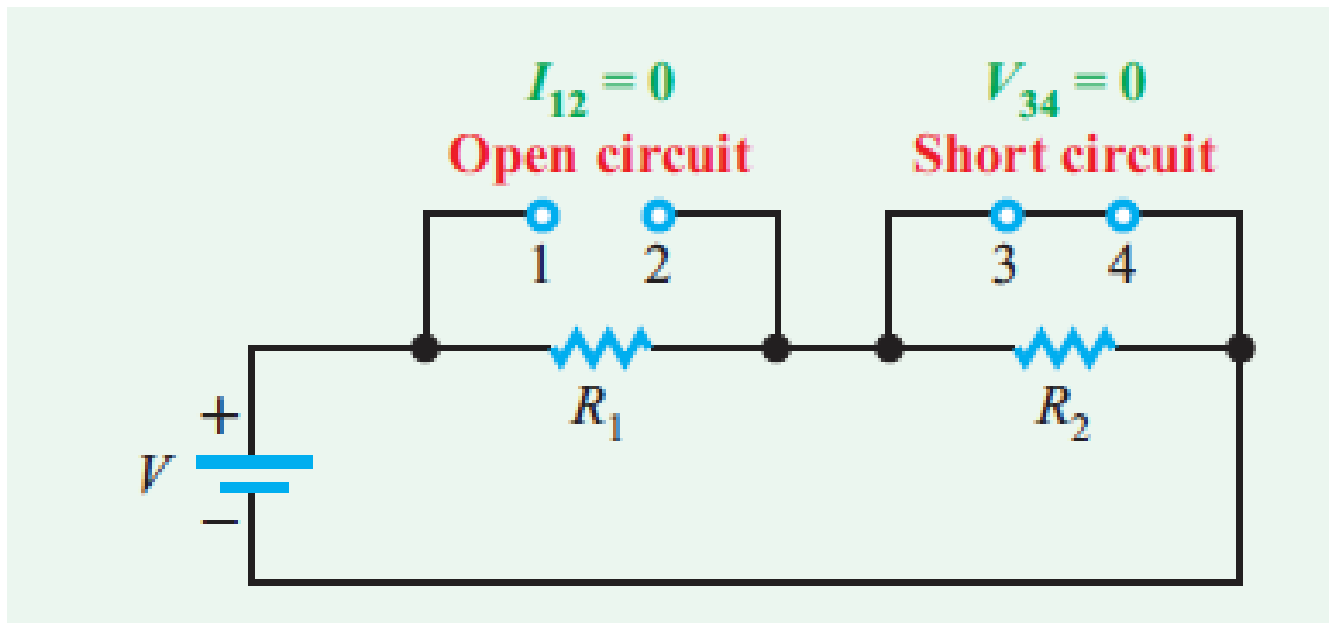(b) Voltmeters connected to measure voltage difference V_{ab} and node voltage V_a (relative to ground)

Open Circuit & Short Circuit

- **Open circuit:** no path for current flow ($R = \infty$)
- **Short circuit:** no voltage drop ($R = 0$)



Power

Rate of expending or absorbing energy



$$P = \frac{dw}{dt} = \frac{dw}{dq} \frac{dq}{dt} = vi$$


$$\sum P = 0 \quad \text{Energy conservation}$$

Units: watts

One watt = power rate of one joule of work per second. $1 \text{ W} = 1 \text{ A} \times 1 \text{ V}$

Passive Sign Convention

Passive Sign Convention

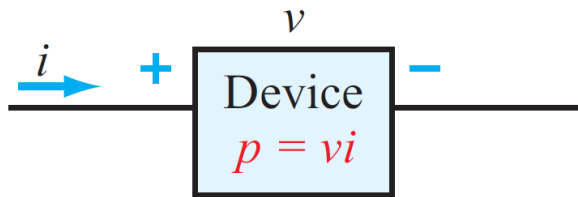


$p > 0$ power delivered to device
 $p < 0$ power supplied by device

*Note that i direction is defined as entering (+) side of v .

Device 1: $P_1 = V_1 I_1 = 18 \times 3 = 54 \text{ W},$

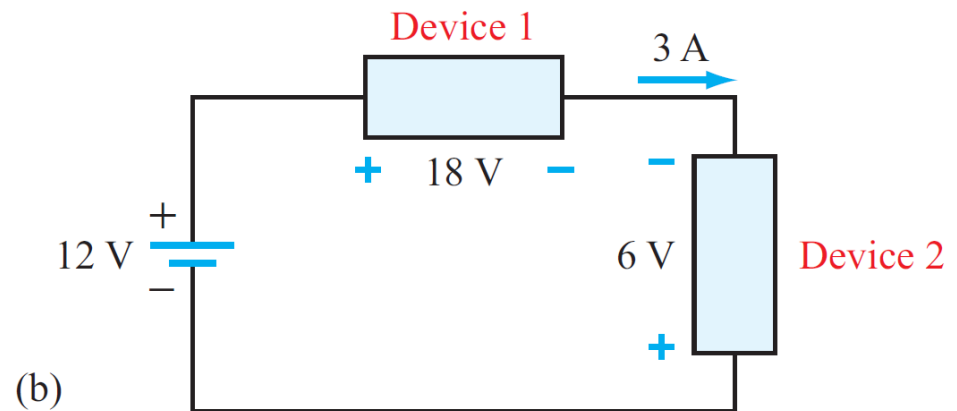Device 2: $P_2 = V_2 I_2 = (-6) \times 3 = -18 \text{ W}$



Battery:

$$P_{\text{bat}} = 12(-3) = -36 \text{ W},$$

Example 1-7: Energy Consumption

- **Given:** Resistor consuming 20 W before switch turned off at $t = 0$.
Also $v(t) = 100e^{-2t}$ V for $t \geq 0$
- **Determine:** Total energy consumed by resistor after $t = 0$.
- **Solution:** $I = P/V = 20/100 = 0.2$ A (before $t = 0$)
 $i(t) = 0.2e^{-2t}$ A for $t \geq 0$.

The instantaneous power is


$$p(t) = v(t) \cdot i(t) = (100e^{-2t})(0.2e^{-2t}) = 20e^{-4t} \text{ W.}$$

$$W = \int_0^{\infty} p(t) dt = \int_0^{\infty} 20e^{-4t} dt = -\frac{20}{4} e^{-4t} \Big|_0^{\infty} = 5 \text{ J.}$$


Circuit Elements: Independent Sources

Independent Sources



Ideal Voltage Source

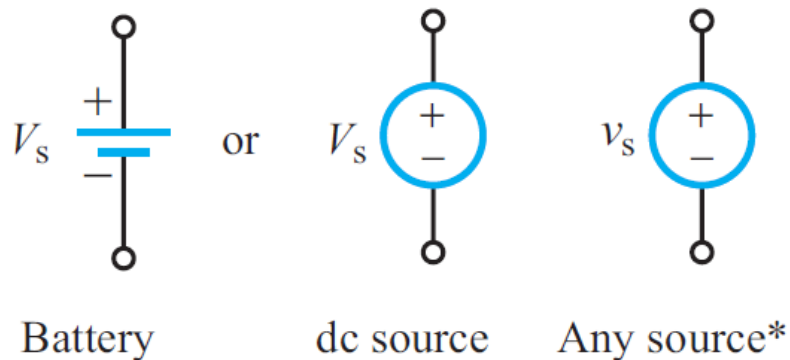

Ideal Current Source

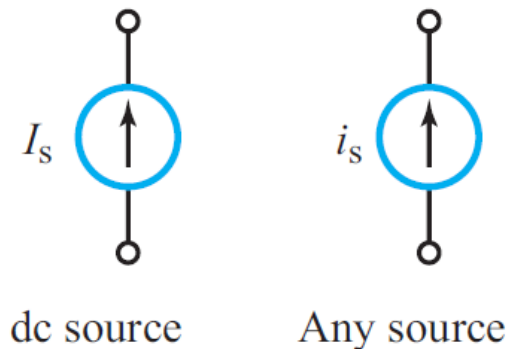


Realistic Voltage Source

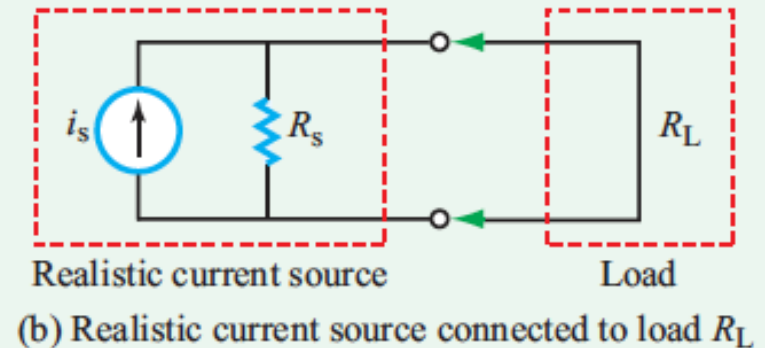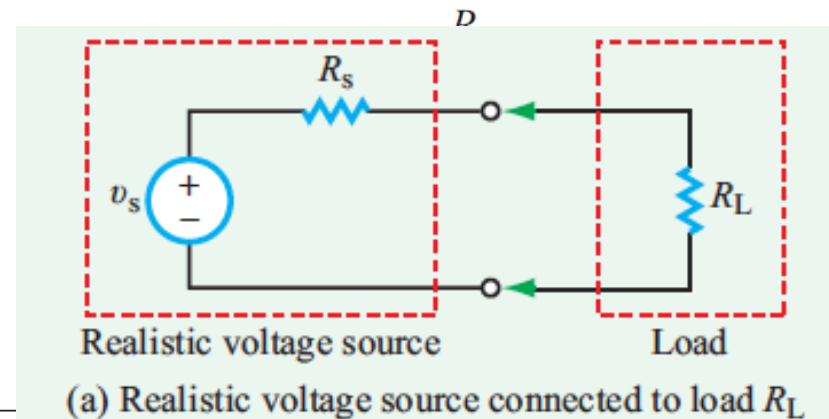


Circuit Elements: Dependent Sources

Dependent Sources


Voltage-Controlled Voltage Source (VCVS)

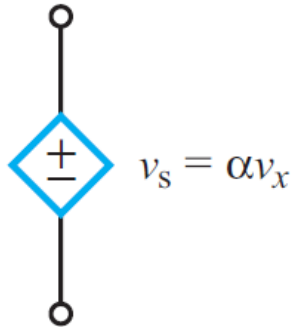


Voltage-Controlled Current Source (VCCS)

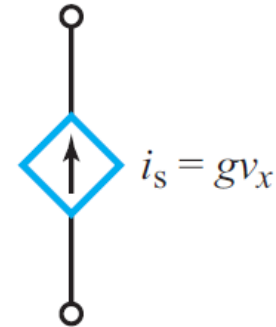

Current-Controlled Voltage Source (CCVS)

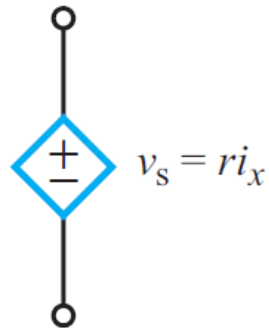



Current-Controlled Current Source (CCCS)

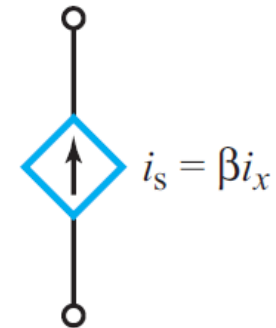


Note: α , g , r , and β are constants; v_x and i_x are a specific voltage and a specific current elsewhere in the circuit. *Lowercase v and i represent voltage and current sources that may or may not be time varying, whereas uppercase V and I denote dc sources.

I-V for Sources

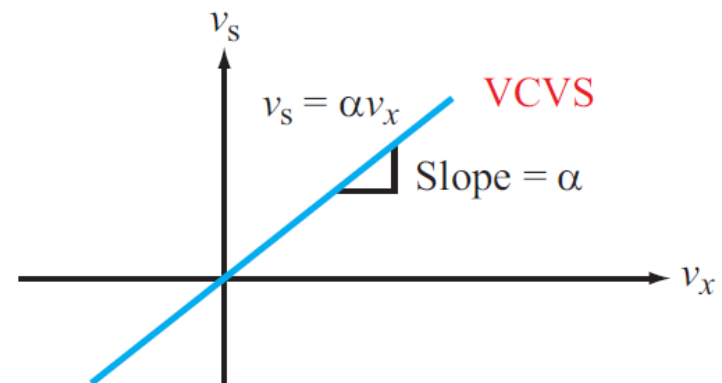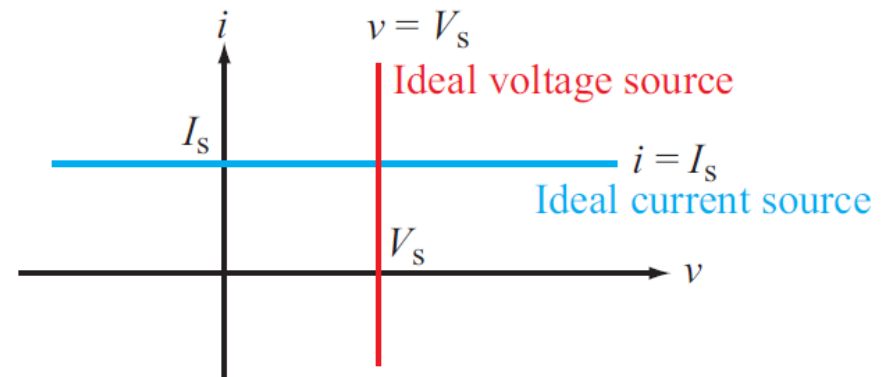
- Current/voltage fixed for independent sources
 - ▣ What does a non-ideal source look like?
- Dependent sources vary with reference voltage/current
 - ▣ What are units for slope?



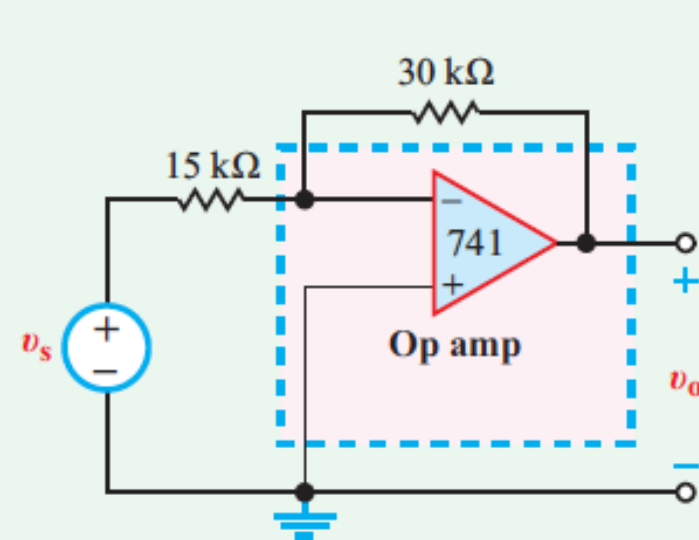Equivalent Circuit Using Dependent Source




(a) Op-amp circuit

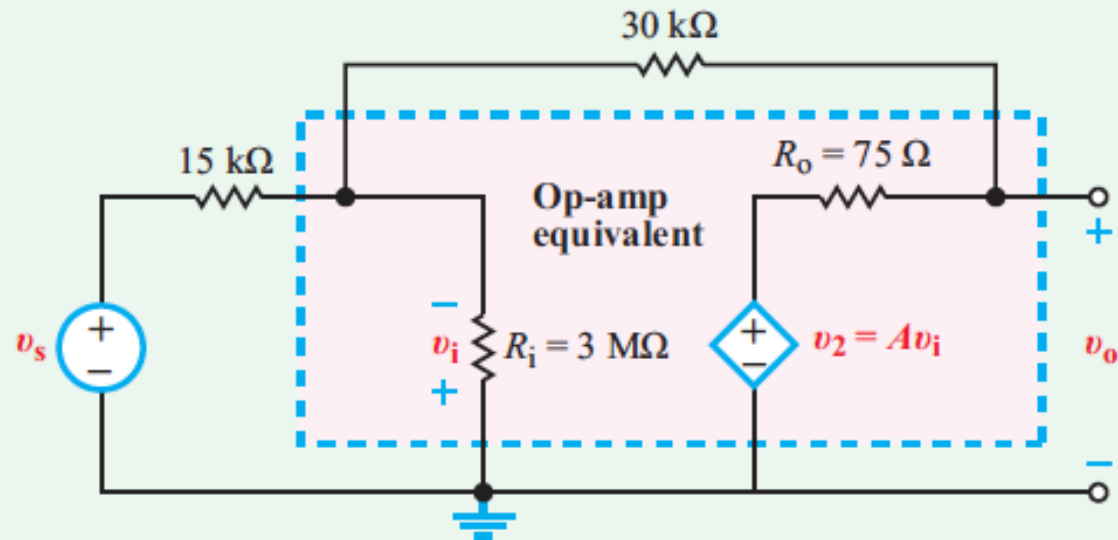

(b) Equivalent circuit with dependent voltage source

Example 1-8: Dependent Source

□ Given:

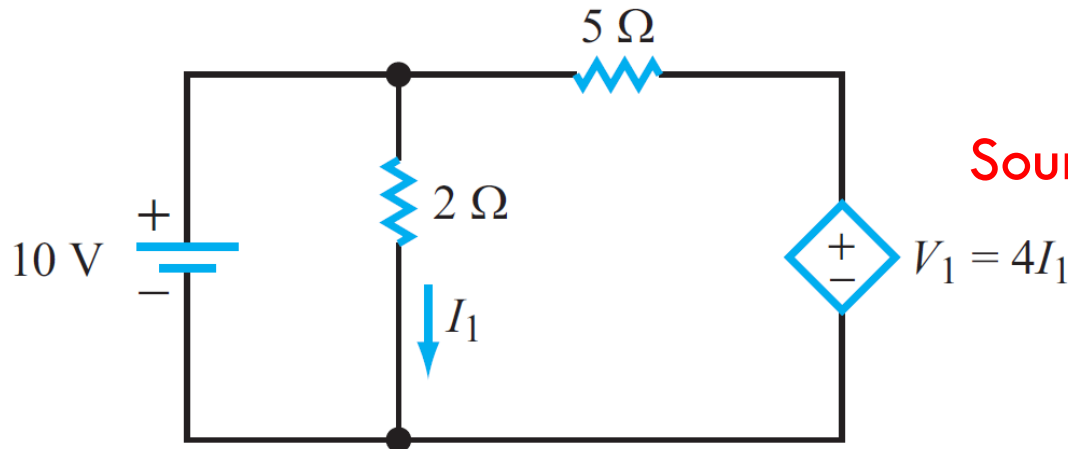

Source is CCVS

Determine: V_1

Solution:
$$I_1 = \frac{10}{2} = 5 \text{ A.}$$

Consequently,

$$V_1 = 4I_1 = 4 \times 5 = 20 \text{ V.}$$

Summary

Mathematical and Physical Models

Ohm's law $i = v/R$

Current $i = dq/dt$


Direction of i = direction of flow of (+) charge

Charge transfer $q(t) = \int_{-\infty}^t i \, dt$

$$\Delta Q = q(t_2) - q(t_1) = \int_{t_1}^{t_2} i \, dt$$

Voltage = potential energy difference per unit charge

Passive sign convention

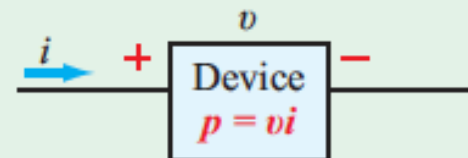

$p > 0$ power delivered to device

$p < 0$ power supplied by device

Note that i direction is defined as entering (+) side of v .

Energy $w = \int_0^{\infty} p(t) \, dt$