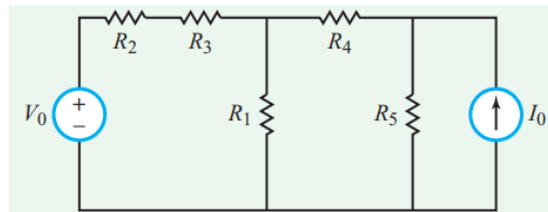


ECEN203 Tutorial 3: Analysis Techniques (with answers)


Answer all 16 questions. Answers provided for your self-checking.

Q1. For the circuit shown below, (a) identify all extraordinary nodes and select one of them as the ground node, (b) develop node-voltage equations at the remaining extraordinary nodes, (c) solve for the node voltages, and then (d) calculate the power consumed by R_5 . The element values are $V_0 = 10\text{ V}$, $I_0 = 0.8\text{ A}$, $R_1 = 5\ \Omega$, $R_2 = 2\ \Omega$, $R_3 = 3\ \Omega$, $R_4 = 10\ \Omega$ and $R_5 = 2.5\ \Omega$.




(Answer: (a) 3 extraordinary nodes, (b) -, (c) $V_1 = 4.5\text{ V}$ and $V_2 = 2.5\text{ V}$, (d) $P @ R_5 = 2.5\text{ W}$)

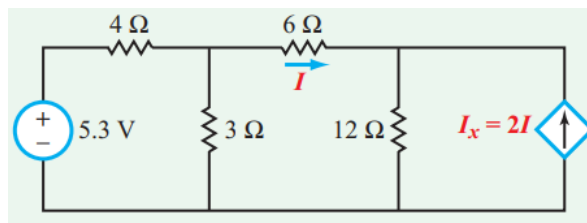Q2. The circuit below contains a current-controlled current source (CCCS) whose magnitude I_x , is governed by the current flowing through the $6\ \Omega$ resistor in the direction shown. Determine I_x .




(Answer: $I_x = 0.1\text{ A}$.)

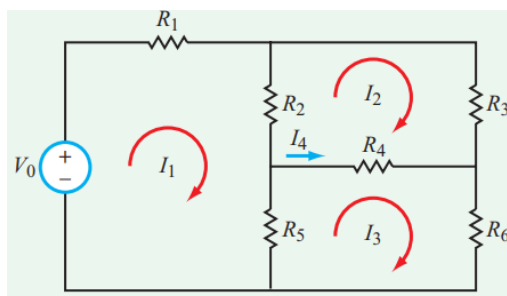Q3. Use mesh analysis to (a) obtain mesh-current equations for the circuit below and then (b) determine the current in R_4 , given that $V_0 = 18\text{ V}$, $R_1 = 6\ \Omega$, $R_2 = R_3 = 2\ \Omega$, and $R_4 = R_5 = R_6 = 4\ \Omega$.




(Answer: $I @ R_4 = 0\text{ A}$; $I_1 = 2\text{ A}$, $I_2 = 1\text{ A}$, $I_3 = 1\text{ A}$.)

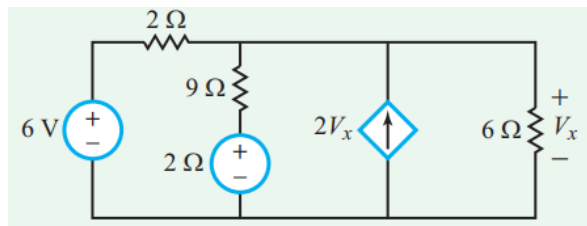Q4. Apply the superposition principle to the circuit shown below to determine V_x .




(Answer: $V_x = -2.63 \text{ V}$.)

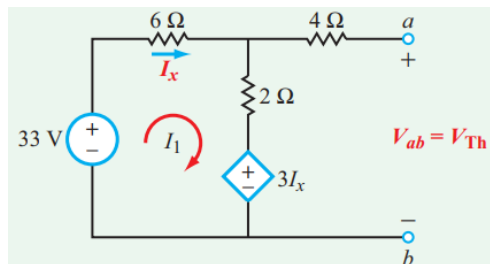Q5. Find the Thevenin equivalent circuit at terminals (a, b) for the circuit below by applying the combination of open-circuit-voltage and external-source methods.




(Answer: $V_{Th} = 15 \text{ V}$, $R_{Th} = 56/11 \Omega$.)

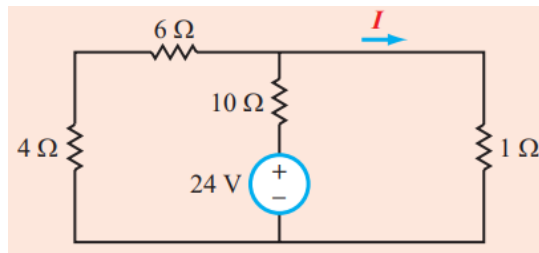Q6. Apply nodal analysis to determine the current I in the circuit below.




(Answer: $I = 2 \text{ A}$.)

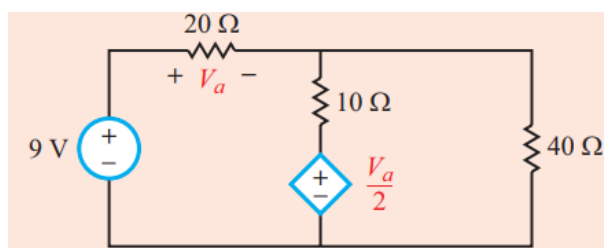Q7. Apply nodal analysis to find V_a in the circuit below.




(Answer: $V_a = 5 \text{ V}$.)

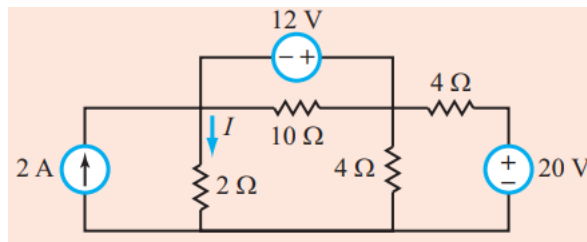Q8. Apply the supernode concept to determine I in the circuit below.




(Answer: $I = 0.5 \text{ A}$.)

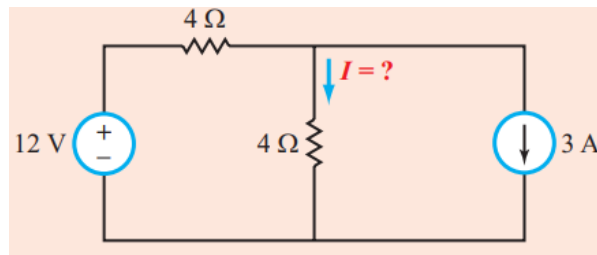Q9. Apply mesh analysis to determine I in the circuit below.




(Answer: $I = 0$.)

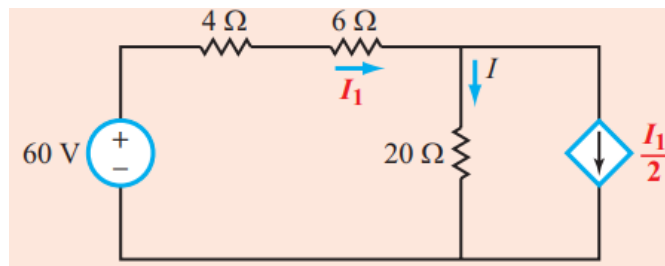Q10. Determine the current I in the circuit below.




(Answer: $I = 1.5 \text{ A}$.)

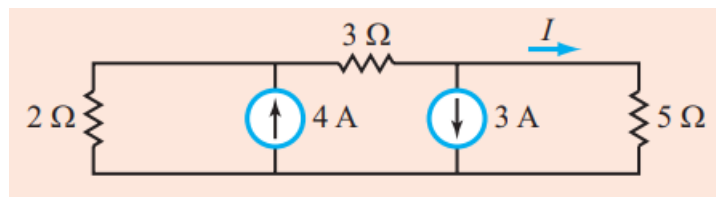Q11. Apply mesh analysis to determine I in the circuit below.




(Answer: $I = -0.7 \text{ A}$.)

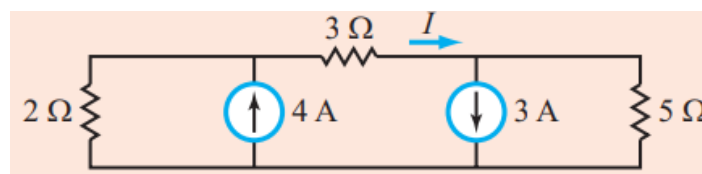Q12. Apply the source-superposition method to determine the current I in the circuit below.




(Answer: $I = 2.3 \text{ A}$.)

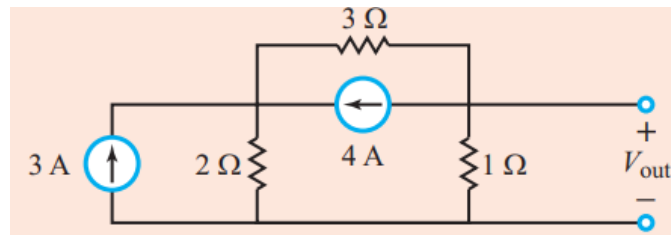Q13. Apply source superposition to determine V_{out} in the circuit below.




(Answer: $V_{out} = -1$ V.)

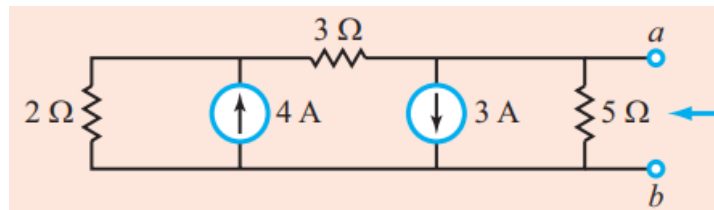Q14. Determine the Thevenin-equivalent circuit at terminals (a, b) in the circuit below.




(Answer: $V_{Th} = -3.5$ V, $I_{sc} = -1.4$ A, $R_{Th} = 2.5$ Ω.)

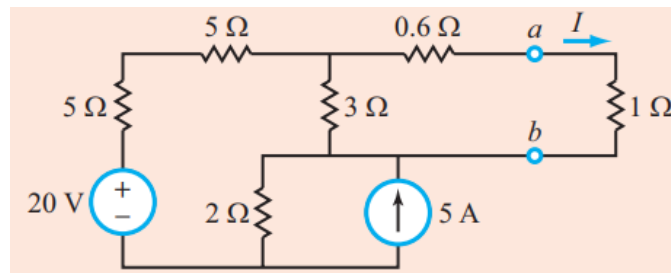Q15. Find the Thevenin equivalent of the circuit to the left of terminals (a, b) in the circuit below, and then determine the current I .





(Answer:

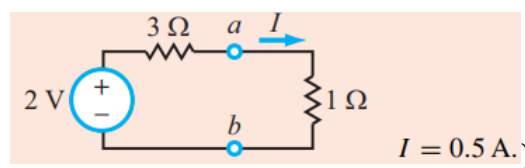

$I = 0.5$ A.)

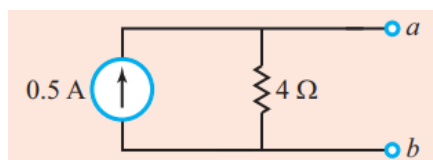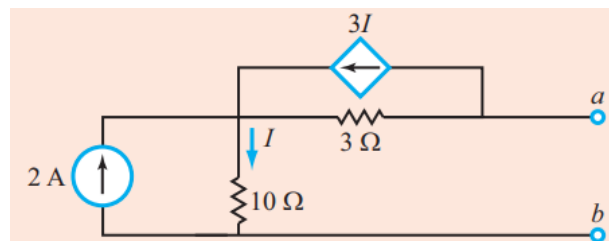Q16. Find the Norton equivalent at terminals (a, b) of the circuit below.



(Answer:)