
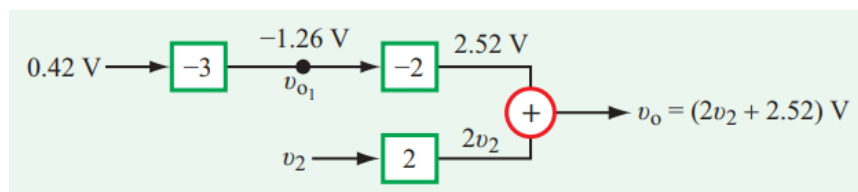



ECEN203 Tutorial 4: Operational Amplifiers (with answers)

Answer all 9 questions. Answers are provided for your self-checking.

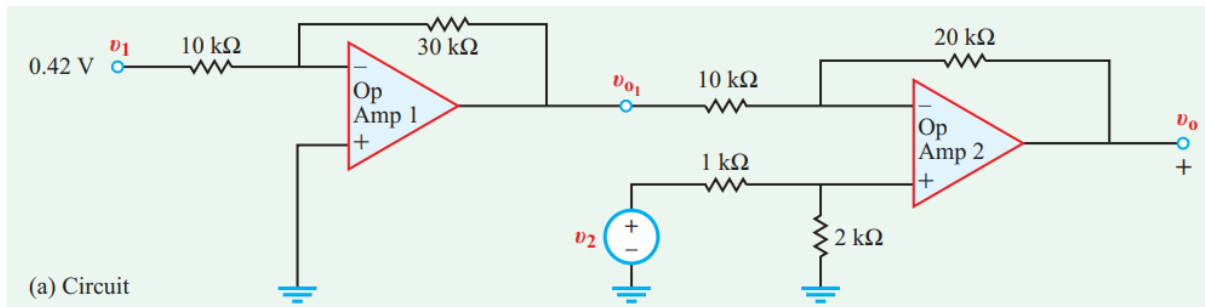Q1. Generate a block-diagram representation for the circuit shown below. See Pg 211 Example 4-4.



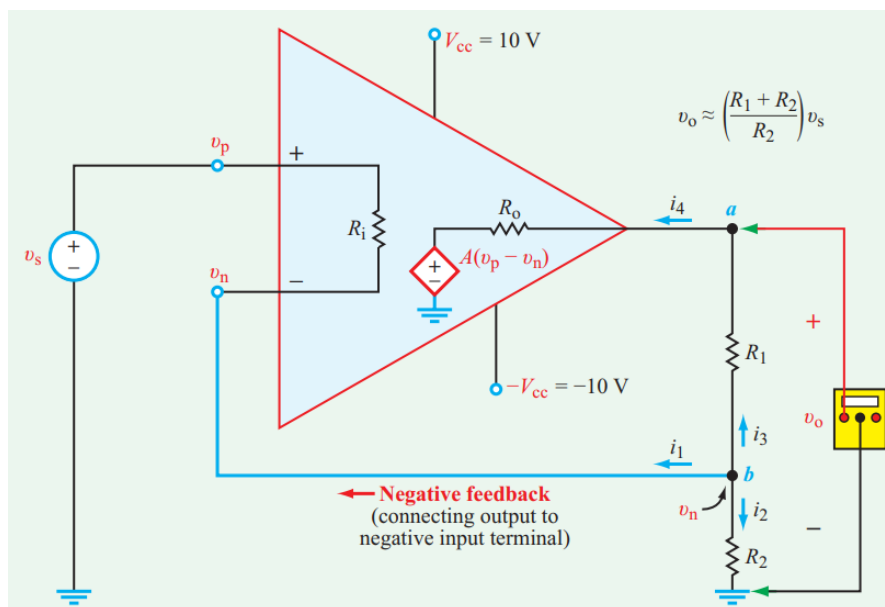Q2. In the circuit shown below, insert a series resistance R_s between v_s and v_p and then repeat the solution to obtain an expression for G . Evaluate G for $R_s = 10$. What impact does the insertion of R_s have on the magnitude of G ? For $V_{cc} = 10$ V, $A = 10^6$, $R_i = 10^7$ Ω , $R_o = 10$ Ω , $R_1 = 80$ k Ω , and $R_2 = 20$ k Ω ,



$$G = \frac{[A(R_i + R_s)(R_1 + R_2) + R_2 R_o]}{[AR_2(R_i + R_s) + R_o(R_2 + R_1 + R_s) + R_1 R_2 + (R_i + R_s)(R_1 + R_2)]}$$

(Answer: $= 4.999977$ (negligible impact).)

Q3. To evaluate the trade-off between the circuit gain G and the linear dynamic range of v_s ,


apply this equation $G = \frac{v_o}{v_s} = \frac{[AR_i(R_1 + R_2) + R_2R_o]}{AR_2R_i + R_o(R_2 + R_i) + R_1R_2 + R_i(R_1 + R_2)}$ to find the magnitude of G and then determine the corresponding dynamic range of v_s for each of the following values of R_2 : 0 (no feedback), 800 Ω , 8.8 k Ω , 40 k Ω , 80 k Ω , and 1 M Ω . Except for R_2 , all other quantities remain unchanged.

For $V_{cc} = 10$ V, $A = 10^6$, $R_i = 10^7$ Ω , $R_o = 10$ Ω ,
 $R_1 = 80$ k Ω , and $R_2 = 20$ k Ω ,

R_2	G	v_s Range
0	10^6	-10 μ V to $+10$ μ V
800 Ω	101	-99 mV to $+99$ mV
8.8 k Ω	10.1	-0.99 V to $+0.99$ V
40 k Ω	3	-3.3 V to $+3.3$ V
80 k Ω	2	-5 V to $+5$ V
1 M Ω	1.08	-9.26 V to $+9.26$ V

(Answer:)

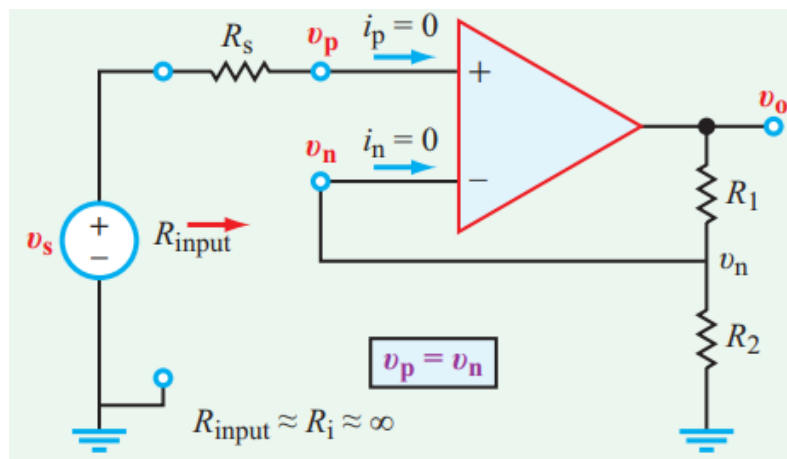Q4. Consider the noninverting amplifier circuit as shown below under the conditions of the ideal op-amp model. Assume $V_{cc} = 10$ V. Determine the value of G and the corresponding dynamic range of v_s for each of the following values of R_1/R_2 : 0, 1, 9, 99, 10^3 , 10^6 .




R_1/R_2	G	v_s Range
0	1	-10 V to $+10$ V
1	2	-5 V to $+5$ V
9	10	-1 V to $+1$ V
99	100	-0.1 V to $+0.1$ V
1000	~ 1000	-10 mV to $+10$ mV (approx.)
10^6	$\sim 10^6$	-10 μ V to $+10$ μ V (approx.)

Answer:)

Q5. The input to an inverting-amplifier circuit consists of $v_s = 0.2$ V and $R_s = 10$ Ω . If $V_{cc} = 12$ V, what is the maximum value that R_f can assume before saturating the op amp?


(Answer: $G_{max} = -60$, $R_f = 600$.)

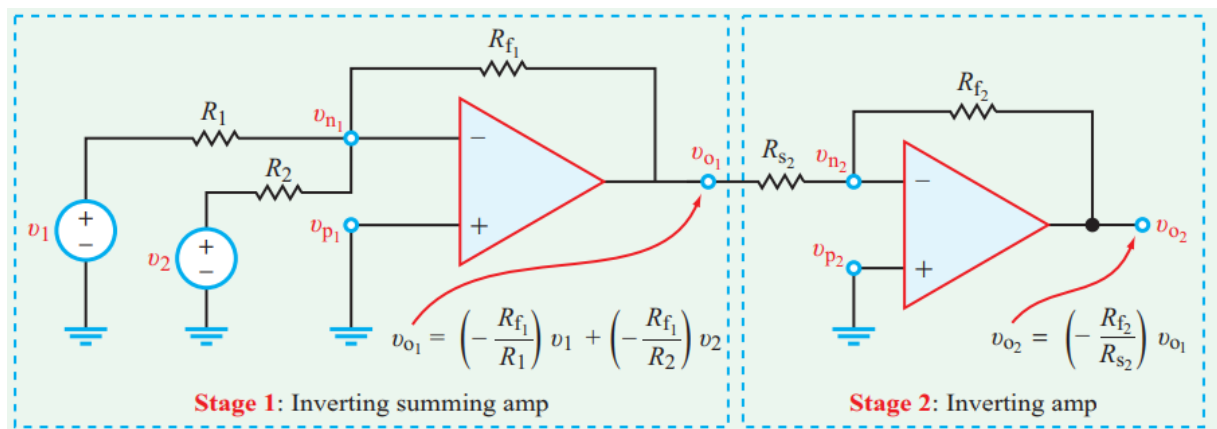Q6. The circuit shown in Fig. 4-14(a) is to be used to perform the operation $v_o = 3v_1 + 6v_2$. If $R_1 = 1.2 \text{ k}$, $R_{s2} = 2 \text{ k}$, and $R_{f2} = 4 \text{ k}$, select values for R_2 and R_{f1} so as to realize the desired result.




(Answer: $R_{f1} = 1.8 \text{ k}$, $R_2 = 600$.)

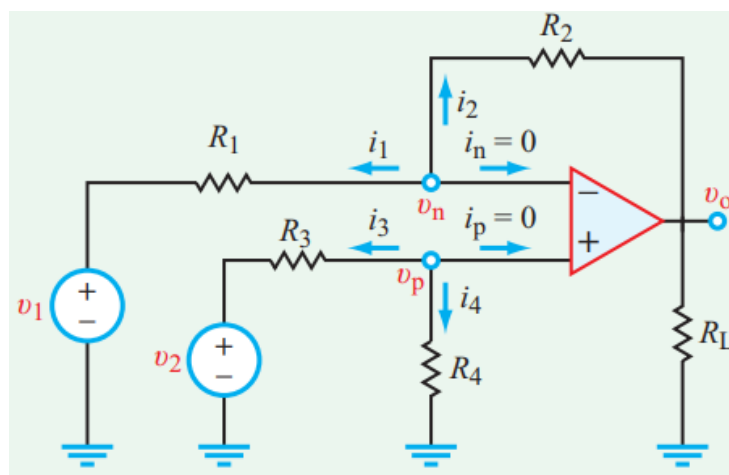Q7. The difference-amplifier circuit below is used to realize the operation $v_o = (6v_2 - 2)v_1$. Given that $R_3 = 5 \text{ k}$, $R_4 = 6 \text{ k}$, and $R_2 = 20 \text{ k}$, specify values for v_1 and R_1 .




(Answer: $v_1 = 0.2 \text{ V}$, $R_1 = 2 \text{ k}$.)

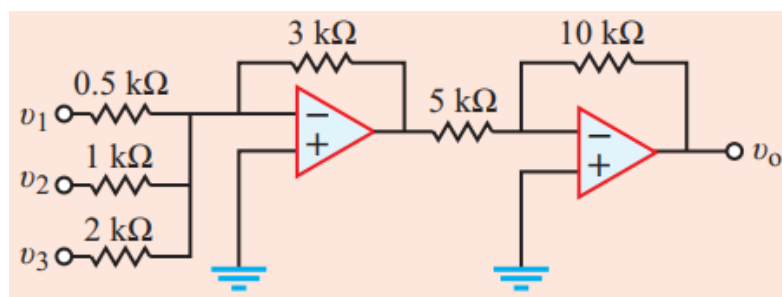Q8. Express v_o in terms of v_1 , v_2 , and v_3 for the circuit below.



(Answer: $v_o = 12v_1 + 6v_2 + 3v_3$.)

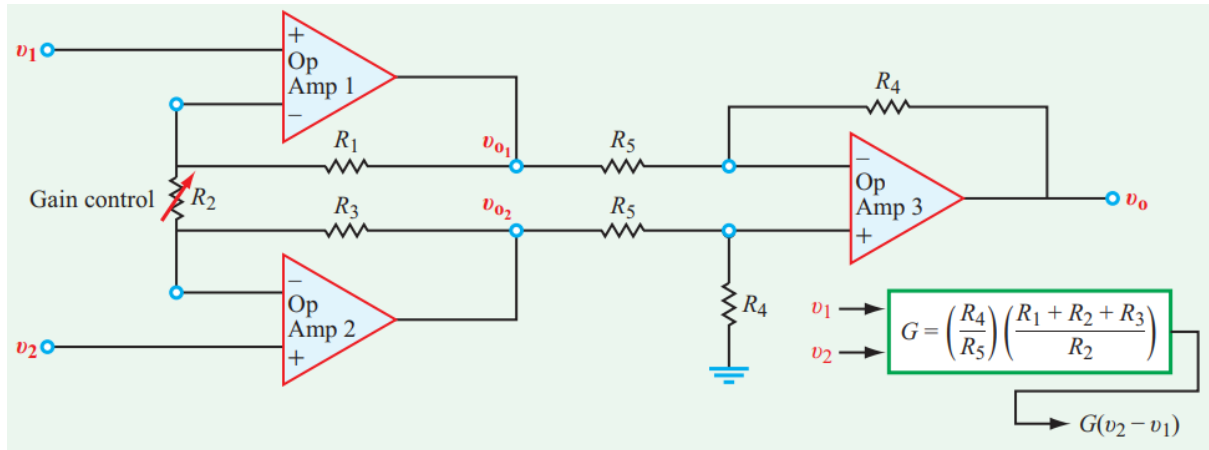Q9. To monitor brain activity, an instrumentation-amplifier sensor uses a pair of needle-like probes inserted at different locations in the brain to measure the voltage difference between them. If the circuit is of the type shown below with $R_1 = R_3 = R_4 = R_5 = R = 50\text{ k}$, $V_{cc} = 12\text{ V}$, and the maximum magnitude of the voltage difference that the brain is likely to exhibit is 3 mV , what should R_2 be to maximize the sensitivity of the brain sensor?



(Answer: $R_2 = 25$.)