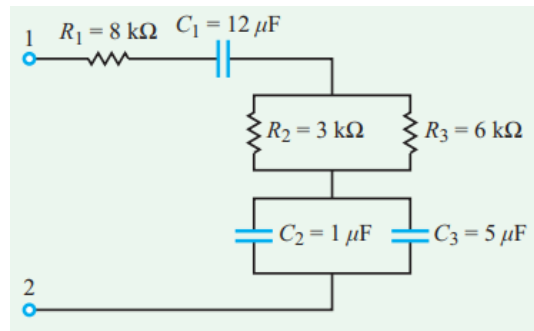



ECEN203 Tutorial 5: RC and RL First Order Circuits (with answers)

Answer all 19 questions. Answers are provided for your self-checking.

Q1. Reduce the circuit below into an equivalent configuration.



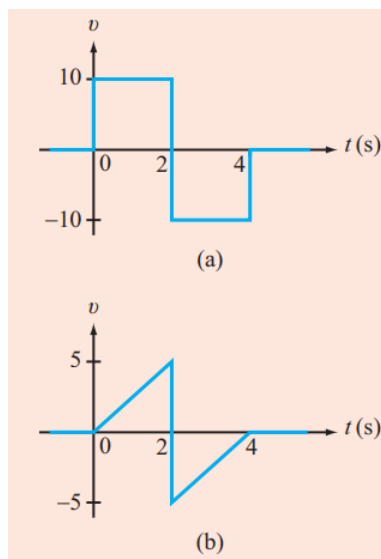Q2. Express the waveforms shown in (a) and (b) below in terms of unit step functions.




(Answer: (a) $v(t) = 10 u(t) - 20 u(t - 2) + 10 u(t - 4)$, (b) $v(t) = 2.5 r(t) - 10 u(t - 2) - 2.5 r(t - 4)$.)

Q3. How is $u(t)$ related to $u(-t)$?

(Answer: They are mirror images of one another (with respect to the y-axis).)

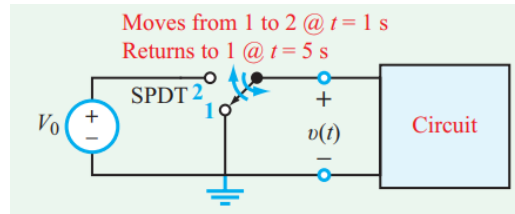Q4. Consider the SPDT switch below. Assume that it started out at position 2, was moved to position 1 at $t = 1$ s, and then moved back to position 2 at $t = 5$ s. This is the reverse of the sequence shown in the figure. Express $v(t)$ in terms of (a) units step functions and (b) the rectangle function.



(Answer: (a) $v(t) = V_0[u(1-t) + u(t-5)]$, (b) $v(t) = V_0[1 - \text{rect}(\frac{t-3}{4})]$.)

Q5. The radioactive decay equation for a certain material is given by $n(t) = n_0 e^{-t/\tau}$, where n_0 is the initial count at $t = 0$. If $\tau = 2 \times 10^8$ s, how long is its half-life? [Half-life $t_{1/2}$ is the time it takes a material to decay to 50 percent of its initial value.]

(Answer: $t_{1/2} = 1.386 \times 10^8$ s = 4 years, 144 days, 12 hours, 10 minutes, 36 s.)

Q6. If the current $i(t)$ through a resistor R decays exponentially with a time constant τ , what is the value of the power dissipated in the resistor at $t = \tau$, compared with its value at $t = 0$?

(Answer: $p(t) = i^2 R = I_0^2 R (e^{-t/\tau})^2 = I_0^2 R e^{-2t/\tau}$, $p(\tau)/p(0) = e^{-2} = 0.135$ or 13.5 percent.)

Q7. It is desired to build a parallel-plate capacitor capable of storing 1 mJ of energy when the voltage across it is 1 V. If the capacitor plates are 2 cm $\times$ 2 cm each and its insulating material is Teflon, what should the separation d be? Is such a capacitor practical?

Table 5-2: Relative electrical permittivity of common insulators: $\epsilon_r = \epsilon/\epsilon_0$ and $\epsilon_0 = 8.854 \times 10^{-12}$ F/m.


Material	Relative Permittivity ϵ_r
Air (at sea level)	1.0006
Teflon	2.1
Polystyrene	2.6
Paper	2-4
Glass	4.5-10
Quartz	3.8-5
Bakelite	5
Mica	5.4-6
Porcelain	5.7

(Answer: $d = 3.72 \times 10^{-12}$ m. No, it is not practical to build a capacitor with such a small d , because it is about two orders of magnitude smaller than the typical spacing between two adjacent atoms in a solid material.)

Q8. Instead of specifying A and calculating the spacing d needed to meet the 1 mJ requirement in Q7, suppose we specify d as 1 μm and then calculate A . How large would A have to be?


(Answer: $A = 10.4 \text{ m} \times 10.4 \text{ m}$, equally impractical!)

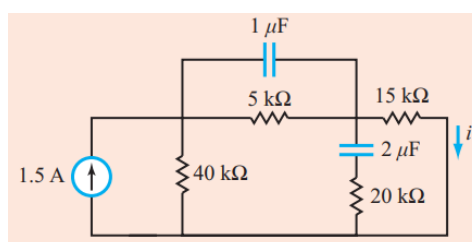Q9. Determine the current i in the circuit below, under dc conditions.



(Answer: $i = 1$ A)

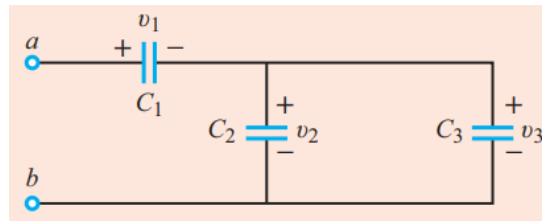Q10. Determine C_{eq} and $v_{eq}(0)$ at terminals (a, b) for the circuit below given that $C_1 = 6 \mu\text{F}$, $C_2 = 4 \mu\text{F}$, $C_3 = 8 \mu\text{F}$, and the initial voltages on the three capacitors are $v_1(0) = 5 \text{ V}$ and $v_2(0) = v_3(0) = 10 \text{ V}$, respectively.



(Answer: $C_{eq} = 4 \mu\text{F}$, $v_{eq}(0) = 15 \text{ V}$.)


Q11. Suppose the circuit in Q10 is connected to a dc voltage source $V_0 = 12 \text{ V}$. Assuming that the capacitors had no charge before they were connected to the voltage source, determine v_1 and v_2 given that $C_1 = 6 \mu\text{F}$, $C_2 = 4 \mu\text{F}$, and $C_3 = 8 \mu\text{F}$.

(Answer: $v_1 = 8 \text{ V}$, $v_2 = 4 \text{ V}$.)

Q12. Calculate the inductance of a 20-turn aircore solenoid if its length is 4 cm and the radius of its circular cross section is 0.5 cm.


(Answer: $L = 9.87 \times 10^{-7} \text{ H} = 0.987 \mu\text{H}$.)

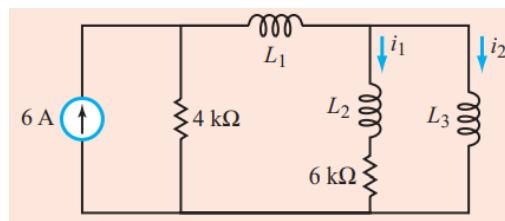Q13. Determine currents i_1 and i_2 in the circuit below, under dc conditions.




(Answer: $i_1 = 0$, $i_2 = 6 \text{ A}$.)

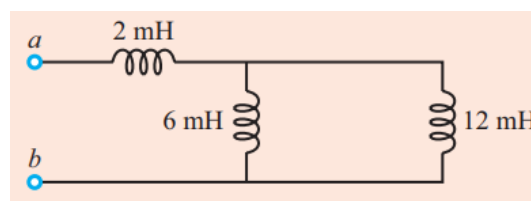Q14. Determine L_{eq} at terminals (a, b) in the circuit below.




(Answer: $L_{eq} = 6 \text{ mH}$.)

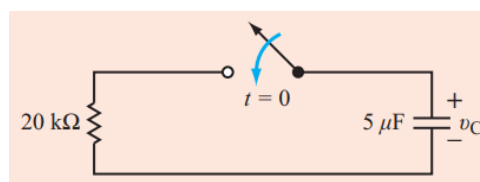Q15. If in the circuit below $v_C(0^-) = 24 \text{ V}$, determine $v_C(t)$ for $t \geq 0$.




(Answer: $v_C(t) = 24e^{-10t} \text{ V}$ for $t \geq 0$.)

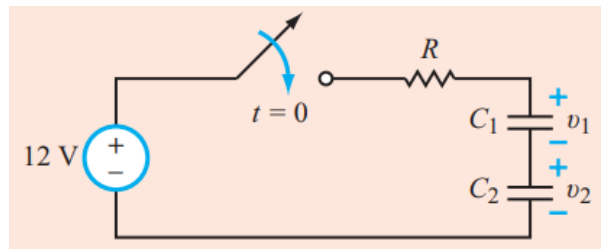Q16. Determine $v_1(t)$ and $v_2(t)$ for $t \geq 0$, given that in the circuit below $C_1 = 6 \mu\text{F}$, $C_2 = 3 \mu\text{F}$, $R = 100 \text{ k}$, and neither capacitor had any charge prior to $t = 0$.



(Answer: $v_1(t) = 4(1 - e^{-5t}) \text{ V}$, for $t \geq 0$, $v_2(t) = 8(1 - e^{-5t}) \text{ V}$, for $t \geq 0$.)

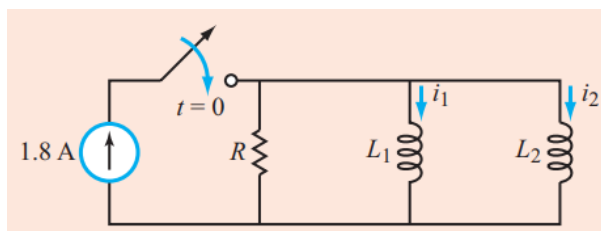Q17. Determine $i_1(t)$ and $i_2(t)$ for $t \geq 0$ given that, in the circuit below, $L_1 = 6 \text{ mH}$, $L_2 = 12 \text{ mH}$, and $R = 2 \Omega$. Assume $i_1(0^-) = i_2(0^-) = 0$.



(Answer: $i_1(t) = 1.2(1 - e^{-500t}) \text{ u}(t) \text{ A}$, $i_2(t) = 0.6(1 - e^{-500t}) \text{ u}(t) \text{ A}$.)

Q18. The input signal to an ideal integrator circuit with $RC = 2 \times 10^{-3} \text{ s}$ and $V_{cc} = 15 \text{ V}$ is given by $v_s(t) = 2 \sin 100t \text{ V}$. What is $v_{out}(t)$?

(Answer: $v_{out}(t) = 10[\cos(100t) - 1] \text{ V}$.)

Q19. Repeat Q18 for a differentiator instead of an integrator.

(Answer: $v_{out}(t) = -0.4 \cos 100t \text{ V}$.)