



# Lab 2 – Diode Characteristics

**XMUT204 Electronic Design**


# Topics

## **Objectives:**

- Measuring the characteristics of a conventional diode
- Determining the operating point of the diode
- Working with basic diode circuits

# Introduction

- Semiconductor diodes consist of p-type and n-type material in contact.
- The diode conducts when forward biased (i.e. the p-type material is made more positive than the n-type) if the bias exceeds a characteristic value ( $V_B$ : typically  $\sim 0.6$  V to 0.8 V for silicon diodes at room temperature).

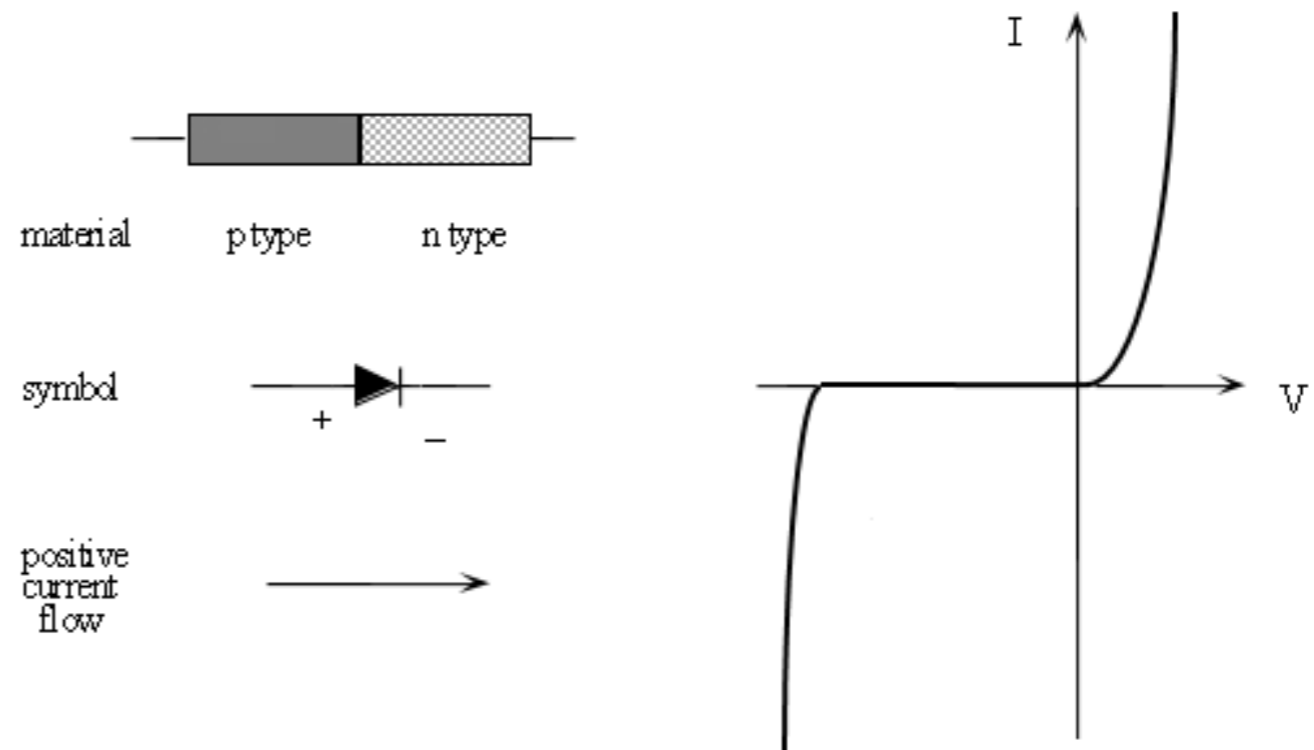

The I-V characteristic of a conventional diode

# Introduction

- When the diode is reverse biased (i.e. the n-type material is made more positive than the p-type) effectively no current flows.
- If the reverse voltage exceeds an upper limit, the diode will "breakdown" and become highly conducting which may lead to permanent damage.
- Some special purpose diodes called Zener diodes are designed to operate in this breakdown region).
- The I - V characteristic of a conventional diode is shown in Fig. 1; clearly, diodes are non-linear circuit elements.

# Introduction

- The forward I - V relationship is most closely represented by the *Ebers-Moll* equation:


$$I = I_S \left( \exp \frac{V}{n V_T} - 1 \right) \quad (\text{Eq. 1})$$

Where:  $I_S$  is a constant for a given diode at fixed temperature  $T$ ,  $V_T = kT/q$  (where  $k$  is the Boltzmann constant and  $q$  the electronic charge), with a value  $\sim 25$  mV at room temperature, and  $n$  is in the range  $1 \rightarrow 2$ .

- In practice the second term in the brackets in equation (1) is negligible.
- Both  $I_S$  and  $V_T$  are temperature dependent.
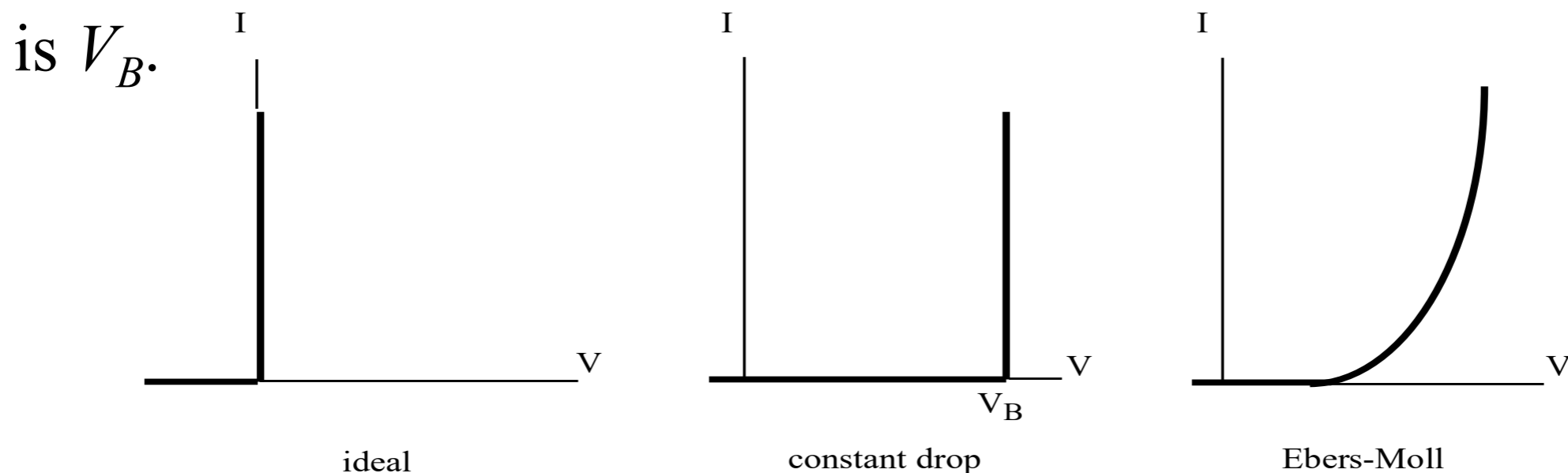
# Introduction

- There is a series of models which may be used to represent diodes in circuit analysis. The two most common, in order of increasing complexity, are shown in Fig. 2 and compared to the Ebers-Moll curve.
- The *ideal model* treats the diode as a perfect switch - open circuit (zero current) when reverse biased, short circuit (zero voltage drop) when forward biased.
- The *constant drop* model assumes that the forward bias voltage drop is  $V_B$ .



V-I graphs of diode

# Introduction

## Load lines

- Circuits containing non-linear elements can be analysed graphically using a *load line*.

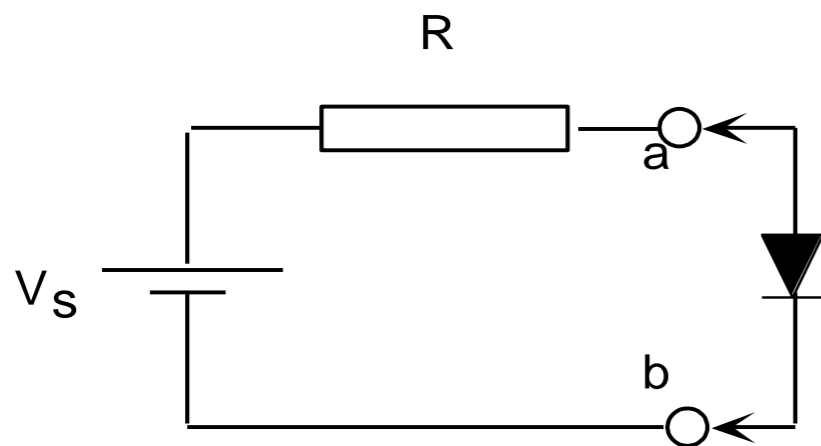


Fig. 3a

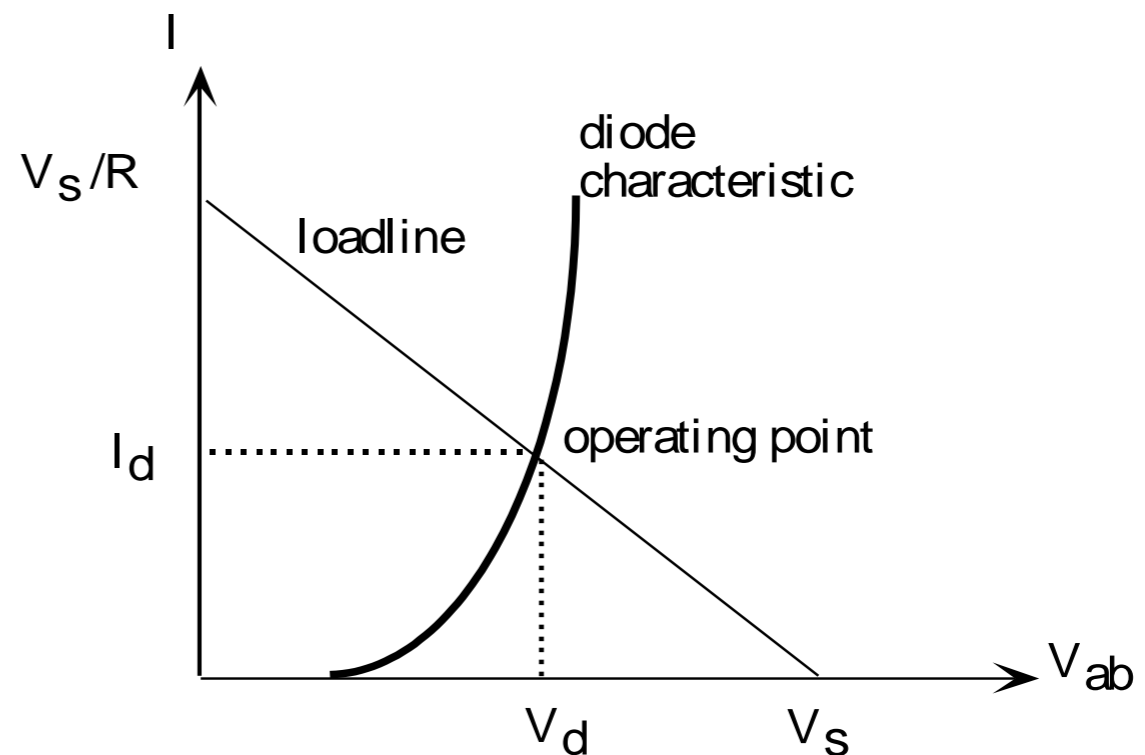


Fig. 3b

- For the circuit of Fig. 3a, each part of the circuit defines a relationship between  $I$  and  $V_{ab}$ .
- If we plot the characteristic curve for the diode, then  $I$  and  $V_{ab}$  must lie somewhere on it.

# Introduction

- On the other hand, the entire circuit must obey Kirchhoff's loop rule, which gives


$$V_S - IR - V_{ab} = 0 \quad (\text{Eq. 2})$$

- This equation (2) may also be shown on an  $I$ - $V$  plot, as a *load line* in Fig.3b.
- It cuts the axes at the open circuit voltage ( $I = 0$ ),  $V_{ab} = V_S$  and the short circuit current ( $V_{ab} = 0$ ),  $I = V_S/R$ .
- Because the actual current and value of  $V_{ab}$  must lie on both the load line and the diode characteristic, the intersection of the two lines determines the values of  $V_{ab}$  and  $I$  (the operating point) for the diode with an applied voltage  $V_S$  and a series resistor  $R$ .



# 1. Measuring the characteristics of a diode (1N4148)

- a. Set up the circuit shown in Fig. 4.

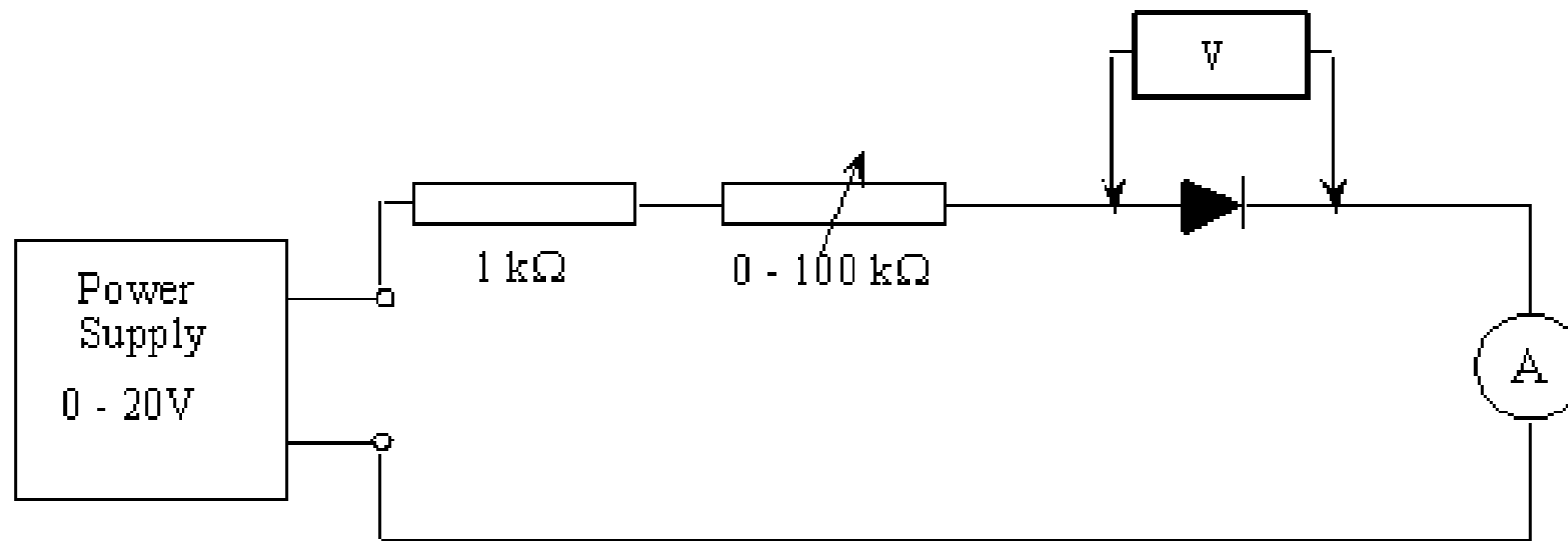

Circuit for measuring characteristics of a diode

- b. Using the two multimeters as DVMs record values of  $V_d$  (forward bias) for the following values of  $I_d$  (approximately):  $3 \mu\text{A}$ ,  $10 \mu\text{A}$ ,  $30 \mu\text{A}$ ,  $60 \mu\text{A}$ ,  $100 \mu\text{A}$ ,  $0.3 \text{ mA}$ ,  $1 \text{ mA}$ ,  $2 \text{ mA}$ ,  $3 \text{ mA}$ ,  $6 \text{ mA}$ .

# 1. Measuring the characteristics of a diode (1N4148)

- c. Rearrange the circuit for reverse bias. Record  $I_d$  for  $V_d$  values of -1, -5, -10 and -20 V. Remember  $I_d$  will be very small.
- d. In a piece of paper initially (because of different scales), plot the data for both forward and reverse bias (e.g.  $I$  on the vertical axis,  $V$  on the horizontal axis).

As the range of currents and voltages are so different for forward and reverse bias you will need to think carefully about the scales to use: suitable values will be 0 to 1.5 volt, 0 to 10 mA for the forward biased data, and 0 to -20 V, 0 to -2  $\mu$ A for the reverse biased data.

Also, produce a plot on the computer of the forward bias part of the characteristic.

## 2. Determining the operating point of the diode

- a. In the circuit of Fig. 4, replace the 20 V power supply with a 1.5 V battery and remove the 0 - 100 k $\Omega$  resistor.
- b. For this circuit use equation (3.2) with  $R = 1 \text{ k}\Omega$  and  $V_S = 1.5 \text{ V}$  to plot the load line on your graph of the forward bias diode characteristic.

From the intersection of the two lines, determine the theoretical operating point for the diode.


- c. Measure  $I_d$  and  $V_d$  for the circuit.

Compare the measured values with the graphically deduced operating point.

## 2. Determining the operating point of the diode

### Working with basic diode circuits

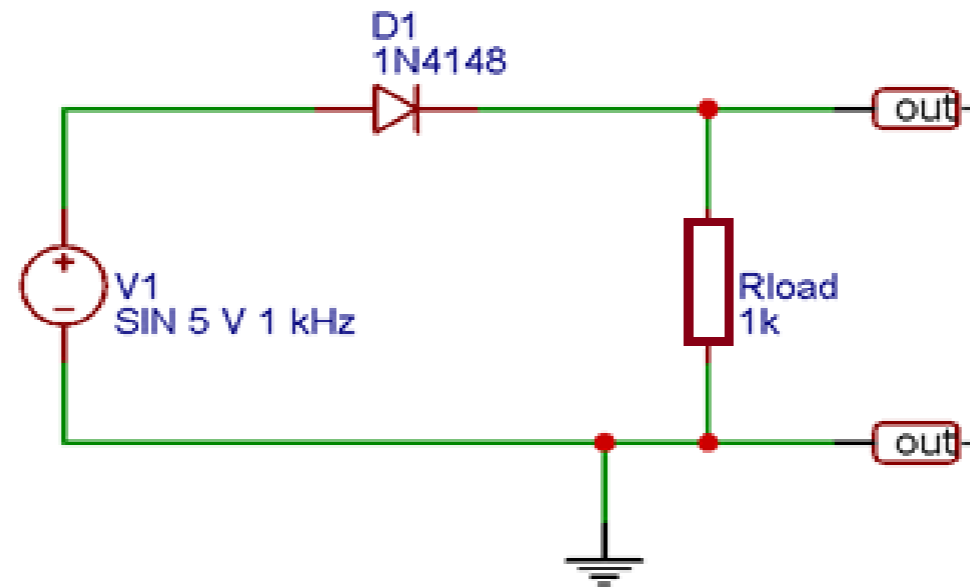a. Construct the following half-wave rectifier circuit.




Half-wave diode rectifier circuit

For the above circuit:

- i. Sketch the waveforms in the input and output.
- ii. Measure the voltage and current across the diode.
- iii. Measure the voltage across the load.

## 2. Determining the operating point of the diode

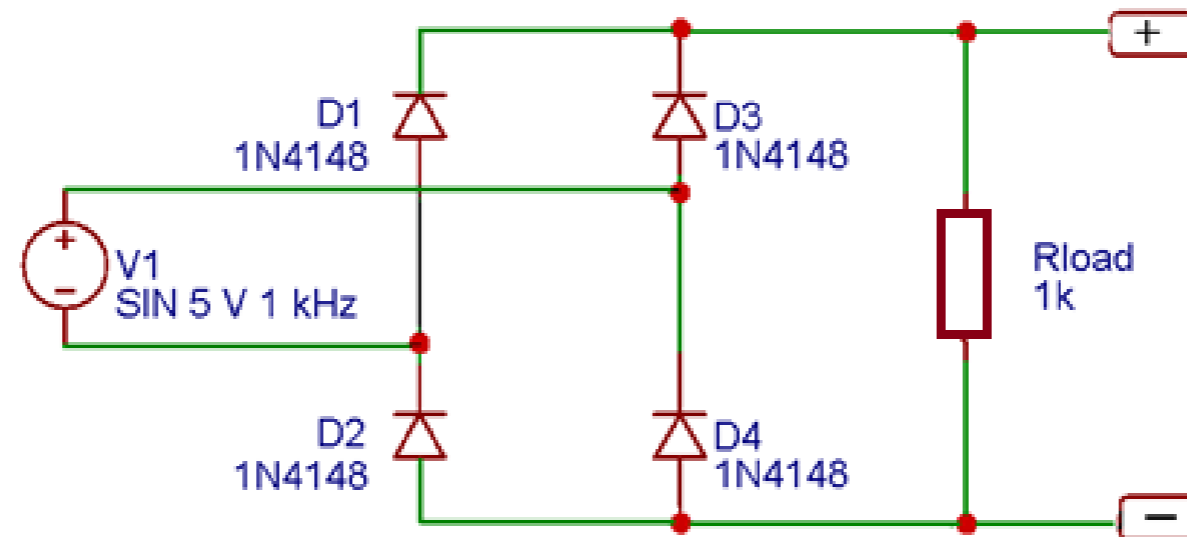b. Construct the following bridge rectifier circuit.



Full-wave diode rectifier circuit

For the above circuit:

- i. Sketch the waveforms in the input and output.
- ii. Measure the voltage and current across the diode.
- iii. Measure the voltage across the load.

# Report

## **Part C: Report**

- Complete a short report by answering the questions from the associated question sheet.

## **Equipment**

- Resistor:  $1\text{k}\Omega$
- Variable resistor:  $100\text{k}\Omega$
- Diode: 1N4148 (4 pieces)
- Battery: 1.5 V