



## Laboratory Instructions

Course Number:	XMUT204
Laboratory Number:	3
Laboratory Title:	Diode Applications
<ol style="list-style-type: none"><li>1. Working with the clipper and clamper circuits.</li><li>2. Measuring the characteristics of zener diode based circuits.</li></ol>	

Name: \_\_\_\_\_

Student Number: \_\_\_\_\_

## Objectives

- Working with diode clipper and clamper circuits.
- Measuring the characteristics of zener diode.
- Measuring voltage regulation.

## Part A: Clipper & Clamper Circuits

### A1. A Diode Clipper

Diodes may be used in a number of ways to change the shape or form of a signal. For example, the diode clipper of Fig. 1a may be used to limit the amplitude of an ac signal.

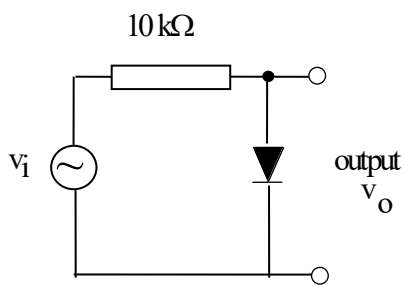


Fig. 1a: Clipper circuit

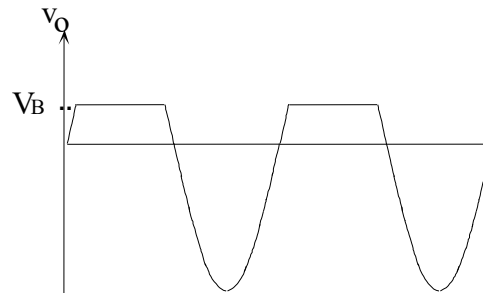


Fig. 1b: Clipper waveforms

- Set up the circuit of Fig. 1a. Use the signal generator at 1 kHz to provide an input sinusoidal signal at 8 V<sub>pp</sub>. Display both  $v_i$  and  $v_o$  on the oscilloscope (use dc coupling). The output  $v_o$  should be as shown in Fig 1b.
- Using the constant drop model for the diode (see Lab 2 handouts) explain this result.

---

---

---


---

---

---


---

- Insert the dc power supply (set to 2V) between the diode and ground as shown in the Fig. 2 given below.

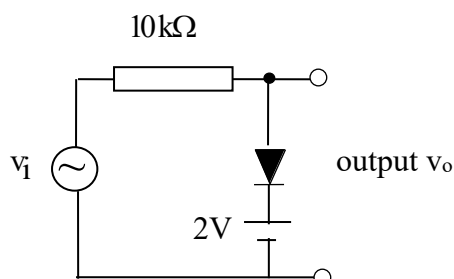

**Figure 2:** Clipper circuit (+ voltage source)

d. Sketch  $v_o$  and explain its form.

 


---

---

---

---

 e. Remove the dc power supply and reverse the diode. Sketch  $v_o$  and explain its form.



---


---

---

---

## A2. A Diode Clamper

Diodes may be used to control the peak values of an ac signal in a circuit, i.e. to hold (clamp) its dc level at a predetermined value.

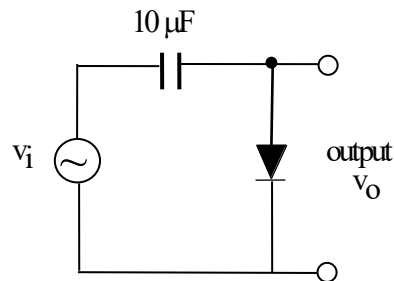

**Figure 3:** Clamper circuit

- Replace the  $10\ \text{k}\Omega$  resistor in Fig. 1a with a  $10\ \mu\text{F}$  capacitor (Fig. 3); again use dc coupling on the oscilloscope coupling.
- Sketch  $v_i$  and  $v_o$ . Measure (using the DVM) the voltage drop  $V_c$  across the capacitor and explain the operation of the circuit.

---

---

---

---

---

---

---

---

---

---


Note:

- As  $v_i$  initially goes positive, the diode conducts and the capacitor is charged up; when  $v_i$  starts to fall from its peak value, the diode becomes reversed biased and the capacitor cannot discharge.
- $v_o = v_d = v_i - V_c$


**Part B: Zener Diode**

**Introduction to Zener diodes**

If a sufficiently large reverse bias is applied to a semiconductor diode, a significant current will start to flow at the "breakdown" voltage. Zener diodes are manufactured to withstand this breakdown effect up to some specified power rating. They are used as voltage regulators.

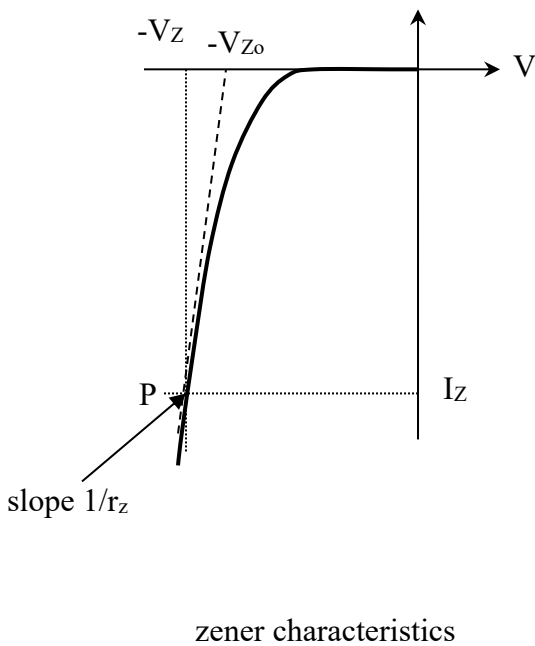

**Fig. 4a:** Zener diode V-I curve

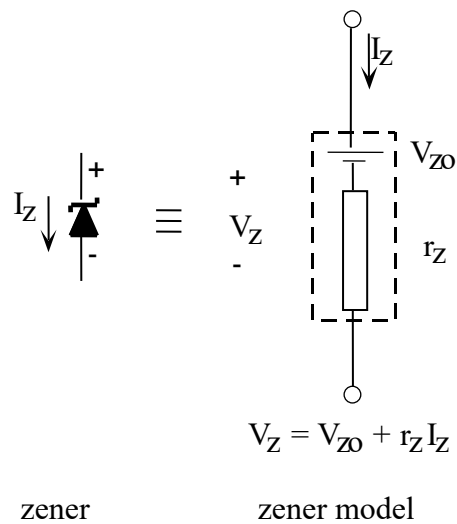


**Fig. 4b:** Zener diode model

The I-V characteristics in the breakdown region are shown in Fig. 4a.

A zener is specified by its voltage  $V_Z$  at some test current  $I_Z$  (point P), its power rating and its incremental resistance  $r_z$ , the inverse of the slope of the characteristic at  $I_Z$ . This line cuts the  $V$  axis at  $V_{Z0}$ . The I-V relationship may be modelled by the combination of a voltage source  $V_{Z0}$  and resistance  $r_z$  shown in Fig. 4b.

### B1. Measuring the Characteristics of a (Nominal) 3.3 V Zener (IN746A)

- a. Set up the circuit of Fig. 5.

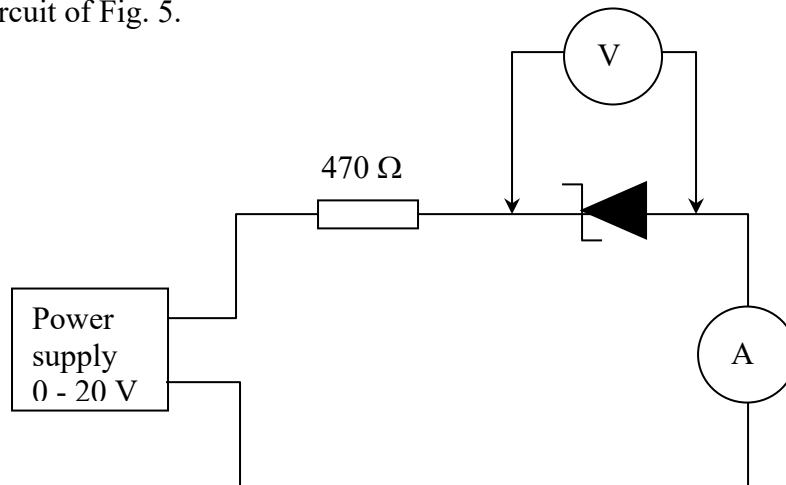

**Fig. 5:** Zener diode measurement circuit

- b. Record values of  $V_Z$  for the following values of  $I_Z$  (in mA): -3, -6, -10, -15, -17.5, -20, -22.5, and -25.

$V_Z$	$I_Z$
-3	
-6	
-10	
-15	
-17.5	
-20	
-22.5	
-25	

- c. Plot  $I_Z$  against  $V_Z$ . For a value of  $I_Z = -20$  mA, determine  $r_z$  and  $V_{Z0}$  (Fig. 4a).


---

---

---

---

---

 

## B2. Measuring Voltage Regulation

- a. For the circuit of Fig.5, measure the change in  $V_z$  when the voltage supply is changed from +12 to +14 V.

Calculate the change in the output / the change in the input. This is known as the *line stability ratio*.

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

- b. By modelling the zener diode as shown in Fig. 4b, calculate (using your measured values for  $r_z$ ) what you would expect the line stability ratio to be. Compare your result with this value.

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---



## **Part C: Report**

Complete a short report by answering the questions from the associated question sheet.

### **Equipment**

Resistor: 470 $\Omega$ , 10k $\Omega$ , 100k $\Omega$ , and 1M $\Omega$

Capacitor: 10  $\mu$ F

Diode: 1N4148, 1N746A (3.3 V)

- End of laboratory -