



Lab 3 – Diode Applications

XMUT204 Electronic Design

Topics

Objectives

- Working with diode clipper and clamper circuits.
- Measuring the characteristics of zener diode.
- Measuring voltage regulation.

Diode Clipper Circuit

- Diodes may be used in a number of ways to change the shape or form of a signal. For example, the diode clipper of Fig. 1a may be used to limit the amplitude of an ac signal.

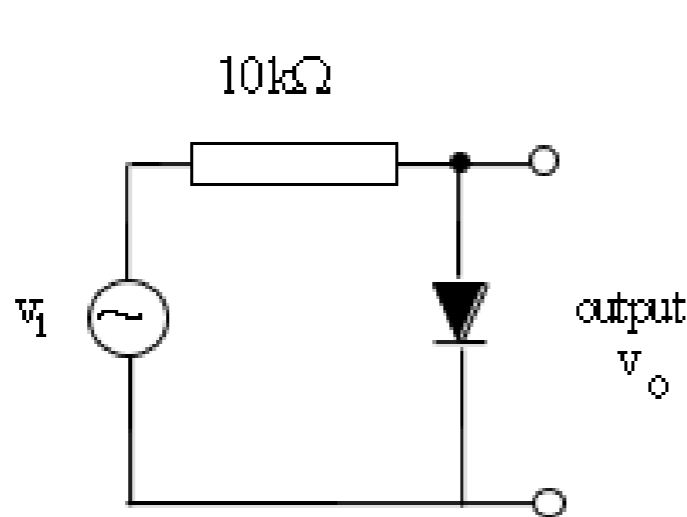


Fig. 1a: Clipper circuit

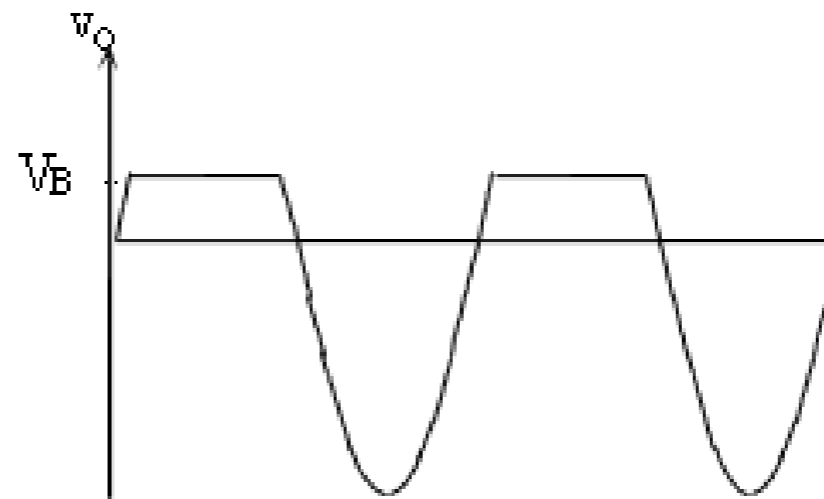



Fig. 1b: Clipper waveforms

- a. Set up the circuit of Fig. 1a. Use the signal generator at 1 kHz to provide an input sinusoidal signal at $8 V_{pp}$. Display both v_i and v_o on the oscilloscope (use dc coupling). The output v_o should be as shown in Fig 1b.

Diode Clipper Circuit

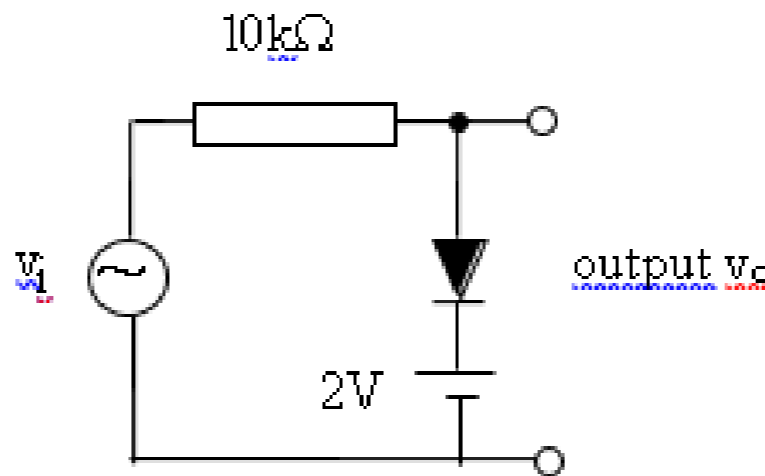- b. Using the constant drop model for the diode (see Lab 2 handouts) explain this result.


Insert the dc power supply (set to 2 V) between the diode and ground as shown in the Fig. 2 given below.



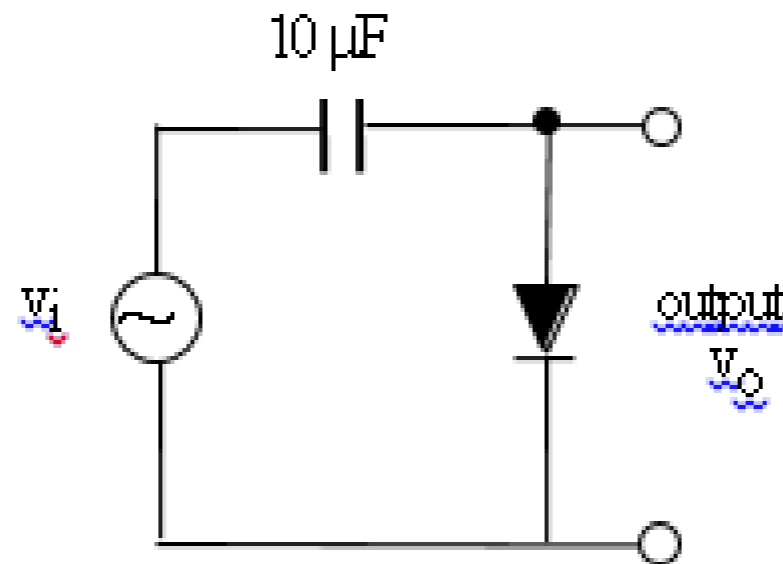- c. Sketch v_o and explain its form.
- d. Remove the dc power supply and reverse the diode. Sketch v_o and explain its form.

Diode Clamper Circuit

- Diodes may be used to control the peak values of an ac signal in a circuit, i.e. to hold (clamp) its dc level at a predetermined value.



- a. Replace the $10\ \text{k}\Omega$ resistor in Fig. 1a with a $10\ \mu\text{F}$ capacitor (Fig. 3); again use dc coupling on the oscilloscope coupling.
- b. Sketch v_i and v_o . Measure (using the DVM) the voltage drop V_C across the capacitor and explain the operation of the circuit.

Diode Clamper Circuit

Note:

- As v_i initially goes positive, the diode conducts and the capacitor is charged up; when v_i starts to fall from its peak value, the diode becomes reversed biased and the capacitor cannot discharge.
- $v_o = v_d = v_i - V_c$

Introduction to Zener diodes

- If a sufficiently large reverse bias is applied to a semiconductor diode, a significant current will start to flow at the "breakdown" voltage.
- Zener diodes are manufactured to withstand this breakdown effect up to some specified power rating. They are used as voltage regulators
- The I-V characteristics in the breakdown region are shown in Fig.

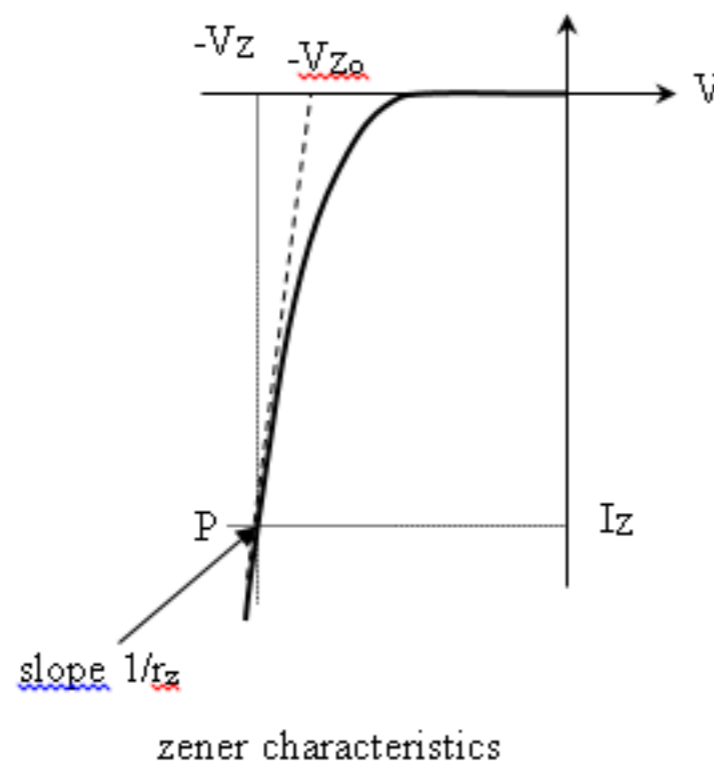


Fig. 4a: Zener diode V-I curve

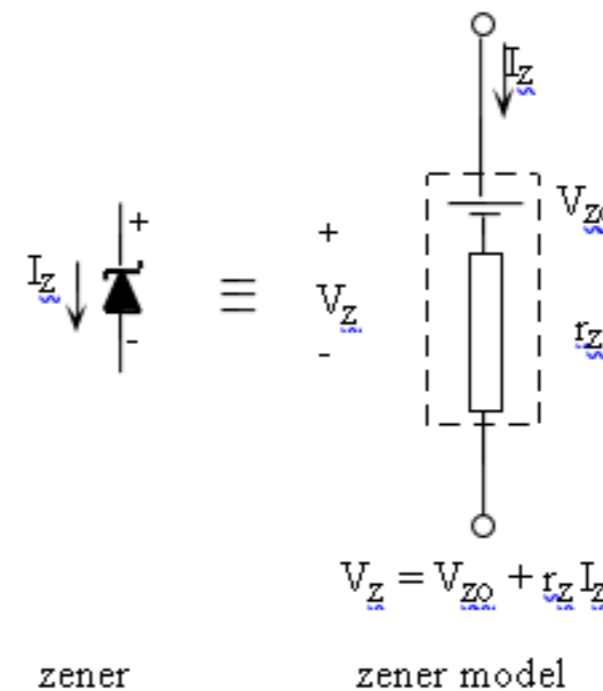


Fig. 4b: Zener diode model

Introduction to Zener diodes

- A zener is specified by its voltage V_Z at some test current I_Z (point P), its power rating and its incremental resistance r_z , the inverse of the slope of the characteristic at I_Z .
- This line cuts the V axis at V_{Z0} .
- The I-V relationship may be modelled by the combination of a voltage source V_{Z0} and resistance r_z shown in Fig. 4b.

Measure the Characteristics of Zener Diode

- Set up the circuit of Fig. 5.

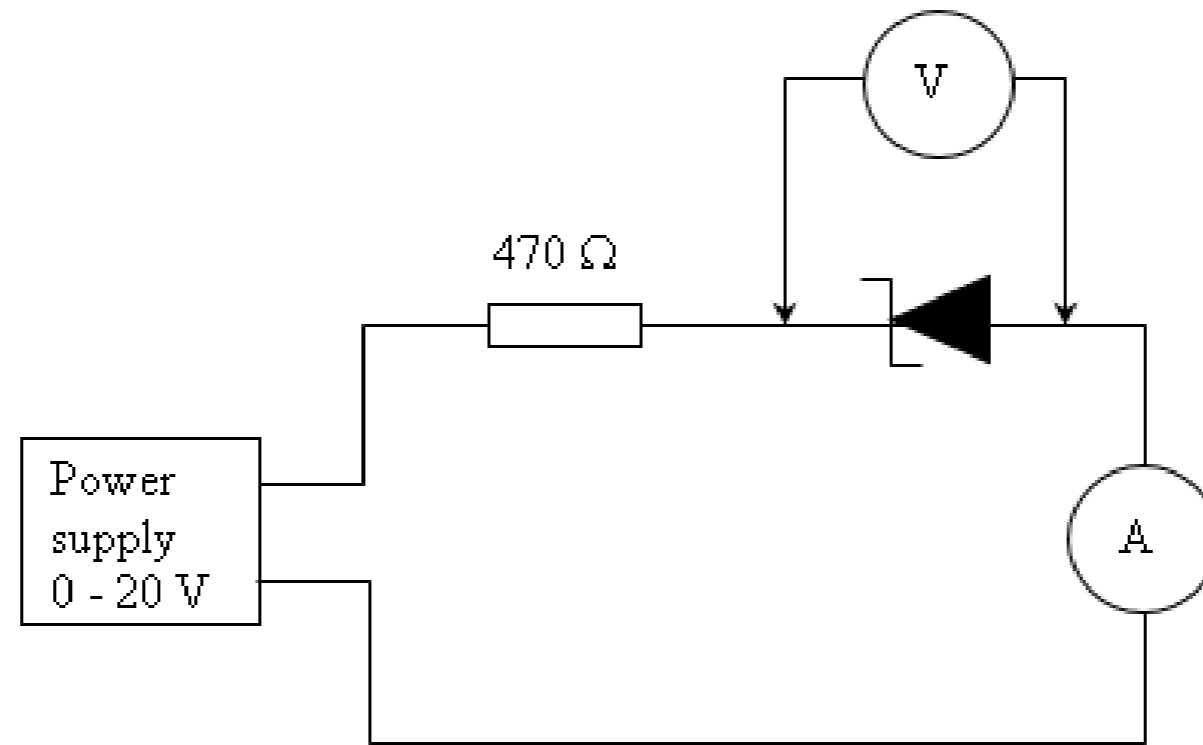


Fig. 5: Zener diode measurement circuit

- Record values of V_Z for the following values of I_Z (in mA): -3, -6, -10, -15, -17.5, -20, -22.5 and -25.
- Plot I_Z against V_Z . For a value of $I_Z = -20$ mA, determine r_z and V_{z0} (Fig. 4a).

Measure Voltage Regulation

- a. For the circuit of Fig.5, measure the change in V_z when the voltage supply is changed from +12 to +14 V.

Calculate the change in the output / the change in the input.
This is known as the *line stability ratio*.

- b. By modelling the zener diode as shown in Fig. 4b, calculate (using your measured values for r_z) what you would expect the line stability ratio to be. Compare your result with this value.

Report

Part C: Report

- Complete a short report by answering the questions from the associated question sheet.

Equipment

- Resistor: 470Ω , $10\text{k}\Omega$, $100\text{k}\Omega$, and $1\text{M}\Omega$
- Capacitor: $10\text{ }\mu\text{F}$
- Diode: 1N4148, 1N746A (3.3 V)