



# Lab 5 – BJT Applications

**XMUT204 Electronic Design**

# Topics

- In laboratory 4, you measured the current – voltage characteristics of a BJT in the common emitter configuration.
- In this lab, we will now look at two applications of this transistor configuration:
  - the use of BJTs as switches in order to construct basic digital logic gates.
  - the use of a BJT as a common emitter amplifier.
- In each case, we will also determine the operating point of the transistor on the current-voltage curve as measured in Lab 4.
- We will use resistor networks as discussed in class to provide the correct bias voltage to place it as close as possible to the correct operating point.

# Theory

## Part A: Theory

- We will be looking at two applications of BJT transistor in this laboratory exercises e.g. switching and amplifier applications.
- For the switching application, we can use the transistor as an ON – OFF switch by switching it between the cut-off region (transistor OFF and  $I_C = 0$ ) and the saturation region (transistor ON and  $I_C = \text{max}$ ).
- For the amplifier application, BJT can be used as current and voltage amplifiers. Transistor has been viewed as a current amplifier as the collector current is much larger than the base current:

$$I_C = \beta_{DC} I_B$$

# Theory

- In the active region of operation, this value of  $\beta$  will be a constant and any increase/decrease in  $I_B$  will lead to a proportional increase/decrease in  $I_C$ .
- We will now look at the transistor as a voltage amplifier where the signals are small AC voltages compared to the DC bias voltages.

# BJT as a switch and a digital logic gate

## 1. The BJT as a switch and a digital logic gate

a. Set up your circuit as shown in the figure below.

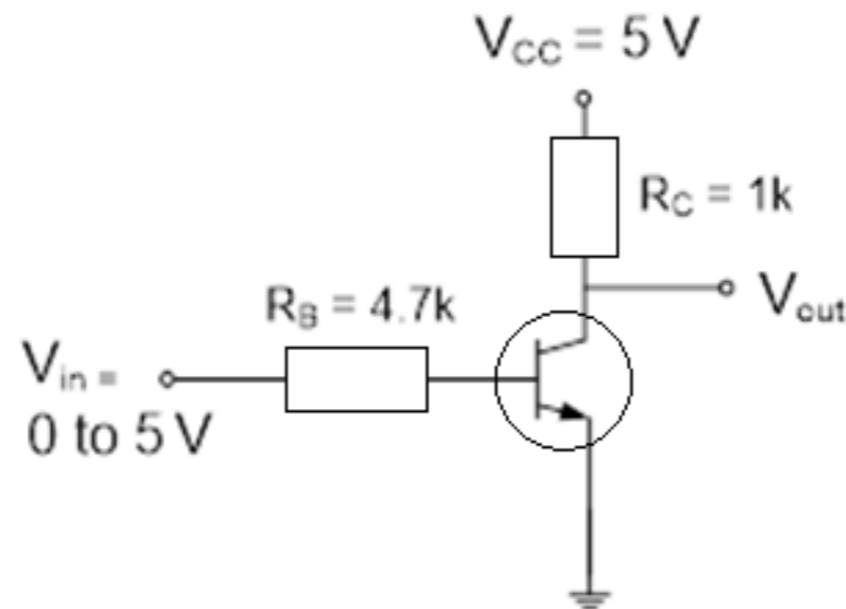


Fig 1: Using the BJT as a switch.

Slowly vary and measure the input voltage while also recording the output voltage.

Take more measurements when sharp changes would be observed. Plot  $V_{out}$  vs  $V_{in}$  and explain your observations.

# BJT as a switch and a digital logic gate

- b. If we associate TRUE & FALSE **logic** values with HI (~ 4-5 V) and LO (0 - ~ 0.8 V) electrical voltage **ranges**, then the results of part (a) show that this circuit may be used for the logic operation of inversion or complementation.

In	Out
LO	
HI	

What logic function does this circuit perform?

# BJT as a switch and a digital logic gate

- c. If we now assume that the input voltage will either be a LO or a HI, look at your current – voltage characteristics from last week and plot the Q point for the midrange of the input = LO as well as the Q point for the midrange of the input = HI.

What regions in the V-I characteristics does this represent?

What will be the operating point if the input voltage is 2.5 V?

Explain what will be the logic output in this case?

# The value of $\beta$ in the active region

## 2. The value of $\beta$ in the active region

- When using the BJT as an amplifier, we may want to use the value  $\beta = I_C/I_B$  to calculate the collector current that will be produced by a selected base current.
- We will now use the BJT transistor in the common emitter configuration and use resistor networks (to be discussed in class) to provide the correct bias and stabilize the point of operation.
  - a. Use your current – voltage curve from Lab 4 and calculate the  $\beta$  value of your transistor in the active region. Do this at several points in the active region and show the values in a table:

# The value of $\beta$ in the active region

$I_B$ ( $\mu A$ )	$V_{CE}$ (Volts)	$I_C$ (mA)	$\beta$

- Calculate the average, minimum and maximum value of  $\beta$  obtained. Also obtain the  $\beta$  values from other students in the lab.

Measurement	B average	B maximum	B minimum
Own			
Another 1			
Another 2			
Another 3			

- For the circuit below as shown in Figure 2, use the minimum and maximum values of  $\beta$  in the table above and calculate the operating point ( $V_{CE}$  and  $I_C$ ) in each case.
- How widely do these operating points differ?

# The value of $\beta$ in the active region

- Hopefully the above calculations is a good illustration that we should not rely on the value of  $\beta$  to determine the operating point, as this value can differ significantly between the same model of transistors.

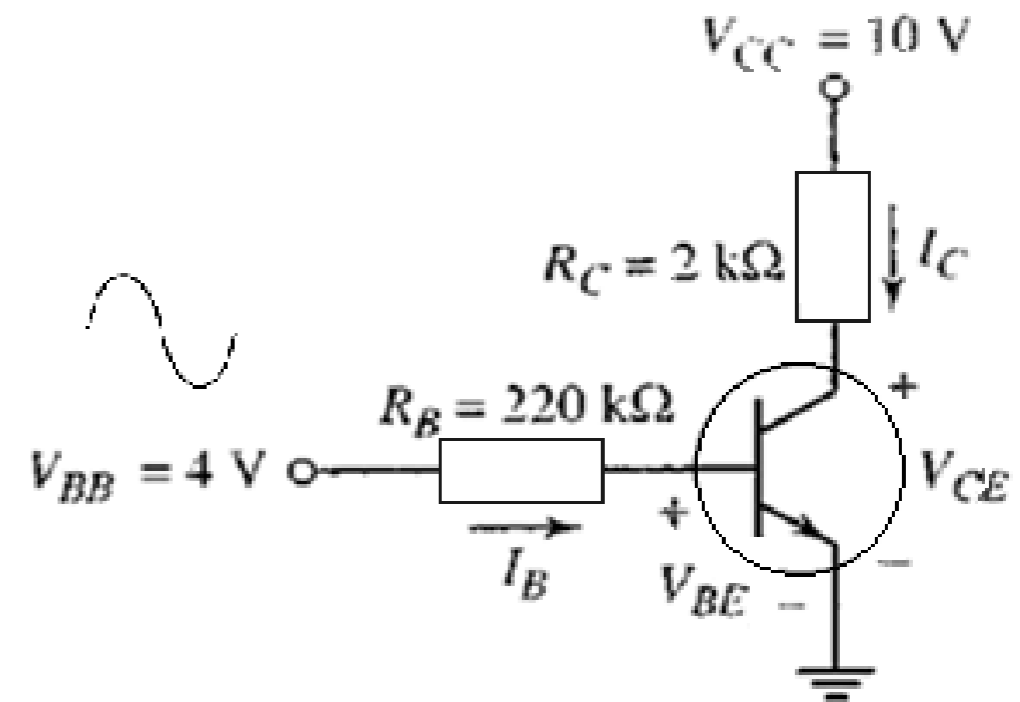


Fig. 2: BJT common emitter circuit

- In addition,  $\beta$  will also vary strongly with temperature. We would then rather use bias circuits (the external components such as resistors and capacitors) to ensure that we obtain a stable bias point.
- The use of voltage divider bias circuits such as in Figure 3 can provide this stability.

# The BJT as an amplifier

## 3. The BJT as an amplifier

a. Connect the circuit of Fig. 3 using the BJT board provided.

The following values apply:

$$\begin{array}{llll} R_{B1} & 50 \rightarrow 500 \text{ k}\Omega & R_C & 0.3 \rightarrow 10 \text{ k}\Omega & C_1 = C_2 = 1 \mu\text{F} \\ R_{B2} & 22 \text{ k}\Omega & R_e & 1 \text{ k}\Omega & C_e = 10 \mu\text{F} \end{array}$$

b. Setting both  $R_{B1}$  and  $R_C$  at mid range, connect a 20 mV pp, 1 kHz sine wave from the signal generator to  $v_i$ .

Examine both  $v_i$  and  $v_o$  on the dual trace oscilloscope.

# The BJT as an amplifier

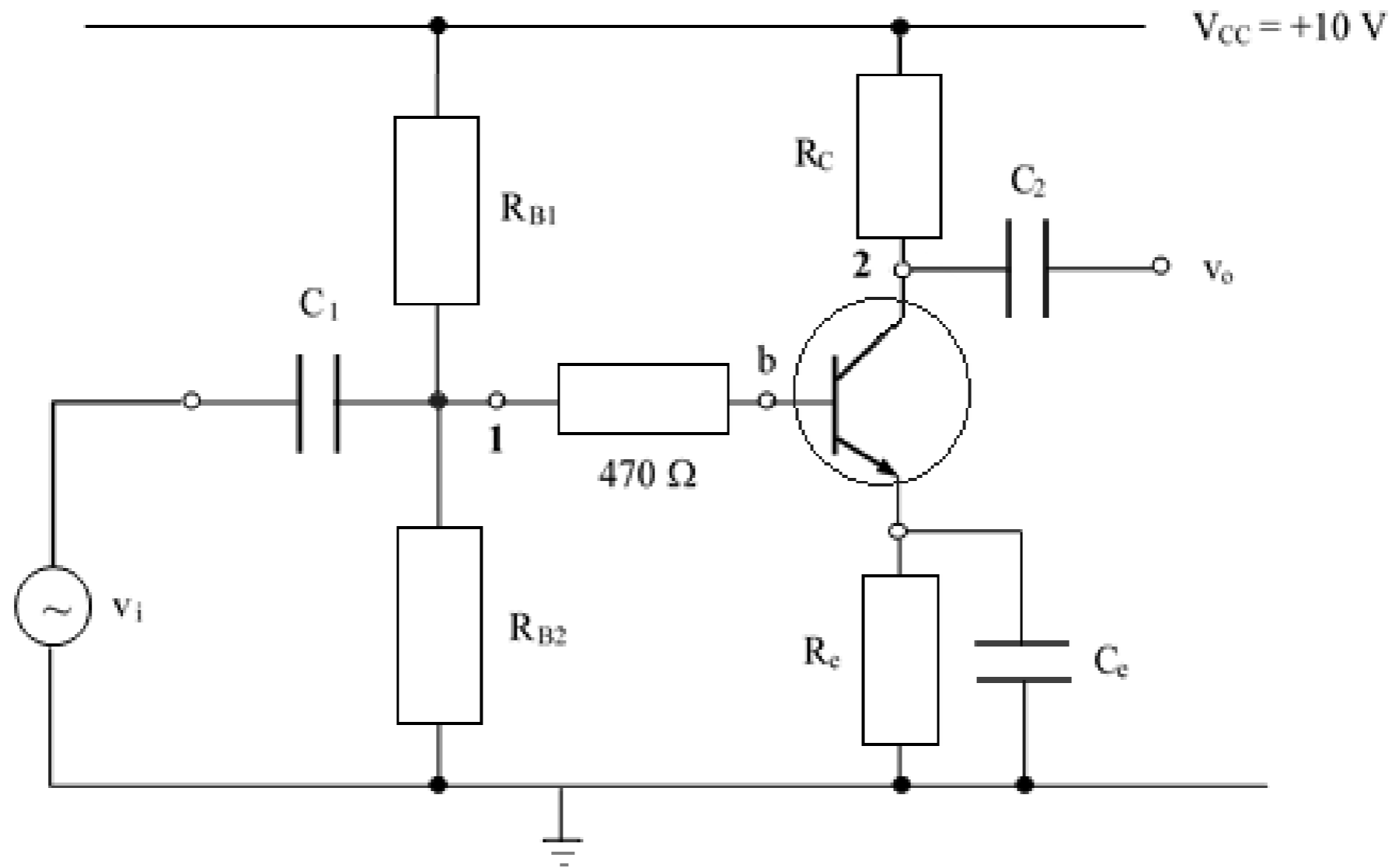


Fig. 3: BJT common emitter amplifier

- c.  $R_{B1}$  and  $R_{B2}$  constitute a potential divider determining the bias (dc operating) condition of the transistor.

# The BJT as an amplifier

- Maintaining  $R_C$  at mid-range, set  $R_{B1}$  at maximum.
- Examine points 1 and 2 with the oscilloscope (set to dc coupling, both traces 2 V/cm, ground near the base of the screen).
- Initially  $V_B \sim 0$  V,  $V_C \sim 10$  V and the transistor is cut-off. Progressively decrease  $R_{B1}$  until the transistor starts to conduct (active mode).

Note the changes to  $V_B$  and  $V_C$  and the output sine wave. Adjust  $R_{B1}$  to provide an undistorted sine wave output. Explain your observations.

# The BJT as an amplifier

- d. Observe  $v_i$  and  $v_o$  again on the oscilloscope and determine the voltage gain. Note any phase difference. Now, remeasure  $A$  with  $C_e$  removed.

$$A = \frac{v_o}{v_i}$$

- e. Explain the operation of the circuit, including the function of the dc blocking capacitors  $C_1$  and  $C_2$  (Note: you may assume that  $R_C = 5.5 \text{ k}\Omega$ ). Finally, reconnect  $C_e$ .
- f. Remove the ac signal part and measure  $I_B$ ,  $V_{CE}$  and  $I_C$  for the DC bias only. Plot this operating point on the  $V_{CE}$  vs  $I_C$  characteristic curves from Lab 4.

# Report

## Part C: Report

- Now, complete a short report by answering the questions from the associated question sheet.

## Equipment:

- Transistor: BC548
- Resistors: 220  $\Omega$ , 470  $\Omega$ , 1 k $\Omega$ , 4.7 k $\Omega$ , 22 k $\Omega$
- Decade resistance box