



VICTORIA UNIVERSITY OF  
**WELLINGTON**  
TE HERENGA WAKA  
NEW ZEALAND

# XMUT204 Electronic Design



## Lecture 3c – BJT Switching Applications

## Overview


1. The Use of Electrical/Electronic Switch in Circuit.
2. Using the Transistor as Switch.
3. The Output Current-Voltage Characteristics.
4. BJT Switching Operation.
5. DC Gain ( $\beta_{DC}$ ) to Use.
6. Load Line of BJT Switching Circuit.
7. Design with Common Emitter Configuration.
8. Logic Device Families.
  
# 1. The Use of Electrical/Electronic Switches in Circuits

- Familiar with the use of mechanical ON/OFF switches in circuits which will make/break a circuit.
- Often need for one part of a circuit to be able to switch ON/OFF a secondary circuit.
- Status of the secondary circuit depends on the status of the primary circuit(s).
- One method to do this is by electromechanical relays.


 
# 1. The Use of Electrical/Electronic Switches in Circuits



- Parts of a typical relay – contact is on/off depends on states of coil.


# 1. The Use of Electrical/Electronic Switches in Circuits

- However, for a number of reasons, the transistors has totally replaced relays as switching elements.
- This is particularly true in low current applications.


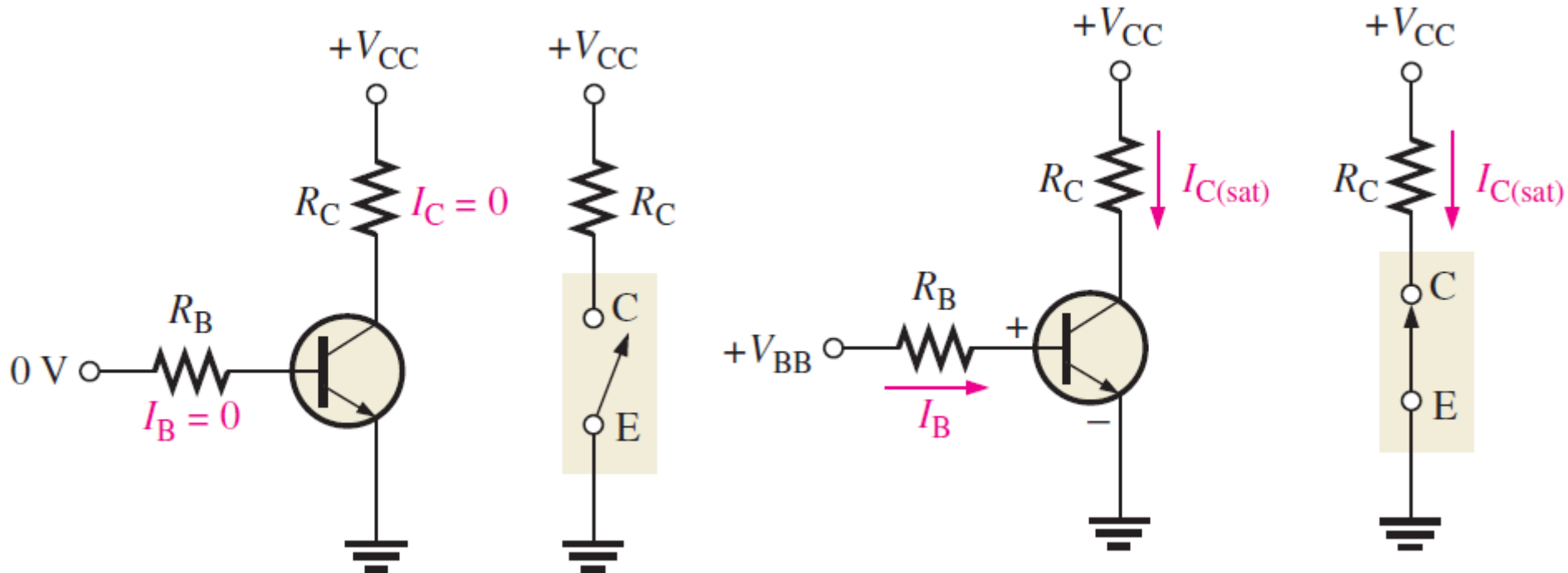
## 2. Using the Transistor as a Switch

- We can use the transistor as an ON – OFF switch by switching it between the cut-off region (transistor OFF and  $I_C = 0$ ) and the saturation region (transistor ON and  $I_C = \text{max}$ )




- Transistor OFF
- Open switch
- Cut-off mode

- Transistor ON
- Closed switch
- Saturation mode
 
## 2. Using the Transistor as a Switch (cont.)


- NPN transistor in the common emitter configuration.
- $V_{BB}$  and  $R_B$  provide biasing current to turn on the BJT.
- With  $I_C$  and emitter,  $I_E$  (as set by  $V_{CC}$  and  $R_C$ ), we observe a voltage drop across CE ( $V_{CE}$ ).



- To be able to do this efficiently, let's have another look at the output characteristic curves of a common emitter NPN transistor.
 
### 3. The Output Current–Voltage Characteristics

- We need to determine the appropriate region for the switching operation of the BJT transistor.
- We look at the graph of the collector-emitter voltage vs. collector current.



### 3. The Output Current–Voltage Characteristics

For the **cut-off region**, we have:

- $I_B = 0$ , thus  $I_C = 0$  and the whole transistor is OFF.
- $V_{BE} < 0.7 \text{ V}$ .
- BE junction then essentially reverse biased, i.e. open circuit.

For the **active region**, we have:

- $V_{BE} = 0.7 \text{ V}$ , so the BE junction is forward biased.
- The CB junction is reverse biased.
- $I_B > 0$  and we have  $I_C = \beta I_B$ .
- The transistor is ON in the mode typically used for amplification.


### 3. The Output Current–Voltage Characteristics

But what is the reason for transistor behaviour in the **saturation region** ? In this region, we would have:

- $V_{BE} = 0.7 \text{ V}$  so the BE junction is forward biased.
- $V_{CE}$  would be very small i.e. if this is the case, we have  $V_{CE} \sim 0 \text{ V}$ .
- The BC junction will thus be forward biased i.e. both the junctions are forward biased, and transistor appears as a short.
- Region modelled as a constant voltage drop of  $V_{CE} = 0.2 \text{ V}$ .
- The  $\beta$  is smaller than the  $\beta$  value in the active region.

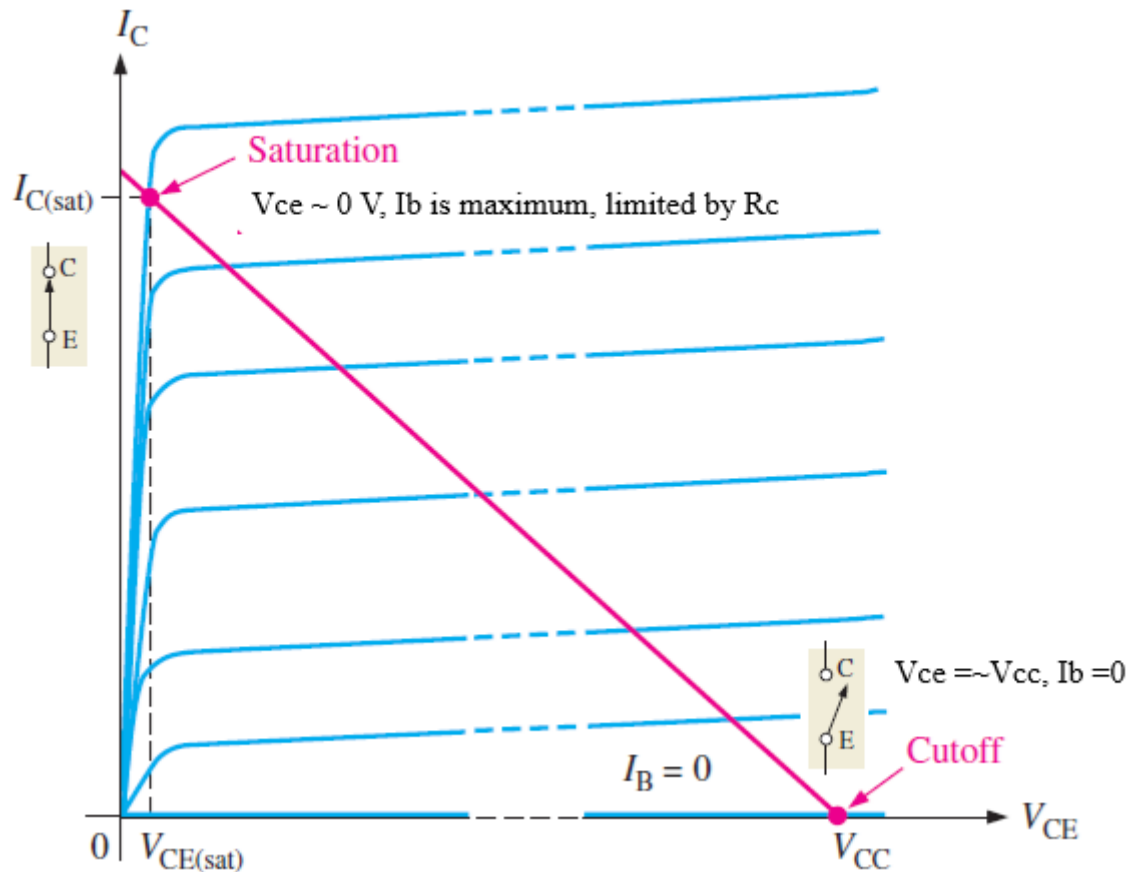
### 3. The Output Current–Voltage Characteristics

- We need to switch efficiently between the cut-off point and saturation point of operation.
- Saturation point:  $V_{CE} \sim 0$  and  $I_B$  is maximum – limited by  $R_C$ .


 
## 4. BJT Switching Operation

- When BJT as switch is off, considering no leakage current, all of the currents,  $I_B$  and  $I_C$  are zero.
- Since  $I_C$  is zero, the  $V_{CE(\text{cutoff})}$ , is equal to  $V_{CC}$ .




## 4. BJT Switching Operation (cont.)

- When the BJT switch is on, the saturated collector current is:

$$I_{C(\text{sat})} = \frac{V_{CC} - V_{CE(\text{sat})}}{R_C}$$

- Maintaining saturation, the minimum base current is:
 
$$I_{B(\text{min})} = \frac{I_{C(\text{sat})}}{\beta_{DC}}$$




## 5. What DC Beta ( $\beta_{DC}$ ) to Use?


- Knowing  $V_{CE(sat)}$ , we can calculate  $I_{C(sat)}$  then  $I_{B(min)}$ .
- However, you may wonder, what is the value of  $\beta_{DC}$ ?
- To make it easier for you to find out, the clue is you can find  $\beta_{DC}$  on the BJT datasheet.

ON CHARACTERISTICS		Symbol	Min	Max	Unit
DC Current Gain (Note 2)		$h_{FE}$			–
( $I_C = 0.1 \text{ mA dc}$ , $V_{CE} = 1.0 \text{ V dc}$ )	2N3903		20	–	
	2N3904		40	–	
( $I_C = 1.0 \text{ mA dc}$ , $V_{CE} = 1.0 \text{ V dc}$ )	2N3903		35	–	
	2N3904		70	–	
( $I_C = 10 \text{ mA dc}$ , $V_{CE} = 1.0 \text{ V dc}$ )	2N3903		50	150	
	2N3904		100	300	
( $I_C = 50 \text{ mA dc}$ , $V_{CE} = 1.0 \text{ V dc}$ )	2N3903		30	–	
	2N3904		60	–	
( $I_C = 100 \text{ mA dc}$ , $V_{CE} = 1.0 \text{ V dc}$ )	2N3903		15	–	
	2N3904		30	–	

Characteristic	Symbol	Min	Max	Unit
Collector - Emitter Saturation Voltage (Note 2) ( $I_C = 10 \text{ mAdc}$ , $I_B = 1.0 \text{ mAdc}$ ) ( $I_C = 50 \text{ mAdc}$ , $I_B = 5.0 \text{ mAdc}$ )	$V_{CE(sat)}$	-	0.2 0.3	Vdc
Base - Emitter Saturation Voltage (Note 2) ( $I_C = 10 \text{ mAdc}$ , $I_B = 1.0 \text{ mAdc}$ ) ( $I_C = 50 \text{ mAdc}$ , $I_B = 5.0 \text{ mAdc}$ )	$V_{BE(sat)}$	0.65	0.85 0.95	Vdc

 

**Collector Saturation Region**

 

**"ON" Voltages**


## 5. What DC Beta to Use? (cont.)

- Since DC beta ( $\beta_{DC}$ ) is equivalent to the hybrid parameter ( $h_{FE}$ ), we look it up in the datasheet.
- But,  $h_{FE}$  in the datasheet is the current gain of a BJT that is operating as an amplifier or in the active region.
- We require the gain of the BJT for the switching circuit.
- The  $\beta_{DC}$  used in the saturation region for the 2N3904 is 10. Notice that the  $I_C/I_B$  ratio is always 10.
- The guaranteed value of  $\beta_{DC}$  is 10 for it to operate in the saturation region.
- Some may use 20 but  $\beta_{DC}$  is not constant, and it changes with the junction temperature. So, it's better to set  $\beta_{DC}$  at 10.
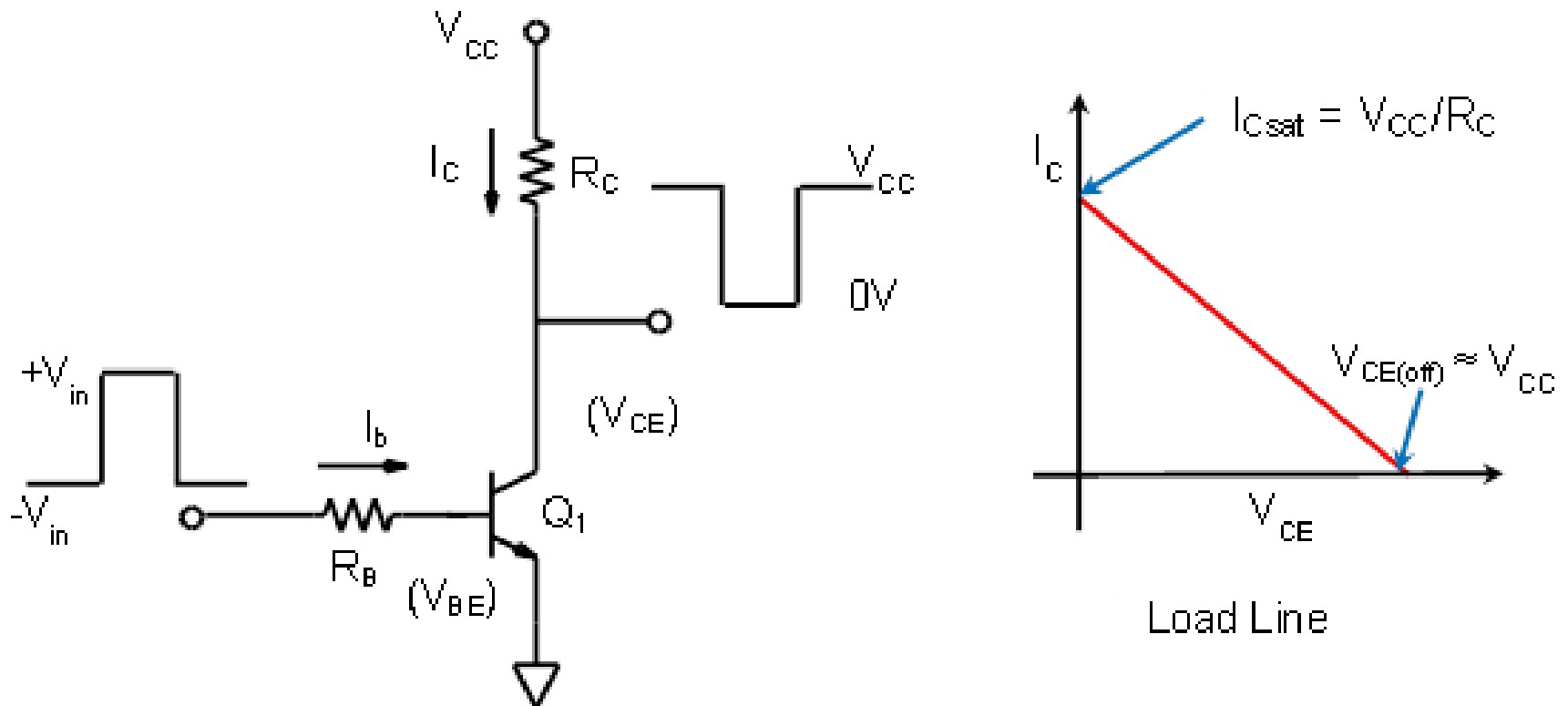
## 6. Load Line of BJT Switching Circuit

- When the BJT is in cut-off, this state is like an open switch.



$$V_{CE} = V_{CC} \quad \text{and} \quad I_C = 0 \text{ A}$$


  
## 6. Load Line of BJT Switching

- When the input equals  $+V_{in}$ , the transistor is driven into saturation, and this state is like a closed switch connecting the bottom of  $R_C$  to ground.

$$V_{CE} \sim 0 \text{ V} \quad \text{and} \quad I_{C(\text{sat})} = V_{CC}/R_C$$




## 6. Load Line of BJT Switching Circuit (cont.)

The characteristics for a BJT switch assume that:

- The  $V_{in}$  is low enough to drive the transistor into cut-off.
- The  $+V_{in}$  must produce enough base current through  $R_B$  to drive the transistor into saturation.
- The transistor is an ideal component.


These conditions can be assured by designing the circuit so that:

 1. The input voltage,  $V_{in} = V_{BE}$ .
2. The voltages at the input:  
 $+V_{in} = V_{BE} + I_B R_B$  ( $V_{CC}$  is a good maximum).
3. The currents,  $I_B > I_{C(sat)}/\beta$ .



 
## 6. Load Line of BJT Switching Circuit (cont.)

- Condition 1 guarantees that the circuit is driven into the cut-off region by the input.
- Conditions 2 and 3 assure that the transistor will be driven into the saturation region.
- An actual BJT switch differs from the ideal switch in several aspects.
- In practice, even in cut-off there is some leakage current through the transistor.
- Also, in saturation, there is always some voltage dropped across the transistor's internal resistance.


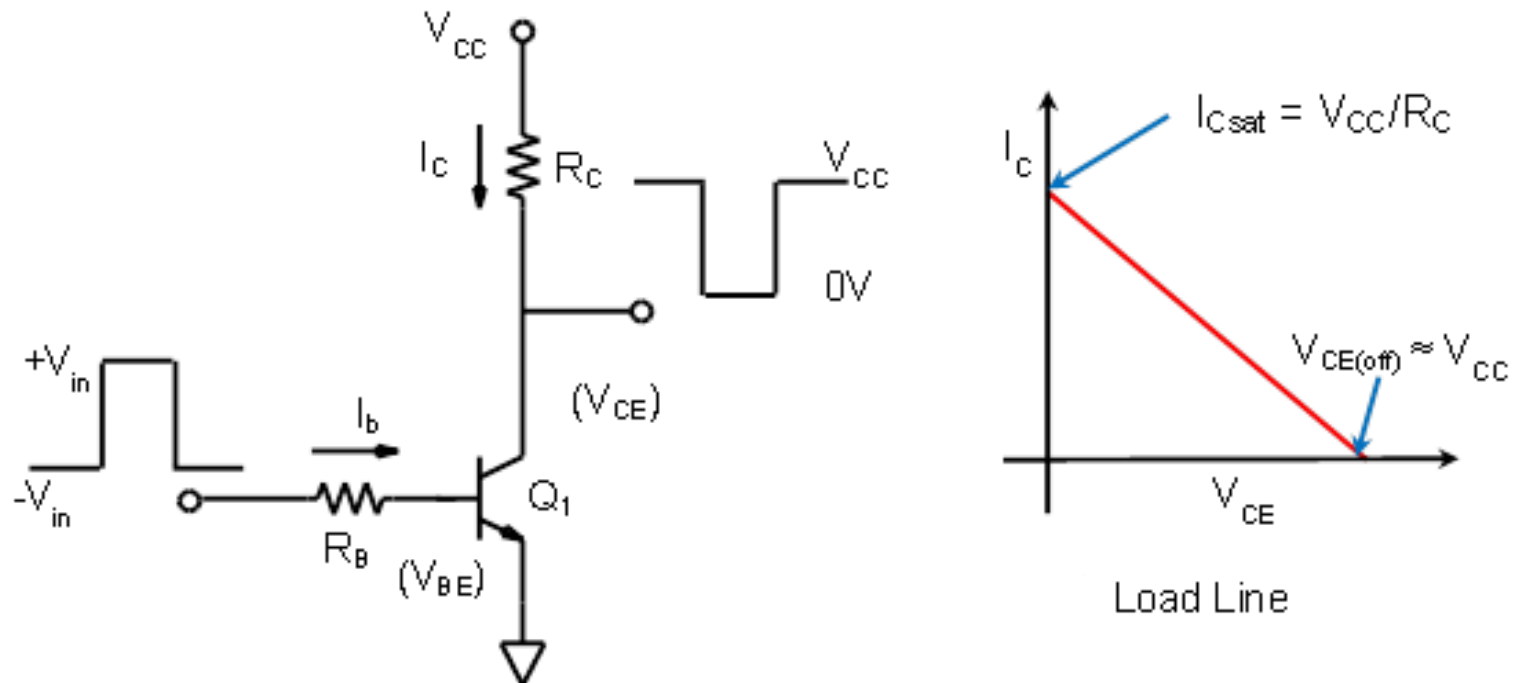
## 6. Load Line of BJT Switching Circuit (cont.)

- Typically, this will be between 0.2 and 0.4 V in saturation depending on the collector current and size of the device.
- These variations from the ideal are generally minor with a properly sized device, so we can assume near ideal conditions when analysing or designing a BJT switch circuit.




## Example 1 – BJT Switching Circuit Biasing

For the BJT circuit as shown in the figure given below, design it for switching application.

- a. What minimum value of  $I_B$  is required to saturate this transistor if  $\beta_{DC}$  is 150? Neglect  $V_{CE(sat)}$ .

[4 marks]

 - b. Describe briefly the significant of this current. Explain what happens when you further increase this current. [2 marks]



## Answer

- a. Since  $V_{CE(\text{sat})}$  is neglected (assumed to be 0 V), the saturation current at the collector is found from:

$$I_{C(\text{sat})} = \frac{V_{CC}}{R_C} = \frac{12 \text{ V}}{2.2 \text{ k}\Omega} = 5.45 \text{ mA}$$

As a result, the minimum current at the base of transistor is:

$$I_{B(\text{min})} = \frac{I_{C(\text{sat})}}{\beta_{DC}} = \frac{5.45 \text{ mA}}{150} = 36.3 \text{ }\mu\text{A}$$

This is the value of  $I_B$  necessary to drive the transistor to the point of saturation.

- b. Any further increase in  $I_B$  will ensure the transistor remains in saturation, but there cannot be any further increase in  $I_C$ .


## 7. Design with Common Emitter Configuration

Consider a common emitter BJT configuration given below.

In the given circuit:

Step 1. Assume initially  $V_{in} \sim 0$  V (OFF)

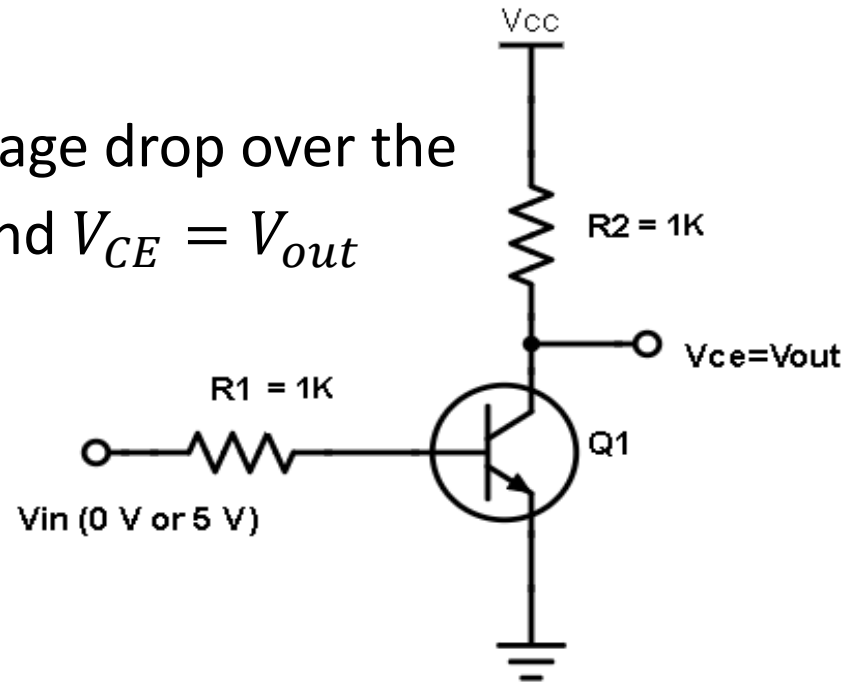
- So, that  $V_{BE} < 0.7$  V, as a result the transistor is OFF with  $I_B = I_C = 0$ .
- If  $I_B = 0$ , then there is no voltage drop over the resistor at the collector ( $R_2$ ) and  $V_{CE} = V_{out}$  which is  $\sim V_{CC}$ .
- The transistor is an open circuit as it is OFF  $\rightarrow$  *cut-off*.


 
## 7. Design with Common Emitter Configuration (cont.)

Step 2. Now, increase  $V_{in}$  to produce  $V_{BE} \sim 0.7$  V.


- As  $I_B$  increases,  $I_C$  will rapidly increase as  $I_C = \beta I_B$  in *active region*.
- The current  $I_C$  will eventually be limited by the value of collector resistor ( $R_2$ ).


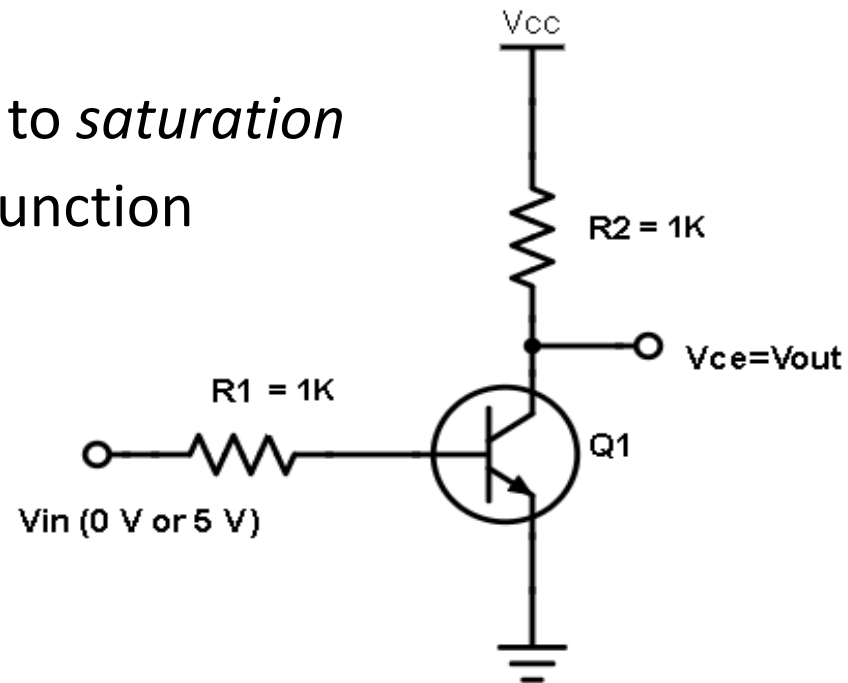
## 7. Design with Common Emitter Configuration (cont.)

Step 3. Keep on increasing  $I_C$


- As  $I_C$  increases, the voltage drop over the resistor at the collector ( $R_2$ ) will increase  $\rightarrow$  the voltage drop  $V_{CE}$  will decrease
- This will eventually decrease to *saturation level* ( $V_{CE} \sim 0.2 \text{ V}$ ) as the BC junction becomes forward biased.


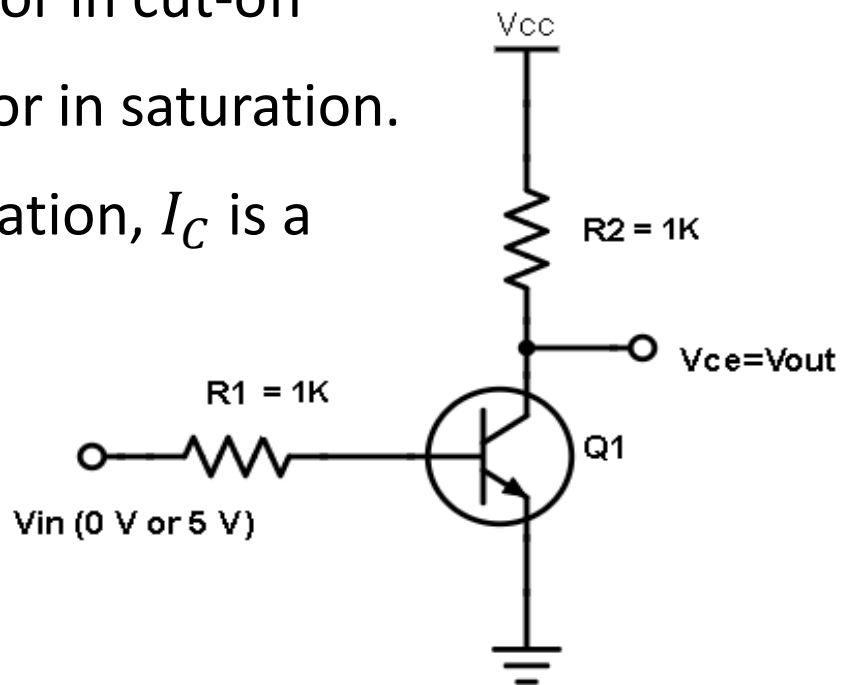
## 7. Design with Common Emitter Configuration (cont.)


Step 4. For switch operation, we want to use a binary signal level on  $V_{in}$ :

- $V_{in} = LO$  must put transistor in cut-off
- $V_{in} = HI$  must put transistor in saturation.
- Since transistor is in saturation,  $I_C$  is a maximum.


 
## 7. Design with Common Emitter Configuration (cont.)

Step 5. Plot a typical graph of  $V_{in}$  vs.  $I_C$




## 7. Design with Common Emitter Configuration (cont.)

Step 5. Plot a typical graph of  $V_{in}$  vs.  $I_C$

- When the transistor is turned on at around 600 mV of the input voltage, the collector current starts to flow.
- There is a limit on the collector current is set by the value of the resistor at the collector ( $R_2$ ) in the circuit.
- Region between the turn on and the maximum point is called active region.
 
## 7. Design with Common Emitter Configuration (cont.)

Step 6. Plot a typical graph of  $V_{in}$  vs  $V_{CE}$ .



## 7. Design with Common Emitter Configuration (cont.)

Step 6. Plot a typical graph of  $V_{in}$  vs  $V_{CE}$  (cont..)


- When the BJT transistor is off,  $V_{CE}$  is found to be equal to  $V_{CC}$ .
- When the transistor is on, it is held to a value of 0.2 V.
- Notice the **inverter** behaviour of this circuit i.e. the output voltage is the inverse voltage of the input.

## Example 2 – BJT Switching Circuit


The circuit below must be used to switch on a LED when a 5 V logic signal is used as the input voltage on the base of the transistor.

Calculate sensible values for  $R_1$  (at the base) and  $R_2$  (at the collector) to ensure that the transistor operates effectively as a switch.

[6 marks]

 

 - The circuit is to be supplied with a  $V_{CC} = 12\text{ V}$  and saturation level voltage across the collector-emitter junction of the BJT transistor  $Q_1$ ,  $V_{CE} = 0.2\text{ V}$ .



- The LED needs 20 mA for operation with optimum brightness and has a voltage drop of  $V_D = 1.8\text{ V}$  over it when forward biased (e.g. a red LED).
- You will be using a microcontroller to provide the  $V_{in}$  signal and the output of the microcontroller can provide a maximum current of 8 mA.

## Answer


For the CE loop we can write a KVL for the saturation case:

$$V_{CC} - V_D - I_C R_2 - V_{CE} = 0$$

- Entering values into the equation:


$$12\text{ V} - 1.8\text{ V} - (20\text{ mA})(R_2) - 0.2\text{ V} = 0$$

 - Solve for the resistor at the collector ( $R_2$ ) to find  $R_2 = 500\ \Omega$ .
- Do we get a  $500\ \Omega$  resistor?  
-> choose  $470\ \Omega$  resistor from the E12 resistor series.




- Now, need to find the base current  $I_B$  that will be sufficient to generate this collector current we have:  $I_C = \beta I_B$  with  $\beta$  typically 100 to 500 in the active region.
- But we are operating in the saturation region where  $\beta$  is considerably lower – thus take  $\beta = 50$ .
- We would then need a base current of:
 
$$I_B = \frac{I_C}{\beta} = \frac{20 \text{ mA}}{50} = 0.4 \text{ mA}$$




- The calculated value of  $I_B = 0.4 \text{ mA}$  represents the minimum value of base current that would be able to drive the transistor into saturation.
- However, when we use a transistor in a switch configuration, we would typically overdrive the transistor to ensure that we are in saturation.
- A typical overdrive factor of 10x can be used.
- The base current to aim for would thus be  $I_B = 4 \text{ mA}$ .

 

- Solve for the resistor at the base ( $R_1$ ) by looking at the BE current loop:

$$V_{in} - I_{R1}R_1 - V_{BE} = 5\text{ V} - (4\text{ mA})R_1 - 0.7\text{ V} = 0$$

 - Thus  $R_1 \approx 1.1\text{ k}\Omega$
- This will ensure cut-off and saturation behaviour.
- $I_B$  will be within the output capability of the microcontroller.



## 8. BJT Switching Application for Logic Devices


- Use BJT to design and construct logic gates.
- For logic gate design, like BJT switching applications, there are two states of operation:
  - Saturation, or
  - Off.
- The voltages and resistors are picked -> the above conditions hold.
- In short, the transistor now behaves as a switch.

## Logic Gates Using BJT

- Consider the following BJT's NOT gate circuit ( $V_{CC} = 10\text{ V}$ ,  $R_B = 1\text{ k}\Omega$ ,  $R_C = 1\text{ k}\Omega$ , and  $V_{BE} = 0.7\text{ V}$ ).

- Let.

Voltage (Volt)	Logic Gate
10	1
0	0

 

- Thus, the conditions and states of the circuit are:

$V_i$ (Volt)	$V_i$ State	Q1 State	$V_o$ (Volt)	$V_o$ State
0	0	OFF	10	1
10	1	SAT	0.2	0

- The circuit performs the NOT function -> NOT logic gate.

## Note:

- The current at the input is:

$$I_B = \frac{V_i - V_{BE}}{R_i} = \frac{10 \text{ V} - 0.7 \text{ V}}{1 \text{ k}\Omega} = 9.3 \text{ mA}$$

- If we assume the transistor is :

$$I_C = \beta I_i = (100)(9.3 \text{ mA}) = 930 \text{ mA}$$

- Thus

$$\begin{aligned} V_o &= V_{CC} - I_C R_C = 10 - (930 \text{ mA})(1 \text{ k}\Omega) \\ &= -920 \text{ V (saturated)} \end{aligned}$$

- The current at the output is:

$$I_C = \frac{V_{CC} - V_{CE(\text{sat})}}{R_C} = \frac{10 \text{ V} - 0.2 \text{ V}}{1 \text{ k}\Omega} = 9.8 \text{ mA}$$


## Design of BJT as Logic Devices

- Consider BJT's NOT-  
NOT gate circuit

$$(V_{BE(\text{on})} = 0.7 \text{ V};$$

$$V_{CE(\text{sat})} = 0.2 \text{ V};$$

$$\beta = 100).$$

 

- The conditions and states of the circuit are listed below.


$V_i$ (Volt)	$Q_1$ State	$V_{C1}$ (Volt)	$Q_2$ State	$V_{C2} = V_O$ (Volt)
0	OFF	10	SAT	0.2
10	SAT	0.2	OFF	10

- Assuming high: 8 V - 10 V  
and low: 0 V - 1 V, thus:


Input	Output
0	0
1	1

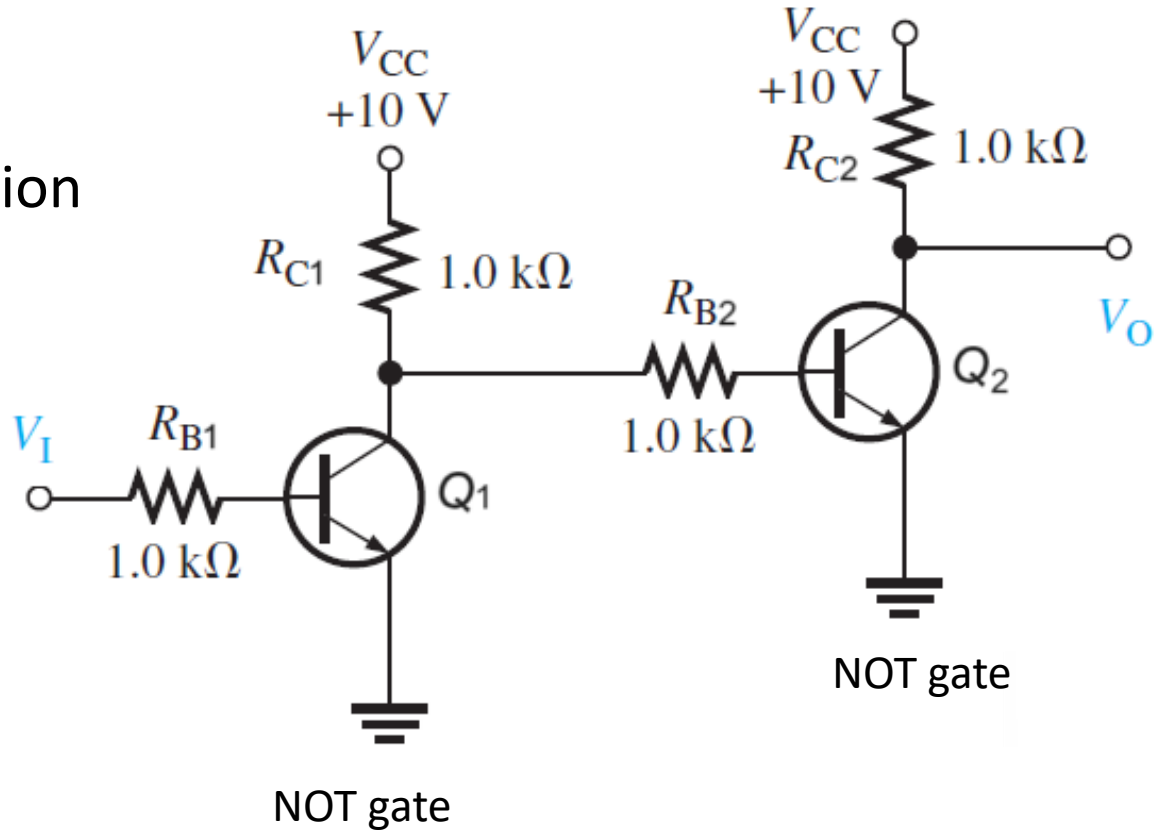**Note:**


- The overall operation of the circuit is as shown below.



 - Thus, the logic gate is realised as outlined below.



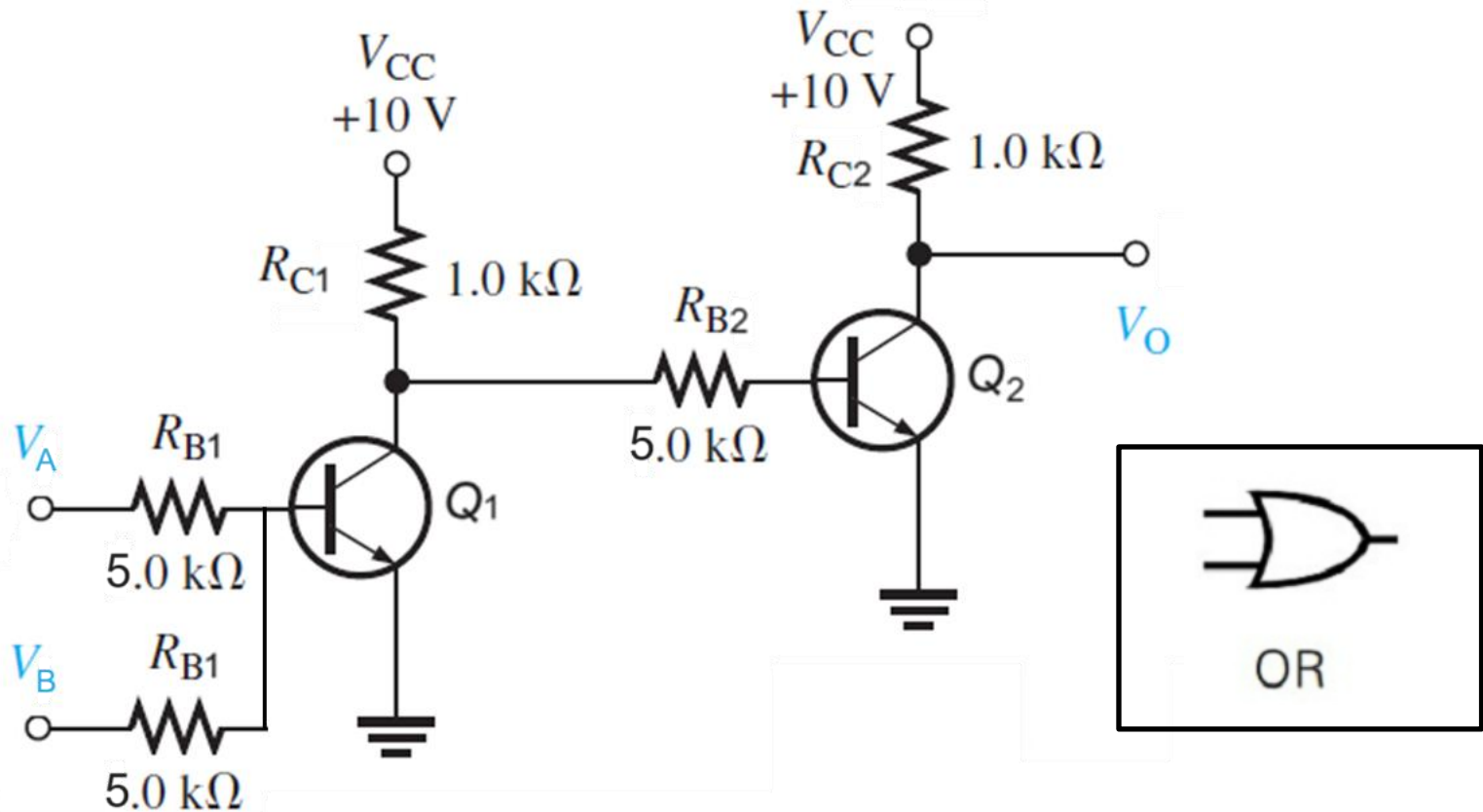- Consider two BJTs in series as OR gate circuit given below ( $V_{BE(\text{on})} = 0.7 \text{ V}$ ;  $\beta = 100$ ).
- Two inputs i.e.  $V_A$  and  $V_B$ .




- The conditions and states of the circuit are listed below:

$V_A$ (Volt)	$V_B$ (Volt)	$Q_1$ State	$Q_2$ State	$V_O$ (Volt)
0	0	OFF	SAT	0.2
0	10	SAT	OFF	10
10	0	SAT	OFF	10
10	10	SAT	OFF	10


- The logic function is shown below. This is the operation of an OR logic gate.

$A$	$B$	$Z$
0	0	0
0	1	1
1	0	1
1	1	1

 
- Transistor as a switch (i.e. knowing  $V_{CC} = 10\text{ V}$  and  $V_{CE(\text{sat})} = 0.2\text{ V}$ ).




$V_i = 0 \rightarrow Q_1$  (OFF)

 


$V_o = V_{CC}$

 

 $V_i = 10\text{ V} \rightarrow Q_1$  (SAT; ON)





$V_o = 0.2\text{ V} \cong 0\text{ V}$

 


Consider two BJTs in series as NAND gate circuit:

  
- Knowing  $V_{CC} = 10\text{ V}$  and  $V_{CE(\text{sat})} = 0.2\text{ V}$ .



 
$V_1 = 0\text{ V}$   
 $V_2 = 0\text{ V}$   
 $V_o = 10\text{ V}$



 $V_1 = 10\text{ V}$   
 $V_2 = 0\text{ V}$   
 $V_o = 10\text{ V}$



 $V_1 = 0\text{ V}$   
 $V_2 = 10\text{ V}$   
 $V_o = 10\text{ V}$



$V_1 = 10\text{ V}$   
 $V_2 = 10\text{ V}$   
 $V_o = 0\text{ V}$

- The conditions and states of the circuit are listed below:

$V_A$ (Volt)	$V_B$ (Volt)	$Q_1$ State	$Q_2$ State	$V_o$ (Volt)
0	0	OFF	OFF	10
10	0	SAT	OFF	10
0	10	OFF	SAT	10
10	10	SAT	SAT	0

- The logic function is shown below. This is the operation of a NAND logic gate.



$A$	$B$	$Z$
0	0	1
0	1	1
1	0	1
1	1	0

## 9. Logic Device Families

- Logic devices can be designed and constructed from diodes, transistors, and a few passive components.
- Based on their histories, logic device families are:
  - Diode Logic (DL).
  - Resistor-Transistor Logic (RTL).
  - Diode-Transistor Logic (DTL).
  - Transistor-Transistor Logic (TTL).
  - Emitter-Coupled Logic (ECL).
  - (Complementary) FET:
    - Complementary Metal Oxide Semiconductor (CMOS).
    - BiCMOS.

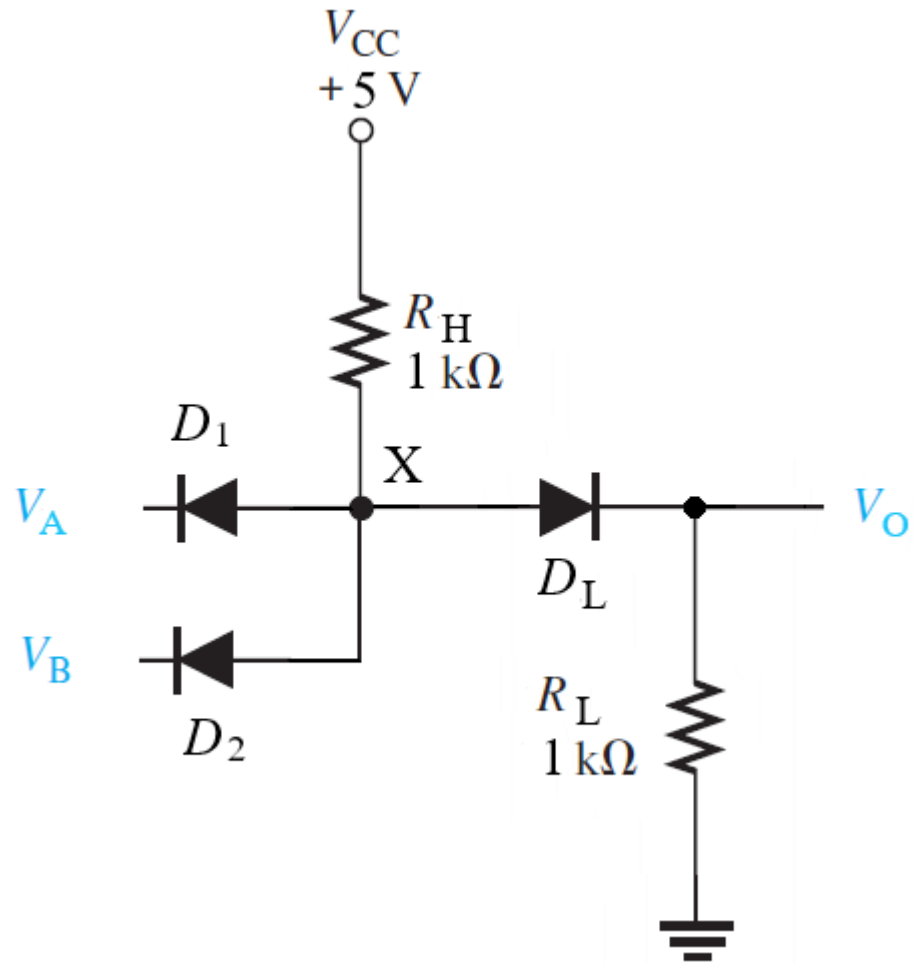
 
## Diode Logic (DL)

- Simplest form of logic.
- Does not scale.
- NOT logic is not possible (need an active element).
- Example of DL's AND logic circuit.



 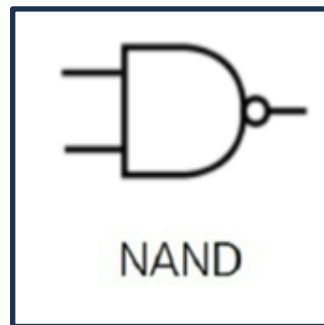
## Resistor-Transistor Logic (RTL)

- Replace diode switch with a transistor switch.
- Can be cascaded.
- Large power draw.
- Example of RTL's NAND logic circuit.


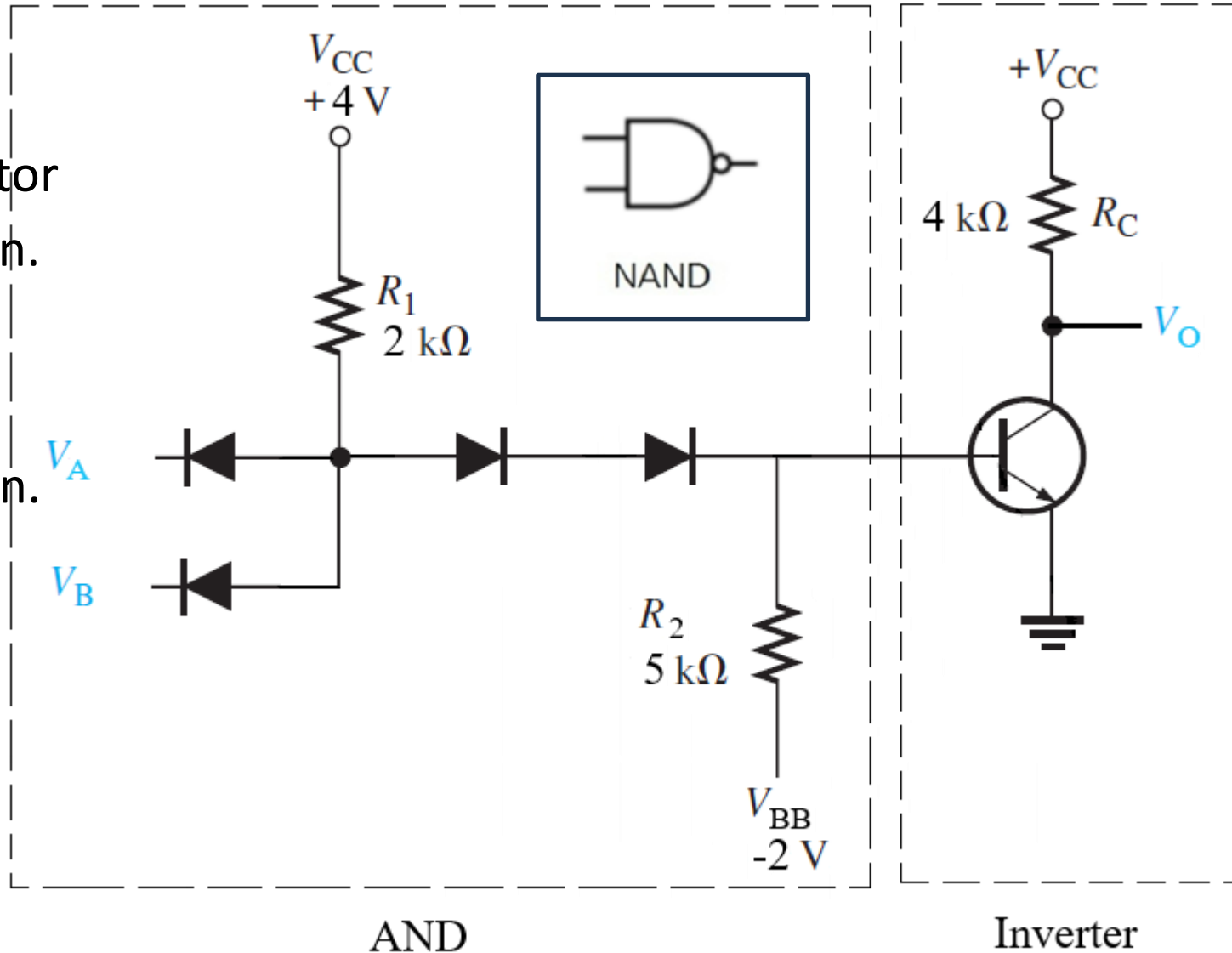
# Diode-Transistor Logic (DTL)



- Essentially diode logic with transistor amplification.
- Reduced power consumption.
- Faster than RTL.
- Example of ECL's NAND logic circuit





## **Transistor-Transistor Logic (TTL)**

- First introduced by Texas Instruments in 1964.
- TTL has shaped digital technology in many ways.
- Standard TTL family (e.g. 7400) is obsolete.
- Newer TTL families still used (e.g. 74ALS00).
- Distinct features:
  - Multi-emitter transistors.
  - Totem-pole transistor arrangement.

- Examples of TTL's NOT logic circuit:

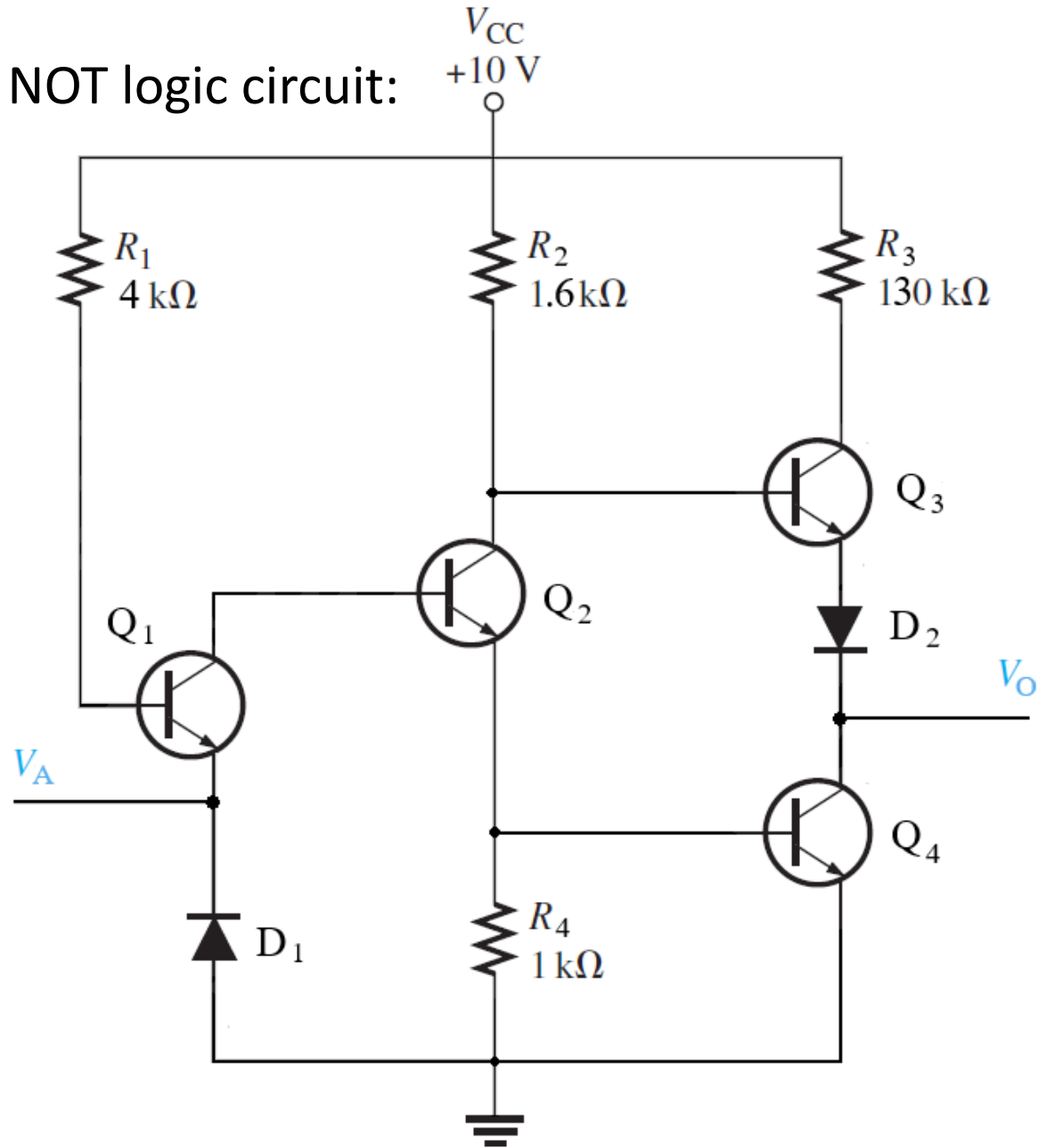 


- Example of TTL's NOR logic circuit:

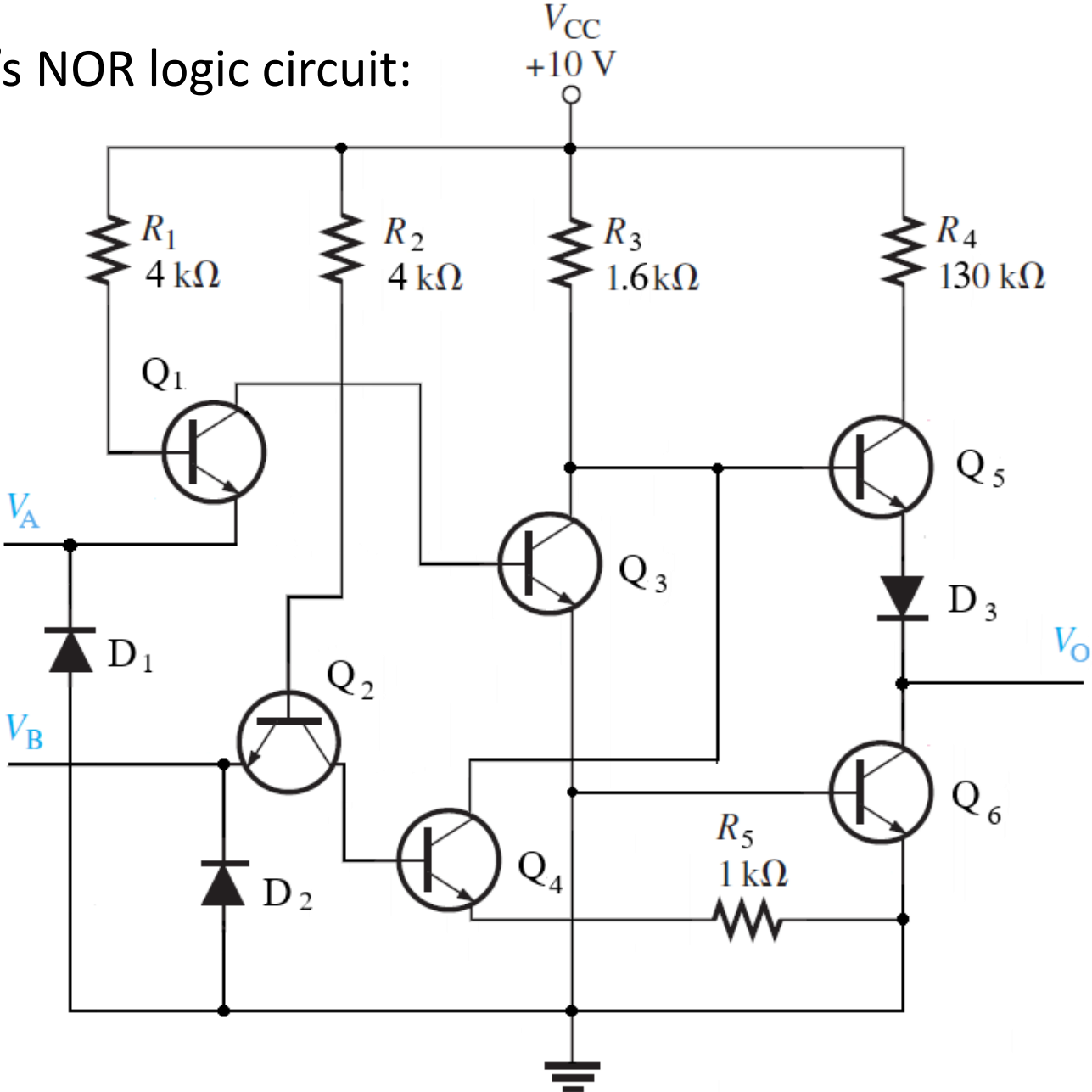 


## Emitter-Coupled Logic (ECL)

- Fastest logic family available ( $\sim 1$  ns) (pros).
- Low noise margin and high-power dissipation (cons).
- Operated in emitter coupled geometry (i.e. emitter-follower), transistors are biased and operate near their Q-point (i.e. never near saturation).
- Logic levels. “0”:  $-1.7$  V. “1”:  $-0.8$  V.
- Such uncommon logic levels require extra effort when interfacing to TTL/CMOS logic families.

- Example of ECL's NOR logic circuit.

 



X	Y	Out1	Out2
0	0	1	0
0	1	0	1
1	0	0	1
1	1	0	1

 

- Comparison of families of the logic gate circuits:

SPECIFICATION	TTL	ECL	CMOS
Components	Transistors & passive elements	Transistors & passive elements	MOSFETs
Basic Gate	NAND	OR/NOR	NAND/NOR
Noise Immunity	Strong	Good	Very strong
Fan-out	10	25	More than 50
tPD in ns	1.5-30	1-4	1-210
Noise margin	Moderate	Low	High
Power/gate in mWatt	10	40-55	0.0025
Clock rate in MHz	35	>60	10
Figure of Merit	100	40-100	0.7


### Example 3 – TTL Based Logic Device

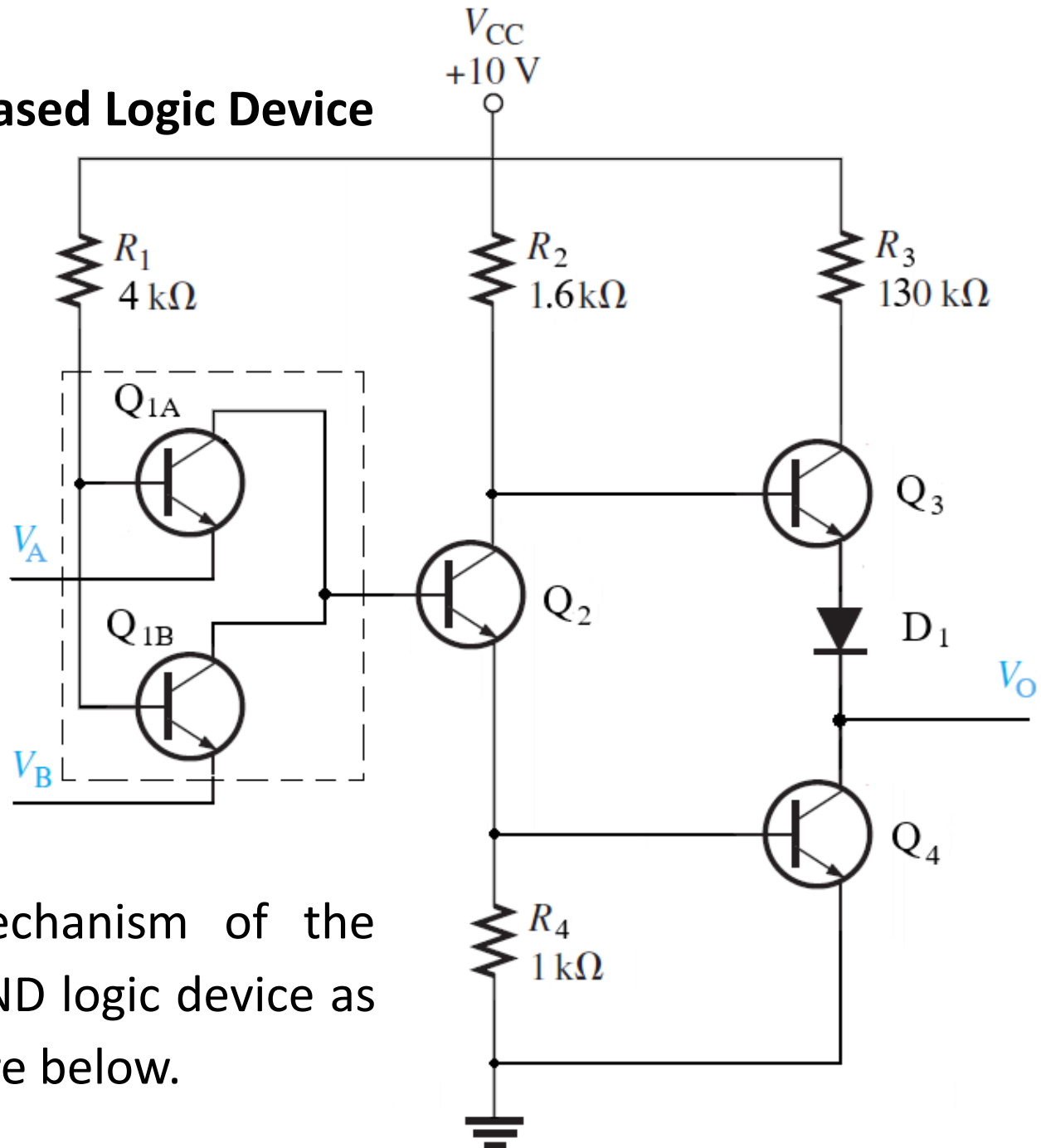 


Describe the mechanism of the following TTL NAND logic device as shown in the figure below.
 
## Answer



- Transistor  $Q_3$  is cutoff (i.e. act like a high RC) when output transistor  $Q_4$  is saturated, and  $Q_3$  is saturated



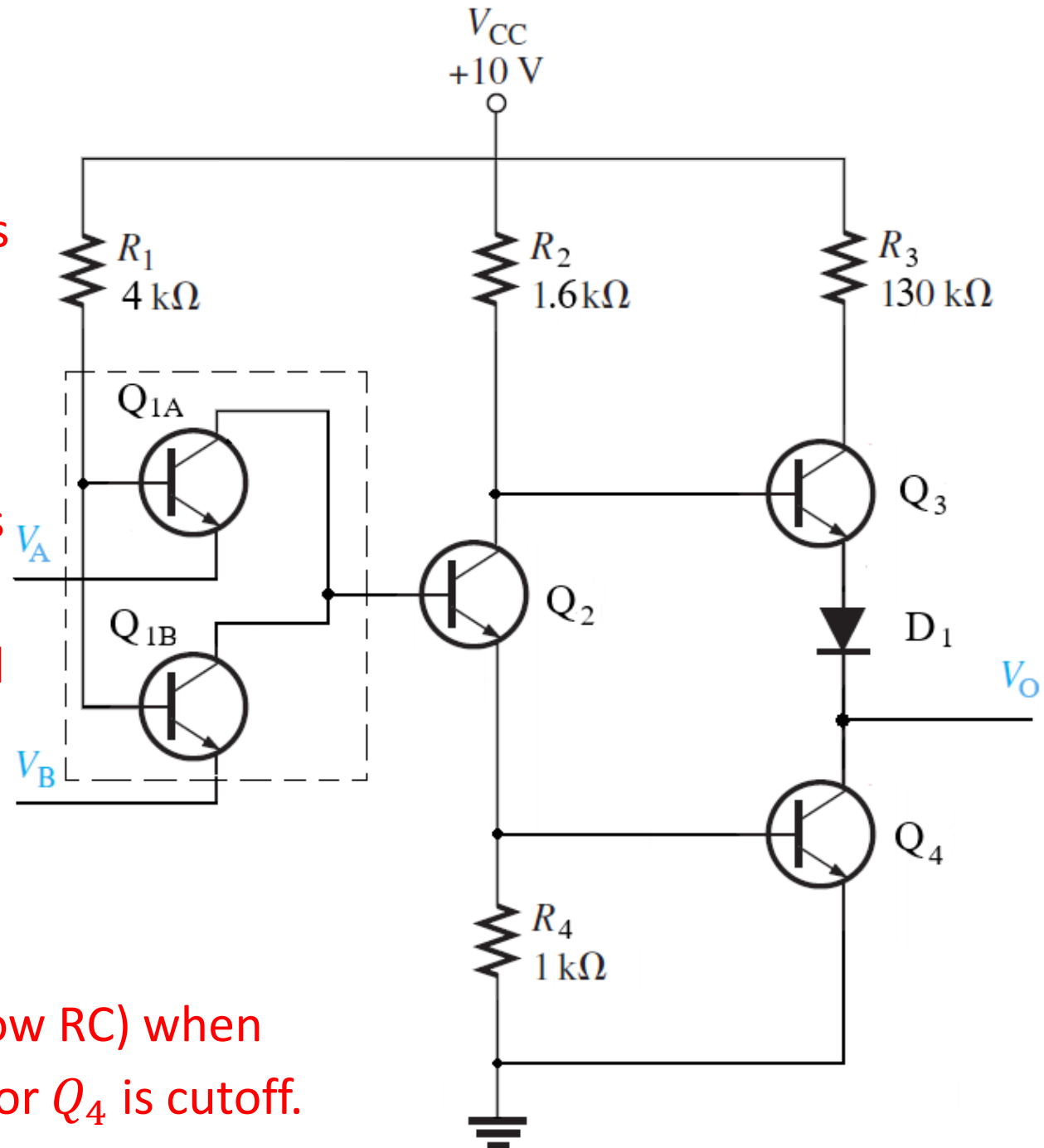
(i.e. act like a low RC) when output transistor  $Q_4$  is cutoff.



 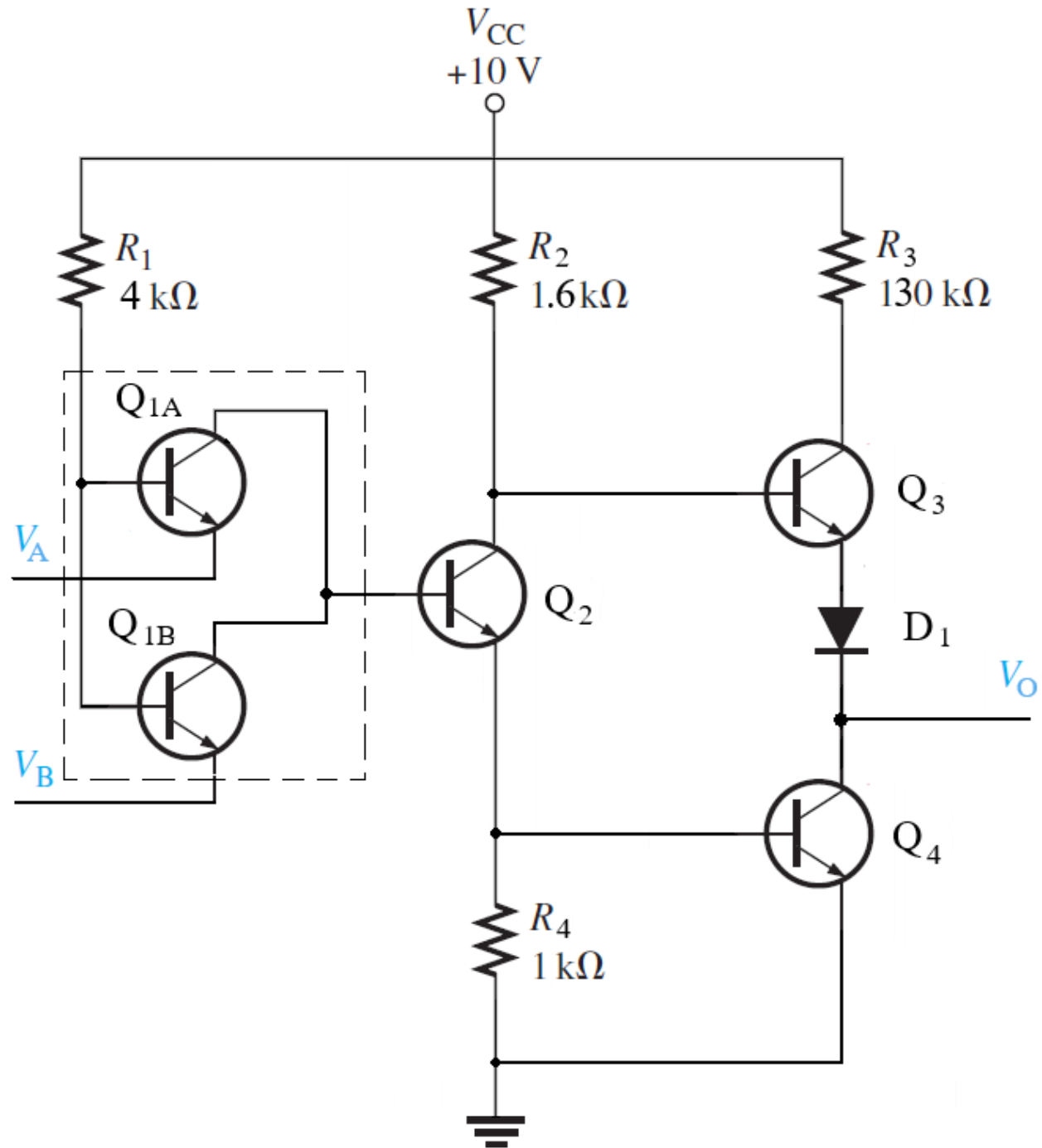
- Thus, one transistor is ON at one time.
- The combination of  $Q_3$  and  $Q_4$  is called TOTEM POLE arrangement.




 - Transistor  $Q_1$  is called input transistor, which is multi emitter transistor, that drive transistor  $Q_2$  which is used to control  $Q_3$  and  $Q_4$ .




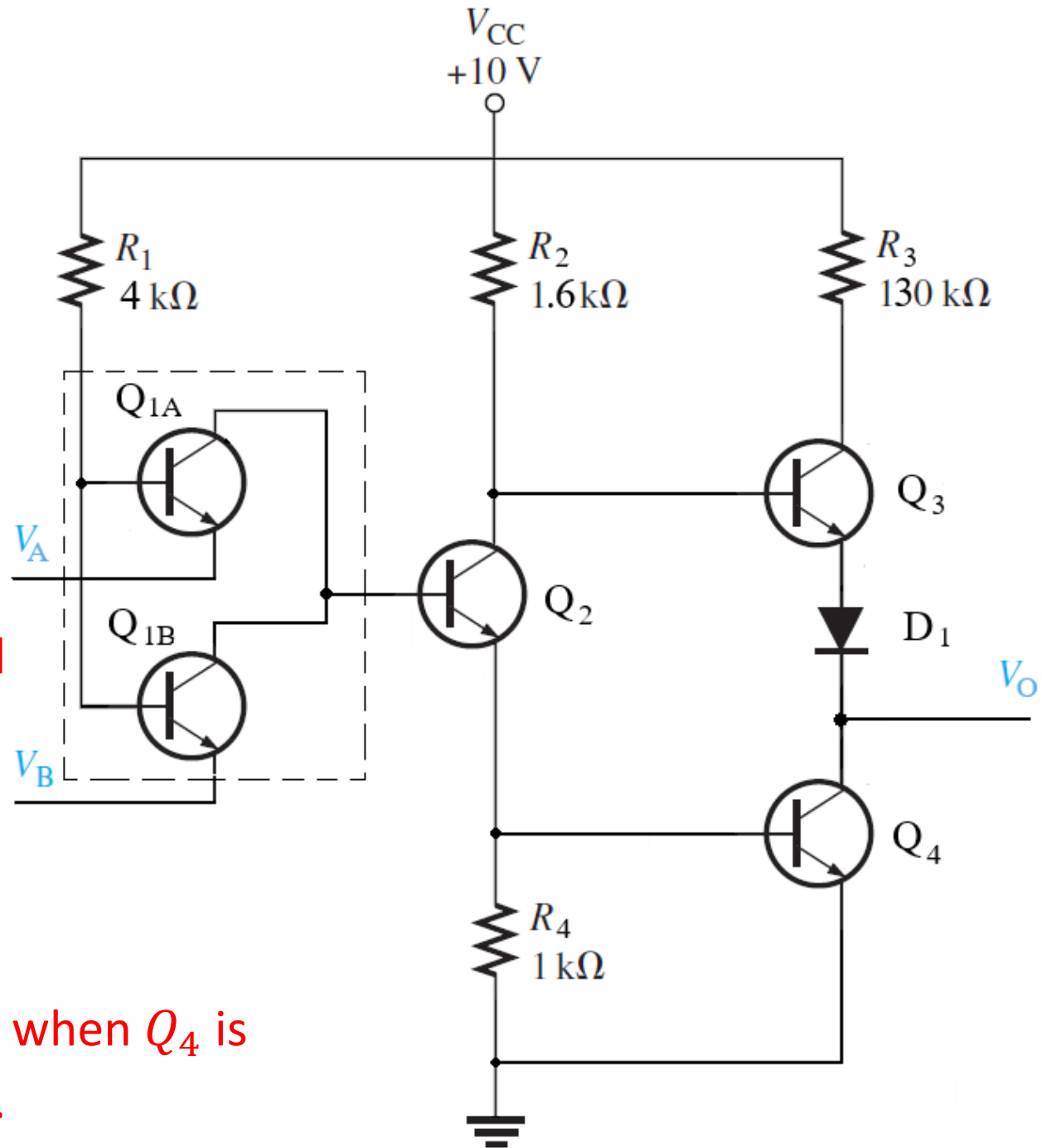- Diode  $D_1$  ensures when  $Q_4$  is ON and  $Q_3$  is OFF.



 

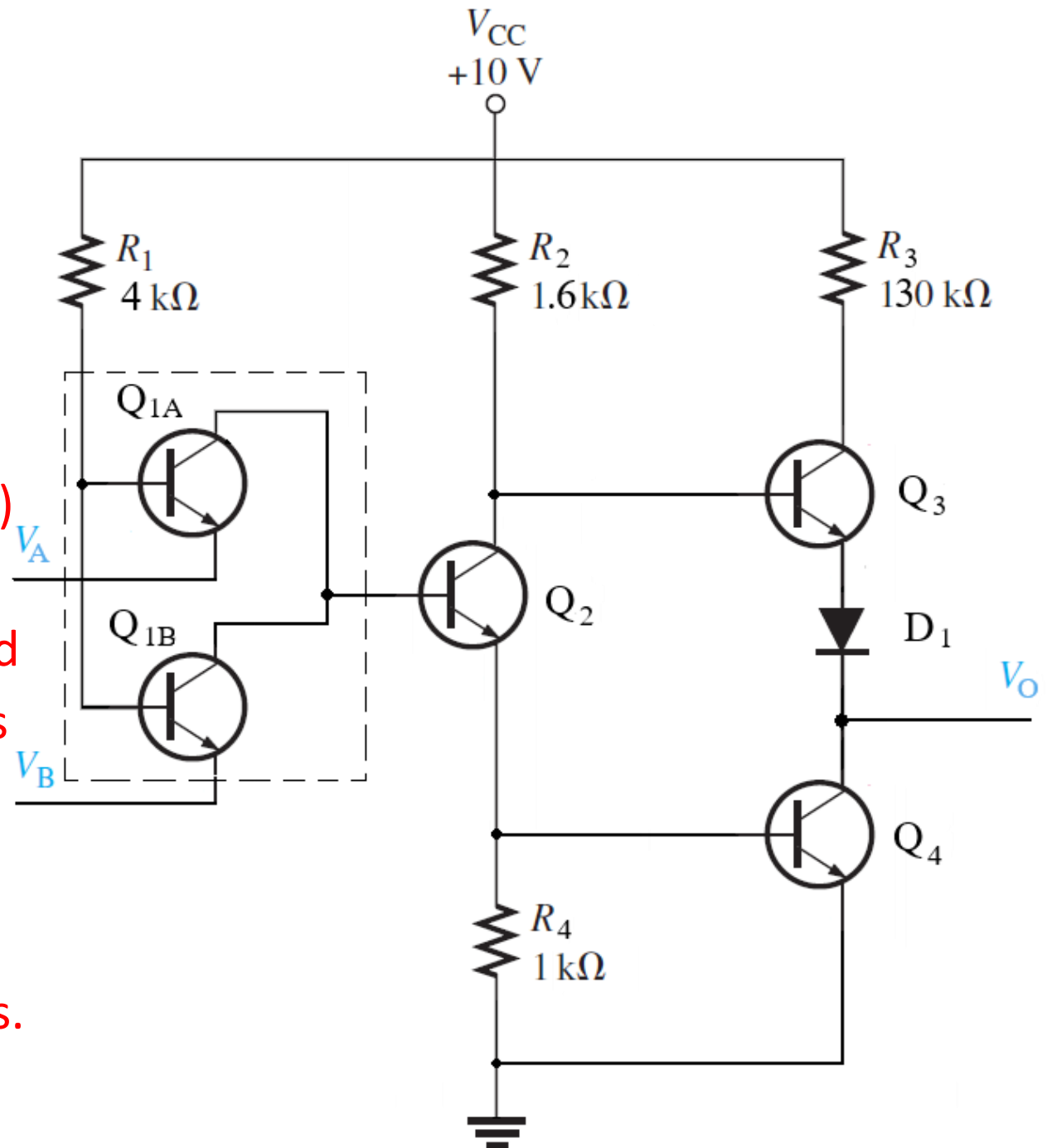- (In some designs) two additional diodes connected to  $V_A$  and  $V_B$  pins are used to protect  $Q_1$  from unwanted negative voltages.



- The conditions and states of the circuit are listed below:

$V_A$ (Volt)	$V_B$ (Volt)	$Q_{1A}$ State	$Q_{1B}$ State	$Q_2$ State	$Q_3$ State	$Q_4$ State	$V_O$ (Volt)
0	0	OFF	OFF	SAT	SAT	SAT	10
10	0	SAT	OFF	SAT	SAT	SAT	10
0	10	OFF	SAT	SAT	SAT	SAT	10
10	10	SAT	SAT	OFF	SAT	OFF	0

- The logic function is shown below. This is the operation of a NAND logic gate.

$A$	$B$	$Z$
0	0	1
0	1	1
1	0	1
1	1	0