

SAMPLE TEST QUESTIONS - ANSWERS

1. Using 9-bit binary plus a sign bit, the base-10 number +338 is represented by:

(a) 1011010010

(b) 0101010010

(c) 0011010011

(d) 1011001001

<u>S</u>	<u>256</u>	<u>128</u>	<u>64</u>	<u>32</u>	<u>16</u>	<u>8</u>	<u>4</u>	<u>2</u>	<u>1</u>
0	1	0	1	0	1	0	0	1	0

2. Using 7-bit binary plus a sign bit, the 1's complement representation of the binary for -73 is:

(a) 00110110

(b) 10110101

(c) 10110111

(d) 10110110

<u>S</u>	<u>64</u>	<u>32</u>	<u>16</u>	<u>8</u>	<u>4</u>	<u>2</u>	<u>1</u>	
1	1	0	0	1	0	0	1	binary
1	0	1	1	0	1	1	0	1's comp


3. The logic gate combination on the right represents the Boolean expression:

(a) $\overline{(A \cdot B) + C}$

(b) $\overline{A \cdot (B + C)}$

(c) $(A \cdot B) \oplus C$

(d) $A \cdot (B \oplus C)$

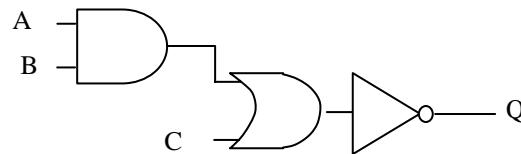

4. Select the truth table which corresponds to the Boolean expression $\overline{(A + B)}$.:

(a)

<u>A</u>	<u>B</u>	<u>Q</u>
0	0	0
0	1	1
1	0	1
1	1	0

(b)

<u>A</u>	<u>B</u>	<u>Q</u>
0	0	1
0	1	0
1	0	0
1	1	1

(c)

<u>A</u>	<u>B</u>	<u>Q</u>
0	0	1
0	1	0
1	0	0
1	1	0

(d)

<u>A</u>	<u>B</u>	<u>Q</u>
0	0	0
0	1	0
1	0	0
1	1	1

5. Use 2's complement addition, representing numbers with 7-bits plus a sign bit, to perform the subtraction 76 - 119.

	S	64	32	16	8	4	2	1
+76 in binary	0	1	0	0	1	1	0	0
- 119 in binary	1	1	1	1	0	1	1	1
- 119 in 1's comp	1	0	0	0	1	0	0	0
- 119 in 2's comp	1	0	0	0	1	0	0	1

So sum is:

$$\begin{array}{r}
 01001100 \\
 + 10001001 \\
 \hline
 11010101
 \end{array}$$


Sign bit is 1 so : (i) answer is negative

(ii) answer is in 2's comp

2's comp	1	1	0	1	0	1	0	1
1's comp	1	1	0	1	0	1	0	0
binary	1	0	1	0	1	0	1	1

This is: $-(32 + 8 + 2 + 1) = -43$

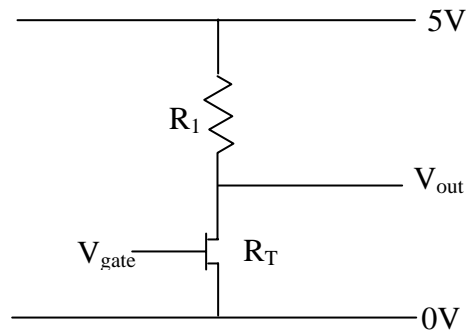6. The diagram on the right illustrates the use of a transistor as a switch in an electrical circuit (i.e. the use of the gate voltage V_{gate} applied to the transistor to control the output voltage V_{out} . Explain briefly how this is done and why using a transistor as a switch is preferable to having a mechanical switch.



When a HIGH voltage is applied to the gate terminal of a MOSFET transistor the resistance across the transistor (R_T) is small. When a LOW voltage is applied to the gate R_T is very large.


R_1 and R_T act as a potential divider.

If $R_1 \gg R_T$ then the voltage across R_1 is much larger than that across R_T . As the total voltage across R_1 and R_T combined is 5 V, this means that V_{out} (voltage across R_T) ≈ 0 V.

If $R_1 \ll R_T$ then the voltage across R_1 is much less than that across R_T . This means that $V_{out} \approx 5$ V.

Thus making $V_{gate} = \text{HIGH}$ makes $V_{out} = \text{LOW}$ and when $V_{gate} = \text{LOW}$, $V_{out} = \text{HIGH}$.

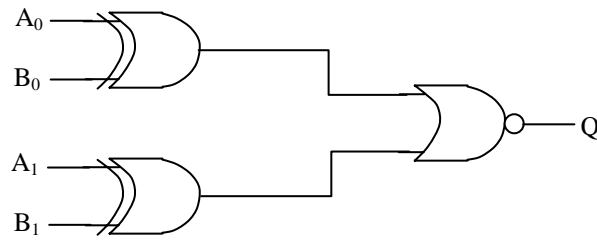7. Explain briefly the operation of the combinational logic circuit shown below.



The top XOR gate has an output of 1 if $A_0 \neq B_0$.

The lower XOR gate has an output of 1 if $A_1 \neq B_1$.

The NOR gate will have an output of 1 only if the outputs of both the XOR gates are 0.

Thus Q will be 1 ONLY if $A_0 = B_0$ and $A_1 = B_1$.


Thus the circuit tests for $A_0 = B_0$ AND $A_1 = B_1$.

8. Design a logic circuit whose output is HIGH whenever A and B are both HIGH as long as C and D are either both HIGH or both LOW.

A gate that gives a 1 when only both its inputs are 1 is and AND gate.

A gate that gives a 1 when either both inputs are 1 or both inputs are 0 is an XNOR gate (XOR gate followed by a NOT gate).

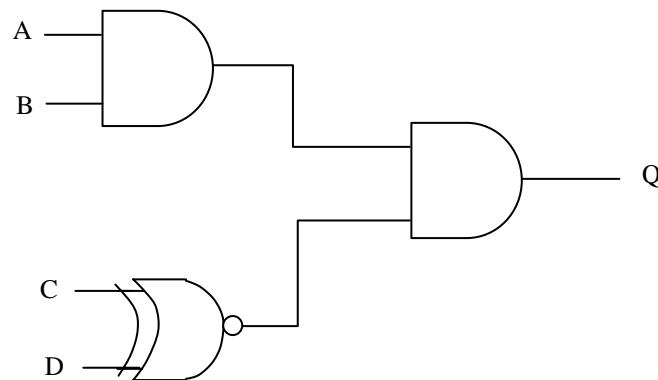If both these conditions are to be met the outputs must go into a second AND gate.



In terms of Boolean algebra: $AB(\overline{C \oplus D}) = Q$